

# **ELECTRICAL MEASUREMENT & MEASURING INSTRUMENTS**

# UNIT 3

## **Measurement of Parameters**

# Hay Bridge


- The Hay circuit is more convenient for measuring high-Q coils
- Hay bridge for inductance measurements

- $L_x = \frac{R_2 R_3 C_1}{1 + \omega^2 R_1^2 C_1^2} \quad \text{Where } Q = \frac{R_2 R_3 C_1}{R_x L_x}$

$$R_x = \frac{\omega^2 C_1^2 R_1 R_2 R_3}{1 + \omega^2 R_1^2 C_1^2}$$

Where, Q is the quality factor.
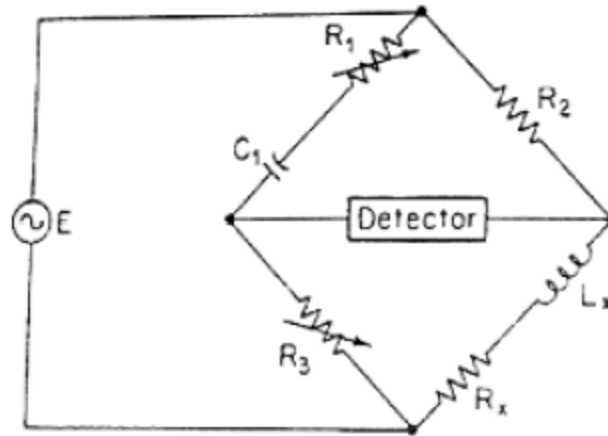
$$L_x = \frac{R_2 R_3 C_1}{1 + (1/Q)^2}$$




# Schering Bridge

- The Schering Bridge, one of the most important bridges, is used extensively for the measurement of capacitors.
- Schering bridge for measurement of capacitance

$$R_1 = R_2 \frac{C_1}{C_3} \quad \text{Dissipation factor :}$$
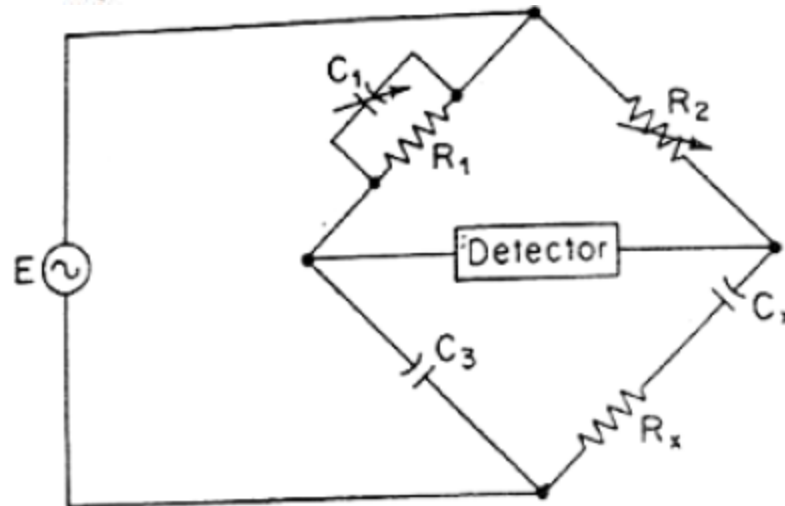
$$C_x = C_3 \frac{R_1}{R_2} \quad D = \omega R_1 C_1$$



# Wien Bridge

- Series RC combination in one and a parallel combination in the adjoining arm
- Its basic form is designed to measure  $f$  frequency
- used for instrument of an unknown capacitor with great accuracy


$$\frac{1}{\omega C_1 R_3} = \omega C_3 R_1$$

$$\omega^2 = \frac{1}{C_1 R_1 R_3 C_3}$$

$$\omega = \frac{1}{\sqrt{C_1 R_1 C_3 R_3}}$$

$$\omega = 2 \pi f$$
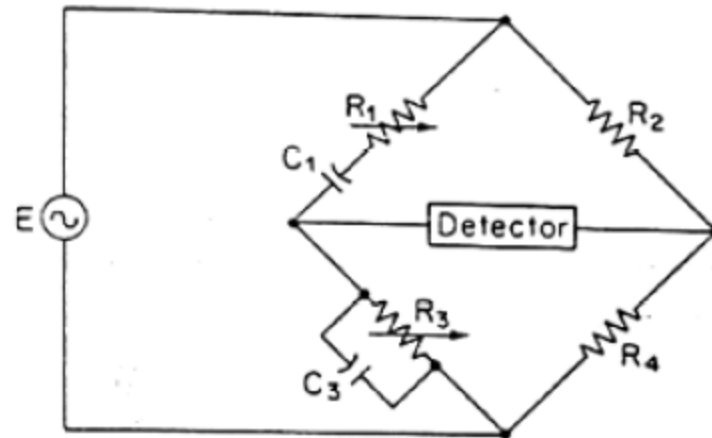
$$f = \frac{1}{2 \pi \sqrt{C_1 R_1 C_3 R_3}}$$



# Anderson Bridge

- The unknown inductance is measured in terms of a known capacitance and resistance.
- Method is capable of precise measurements of inductance over a wide range of values from a few micro-henrys to several henrys and is the best bridge method

By solving the balance equation  
 $L = C [(R_1 + R_2) R_3 + R_2 R_4]$

