
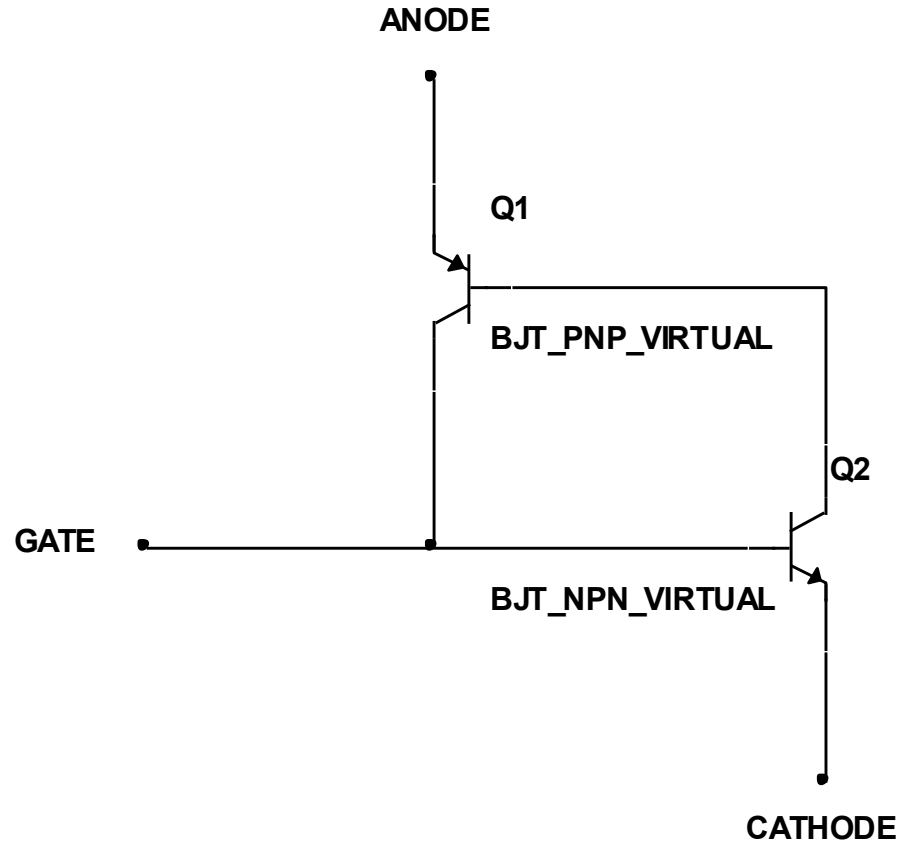



# Equivalent Circuit

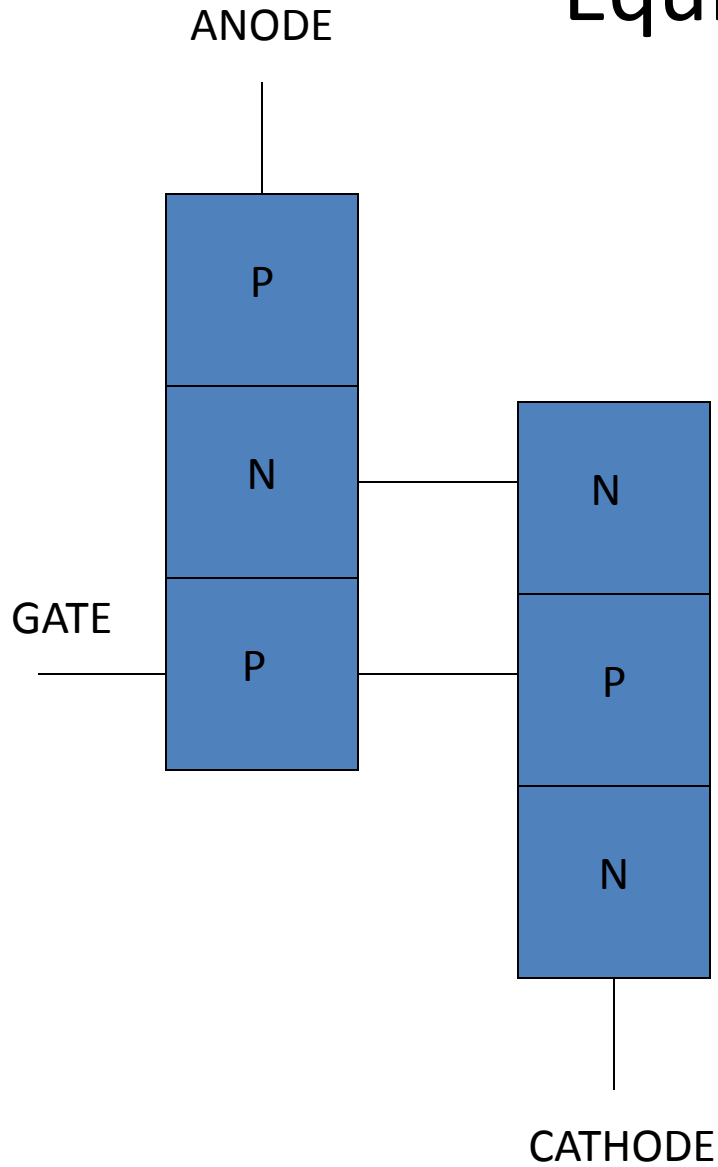

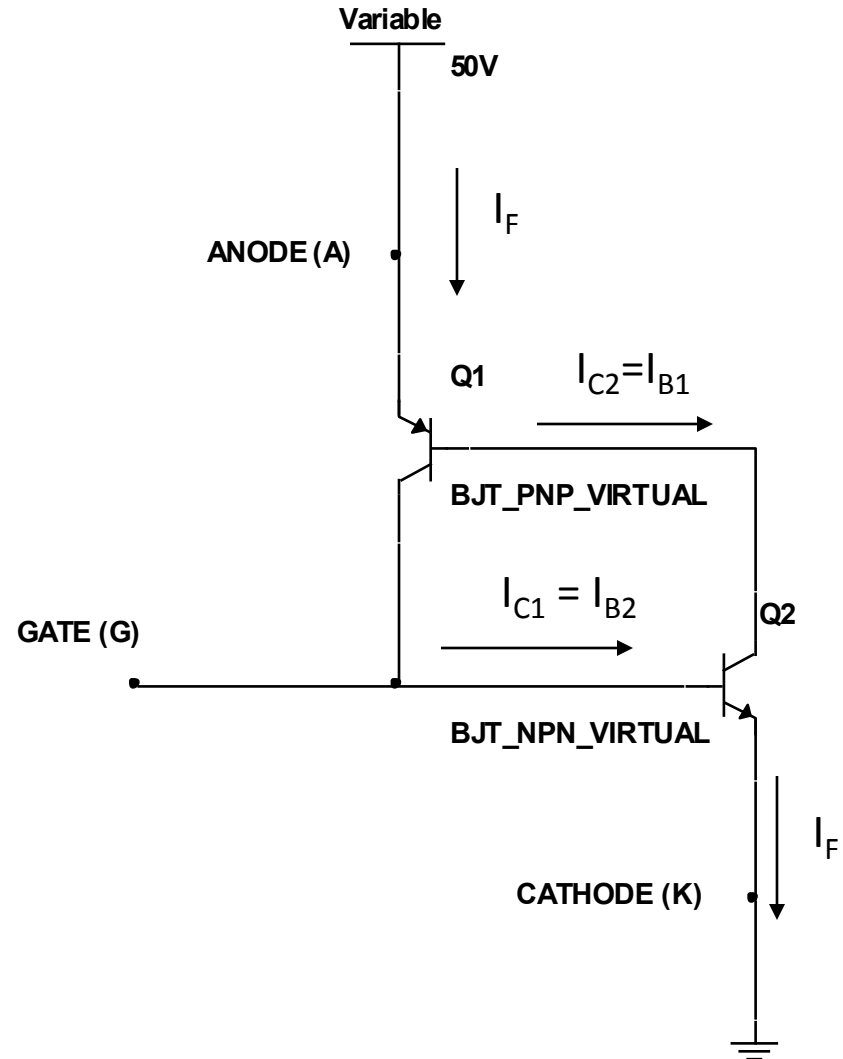
# Apply Biasing

With the Gate terminal OPEN, both transistors are OFF. As the applied voltage increases, there will be a “breakdown” that causes both transistors to conduct (saturate) making  $I_F > 0$  and  $V_{AK} = 0$ .

$$V_{\text{Breakdown}} = V_{\text{BR(F)}}$$



# Static I-V Characteristics of SCR

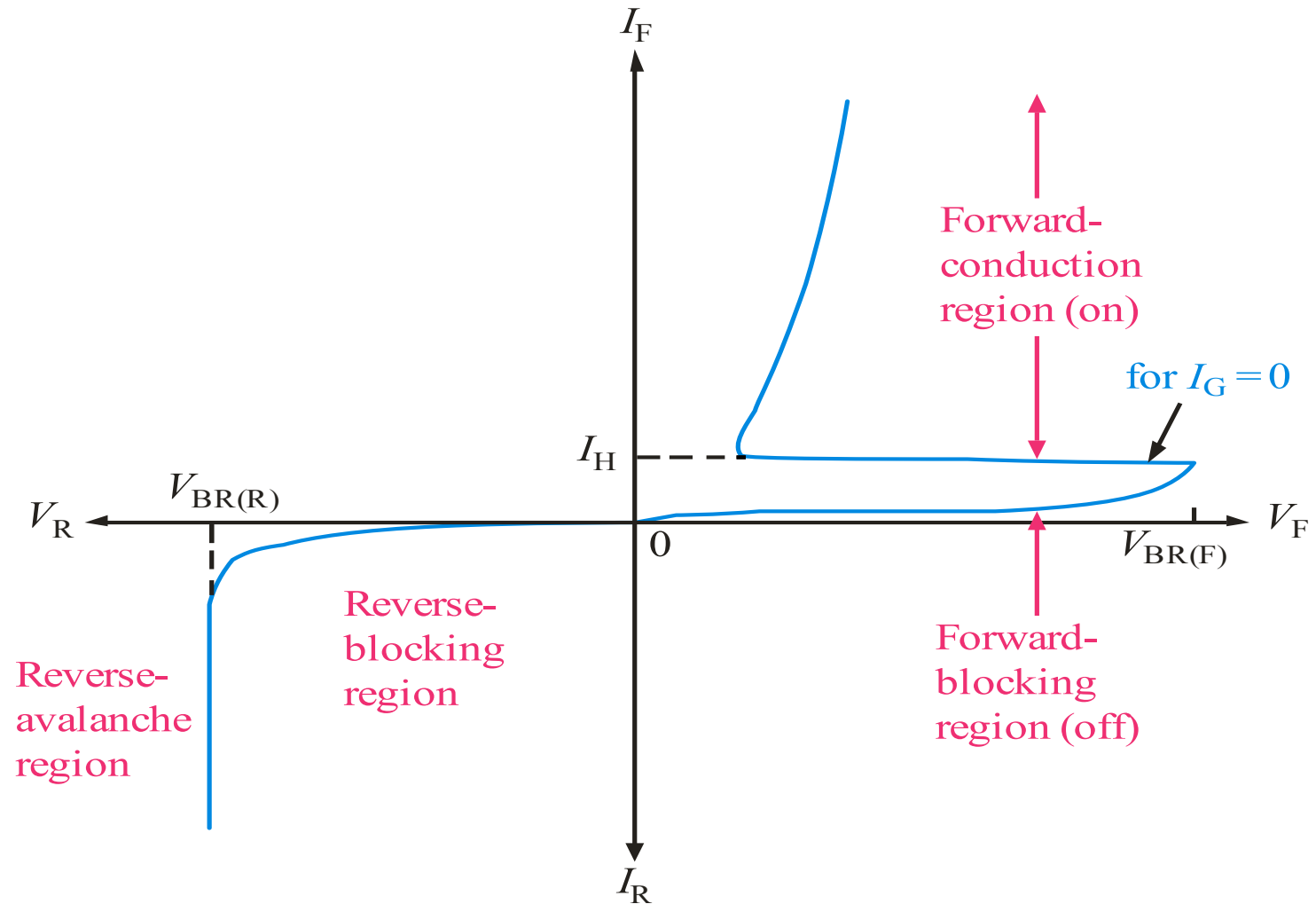

# Apply a Gate Current


For  $0 < V_{AK} < V_{BR(F)}$ ,

Turn  $Q_2$  ON by applying a current into the Gate

This causes  $Q_1$  to turn ON, and eventually both transistors SATURATE

$$V_{AK} = V_{CEsat} + V_{BEsat}$$

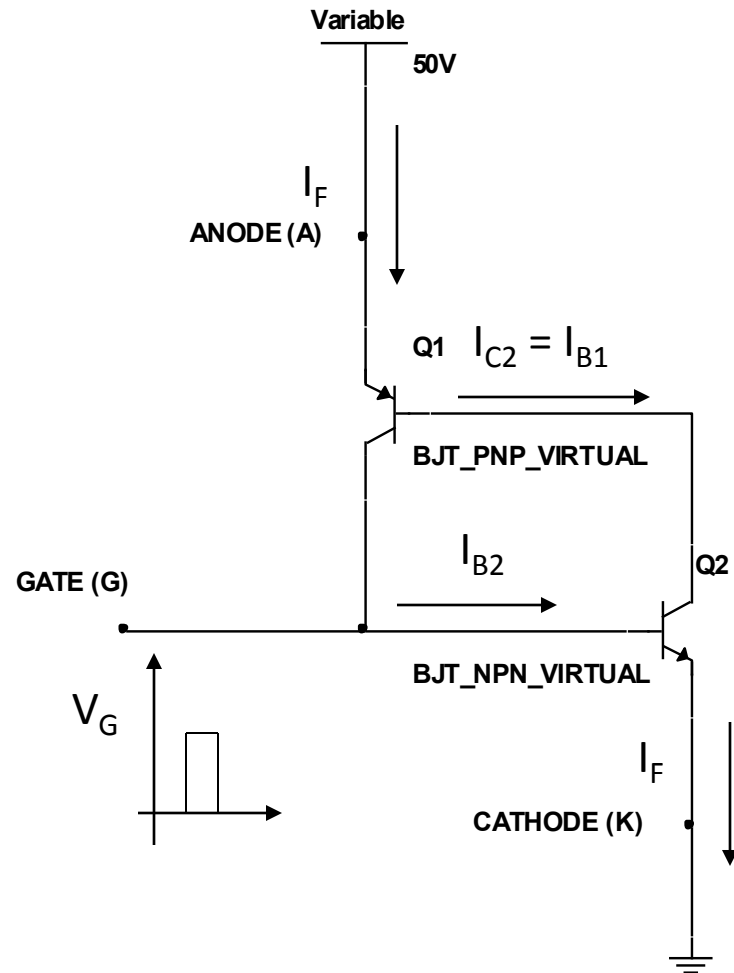If the Gate pulse is removed,  $Q_1$  and  $Q_2$  still stay ON!



# Latching & Holding Current

## Latching current

Minimum anode current that must flow through the SCR in order for it to stay on initially after gate signal is removed.

## Holding Current

Minimum value of anode current, required to maintain SCR in conducting state.