

# Performance Parameters Of Phase Controlled Rectifiers

Output dc power (avg. or dc o/p  
power delivered to the load)

$$P_{O(dc)} = V_{O(dc)} \times I_{O(dc)} ; \text{ i.e., } P_{dc} = V_{dc} \times I_{dc}$$

Where

$$V_{O(dc)} = V_{dc} = \text{avg./ dc value of o/p voltage.}$$

$$I_{O(dc)} = I_{dc} = \text{avg./dc value of o/p current}$$

Output ac power

$$P_{O(ac)} = V_{O(RMS)} \times I_{O(RMS)}$$

Efficiency of Rectification (Rectification Ratio)

$$\text{Efficiency } \eta = \frac{P_{O(dc)}}{P_{O(ac)}}; \quad \% \text{ Efficiency } \eta = \frac{P_{O(dc)}}{P_{O(ac)}} \times 100$$

The o/p voltage consists of two components

The dc component  $V_{O(dc)}$

The ac /ripple component  $V_{ac} = V_{r(rms)}$

The total RMS value of output voltage is given by

$$V_{O(RMS)} = \sqrt{V_{O(dc)}^2 + V_{r(rms)}^2}$$

$$\therefore V_{ac} = V_{r(rms)} = \sqrt{V_{O(RMS)}^2 - V_{O(dc)}^2}$$

Form Factor (FF) which is a measure of the shape of the output voltage is given by

$$FF = \frac{V_{O(RMS)}}{V_{O(dc)}} = \frac{\text{RMS output (load) voltage}}{\text{DC load output (load) voltage}}$$

The Ripple Factor (RF) w.r.t. o/p voltage w/f

$$r_v = RF = \frac{V_{r(rms)}}{V_{O(dc)}} = \frac{V_{ac}}{V_{dc}}$$

$$r_v = \frac{\sqrt{V_{O(RMS)}^2 - V_{O(dc)}^2}}{V_{O(dc)}} = \sqrt{\left[ \frac{V_{O(RMS)}}{V_{O(dc)}} \right]^2 - 1}$$

$$\therefore r_v = \sqrt{FF^2 - 1}$$

Current Ripple Factor  $r_i = \frac{I_{r(rms)}}{I_{O(dc)}} = \frac{I_{ac}}{I_{dc}}$

Where  $I_{r(rms)} = I_{ac} = \sqrt{I_{O(RMS)}^2 - I_{O(dc)}^2}$

$V_{r(pp)}$  = peak to peak ac ripple output voltage

$$V_{r(pp)} = V_{O(max)} - V_{O(min)}$$

$I_{r(pp)}$  = peak to peak ac ripple load current

$$I_{r(pp)} = I_{O(max)} - I_{O(min)}$$


## Transformer Utilization Factor (TUF)

$$TUF = \frac{P_{O(dc)}}{V_S \times I_S}$$

Where

$V_S$  = RMS supply (secondary) voltage

$I_S$  = RMS supply (secondary) current

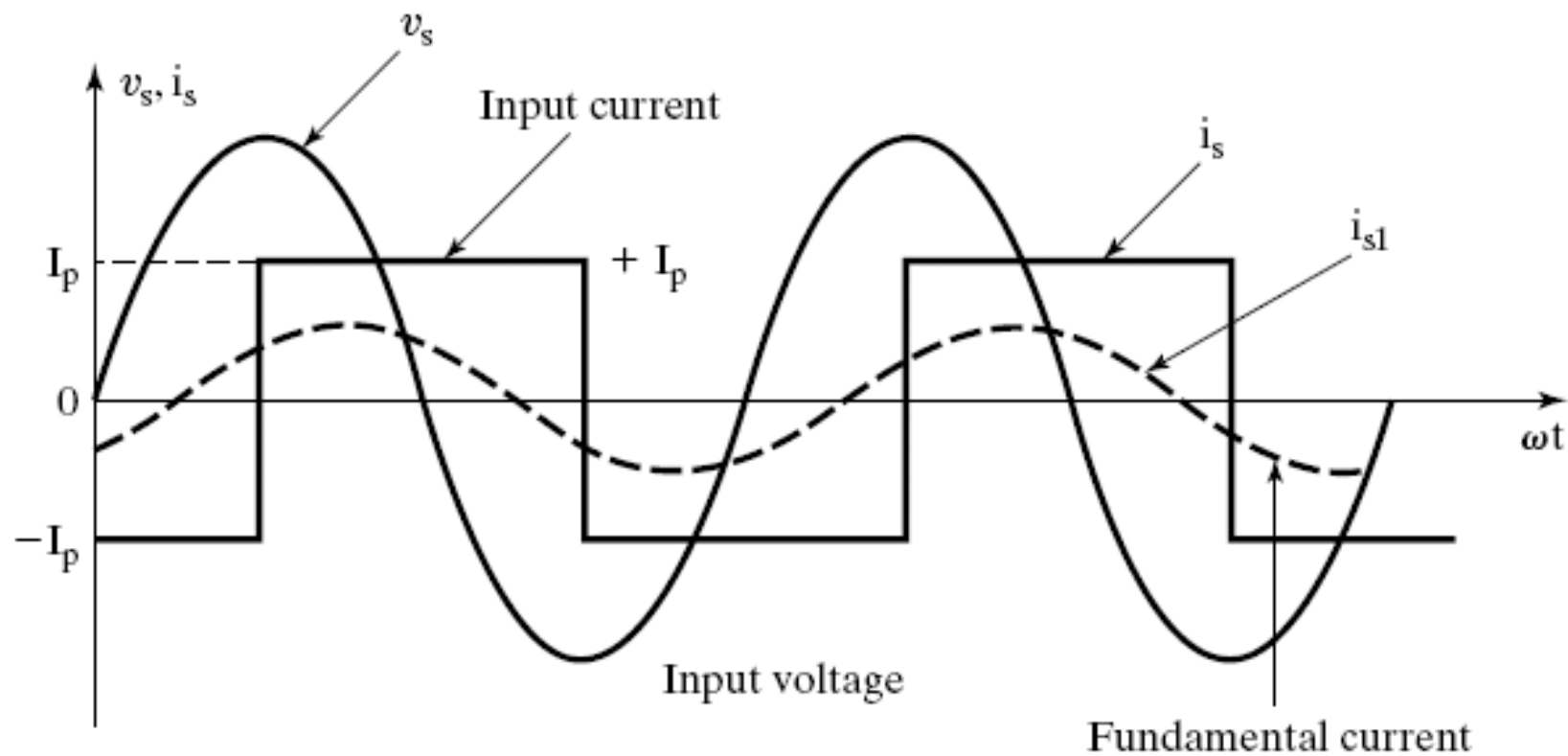



Where

$v_s$  = Supply voltage at the transformer secondary side

$i_s$  = i/p supply current

(transformer secondary winding current)

$i_{s1}$  = Fundamental component of the i/p supply current

$I_P$  = Peak value of the input supply current

$\phi$  = Phase angle difference between (sine wave components) the fundamental components of i/p supply current & the input supply voltage.

$\phi$  = Displacement angle (phase angle)

For an RL load

$\phi$  = Displacement angle = Load impedance angle

$$\therefore \phi = \tan^{-1} \left( \frac{\omega L}{R} \right) \text{ for an RL load}$$

Displacement Factor (DF) or

Fundamental Power Factor

$$DF = \cos \phi$$

Harmonic Factor (HF) or

Total Harmonic Distortion Factor ; THD

$$HF = \left[ \frac{I_S^2 - I_{S1}^2}{I_{S1}^2} \right]^{\frac{1}{2}} = \left[ \left( \frac{I_S}{I_{S1}} \right)^2 - 1 \right]^{\frac{1}{2}}$$

Where

$I_S$  = RMS value of input supply current.

$I_{S1}$  = RMS value of fundamental component of the i/p supply current.

## Input Power Factor (PF)

$$PF = \frac{V_S I_{S1}}{V_S I_S} \cos \phi = \frac{I_{S1}}{I_S} \cos \phi$$

## The Crest Factor (CF)


$$CF = \frac{I_{S(\text{peak})}}{I_S} = \frac{\text{Peak input supply current}}{\text{RMS input supply current}}$$

## For an Ideal Controlled Rectifier


$$FF = 1; \quad \eta = 100\% ; \quad V_{ac} = V_{r(\text{rms})} = 0 ; \quad TUF = 1;$$

$$RF = r_v = 0 ; \quad HF = THD = 0; \quad PF = DPF = 1$$

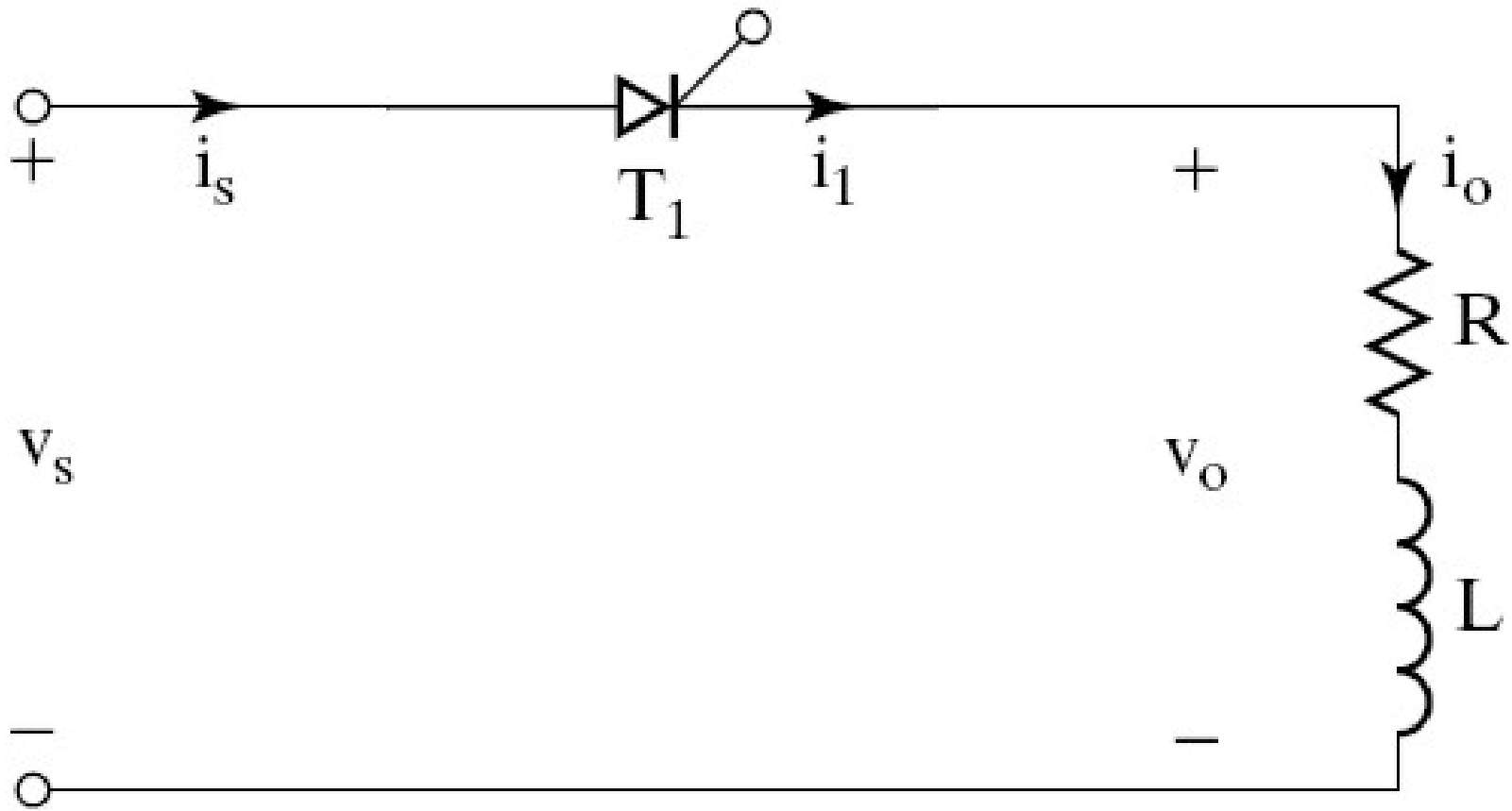Single Phase Half Wave  
Controlled Rectifier  
With  
An  
RL Load




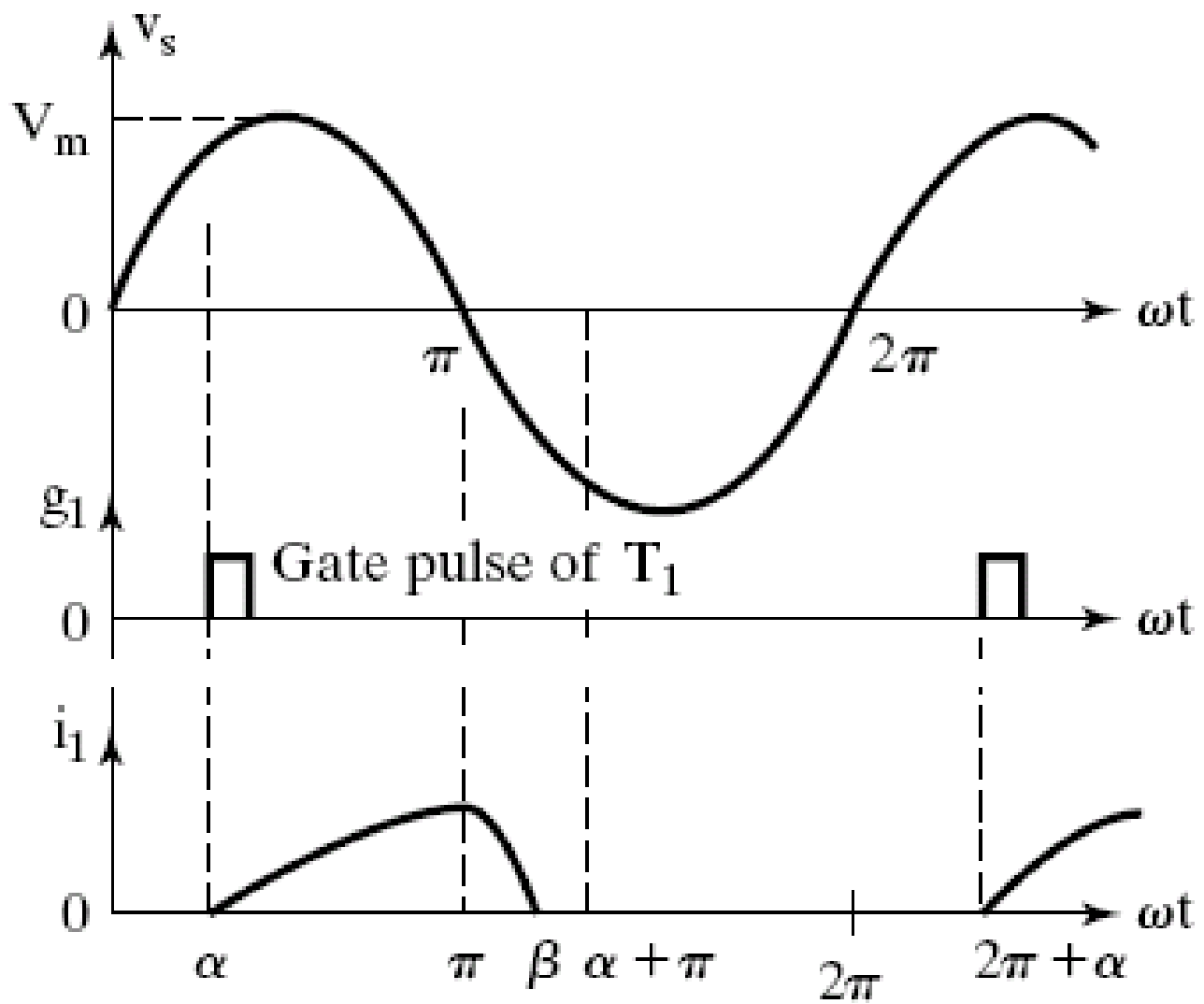Input Supply Voltage ( $V_s$ )  
&  
Thyristor (Output) Current  
Waveforms





# Output (Load) Voltage Waveform

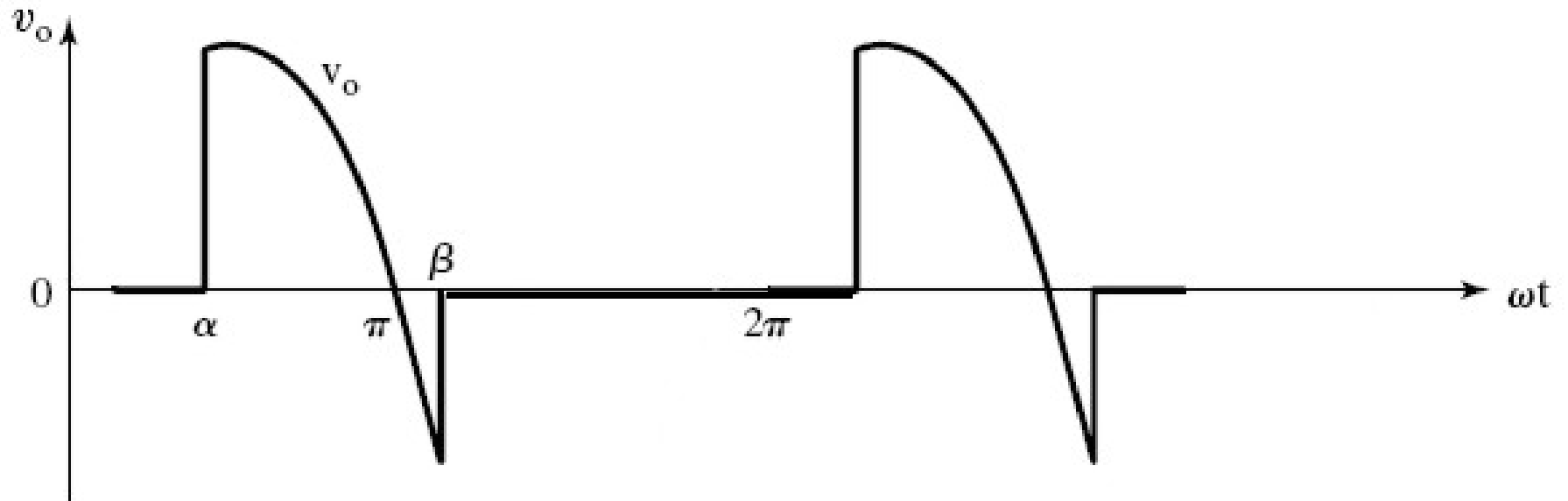

To Derive An Expression For  
The Output  
(Load) Current, During  $\omega t = \alpha$  to  $\beta$   
When Thyristor  $T_1$  Conducts

Assuming  $T_1$  is triggered  $\omega t = \alpha$ ,  
we can write the equation,

$$L \left( \frac{di_o}{dt} \right) + Ri_o = V_m \sin \omega t ; \alpha \leq \omega t \leq \beta$$

General expression for the output current,

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-t}{\tau}}$$

$$V_m = \sqrt{2}V_s = \text{maximum supply voltage.}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load impedance.}$$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right) = \text{Load impedance angle.}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

$\therefore$  general expression for the output load current

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-R}{L} t}$$

Constant  $A_1$  is calculated from

initial condition  $i_o = 0$  at  $\omega t = \alpha$  ;  $t = \left( \frac{\alpha}{\omega} \right)$

$$i_o = 0 = \frac{V_m}{Z} \sin(\alpha - \phi) + A_1 e^{\frac{-R}{L} t}$$

$$\therefore A_1 e^{\frac{-R}{L} t} = \frac{-V_m}{Z} \sin(\alpha - \phi)$$

We get the value of constant  $A_1$  as

$$A_1 = e^{\frac{R(\alpha)}{\omega L}} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

Substituting the value of constant  $A_1$  in the general expression for  $i_o$

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + e^{\frac{-R}{\omega L}(\omega t - \alpha)} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

$\therefore$  we obtain the final expression for the inductive load current

$$i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right];$$

Where  $\alpha \leq \omega t \leq \beta$

Extinction angle  $\beta$  can be calculated by using the condition that  $i_o = 0$  at  $\omega t = \beta$

$$i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right] = 0$$

$$\therefore \sin(\beta - \phi) = e^{\frac{-R}{\omega L}(\beta - \alpha)} \times \sin(\alpha - \phi)$$

$\beta$  can be calculated by solving the above eqn.

To Derive An Expression  
For  
Average (DC) Load Voltage of a Single  
Half Wave Controlled Rectifier with  
RL Load



$$V_{O(dc)} = V_L = \frac{1}{2\pi} \int_0^{2\pi} v_O \cdot d(\omega t)$$

$$V_{O(dc)} = V_L = \frac{1}{2\pi} \left[ \int_0^{\alpha} v_O \cdot d(\omega t) + \int_{\alpha}^{\beta} v_O \cdot d(\omega t) + \int_{\beta}^{2\pi} v_O \cdot d(\omega t) \right]$$

$v_O = 0$  for  $\omega t = 0$  to  $\alpha$  & for  $\omega t = \beta$  to  $2\pi$

$$\therefore V_{O(dc)} = V_L = \frac{1}{2\pi} \left[ \int_{\alpha}^{\beta} v_O \cdot d(\omega t) \right];$$

$v_O = V_m \sin \omega t$  for  $\omega t = \alpha$  to  $\beta$

$$V_{O(dc)} = V_L = \frac{1}{2\pi} \left[ \int_{\alpha}^{\beta} V_m \sin \omega t \cdot d(\omega t) \right]$$

$$V_{O(dc)} = V_L = \frac{V_m}{2\pi} \left[ -\cos \omega t \Big|_{\alpha}^{\beta} \right]$$

$$V_{O(dc)} = V_L = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

$$\therefore V_{O(dc)} = V_L = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

## Effect of Load


### Inductance on the Output


During the period  $\omega t = \pi$  to  $\beta$  the instantaneous o/p voltage is negative and this reduces the average or the dc output voltage when compared to a purely resistive load.
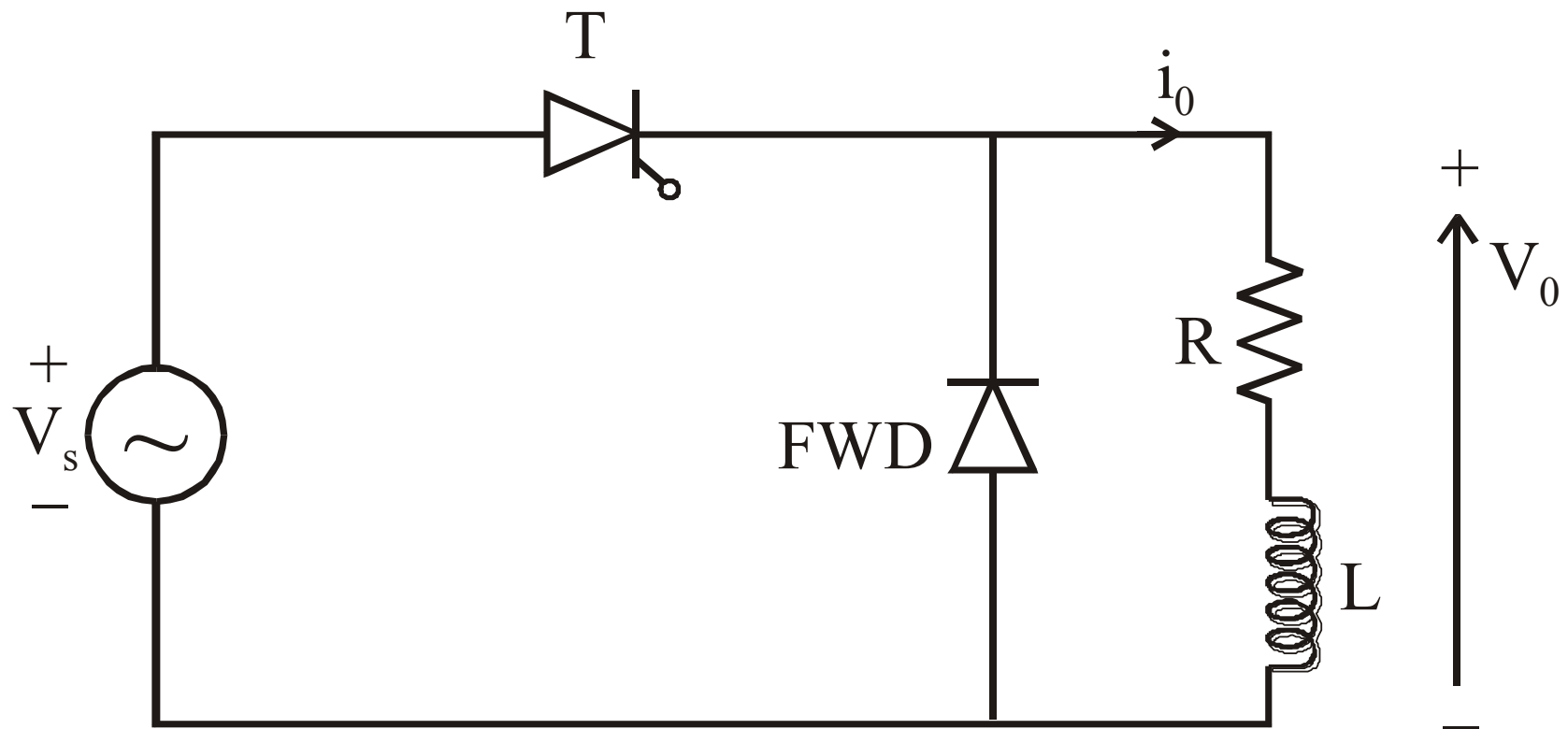
# Average DC Load Current

$$I_{O(dc)} = I_{L(Avg)} = \frac{V_{O(dc)}}{R_L} = \frac{V_m}{2\pi R_L} (\cos \alpha - \cos \beta)$$

Single Phase Half Wave  
Controlled Rectifier  
With RL Load  
&  
Free Wheeling Diode



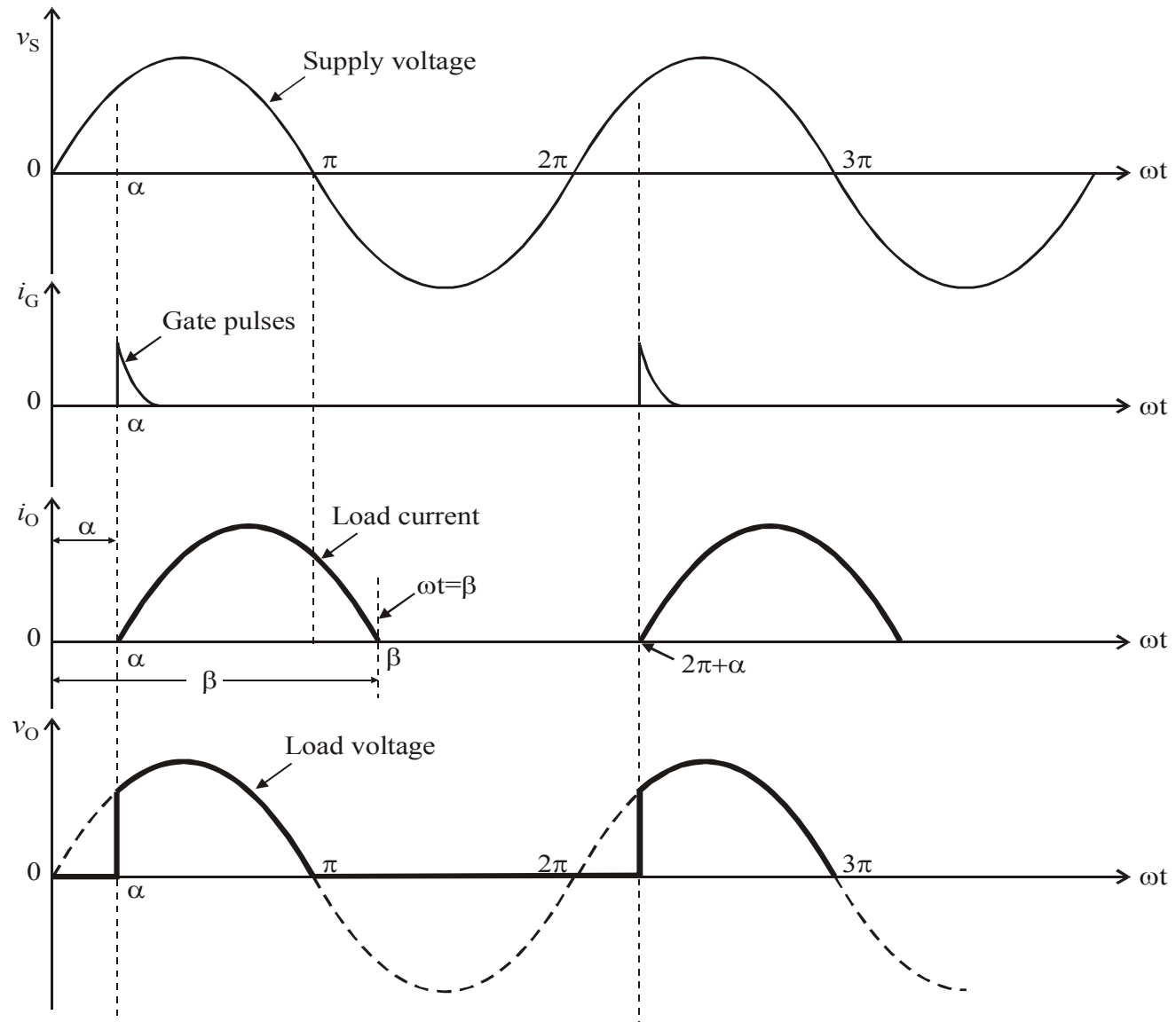

The average output voltage

$V_{dc} = \frac{V_m}{2\pi} [1 + \cos \alpha]$  which is the same as that of a purely resistive load.

**The following points are to be noted**

For low value of inductance, the load current tends to become discontinuous.



During the period  $\alpha$  to  $\pi$

the load current is carried by the SCR.

During the period  $\pi$  to  $\beta$  load current is carried by the free wheeling diode.

The value of  $\beta$  depends on the value of R and L and the forward resistance of the FWD.

For Large Load Inductance  
the load current does not reach zero, & we  
obtain continuous load current

