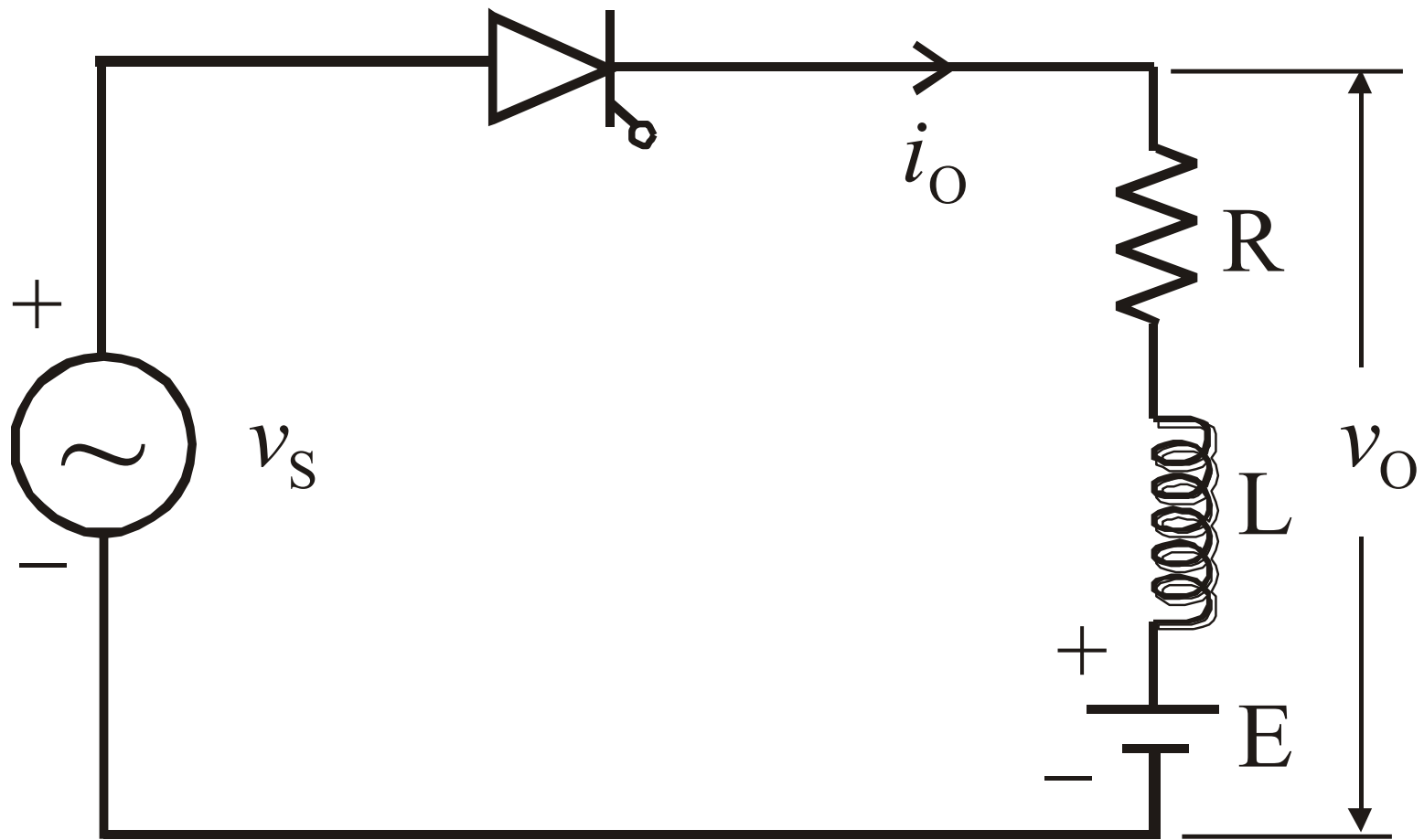


Single Phase Half Wave Controlled Rectifier With A General Load




$$\gamma = \sin^{-1} \left(\frac{E}{V_m} \right)$$

For trigger angle $\alpha < \gamma$,

the Thyristor conducts from $\omega t = \gamma$ to β

For trigger angle $\alpha > \gamma$,

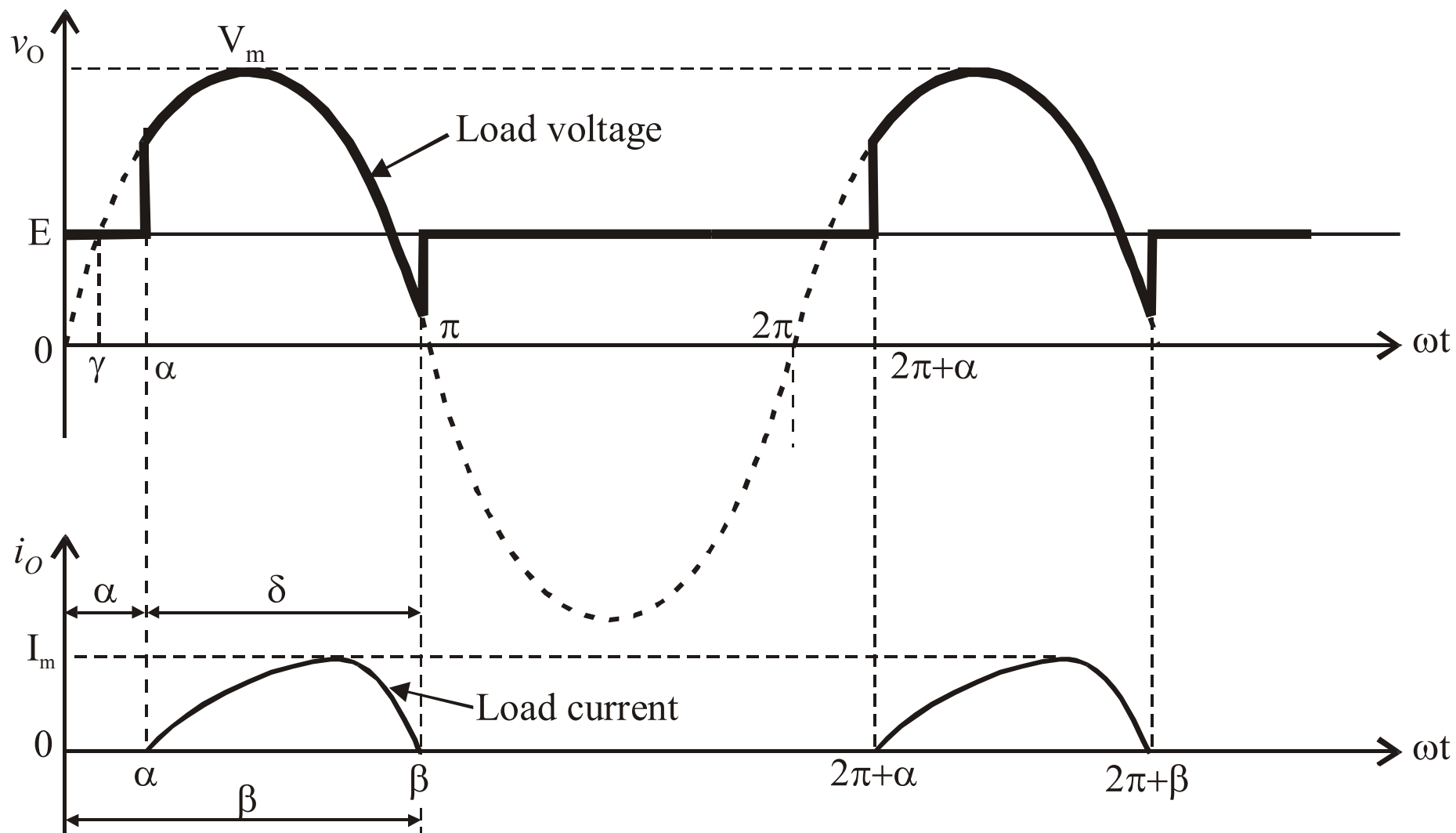the Thyristor conducts from $\omega t = \alpha$ to β



Equations

$$v_S = V_m \sin \omega t = \text{Input supply voltage.}$$

$$v_O = V_m \sin \omega t = \text{o/p (load) voltage}$$

$$\text{for } \omega t = \alpha \text{ to } \beta.$$

$$v_O = E \text{ for } \omega t = 0 \text{ to } \alpha \text{ \&}$$

$$\text{for } \omega t = \beta \text{ to } 2\pi.$$

Expression for the Load Current

When the thyristor is triggered at a delay angle of $\alpha > \gamma$, the eqn. for the circuit can be written as

$$V_m \sin \omega t = i_o \times R + L \left(\frac{di_o}{dt} \right) + E ; \alpha \leq \omega t \leq \beta$$

The general expression for the output load current can be written as

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + A e^{\frac{-t}{\tau}}$$

Where

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load Impedance.}$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = \text{Load impedance angle.}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

The general expression for the o/p current can

be written as

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + A e^{\frac{-R}{L}t}$$

To find the value of the constant 'A' apply the initial conditions at $\omega t = \alpha$, load current $i_o = 0$, Equating the general expression for the load current to zero at $\omega t = \alpha$, we get

$$i_o = 0 = \frac{V_m}{Z} \sin(\alpha - \phi) - \frac{E}{R} + A e^{\frac{-R}{L} \times \frac{\alpha}{\omega}}$$

We obtain the value of constant 'A' as

$$A = \left[\frac{E}{R} - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{\frac{R}{\omega L} \alpha}$$

Substituting the value of the constant 'A' in the expression for the load current; we get the complete expression for the output load current as

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + \left[\frac{E}{R} - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{\frac{-R}{\omega L}(\omega t - \alpha)}$$

To Derive
An
Expression For The Average
Or
DC Load Voltage

$$V_{O(dc)} = \frac{1}{2\pi} \int_0^{2\pi} v_O \cdot d(\omega t)$$

$$V_{O(dc)} = \frac{1}{2\pi} \left[\int_0^{\alpha} v_O \cdot d(\omega t) + \int_{\alpha}^{\beta} v_O \cdot d(\omega t) + \int_{\beta}^{2\pi} v_O \cdot d(\omega t) \right]$$

$v_O = V_m \sin \omega t =$ Output load voltage for $\omega t = \alpha$ to β

$v_O = E$ for $\omega t = 0$ to α & for $\omega t = \beta$ to 2π

$$V_{O(dc)} = \frac{1}{2\pi} \left[\int_0^{\alpha} E \cdot d(\omega t) + \int_{\alpha}^{\beta} V_m \sin \omega t + \int_{\beta}^{2\pi} E \cdot d(\omega t) \right]$$

$$V_{O(dc)} = \frac{1}{2\pi} \left[E(\omega t) \Big|_0^\alpha + V_m (-\cos \omega t) \Big|_\alpha^\beta + E(\omega t) \Big|_\beta^{2\pi} \right]$$

$$V_{O(dc)} = \frac{1}{2\pi} \left[E(\alpha - 0) - V_m (\cos \beta - \cos \alpha) + E(2\pi - \beta) \right]$$

$$V_{O(dc)} = \frac{V_m}{2\pi} [\cos \alpha - \cos \beta] + \frac{E}{2\pi} [(2\pi - \beta + \alpha)]$$


$$V_{O(dc)} = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta) + \left[\frac{2\pi - (\beta - \alpha)}{2\pi} \right] E$$

Conduction angle of thyristor $\delta = (\beta - \alpha)$

RMS Output Voltage can be calculated
by using the expression


$$V_{O(RMS)} = \sqrt{\frac{1}{2\pi} \left[\int_0^{2\pi} v_o^2 \cdot d(\omega t) \right]}$$

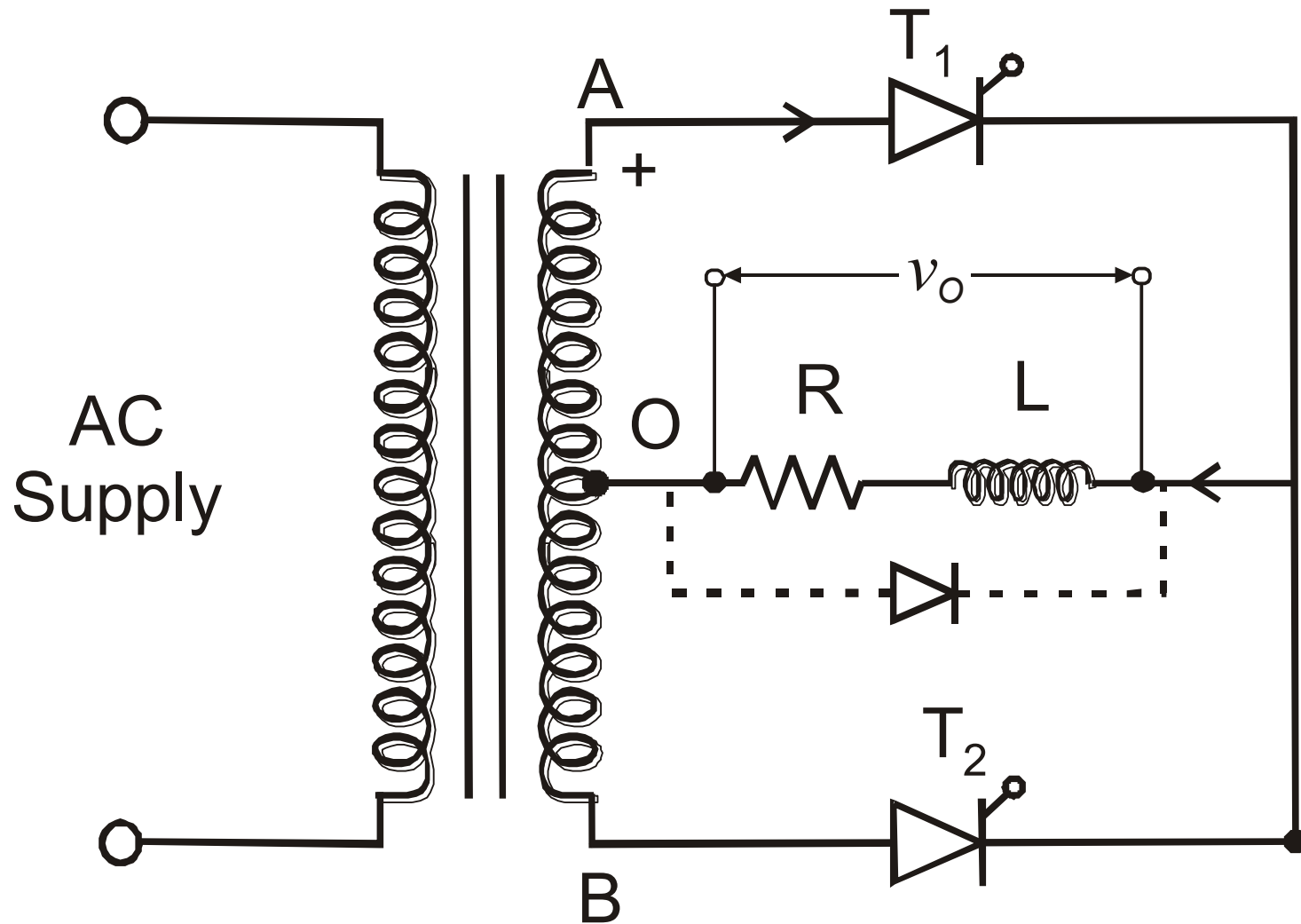Single Phase
Full Wave Controlled Rectifier Using
A
Center Tapped Transformer



Discontinuous
Load Current Operation
without FWD
for

$$\pi < \beta < (\pi + \alpha)$$

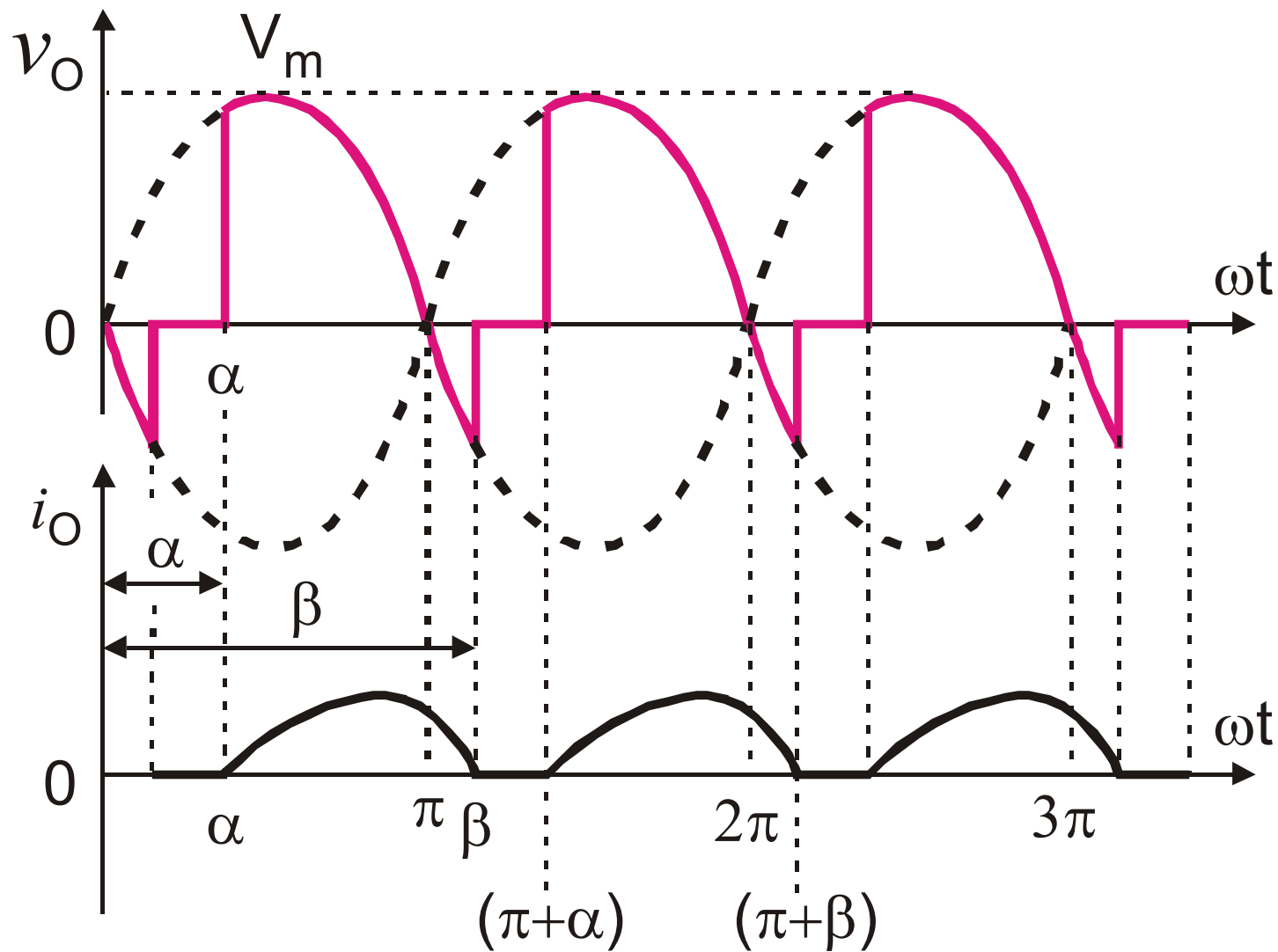

To Derive An Expression For
The Output
(Load) Current, During $\omega t = \alpha$ to β
When Thyristor T_1 Conducts

Assuming T_1 is triggered $\omega t = \alpha$,
we can write the equation,

$$L \left(\frac{di_o}{dt} \right) + Ri_o = V_m \sin \omega t ; \alpha \leq \omega t \leq \beta$$

General expression for the output current,

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-t}{\tau}}$$

$$V_m = \sqrt{2}V_s = \text{maximum supply voltage.}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load impedance.}$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = \text{Load impedance angle.}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

\therefore general expression for the output load current

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-R}{L} t}$$

Constant A_1 is calculated from

initial condition $i_o = 0$ at $\omega t = \alpha$; $t = \left(\frac{\alpha}{\omega} \right)$

$$i_o = 0 = \frac{V_m}{Z} \sin(\alpha - \phi) + A_1 e^{\frac{-R}{L} t}$$

$$\therefore A_1 e^{\frac{-R}{L} t} = \frac{-V_m}{Z} \sin(\alpha - \phi)$$

We get the value of constant A_1 as

$$A_1 = e^{\frac{R(\alpha)}{\omega L}} \left[\frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

Substituting the value of constant A_1 in the general expression for i_o

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + e^{\frac{-R}{\omega L}(\omega t - \alpha)} \left[\frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

\therefore we obtain the final expression for the inductive load current

$$i_o = \frac{V_m}{Z} \left[\sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right];$$

Where $\alpha \leq \omega t \leq \beta$


Extinction angle β can be calculated by using the condition that $i_o = 0$ at $\omega t = \beta$

$$i_o = \frac{V_m}{Z} \left[\sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right] = 0$$

$$\therefore \sin(\beta - \phi) = e^{\frac{-R}{\omega L}(\beta - \alpha)} \times \sin(\alpha - \phi)$$

β can be calculated by solving the above eqn.

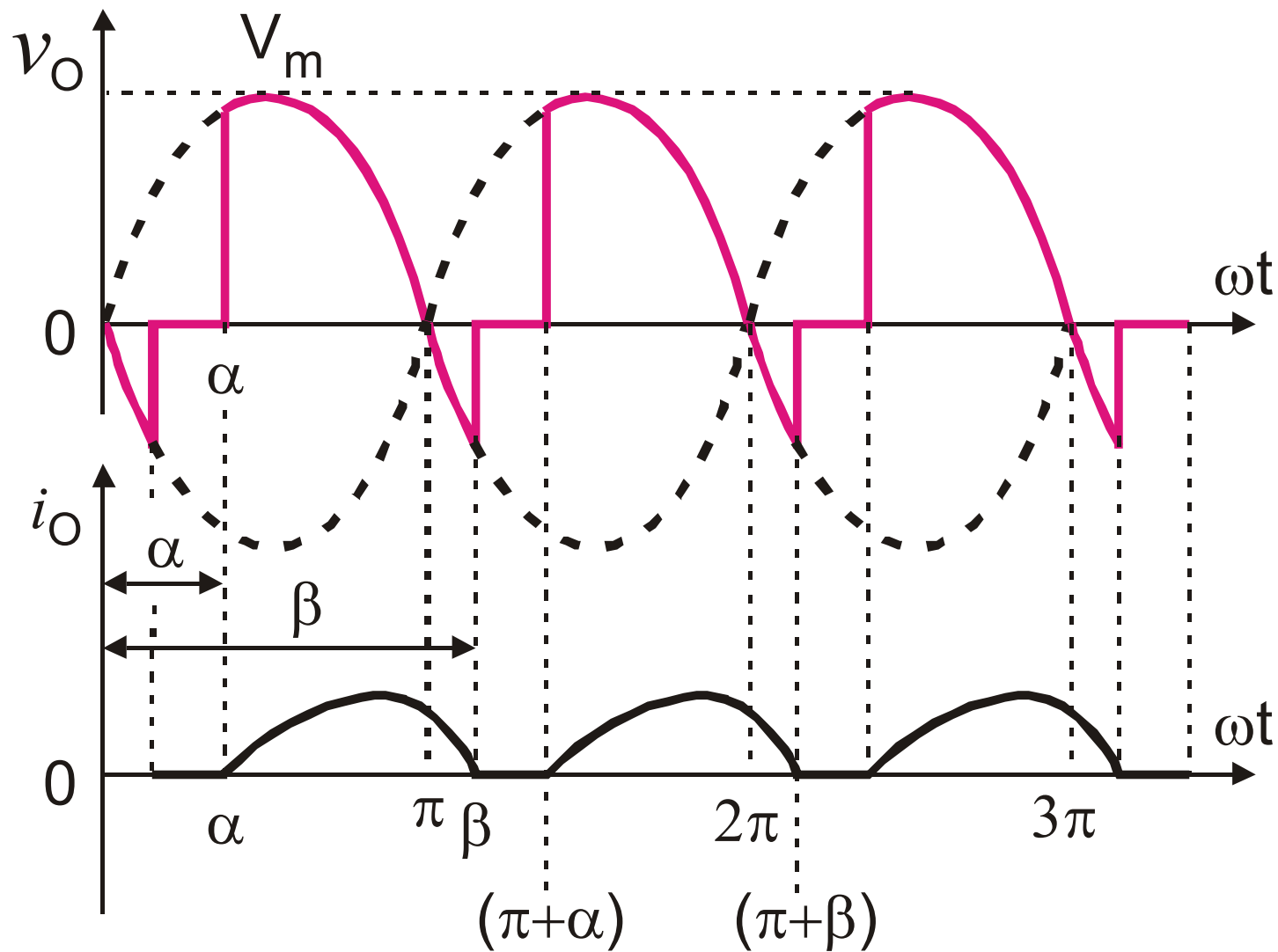To Derive An Expression For The DC Output
Voltage Of
A Single Phase Full Wave Controlled Rectifier
With RL Load
(Without FWD)



$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t = \alpha}^{\beta} v_o . d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \left[\int_{\alpha}^{\beta} V_m \sin \omega t . d(\omega t) \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[-\cos \omega t \Big/_{\alpha}^{\beta} \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} (\cos \alpha - \cos \beta)$$

When the load inductance is negligible(i.e., $L \approx 0$)

Extinction angle $\beta = \pi$ radians

Hence the average or dc output voltage for R load

$$V_{O(dc)} = \frac{V_m}{\pi} (\cos \alpha - \cos \pi)$$


$$V_{O(dc)} = \frac{V_m}{\pi} (\cos \alpha - (-1))$$

$$V_{O(dc)} = \frac{V_m}{\pi} (1 + \cos \alpha); \text{ for R load, when } \beta = \pi$$

To calculate the RMS output voltage we use the expression

$$V_{O(RMS)} = \sqrt{\frac{1}{\pi} \left[\int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t . d(\omega t) \right]}$$

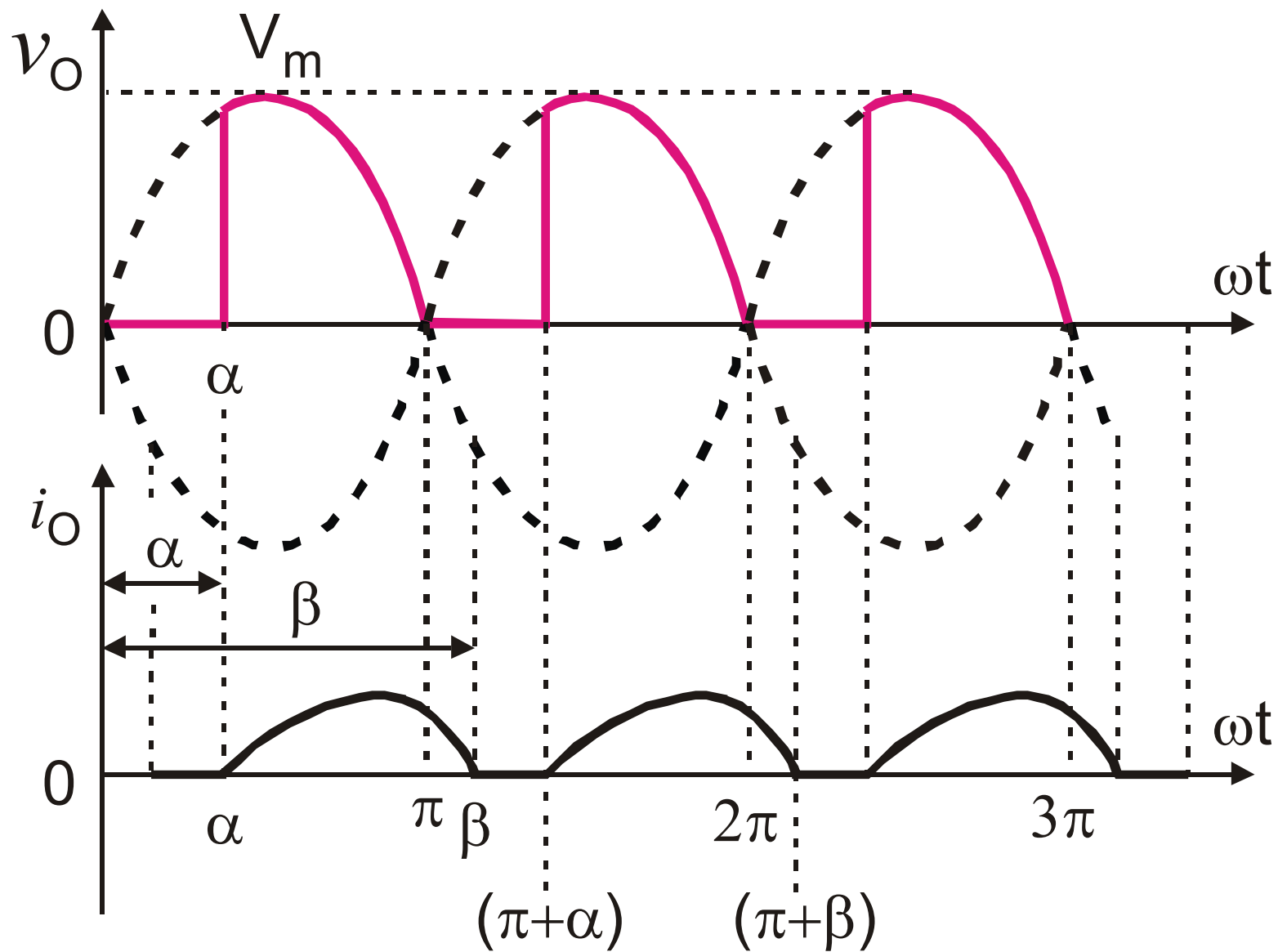Discontinuous Load Current Operation with FWD



Thyristor T_1 is triggered at $\omega t = \alpha$;

T_1 conducts from $\omega t = \alpha$ to π

Thyristor T_2 is triggered at $\omega t = (\pi + \alpha)$;

T_2 conducts from $\omega t = (\pi + \alpha)$ to 2π

FWD conducts from $\omega t = \pi$ to β &

$v_o \approx 0$ during discontinuous load current.

To Derive an Expression
For The
DC Output Voltage For
A
Single Phase Full Wave Controlled
Rectifier
With RL Load & FWD

$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t=0}^{\pi} v_o . d(\omega t)$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t . d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[-\cos \omega t \Big/_{\alpha}^{\pi} \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[-\cos \pi + \cos \alpha \right] \quad ; \quad \cos \pi = -1$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

- The load current is discontinuous for low values of load inductance and for large values of trigger angles.
- For large values of load inductance the load current flows continuously without falling to zero.
- Generally the load current is continuous for large load inductance and for low trigger angles.