
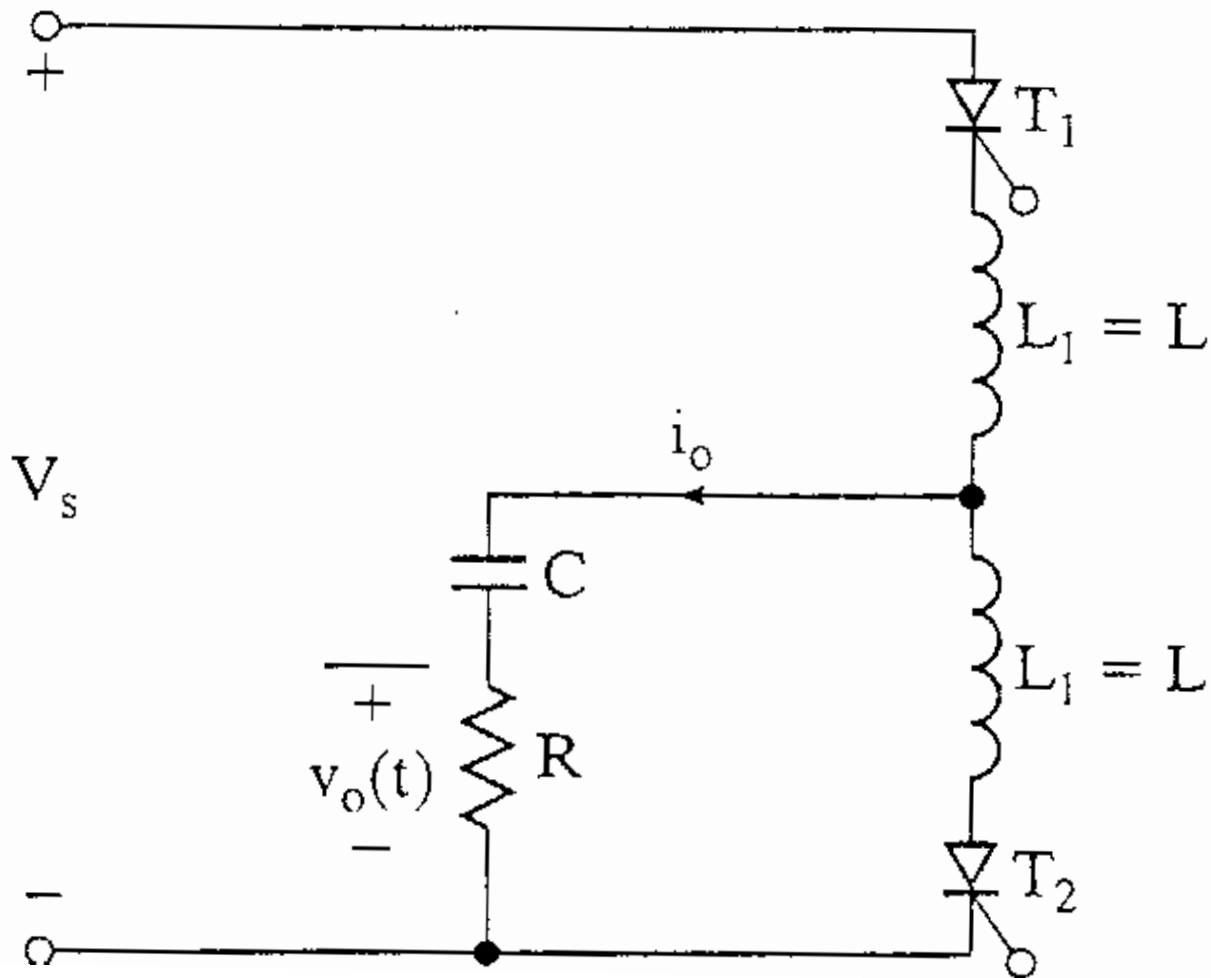


Series-Resonant Inverter

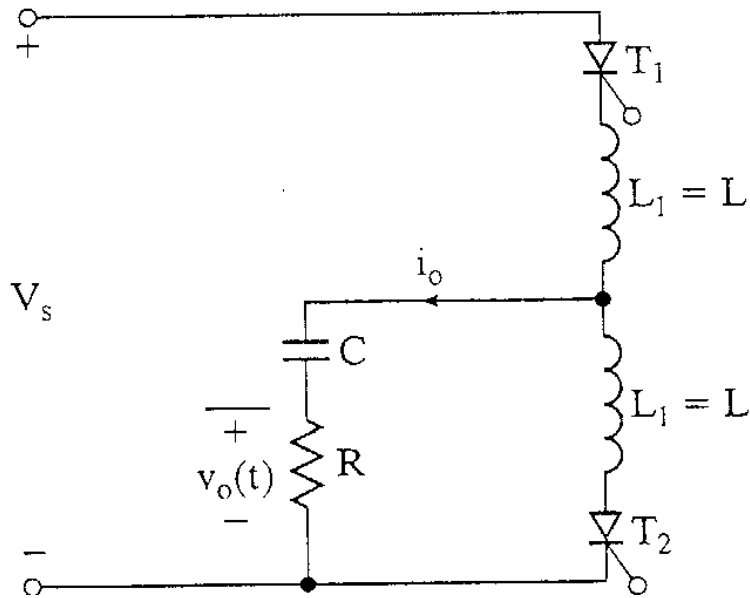

Operation




T_1 fired, resonant pulse of current flows through the load. The current falls to zero at $t = t_{1m}$ and T_1 is “self-commutated”.

T_2 fired, reverse resonant current flows through the load and T_2 is also “self-commutated”.

The series resonant circuit must be underdamped,

$$R^2 < (4L/C)$$

Operation in Mode 1 – Fire T_1

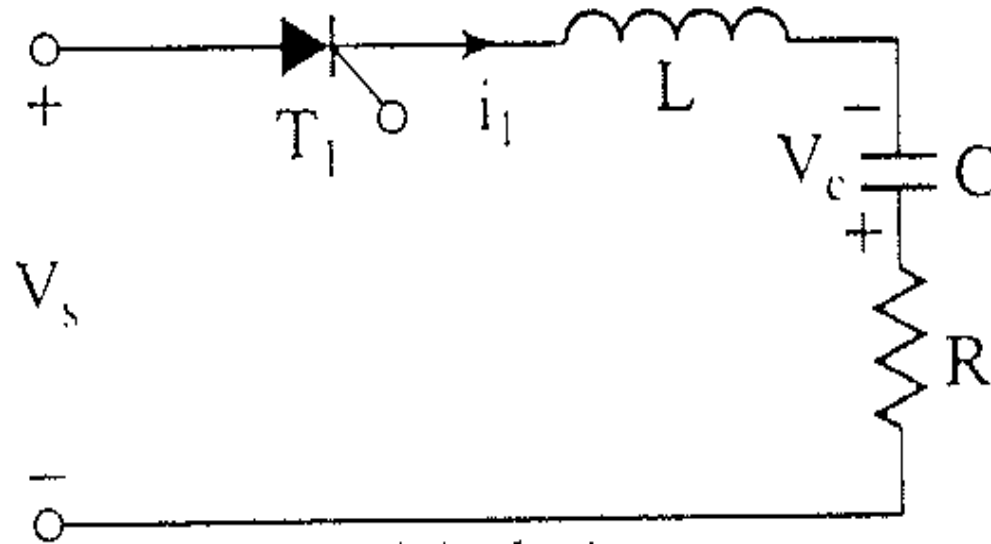

$$L \frac{di_1}{dt} + Ri_1 + \frac{1}{C} \int i_1 dt + v_c(0) = V_s$$

$$i_1(0) = 0$$

$$v_c(0) = -V_c$$

$$i_1(t) = A_1 e^{-\frac{R}{2L}t} \sin \omega_r t$$

$$\omega_r = \left(\frac{1}{LC} - \frac{R^2}{4L^2} \right)^{\frac{1}{2}}$$

$$\left. \frac{di_1}{dt} \right|_{t=0} = \frac{V_s + V_c}{\omega_r L} = A_1$$

$$i_1(t) = \frac{V_s + V_c}{\omega_r L} e^{-\alpha t} \sin \omega_r t$$

$$\alpha = \frac{R}{2L}$$

To find the time when the current is maximum, set the first derivative = 0

$$\frac{di_1}{dt} = 0$$

$$\left(\frac{V_s + V_c}{\omega_r L} \right) \left(-\alpha e^{-\alpha t} \sin \omega_r t + \omega_r e^{-\alpha t} \cos \omega_r t \right) = 0$$

.....

$$\frac{\omega_r}{\alpha} = \tan \omega_r t_m$$

$$\tan^{-1} \frac{\omega_r t_m}{\alpha} = \omega_r t_m$$

$$t_m = \frac{1}{\omega_r} \tan^{-1} \frac{\omega_r}{\alpha}$$

To find the capacitor voltage, integrate the current

$$v_{C_1}(t) = \frac{1}{C} \int_0^t i_1(t) dt - V_c$$


$$v_{C_1}(t) = \frac{1}{C} \int_0^t \left(\frac{V_s + V_c}{\omega_r L} \right) \left(e^{-\alpha t} \sin \omega_r t \right) dt - V_c$$

...


$$v_{C_1}(t) = -(V_s + V_c) e^{-\alpha t} (\alpha \sin \omega_r t + \omega_r \cos \omega_r t) / \omega_r + V_s$$

$$0 \leq t \leq t_{1m} \left(\frac{\pi}{\omega_r} \right) \longleftarrow \text{The current } i_1 \text{ becomes } = 0 \text{ @ } t=t_{1m}$$
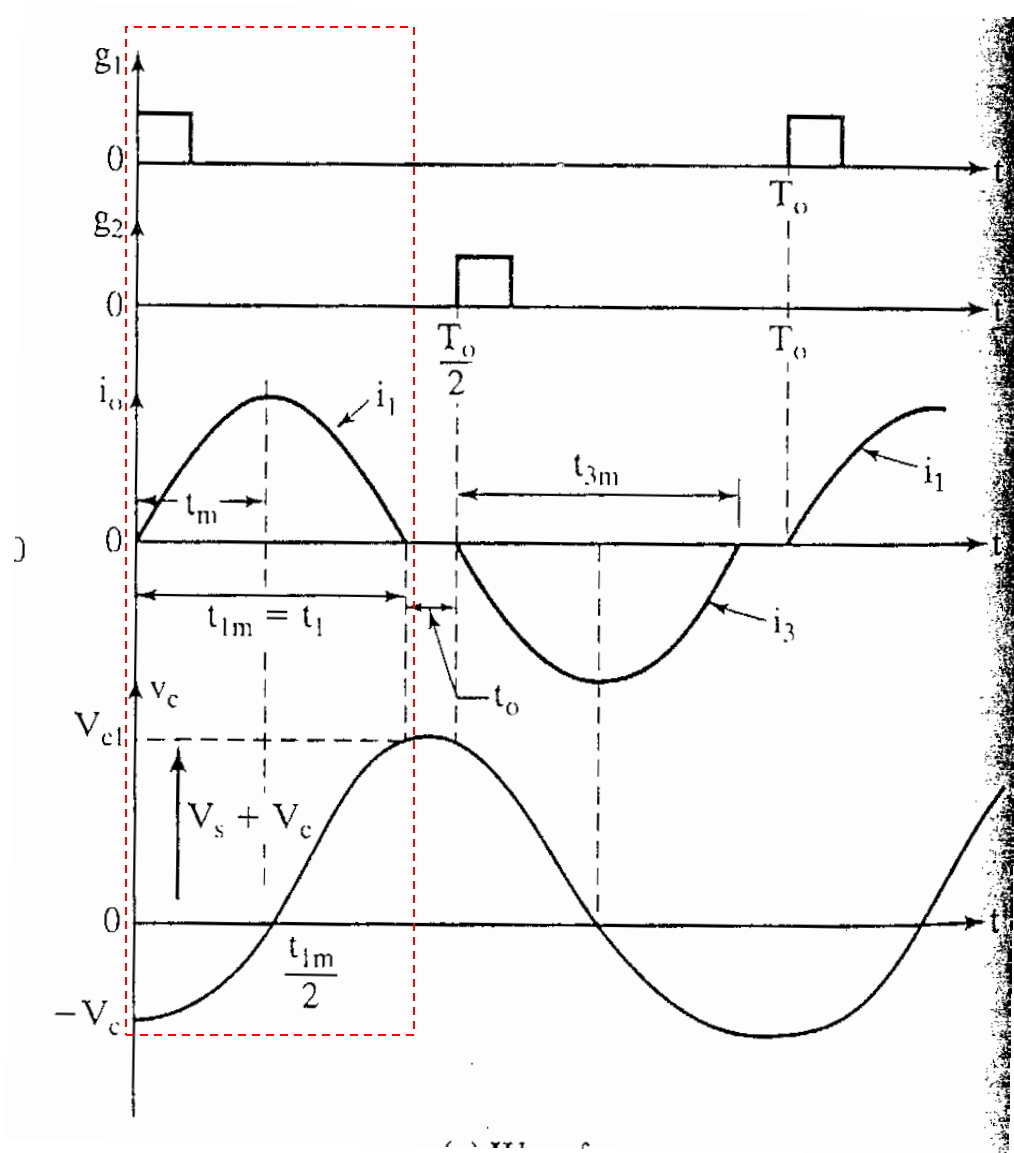
$$v_{C_1}(t_{1m}) = V_{C1} = (V_s + V_c) e^{-\frac{\alpha \pi}{\omega_r}} + V_s$$




Operation in Mode 2 – T_1, T_2 Both OFF

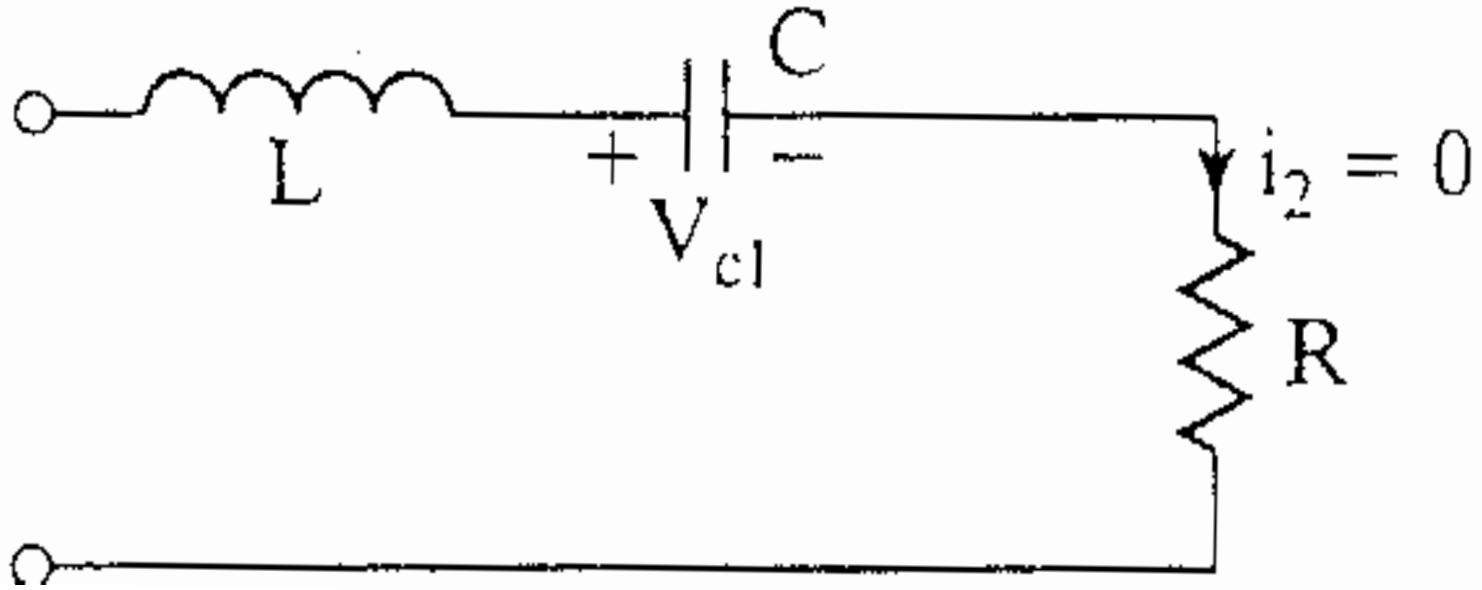


$$i_2(t) = 0$$

$$v_{C_2}(t) = V_{C_1}$$

$$v_{C_2}(t_{2_m}) = V_{C_2} = V_{C_1}$$

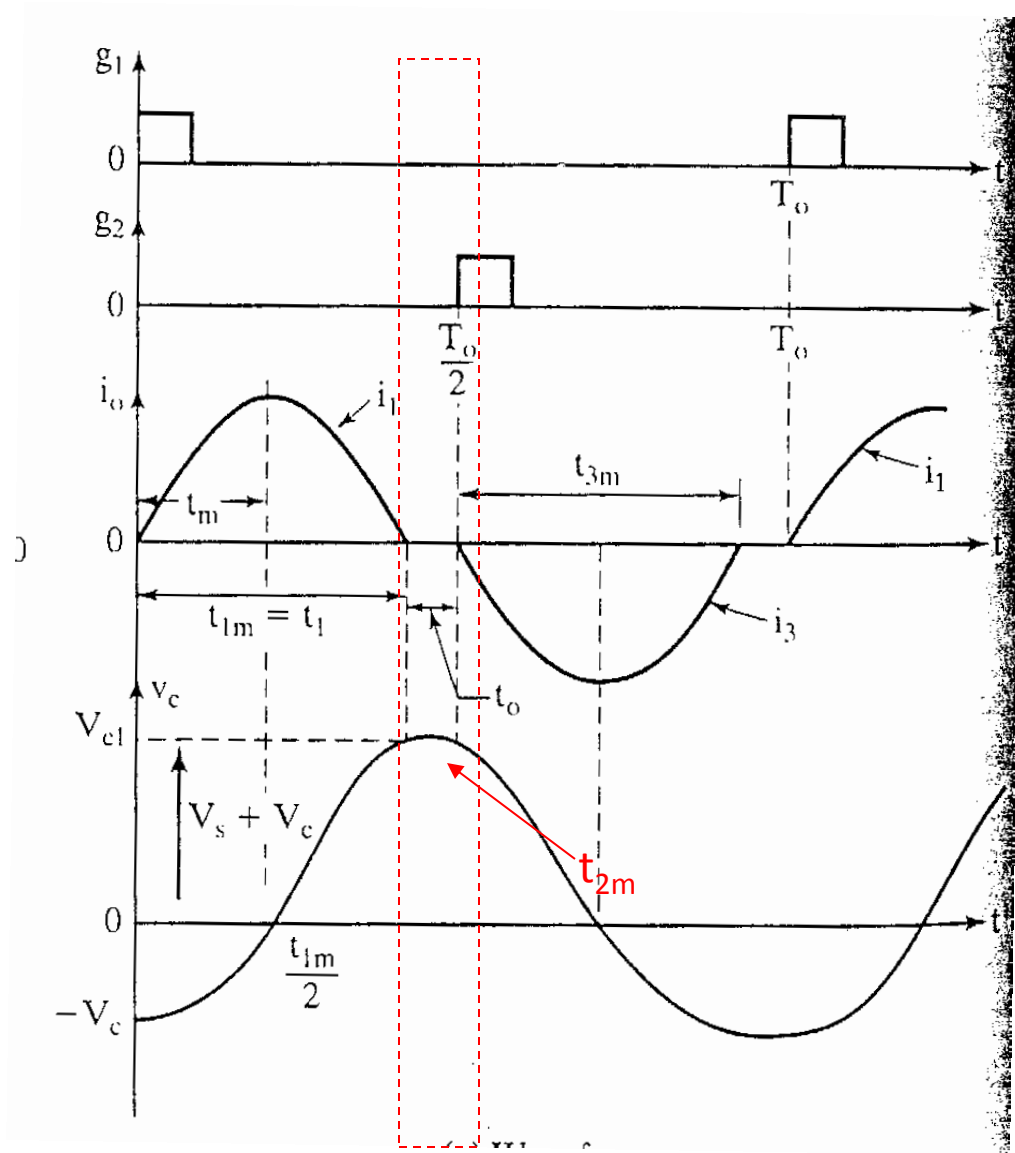

Operation in Mode 3 – Fire T_2

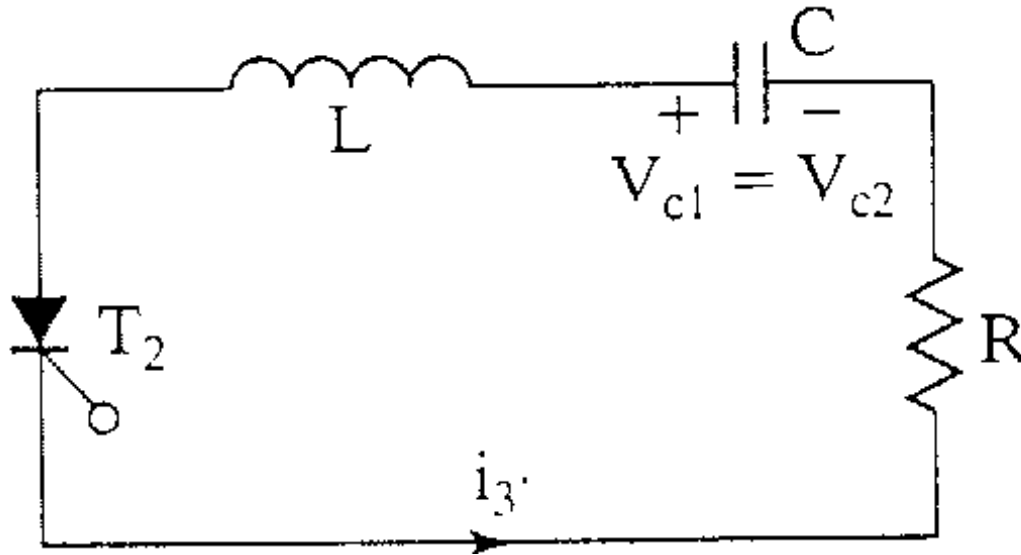

$$L \frac{di_3}{dt} + Ri_3 + \frac{1}{C} \int i_3 dt + v_{C_3}(0) = 0$$

$$i_3(0) = 0$$

$$v_{C_3}(0) = -V_{C_2} = -V_{C_1}$$

$$i_3(t) = \frac{V_{C_1}}{\omega_r L} e^{-\alpha t} \sin \omega_r t$$

$$v_{C_3}(t) = \frac{1}{C} \int_0^t i_3 dt - V_{C_1}$$

$$v_{C_3}(t) = \frac{-V_{C_1} e^{-\alpha t} (\alpha \sin \omega_r t + \omega_r \cos \omega_r t)}{\omega_r}$$

$$0 \leq t \leq t_{3m} \left(\frac{\pi}{\omega_r} \right)$$

$$v_{C_3}(t_{3_m}) = V_{C_3} = V_C = V_{C_1} e^{-\alpha \frac{\pi}{\omega_r}}$$

$$v_{C_1}(t_{1_m}) = V_{C_1} = (V_S + V_C) e^{-\alpha \frac{\pi}{\omega_r}} + V_S$$


.

.


$$V_C = V_S \frac{1}{e^z - 1}$$

$$V_{C_1} = V_S \frac{e^z}{e^z - 1}$$


$$V_C + V_S = V_{C_1}$$

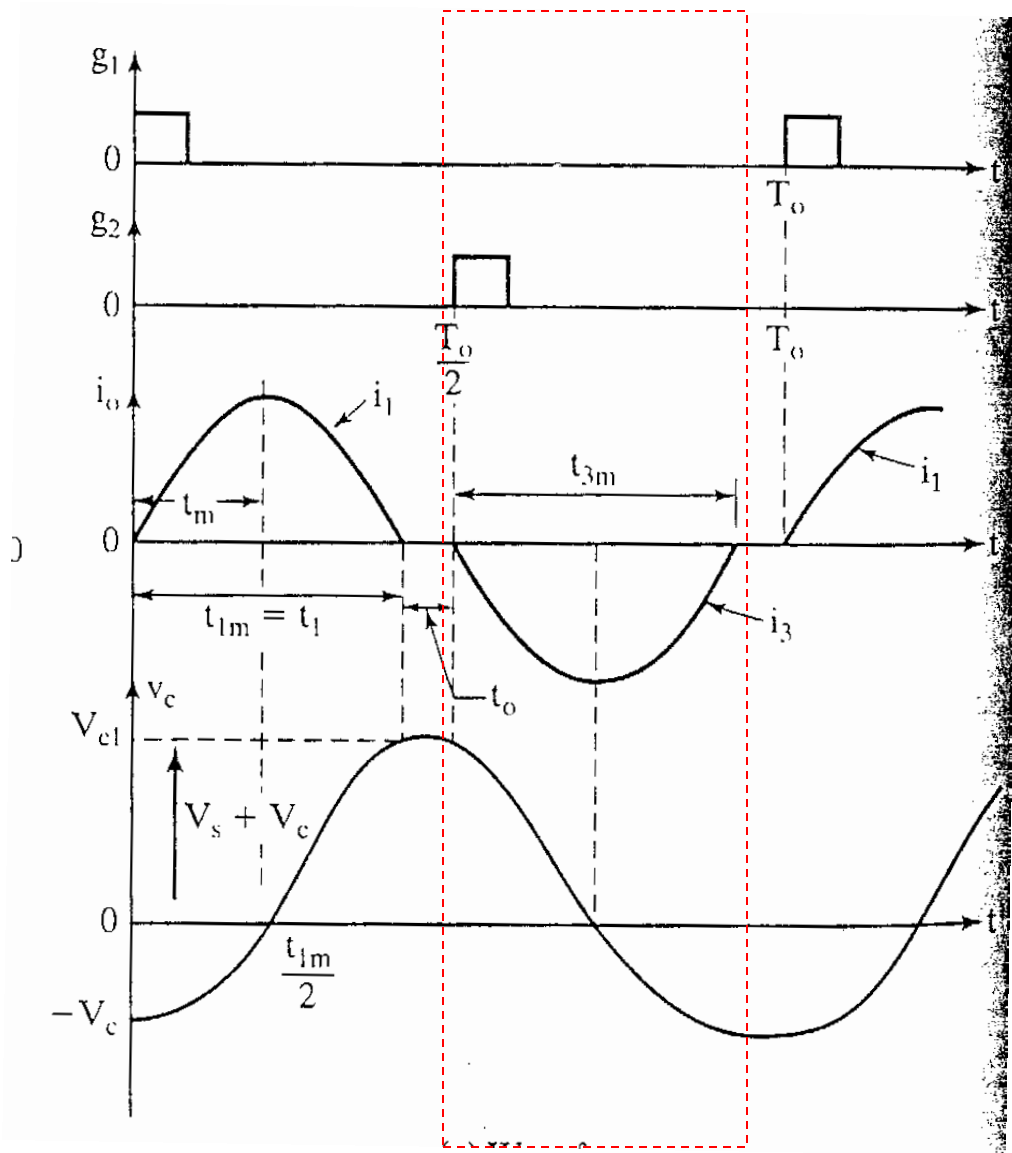

Summary -- Series Resonant Inverter

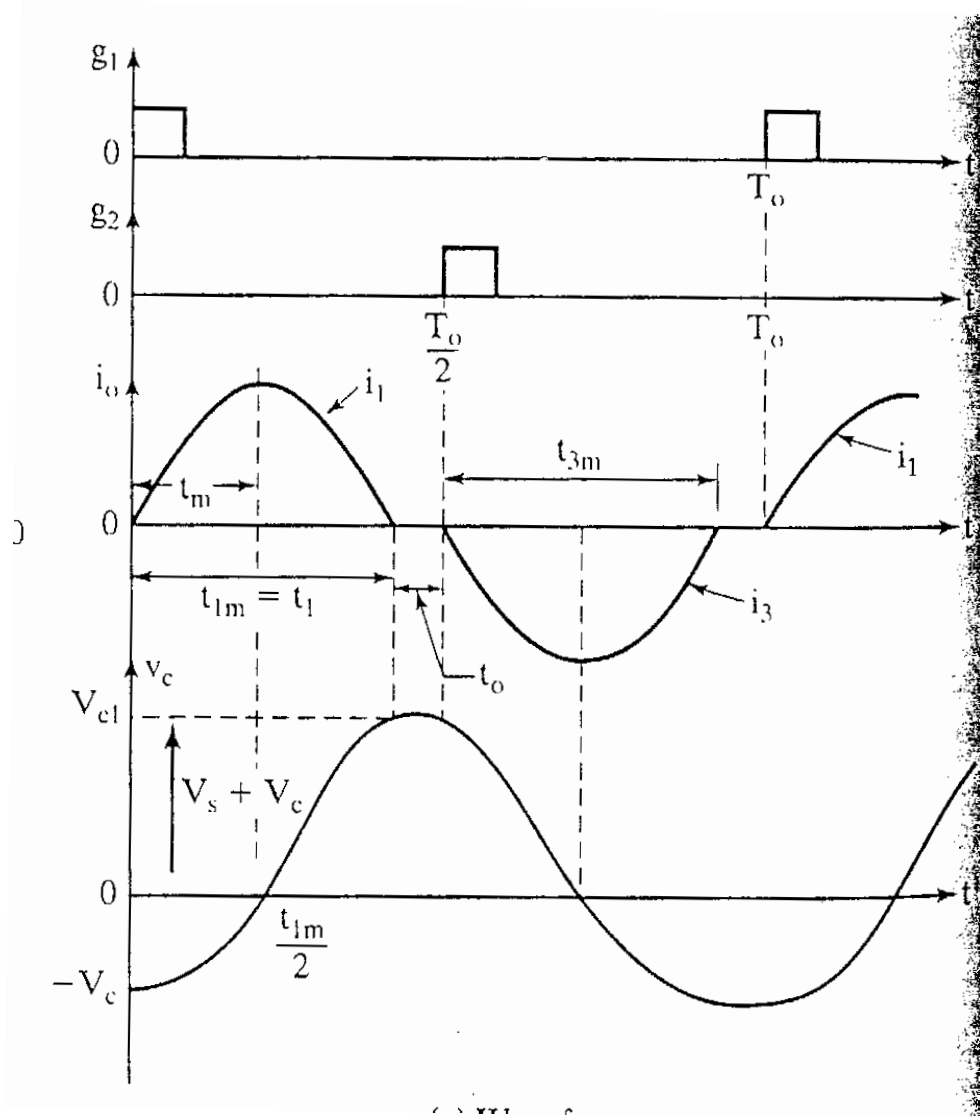

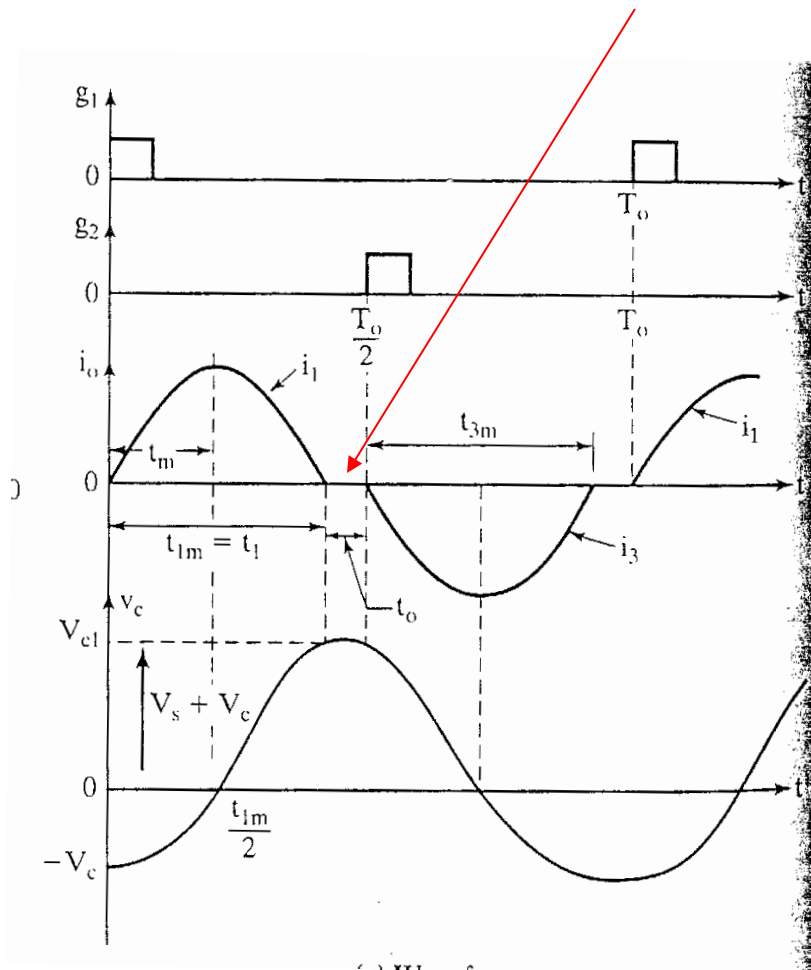To avoid a short-circuit across the main dc supply, T_1 must be turned OFF before T_2 is turned ON, resulting in a “dead zone”.




This “off-time” must be longer than the turn-off time of the thyristors, t_q .

$$\frac{\pi}{\omega_0} - \frac{\pi}{\omega_r} = t_{off} > t_q$$


The maximum possible output frequency is

$$f_0 \leq f_{max} = \frac{1}{2\pi \left(t_q + \frac{\pi}{\omega_r} \right)}$$

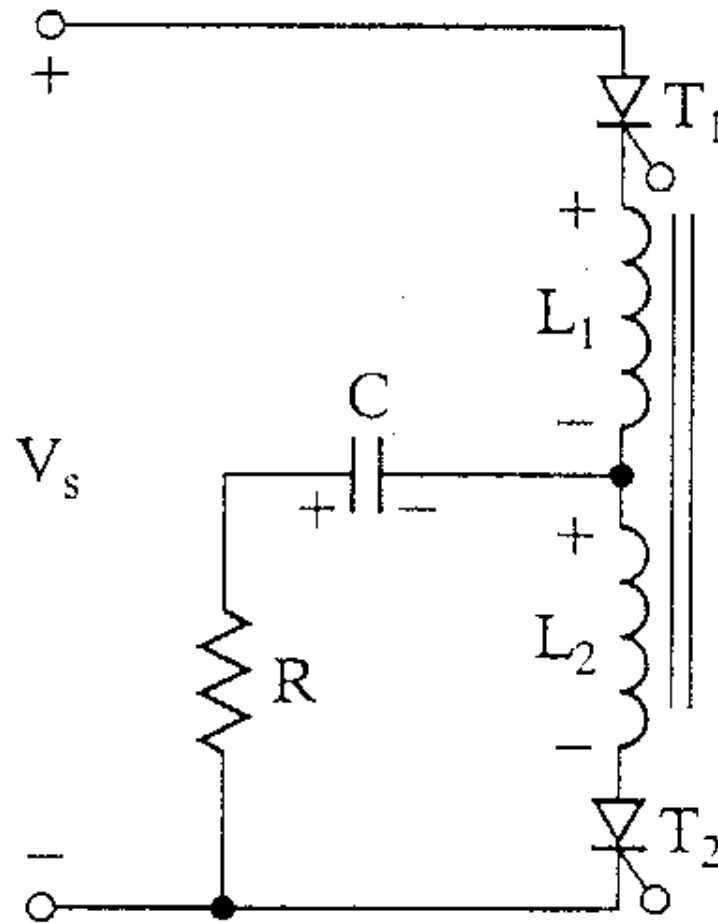Series Resonant Inverter Coupled Inductors



Improvement in performance

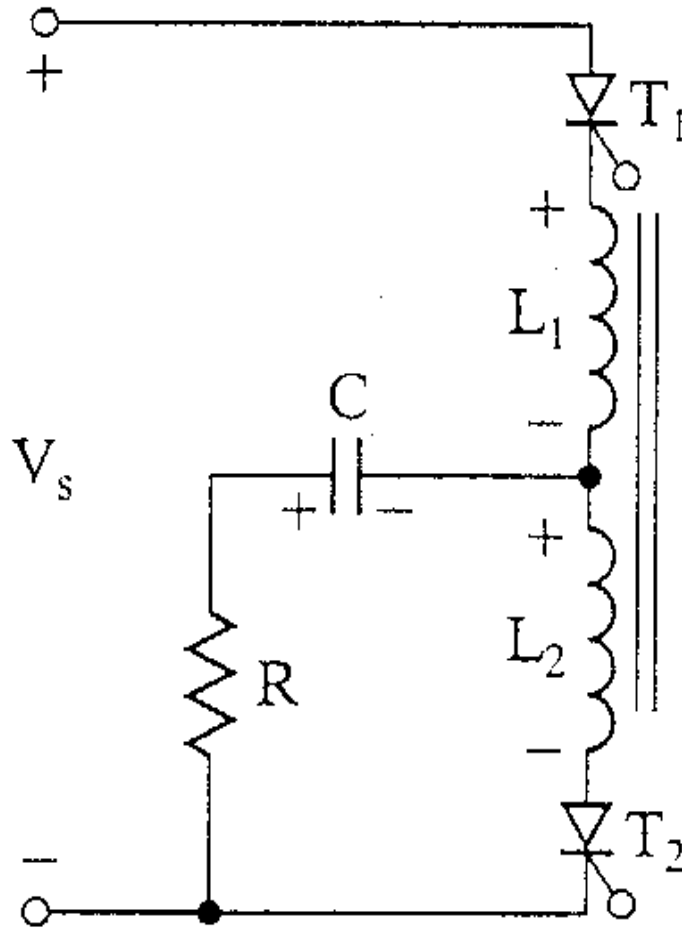

- When T_1 turned ON, voltage @ L_1 is as shown, voltage @ L_2 in same direction, adding to the voltage @ C
- This turns T_2 OFF before the load current falls to 0.