

# Lecture-1

Frequency Response of BJT  
Amplifiers

# The Decibel (dB)

- A logarithmic measurement of the ration of power or voltage
- Power gain is expressed in dB by the formula:

$$A_P = 10 \log a_P$$


where  $a_p$  is the actual power gain,  $P_{out}/P_{in}$

Voltage gain is expressed by:

$$A_{V(dB)} = 20 \log a_v$$

- If  $a_v$  is greater than 1, the dB is +ve, and if  $a_v$  is less than 1, the dB gain is -ve value & usually called *attenuation*

# Amplifier gain vs frequency

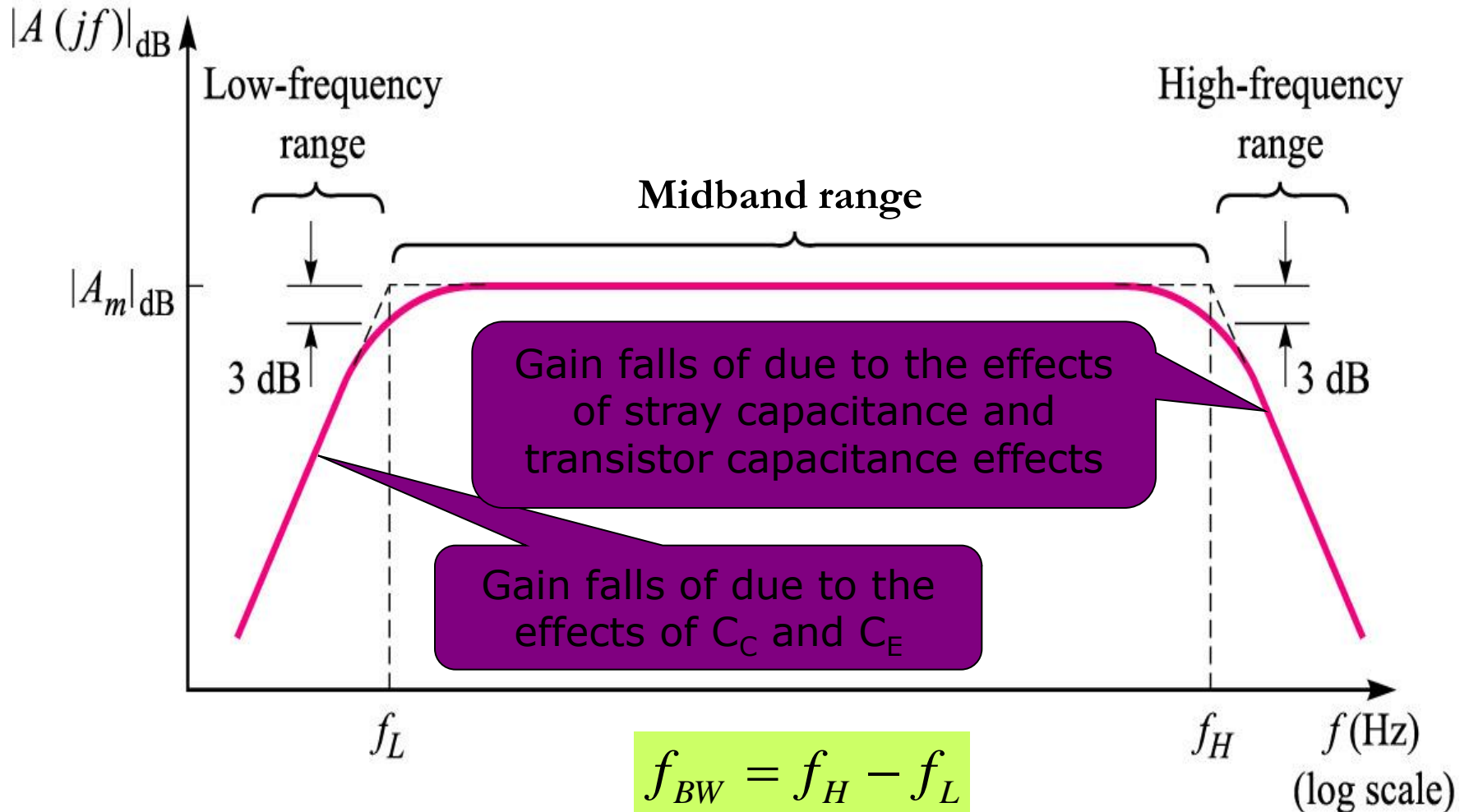

# Definition

- Frequency response of an amplifier is the graph of its *gain versus the frequency*.
- *Cutoff frequencies* : the frequencies at which the voltage gain equals 0.707 of its maximum value.
- *Midband* : the band of frequencies between  $10f_L$  and  $0.1f_H$  where the voltage gain is maximum. The region where coupling & bypass capacitors act as short circuits and the stray capacitance and transistor capacitance effects act as open circuits.
- *Bandwidth* : the band between upper and lower cutoff frequencies
- Outside the midband, the voltage gain can be determined by these equations:

$$A = \frac{A_{mid}}{\sqrt{1 + (f_1 / f)^2}}$$

Below midband

$$A = \frac{A_{mid}}{\sqrt{1 + (f / f_2)^2}}$$

Above midband

# Lower & Upper Critical frequency

- ❑ Critical frequency a.k.a the cutoff frequency
- ❑ The frequency at which output **power** drops by **3 dB**. [in real number, **0.5** of it's midrange value.
- ❑ An output **voltage** drop of **3dB** represents about a **0.707** drop from the midrange value in real number.
- ❑ Power is often measured in units of dBm. This is decibels with reference to 1mW of power. [0 dBm = 1mW], where;

$$10\log\left(\frac{1\text{mW}}{1\text{mW}}\right) = 0\text{dBm}.$$

# Gain & frequencies

- *Gain-bandwidth product* : constant value of the product of the voltage gain and the bandwidth.
- *Unity-gain frequency* : the frequency at which the amplifier's gain is 1

$$f_T = A_{mid} BW$$

# LOW FREQUENCY

- At low frequency range, the gain falloff due to coupling capacitors and bypass capacitors.
- As signal frequency ↓↓, the reactance of the coupling capacitor,  $X_C$  ↑↑ - no longer behave as short circuits.