

# Lecture-2

Common Emitter, RC Coupled and  
Common Source Amplifier

# Short-circuit time-constant method (SCTC)

- To determine the **lower-cutoff frequency** having  $n$  coupling and bypass capacitors:

$$\omega_L \cong \sum_{i=1}^n \frac{1}{R_{iS} C_i}$$

$R_{iS}$  = resistance at the terminals of the  $i$ th capacitor  $C_i$  with all the other capacitors replaced by short circuits.

# Common-emitter Amplifier

Given :


Q-point values : 1.73 mA, 2.32 V

$\beta = 100, V_A = 75 \text{ V}$

Therefore,


$r_\pi = 1.45 \text{ k}\Omega$ ,

$r_o = 44.7 \text{ k}\Omega$

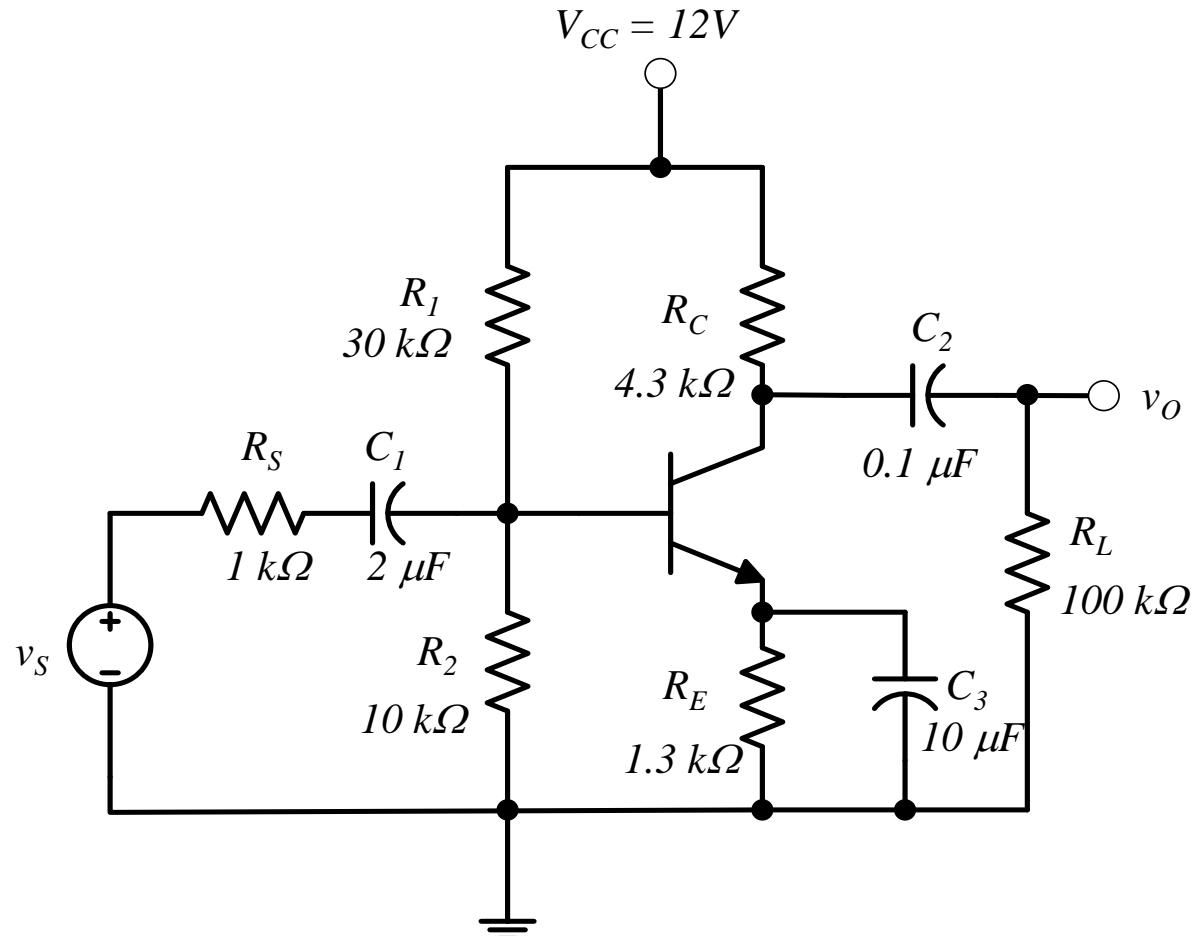


# Common-emitter Amplifier

- Low-frequency ac equivalent circuit

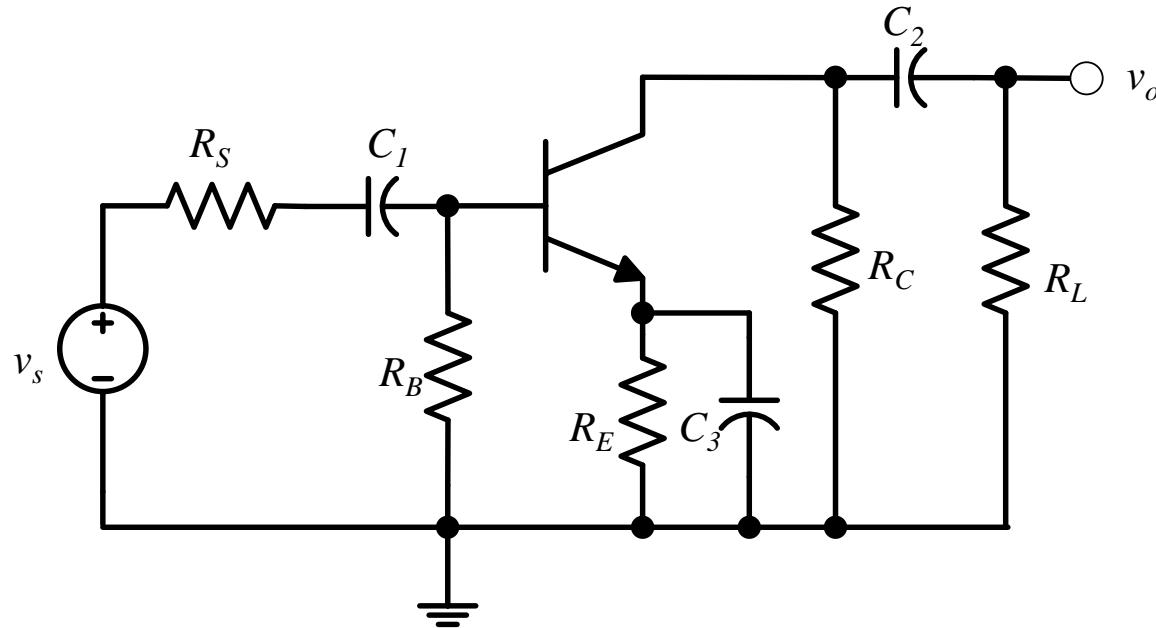

In the above circuit, there are **3 capacitors** (coupling plus bypass capacitors). Hence we need to find **3 resistances at the terminals** of the 3 capacitors in order to find the **lower cut-off frequency** of the amplifier circuit.

# Circuit for finding $R_{IS}$

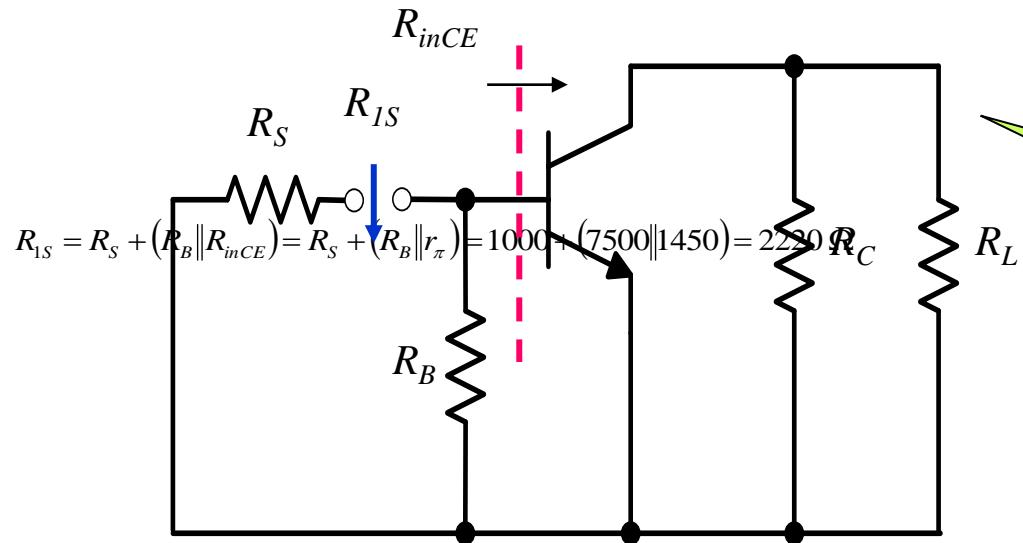

where


Replacing  $C_2$  and  $C_3$  by short circuits

$$\frac{1}{R_{IS} C_1} = \frac{1}{(2.22 k\Omega)(2.00 \mu F)} = 225 \text{ rad/s}$$
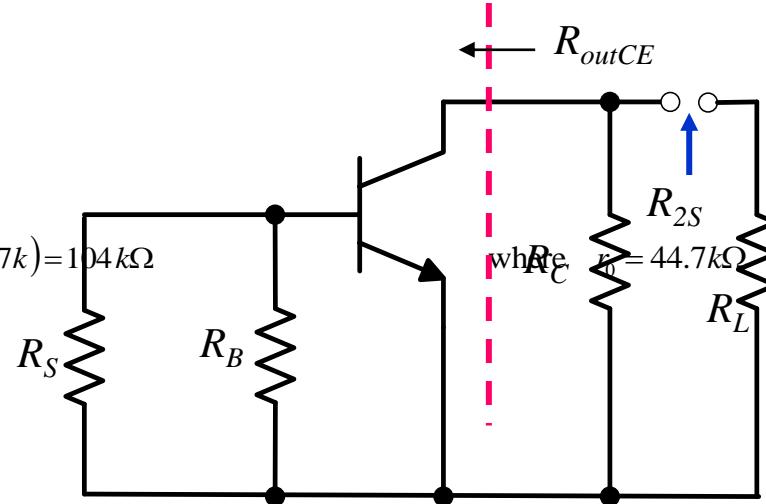
# Circuit for finding $R_{2S}$


$R_{2S} = R_L +$

Replacing  $C_1$  and  $C_3$  by short circuits



$$\frac{1}{R_{2S}C_2} = \frac{1}{(104\text{k}\Omega)(0.100\mu\text{F})} = 96.1 \text{ rad/s}$$

# Circuit for finding $R_{3S}$

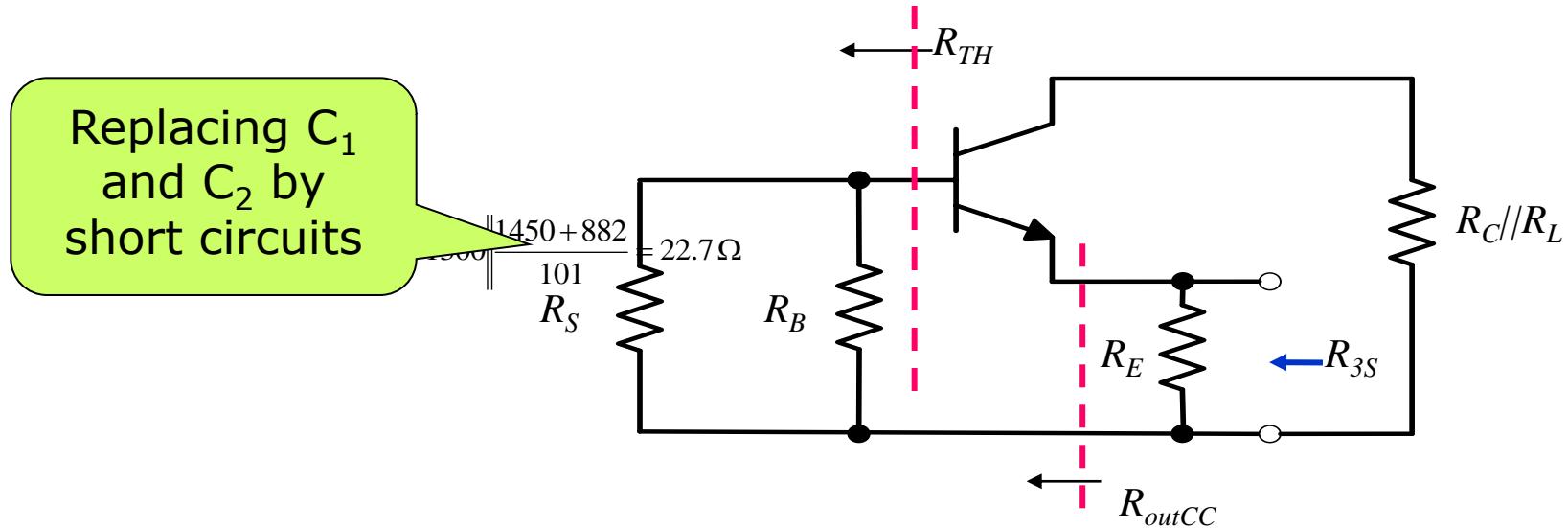


$$\frac{1}{R_{3S}C_3} = \frac{1}{(22.7\Omega)(10\mu F)} = 4410 \text{ rad/s}$$
$$R_{TH} = R_S \parallel R_B = 882\Omega$$

# Estimation of $\omega_L$

$$\omega_L \cong \sum_{i=1}^3 \frac{1}{R_{iS} C_i} = 225 + 96.1 + 4410 = 4730 \text{ rad/s}$$

$$f_L = \frac{\omega_L}{2\pi} = 753 \text{ Hz}$$

# Common-base Amplifier

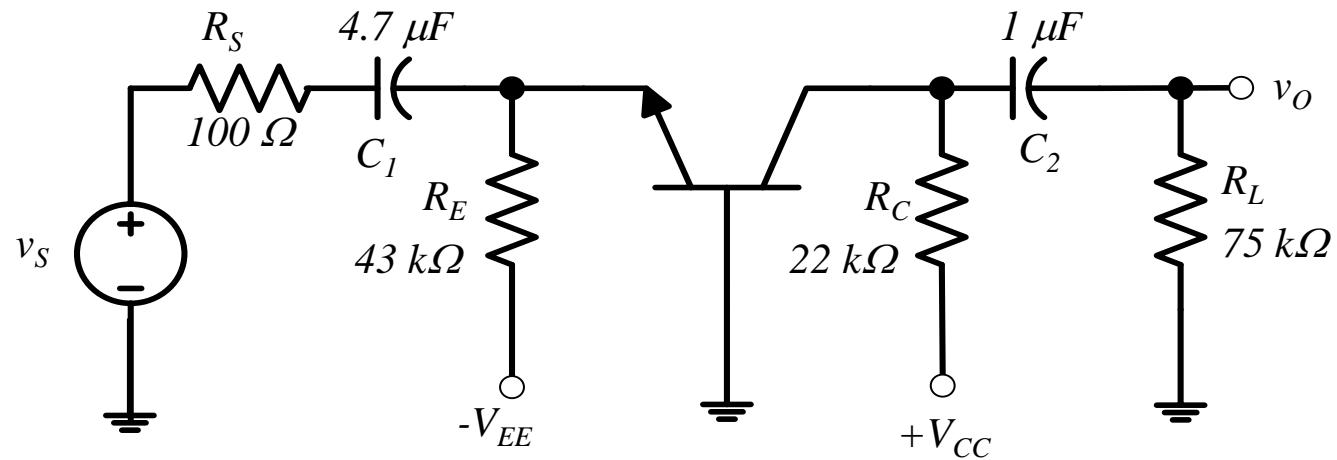

**Given :**

**Q-point values : 0.1**

**mA, 5 V**

**$\beta = 100, V_A = 70 \text{ V}$**


**Therefore,**

$$g_m = 3.85 \text{ mS}, r_o = 700 \text{ k}\Omega$$


$$r_\pi = 26 \Omega$$

# Common-base Amplifier

- Low-frequency ac equivalent circuit

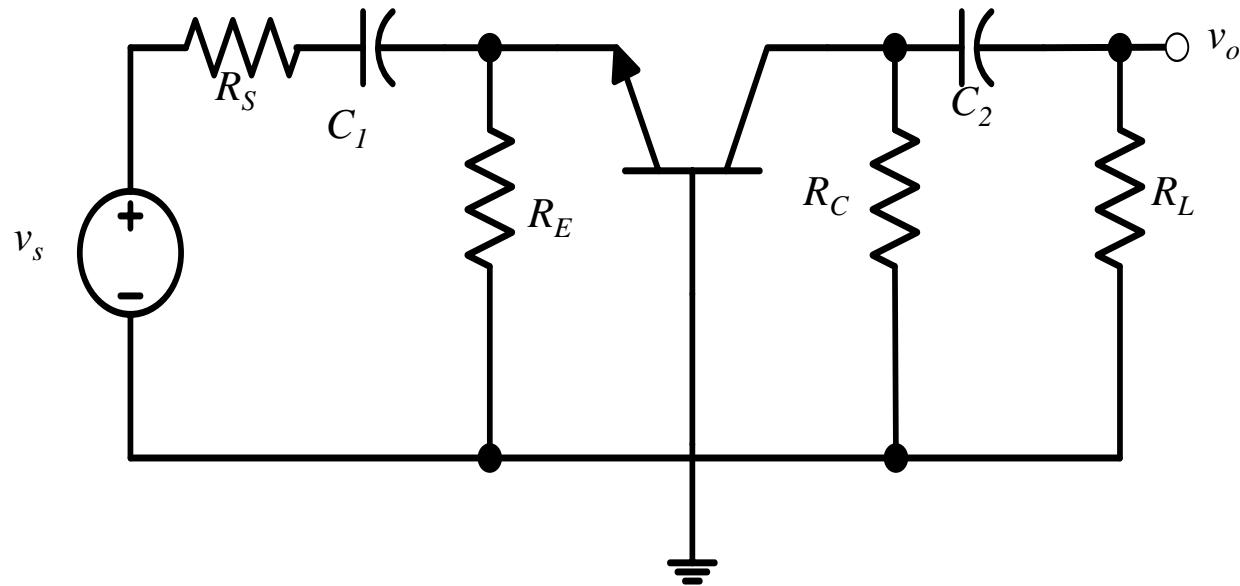

# Circuit for finding $R_{1S}$

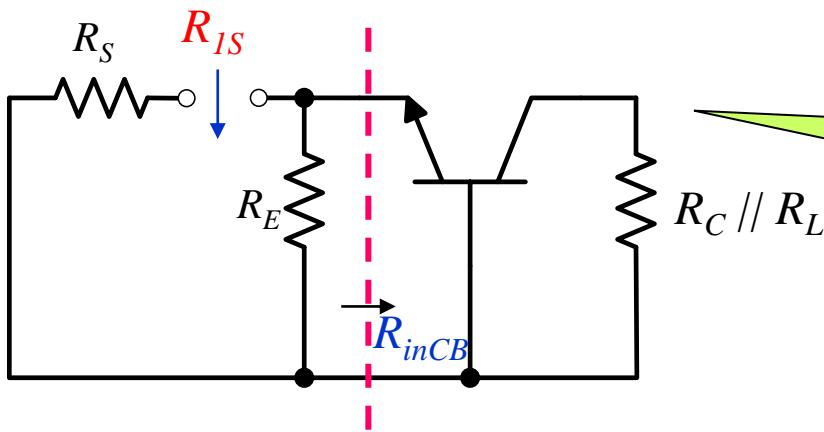


$$R_{1S} = R_S + (R_E \parallel R_{inCB}) \cong R_S + \left( R_E \left\| \frac{r_\pi}{1 + \beta} \right\| \right) = 100 + (4300 \parallel 0.26) \cong 100 \Omega$$

$$\frac{1}{R_{1S}C_1} = \frac{1}{(100\Omega)(4.7\mu F)} = 2.13 \times 10^{-3} \text{ rad/s}$$

# Circuit for finding $R_{2S}$

Replacing  $C_1$   
by short circuit

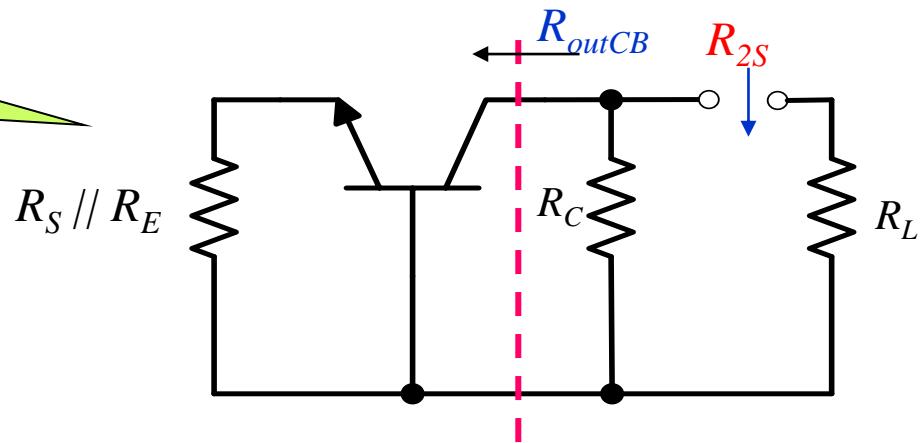

$$R_{2S} = R_L + (R_C \parallel R_{outCB}) \approx R_L + R_C = 75k + 22k = 97k\Omega$$


$$\frac{1}{R_{2S}C_2} = \frac{1}{(97k\Omega)(1\mu F)} = 10.309 \text{ rad/s}$$

# Estimation of $\omega_L$

$$\omega_L \cong \sum_{i=1}^2 \frac{1}{R_{iS} C_i} = 2.13 \times 10^{-3} + 10.309 \cong 10.309 \text{ rad/s}$$

$$f_L = \frac{\omega_L}{2\pi} = 1.64 \text{ Hz}$$

# Common-collector Amplifier

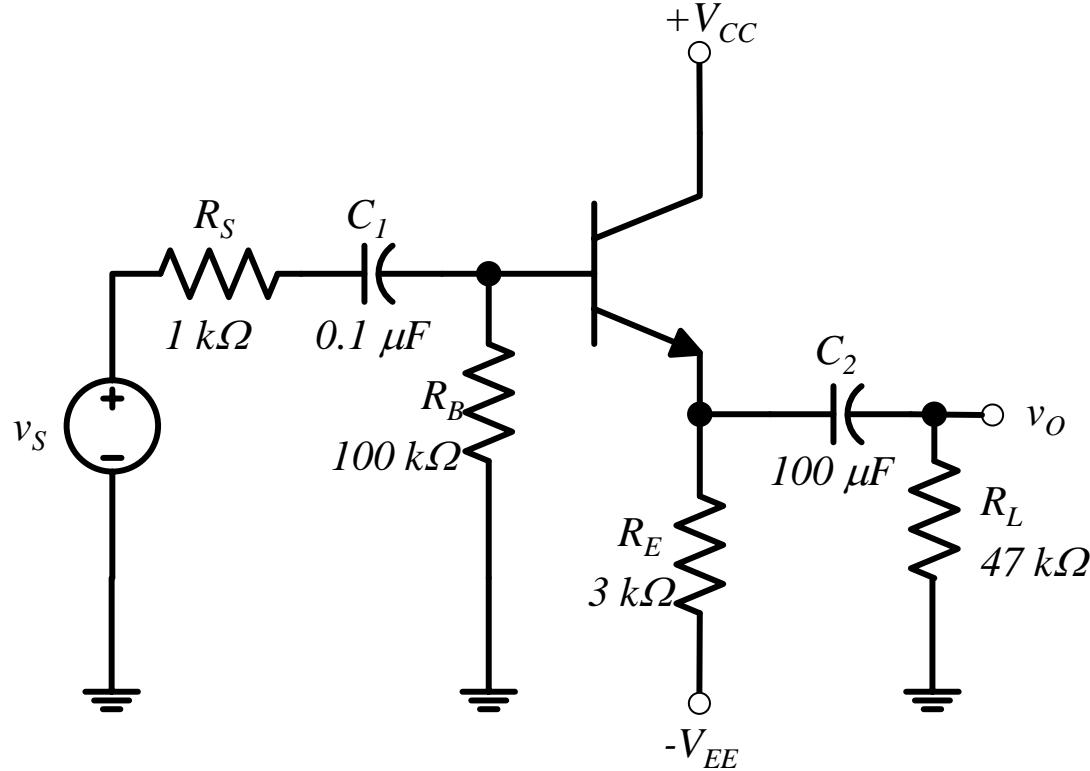

Given :

Q-point values : 1 mA, 5 V


$\beta = 100, V_A = 70$  V

Therefore,


$r_\pi = 2.6 k\Omega, r_o = 70 k\Omega$

# Common-collector Amplifier

- Low-frequency ac equivalent circuit

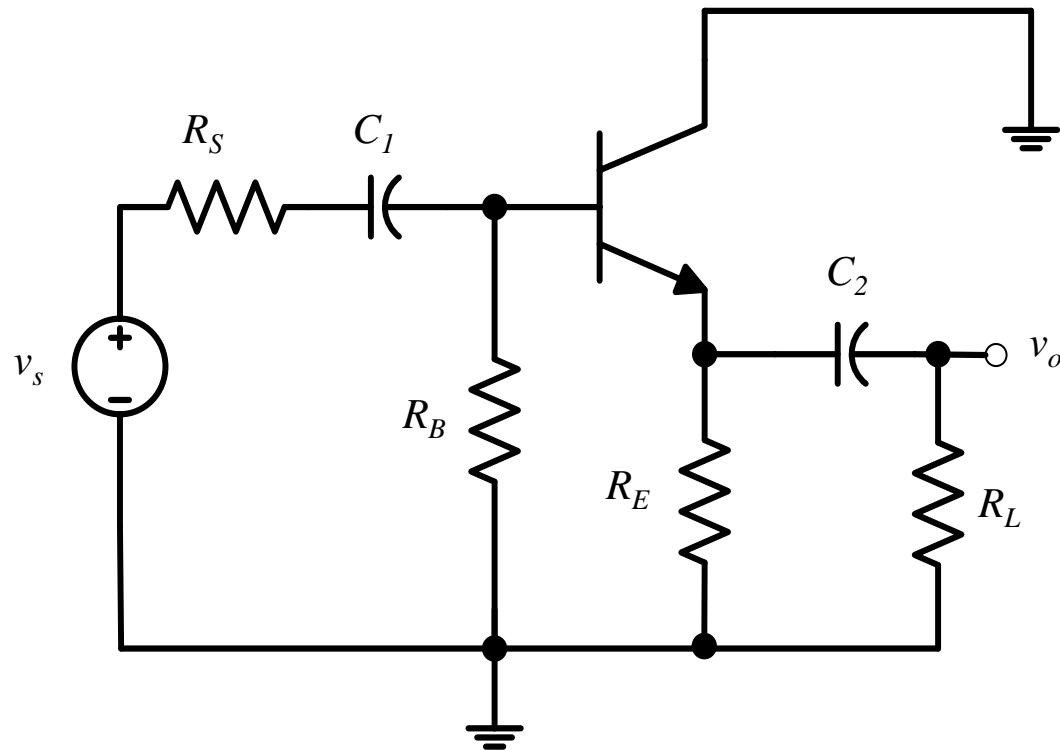

# Circuit for finding $R_{1S}$

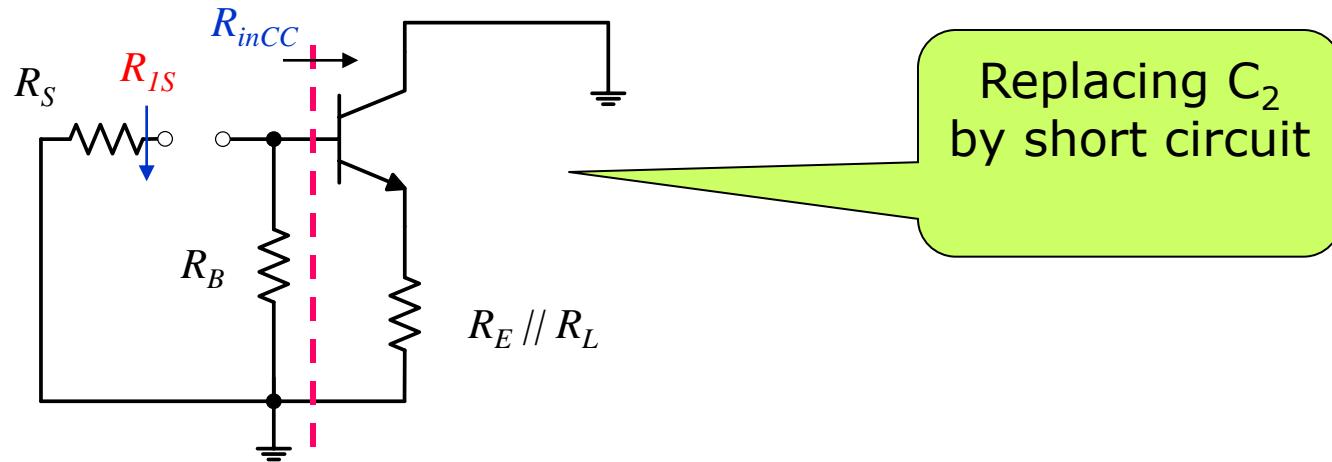


$$R_{1S} = R_S + (R_B \parallel R_{inCC}) = R_S + (R_B \parallel [r_\pi + (\beta + 1)(r_o \parallel R_E \parallel R_L)])$$
$$= 74.43 k\Omega$$

$$\frac{1}{R_{1S}C_1} = \frac{1}{(74.43 k\Omega)(0.1 \mu F)} = 136.18 \text{ rad/s}$$

# Circuit for finding $R_{2S}$

Replacing  $C_1$   
by short circuit

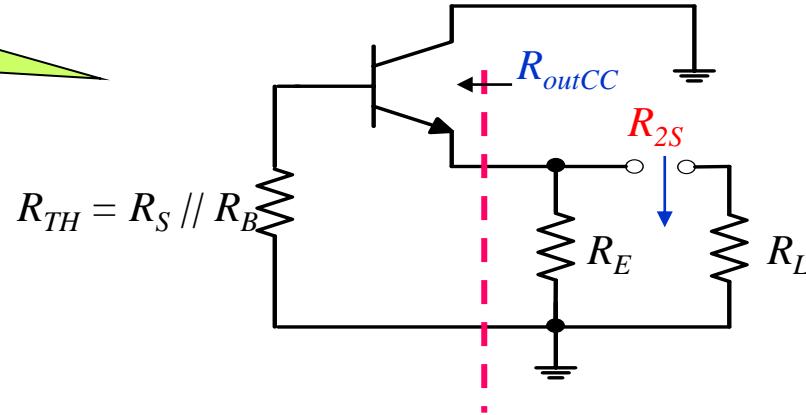

$$= 47.038 \text{ k}\Omega$$

$$R_{2S} = R_L + (R_E \parallel R_{outCC}) = R_L + \left( R_E \left\| \frac{R_{TH} + r_\pi}{\beta + 1} \right\| r_o \right)$$

$$\frac{1}{R_{2S} C_2} = \frac{1}{(47.038 \text{ k}\Omega)(100 \mu\text{F})} = 0.213 \text{ rad/s}$$

# Estimation of $\omega_L$

$$\omega_L \cong \sum_{i=1}^2 \frac{1}{R_{iS} C_i} = 136.18 + 0.213 = 136.393 \text{ rad/s}$$

$$f_L = \frac{\omega_L}{2\pi} = 21.7 \text{ Hz}$$

# Example

Given :

Q-point values : 1.6


mA, 4.86 V

$\beta = 100, V_A = 70 \text{ V}$

Therefore,

$r_\pi = 1.62 \text{ k}\Omega, r_o = 43.75 \text{ k}\Omega, g_m = 61.54 \text{ mS}$

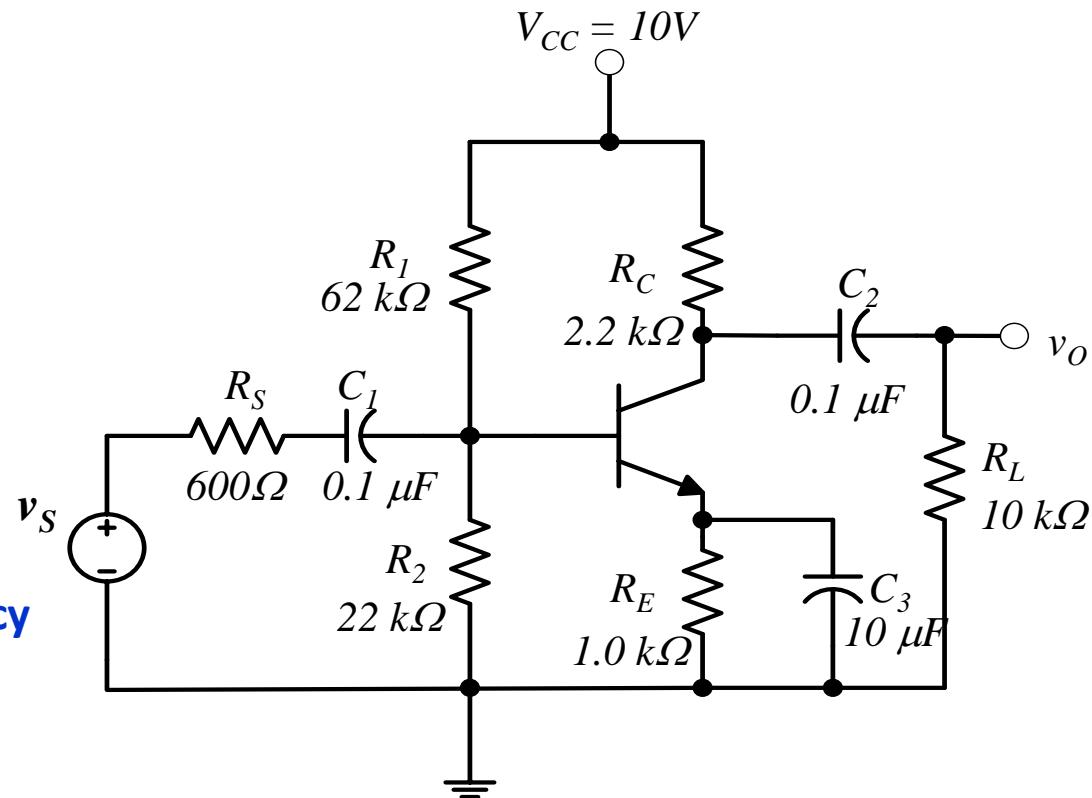Determine the total low-frequency response of the amplifier.



# Low frequency due to C<sub>1</sub> and C<sub>2</sub> C<sub>3</sub>

Low frequency due to C<sub>1</sub>

$$R_{1S} = R_S + (R_B \| r_\pi) = 600 + (16.24k \| 1.62k) = 2.07 \text{ k}\Omega$$

$$R_B = R_1 \| R_2 = 16.24 \text{ k}\Omega$$

$$f_{C_1} = \frac{1}{2\pi R_{1S} C_1} = \frac{1}{2\pi(2.07 \text{ k}\Omega)(0.1 \mu F)} = 768.86 \text{ Hz} \cong 769 \text{ Hz}$$

Low frequency due to C<sub>2</sub>

$$R_{2S} = R_L + (R_C \| r_o) = 10k + (2.2k \| 43.75k) = 12.09 \text{ k}\Omega$$

$$f_{C_2} = \frac{1}{2\pi R_{2S} C_2} = \frac{1}{2\pi(12.09 \text{ k}\Omega)(0.1 \mu F)} = 131.64 \text{ Hz} \cong 132 \text{ Hz}$$

# Low frequency due to $C_3$

Low frequency due to  $C_3$

$$R_{3S} = R_E \left\| \frac{r_\pi + R_{TH}}{\beta + 1} = 1k \right\| \frac{1.62k + 0.58k}{101} = 21.32\Omega$$

$$R_{TH} = R_S \| R_B = 0.58k\Omega$$

$$f_{C_3} = \frac{1}{2\pi R_{3S} C_3} = \frac{1}{2\pi(21.32\Omega)(10\mu F)} = 746.5 \text{ Hz} \cong 747 \text{ Hz}$$