


Lecture-3

Feedback Amplifier and their Topologies

Introduction

- It's impossible to think of electronic circuits without some forms of feedback.
- Negative feedback
 - Desensitize the gain
 - Reduce nonlinear distortion
 - Reduce the effect of noise
 - Control the input and output impedance
 - Extend the bandwidth of the amplifier
- *The basic idea of negative feedback is to trade off gain for other desirable properties.*
- Positive feedback will cause the amplifier oscillation.

The General Feedback Structure

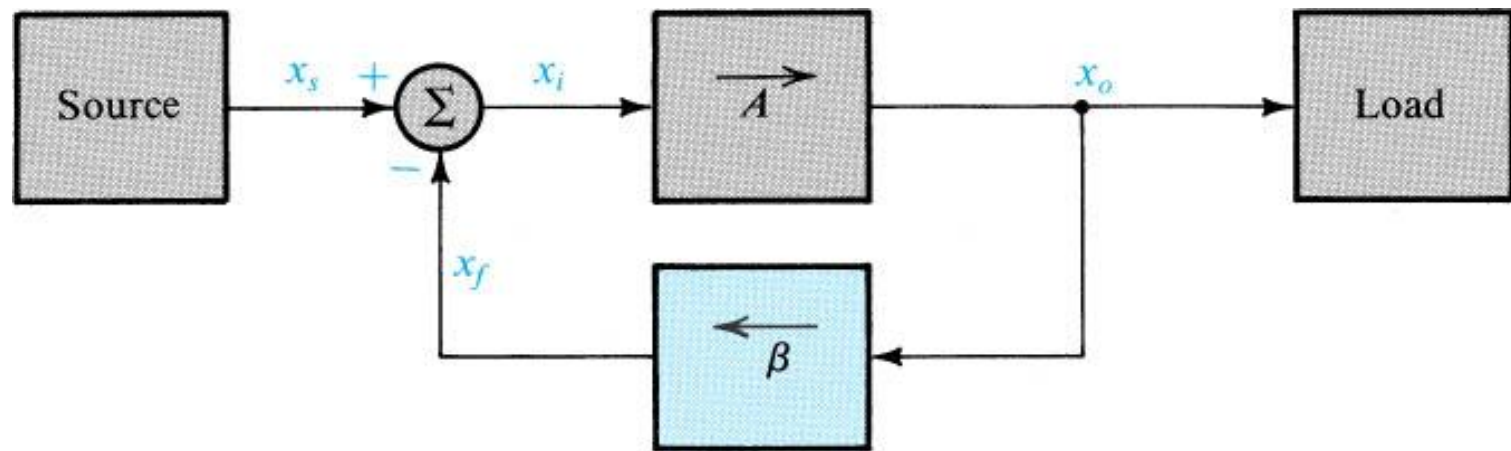

This is a signal-flow diagram, and the quantities x represent either voltage or current signals.

The General Feedback Equation

- Closed loop and open loop
- Closed loop gain

$$A_f \equiv \frac{x_o}{x_s} = \frac{A}{1 + A\beta}$$

- Feedback factor β
- Loop gain $A\beta$
- Amount of feedback $(1 + A\beta)$

Some Properties of Negative Feedback

- Gain desensitivity


$$\frac{dA_f}{A_f} = \frac{1}{1 + A\beta} \frac{dA}{A}$$

- Bandwidth extension
- Noise reduction
- Reduction in nonlinear distortion

The Four Basic Feedback Topologies

- Voltage amplifier---series-shunt feedback
voltage mixing and voltage sampling
- Current amplifier---shunt-series feedback
Current mixing and current sampling
- Transconductance amplifier---series-series feedback
Voltage mixing and current sampling
- Transresistance amplifier---shunt-shunt feedback
Current mixing and voltage sampling


The Series-Shunt Feedback Topologies

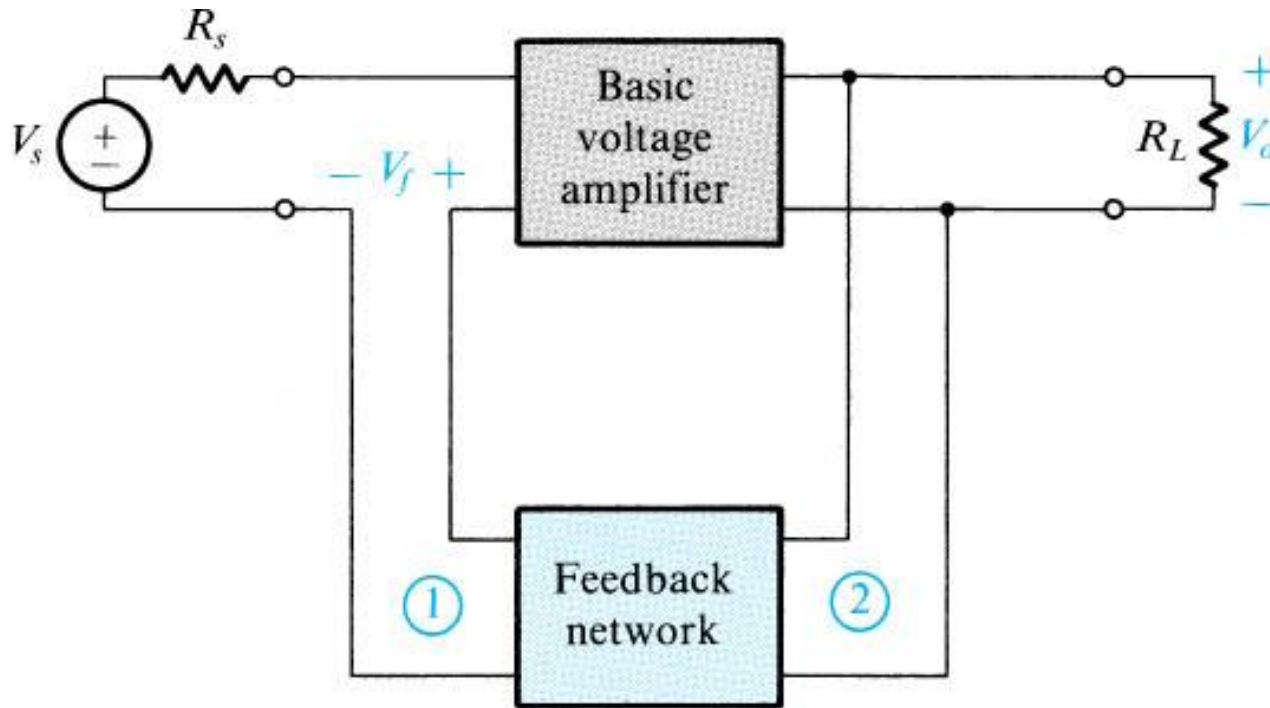

(a)


voltage-mixing voltage-sampling (series–shunt) topology

The Amplifier with Series-Shunt Feedback

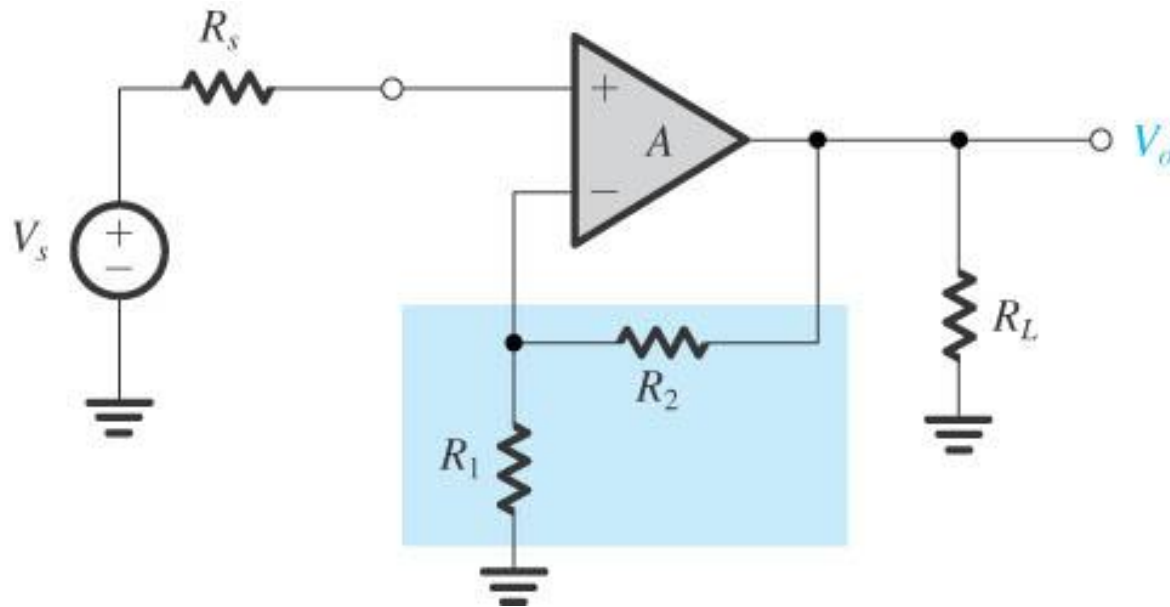

voltage-mixing voltage-sampling (series–shunt) topology


The Shunt-Series Feedback Topologies

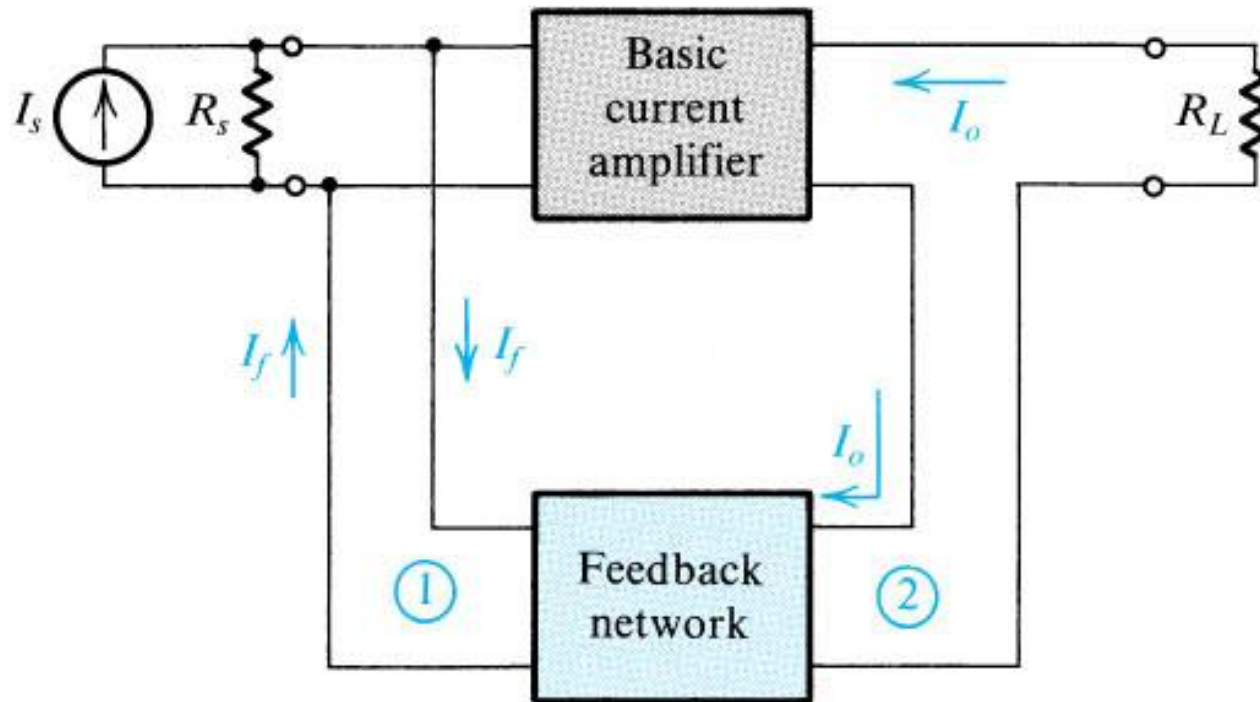

(b)


current-mixing current-sampling (shunt-series) topology

The Amplifier with Shunt-Series Feedback

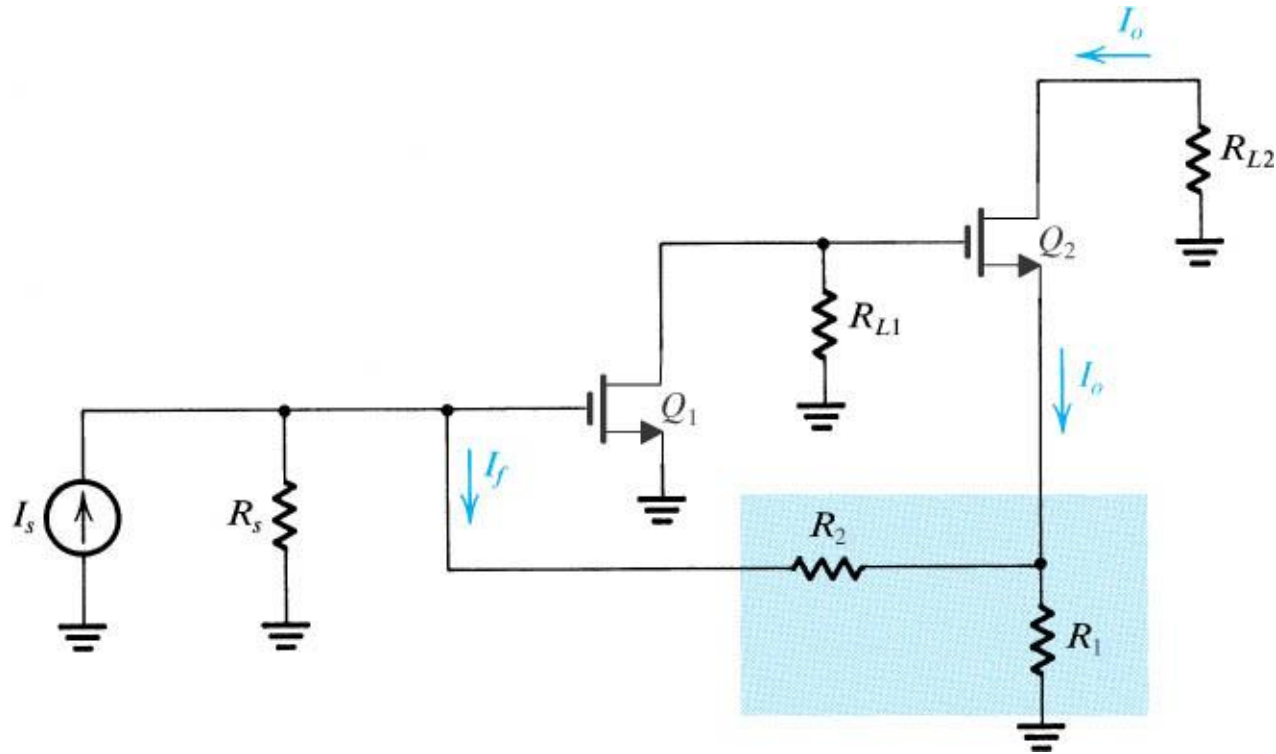


current-mixing current-sampling (shunt-series) topology

The Series-Series Feedback Topologies

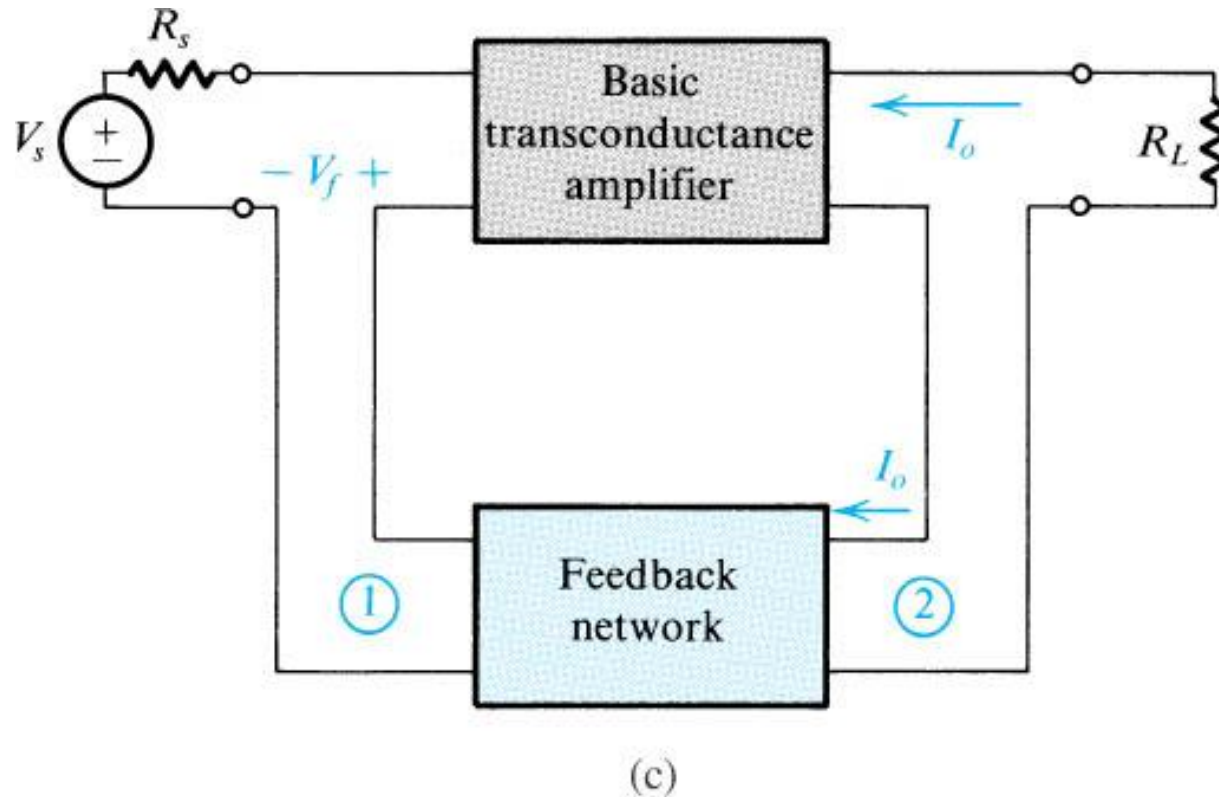


voltage-mixing current-sampling (series-series) topology

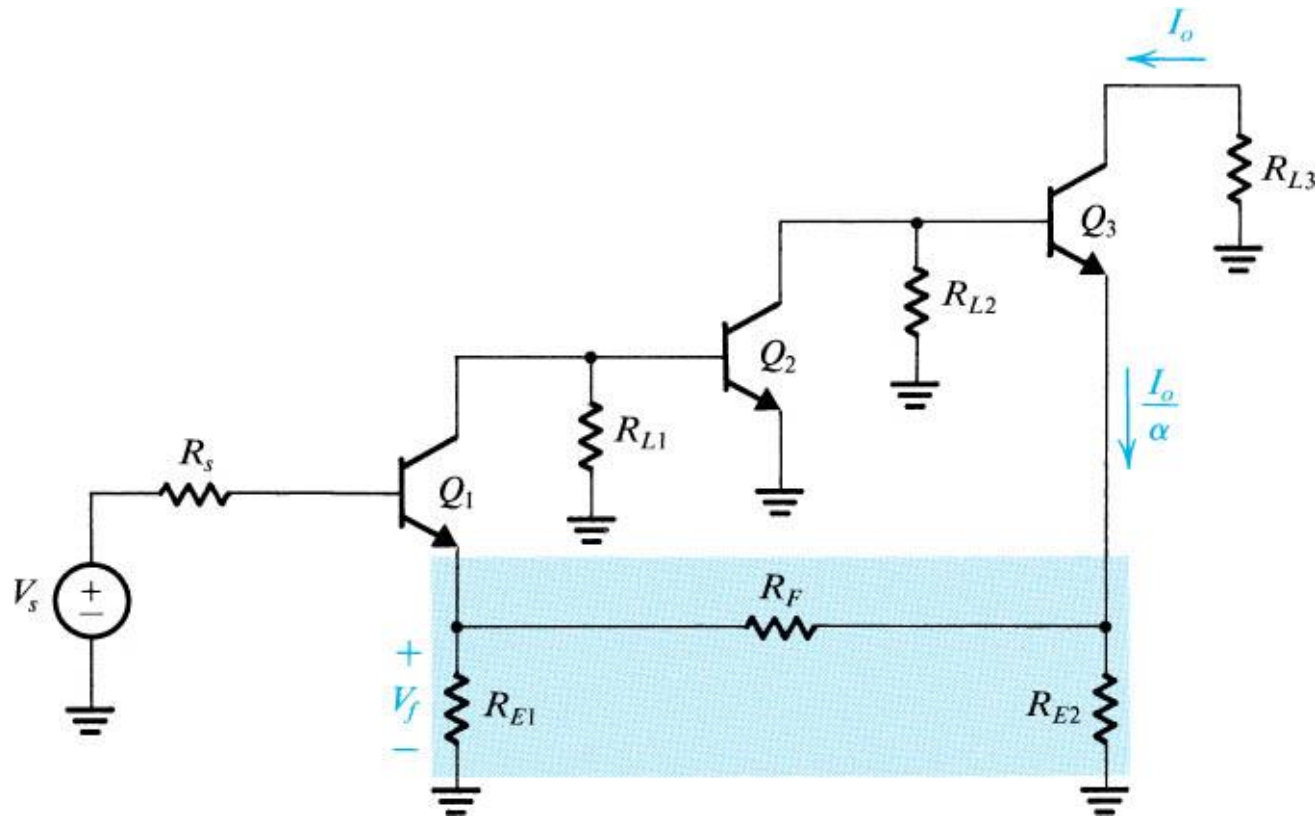The Amplifier with Series-Series Feedback



voltage-mixing current-sampling (series-series) topology

The Shunt-Shunt Feedback Topologies

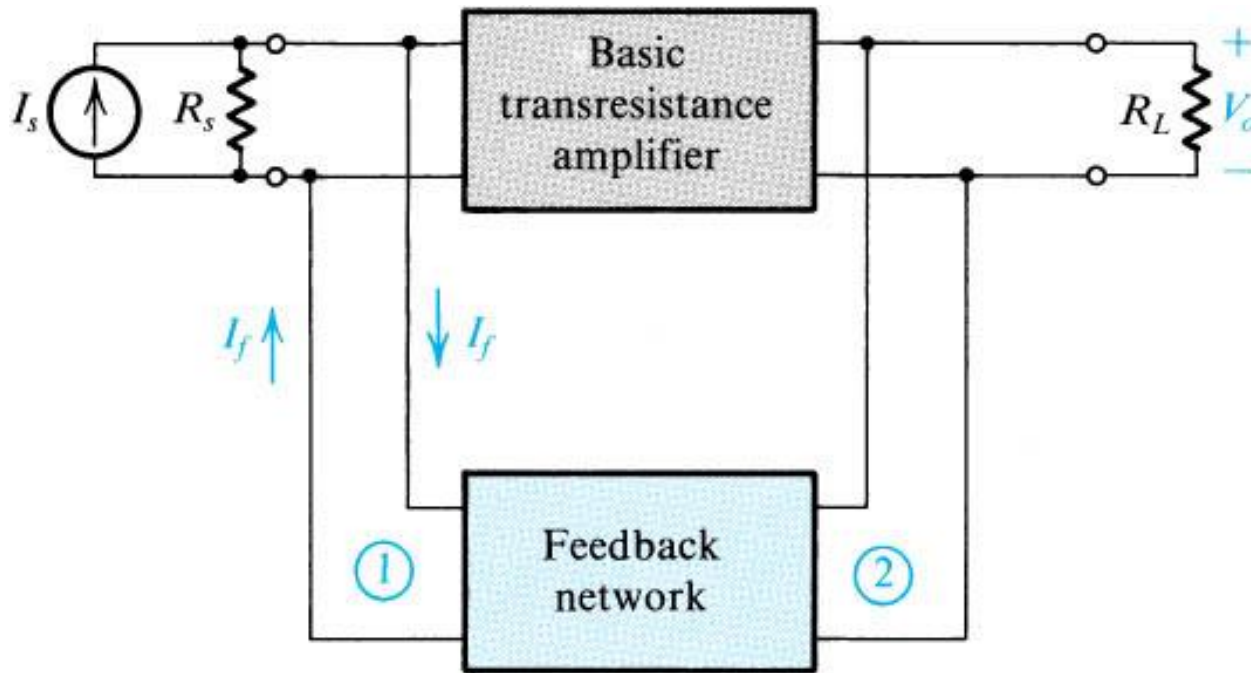

(d)

current-mixing voltage-sampling (shunt–shunt) topology