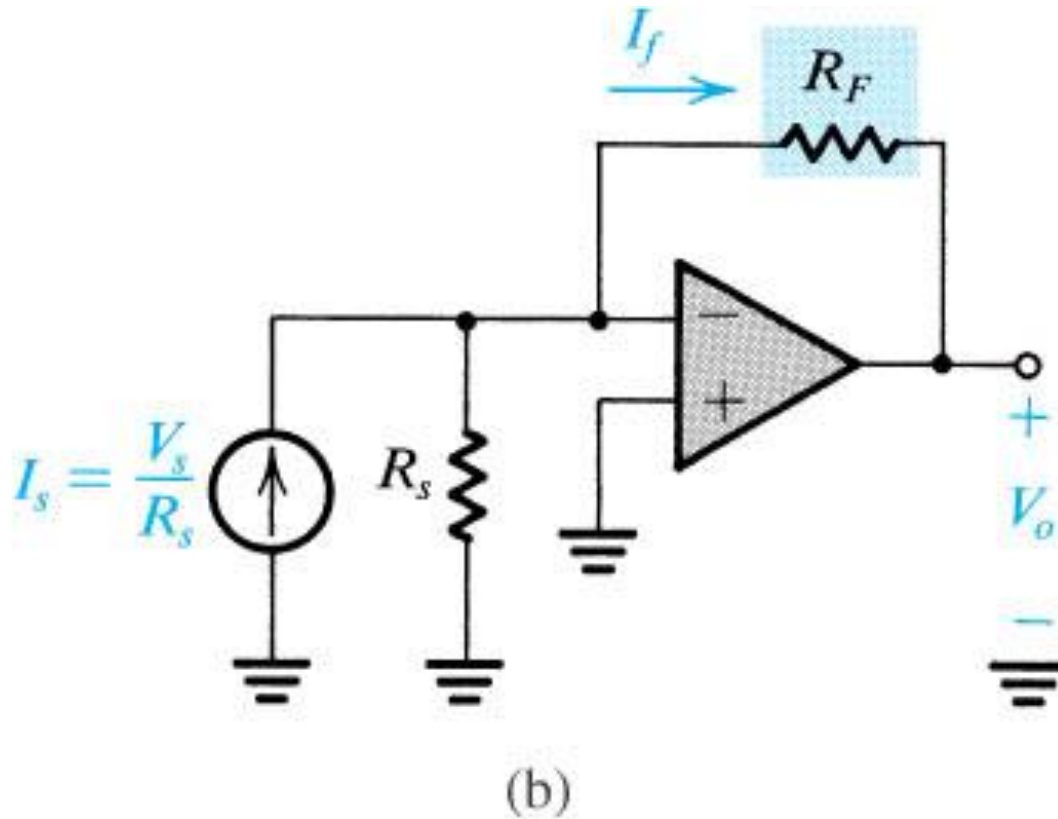


# Lecture-4

## Feedback Amplifier Configuration

# The OP Amplifier with Shunt-Shunt Feedback




current-mixing voltage-sampling (shunt–shunt) topology

# The Series-Shunt Feedback Amplifier


- The ideal situation
- The practical situation
- summary

# The Ideal Situation

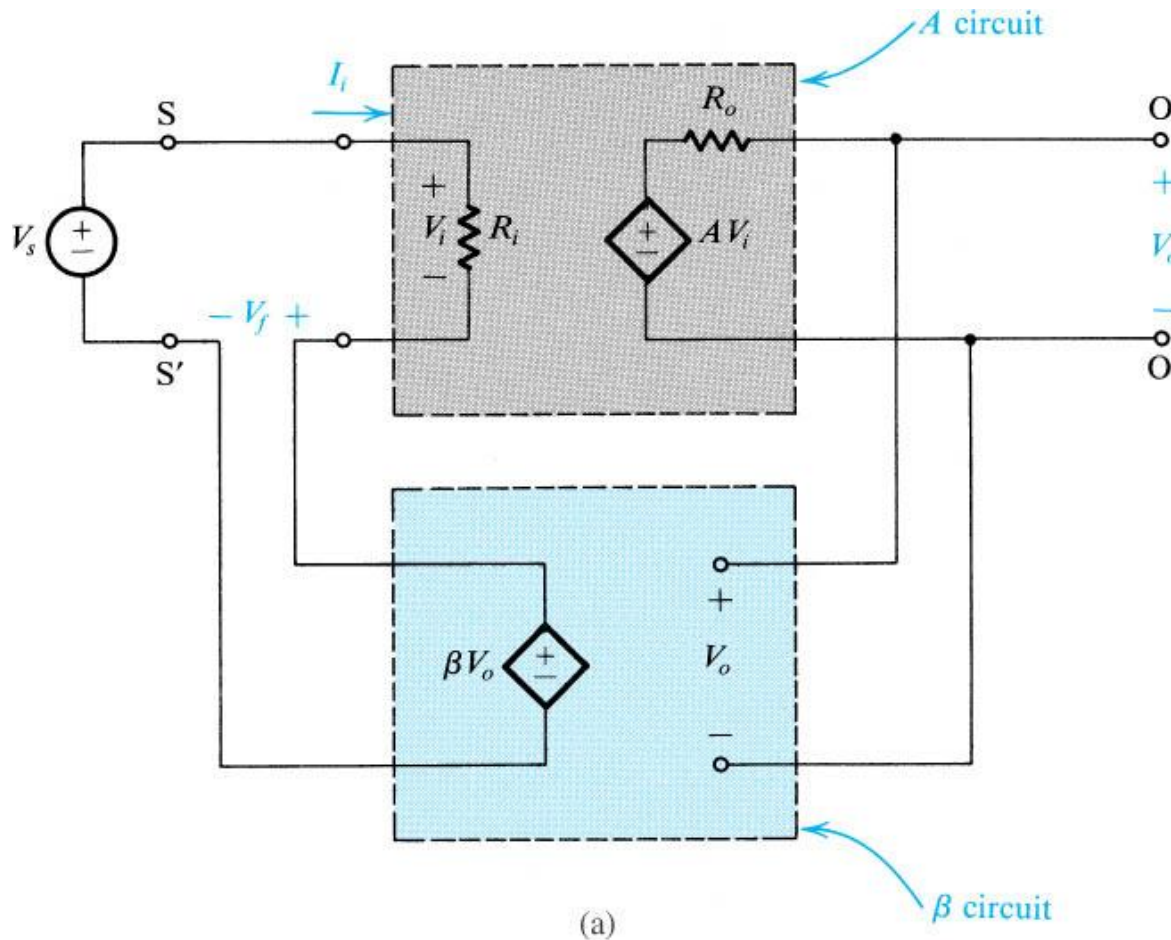

- A unilateral open-loop amplifier (A circuit).
- An ideal voltage mixing voltage sampling feedback network ( $\beta$  circuit).
- Assumption that the source and load resistance have been included inside the A circuit.

# The Ideal Situation

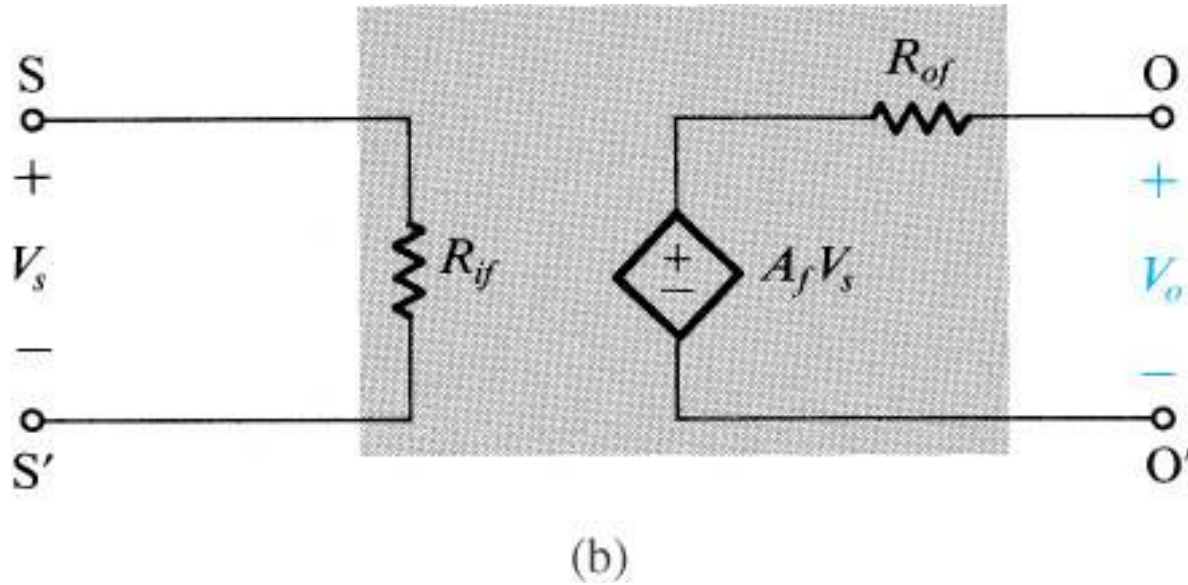

Equivalent circuit.

$R_{if}$  and  $R_{of}$  denote the input and output resistance with feedback.

# Input and Output Resistance with Feedback

- Input resistance

$$R_{if} = R_i(1 + A\beta)$$


*In this case, the negative feedback increases the input resistance by a factor equal to the amount of feedback.*

- Output resistance

$$R_{of} = \frac{R_o}{1 + A\beta}$$

*In this case, the negative feedback reduces the output resistance by a factor equal to the amount of feedback.*


# The Practical Situation

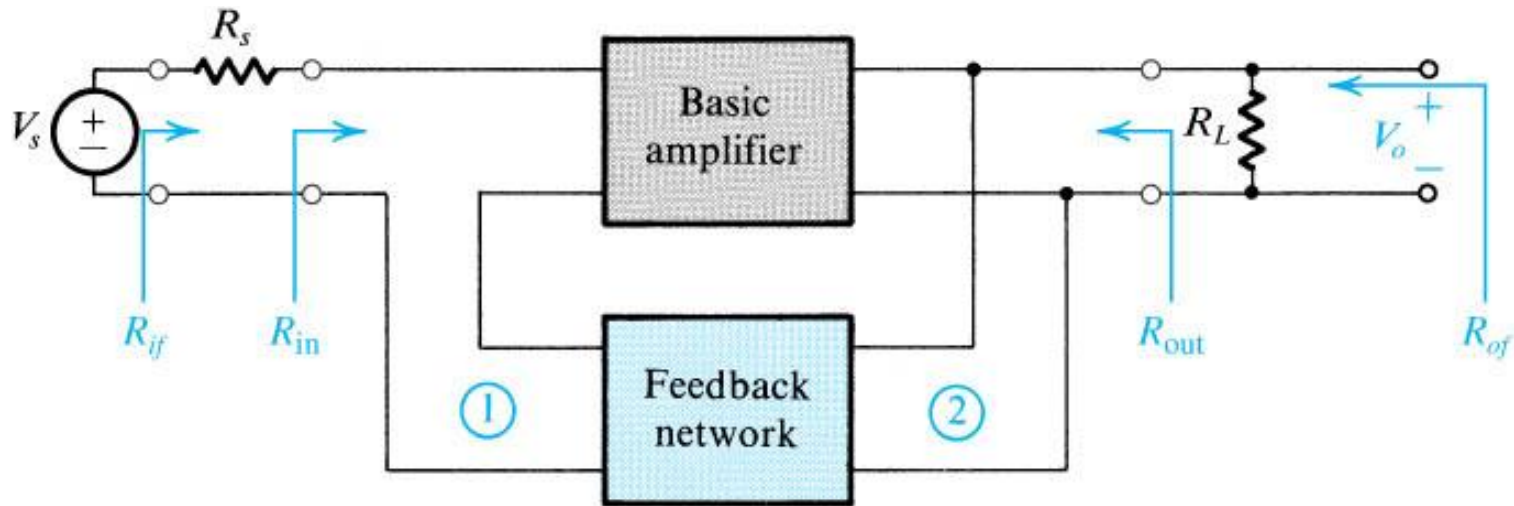

(a)

- Block diagram of a practical series–shunt feedback amplifier.
- Feedback network is not ideal and load the basic amplifier thus affect the values of gain, input resistance and output resistance.

# The Practical Situation

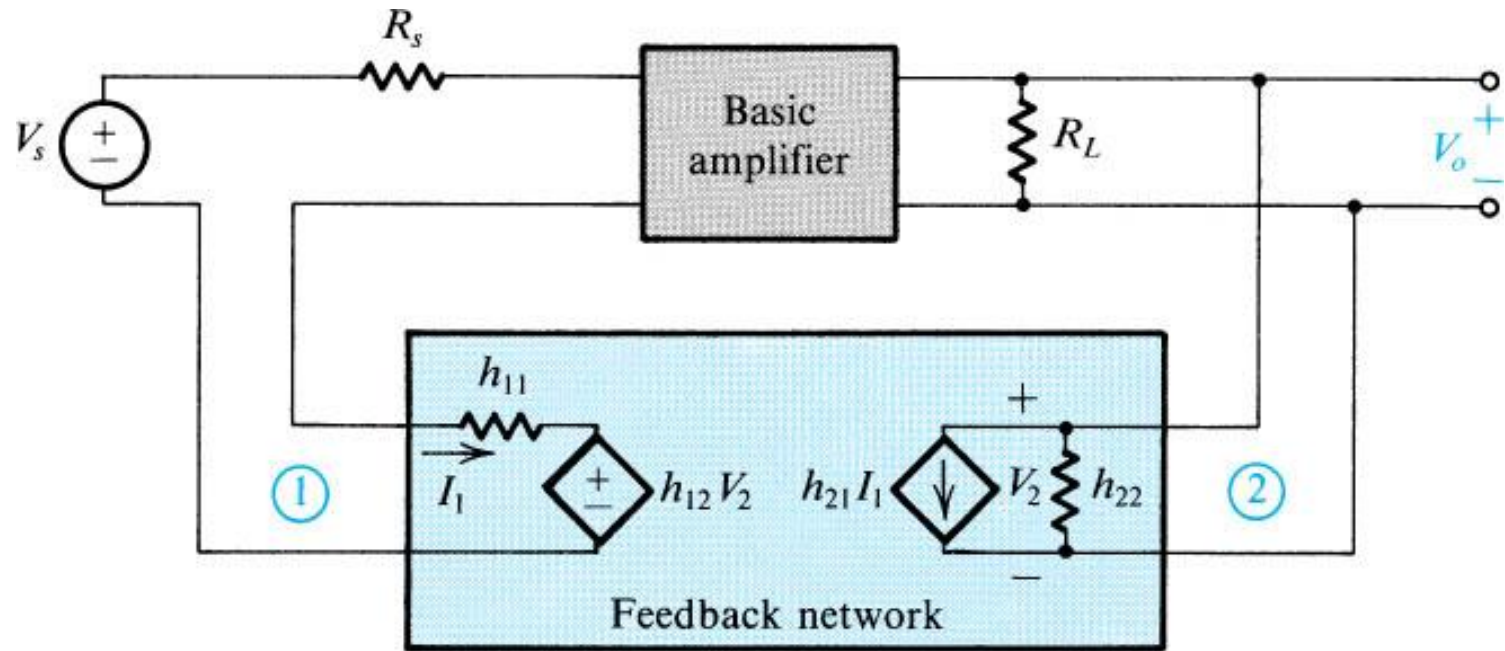


(b)

The circuit in (a) with the feedback network represented by its  $h$  parameters.



# The Practical Situation

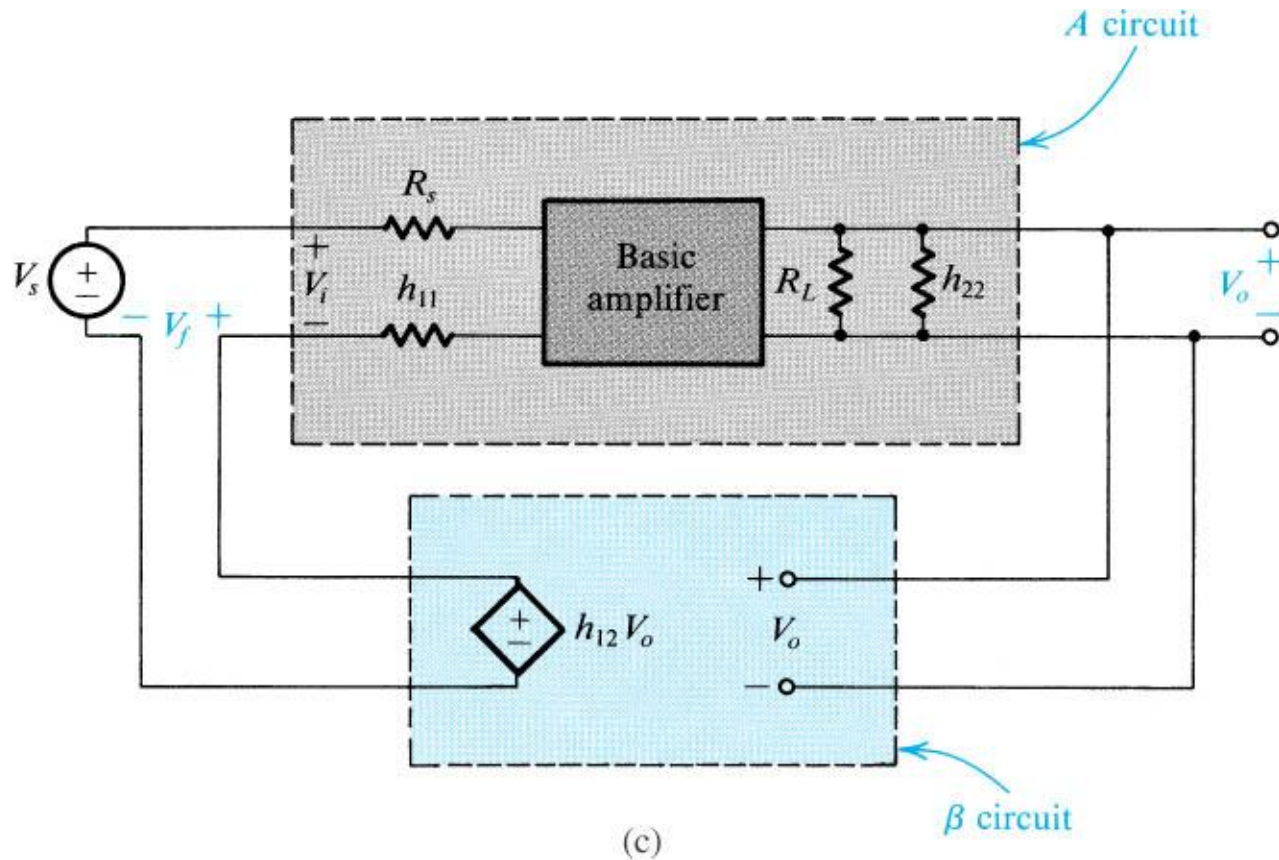


The circuit in (b) with  $h_{21}$  neglected.

# The Practical Situation


- The load effect of the feedback network on the basic amplifier is represented by the components  $h_{11}$  and  $h_{22}$ .
- The loading effect is found by looking into the appropriate port of the feedback network while the port is open-circuit or short-circuit so as to destroy the feedback.
- If the connection is a shunt one, short-circuit the port.
- If the connection is a series one, open-circuit the port.
- Determine the  $\beta$ .

$$\beta = h_{12} \equiv \left. \frac{V_1}{V_2} \right|_{I_1=0}$$


(a) The A circuit is

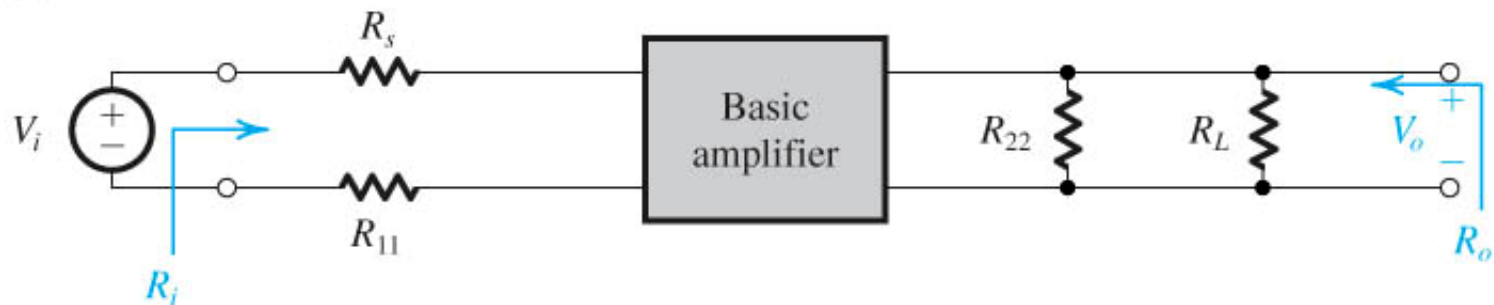

where  $R_{11}$  is obtained from

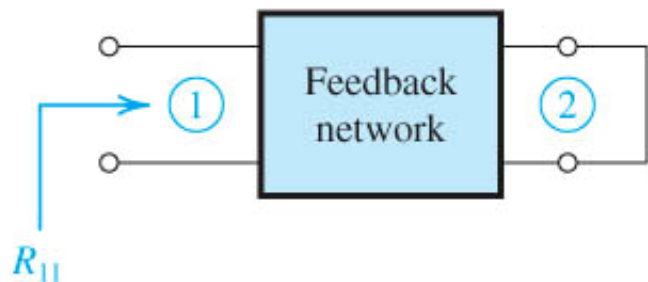


and  $R_{22}$  is obtained from

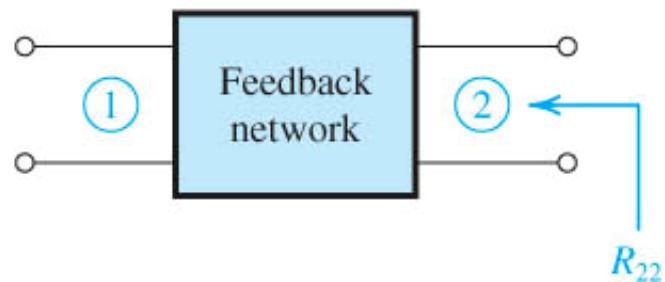

and the gain A is defined  $A \equiv \frac{V_o}{V_i}$

(b)  $\beta$  is obtained from

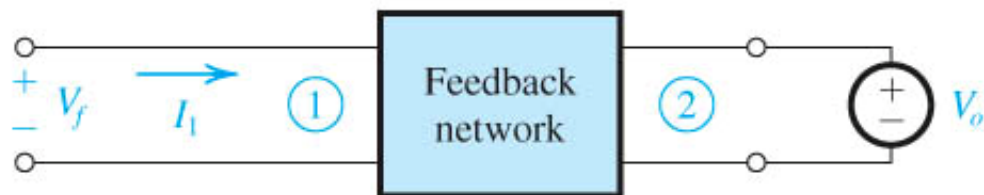

$$\beta \equiv \left. \frac{V_f}{V_o} \right|_{I_1 = 0}$$

# Summary

- $R_i$  and  $R_o$  are the input and output resistances, respectively, of the A circuit.
- $R_{if}$  and  $R_{of}$  are the input and output resistances, respectively, of the feedback amplifier, including  $R_s$  and  $R_L$ .
- The actual input and output resistances exclude  $R_s$  and  $R_L$ .  
$$R_{if} = R_{in} + R_s$$
$$R_{of} = R_{out} // R_L$$