

# Lecture-1


Basics of Op-amp , Operation of Op-  
Amp
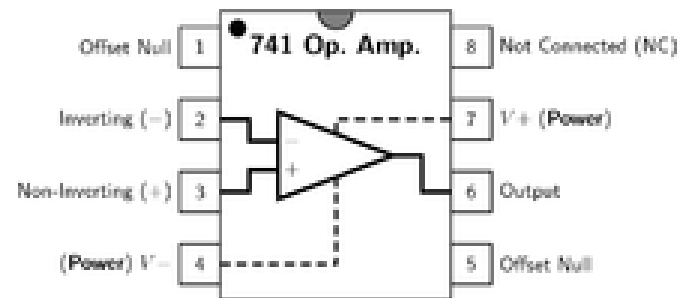
# What is an Op-Amp? – The Surface

- An Operational Amplifier (Op-Amp) is an integrated circuit that uses external voltage to amplify the input through a very high gain.
- We recognize an Op-Amp as a mass-produced component found in countless electronics.




What an Op-Amp looks like to a lay-person



What an Op-Amp looks like to an engineer
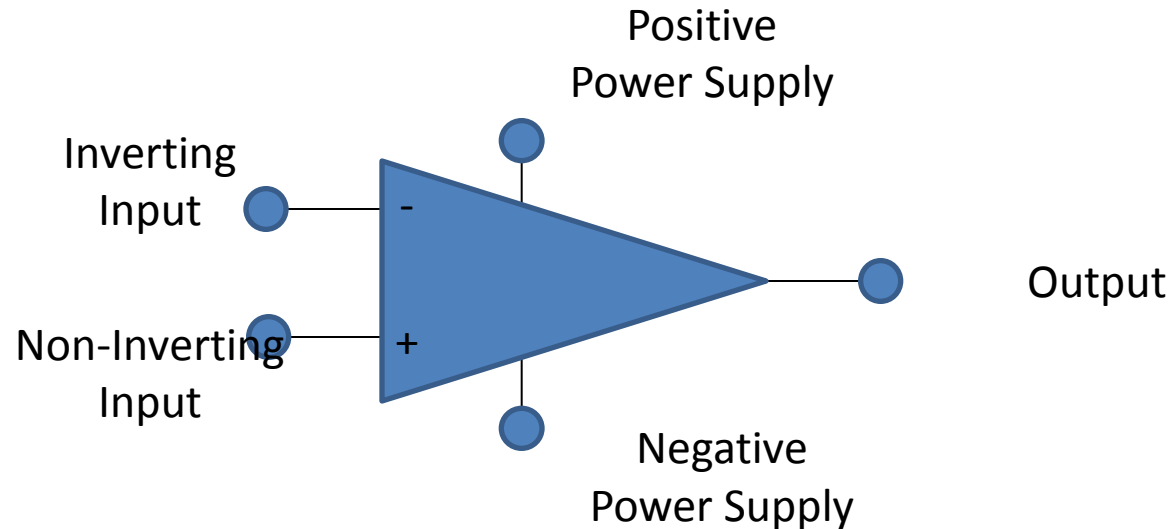
# What is an Op-Amp? – The Inside

- The actual count varies, but an Op-Amp contains several Transistors, Resistors, and a few Capacitors and Diodes.
- For simplicity, an Op-Amp is often depicted as this:



# Mathematics of the Op-Amp

- The gain of the Op-Amp itself is calculated as:


$$G = V_{\text{out}} / (V_{+} - V_{-})$$

- The maximum output is the power supply voltage
- When used in a circuit, the gain of the circuit (as opposed to the op-amp component) is:


$$A_v = V_{\text{out}} / V_{\text{in}}$$
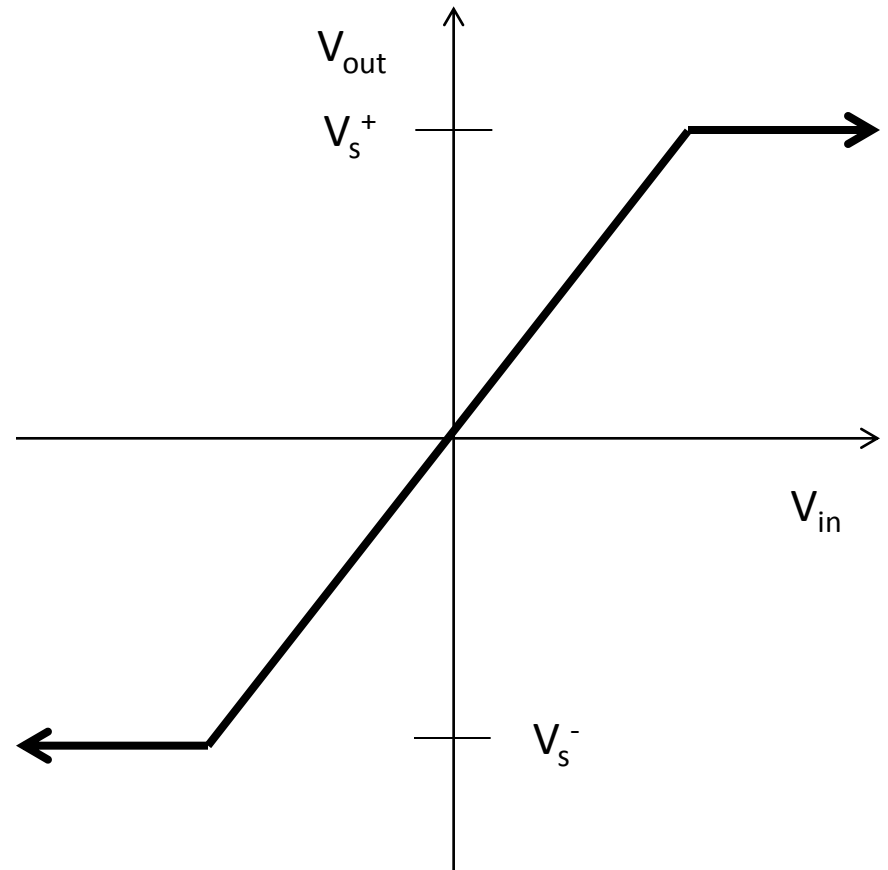
# Op-Amp Saturation

- As mentioned earlier, the maximum output value is the **supply voltage**, positive and negative.
- The gain (G) is the slope between saturation points.




# Op-Amp Characteristics

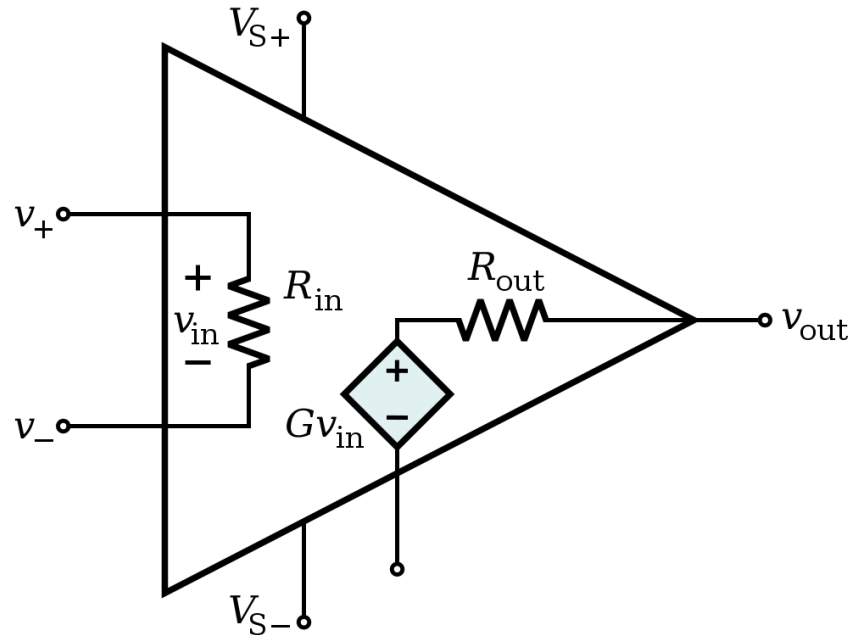


- Open-loop gain  $G$  is typically over 9000
  - But closed-loop gain is much smaller
- $R_{in}$  is very large ( $M\Omega$  or larger)
- $R_{out}$  is small ( $75\Omega$  or smaller)
  - Effective output impedance in closed loop is very small

# Ideal Op-Amp Characteristics

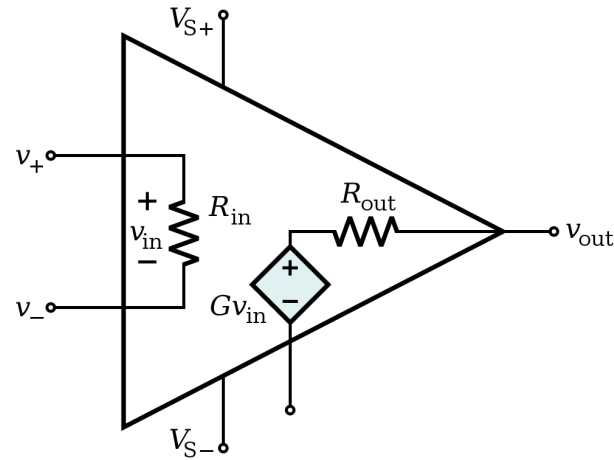

- Open-loop gain  $G$  is infinite
- $R_{in}$  is infinite
  - Zero input current
- $R_{out}$  is zero

# Ideal Op-Amp Analysis

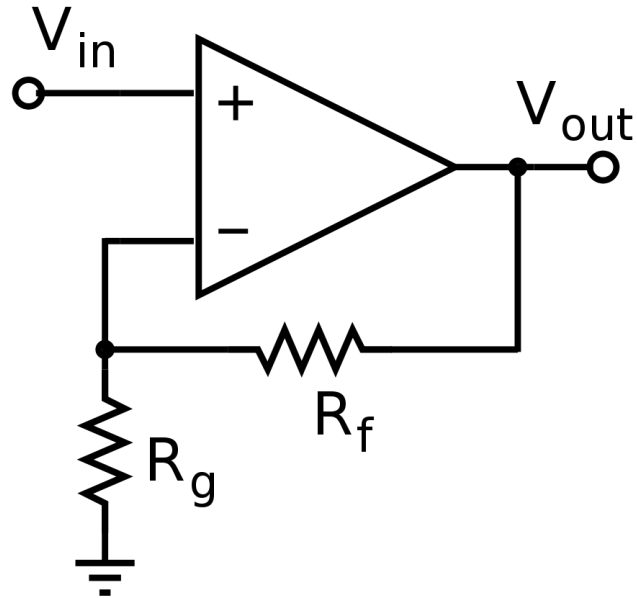


To analyze an op-amp feedback circuit:

- Assume no current flows into either input terminal
- Assume no current flows out of the output terminal
- Constrain:  $V_+ = V_-$




# Inverting Amplifier Analysis

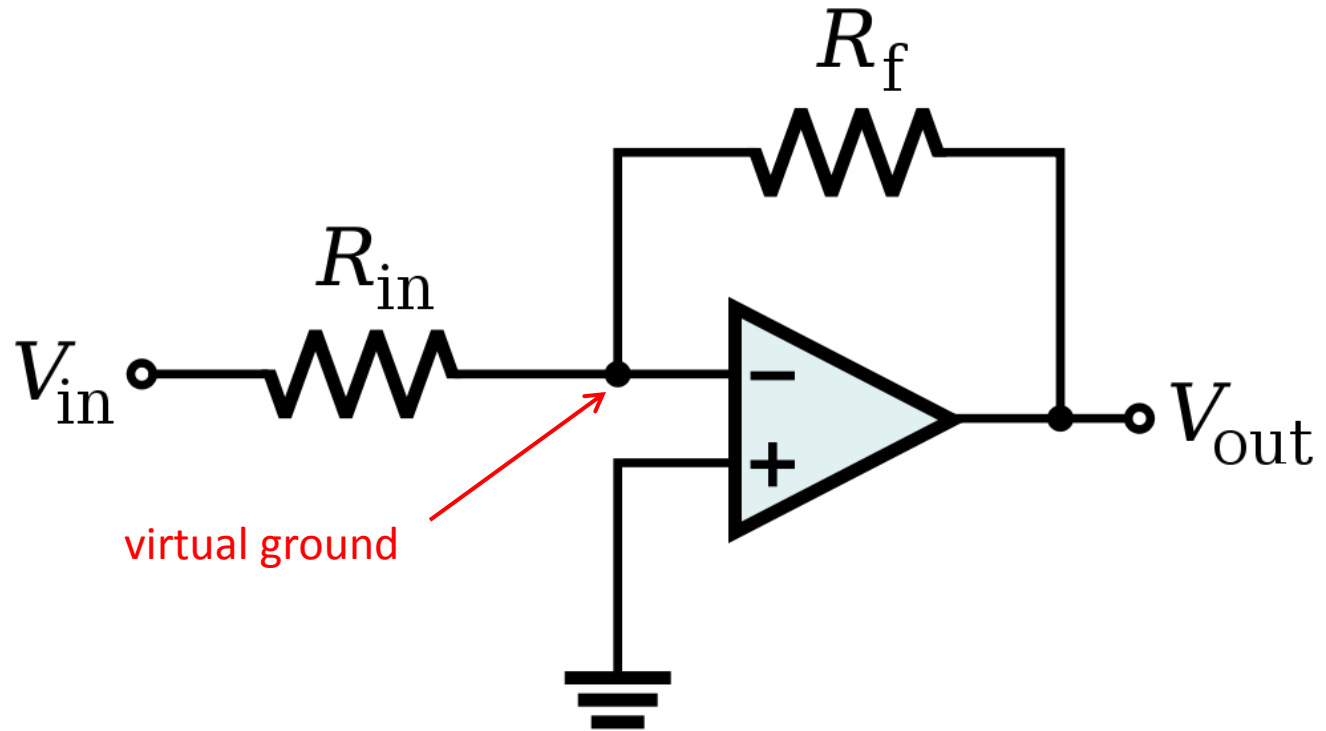


$$V_{out} = -\frac{R_f}{R_{in}} V_{in}$$

# Non-Inverting Amplifier Analysis

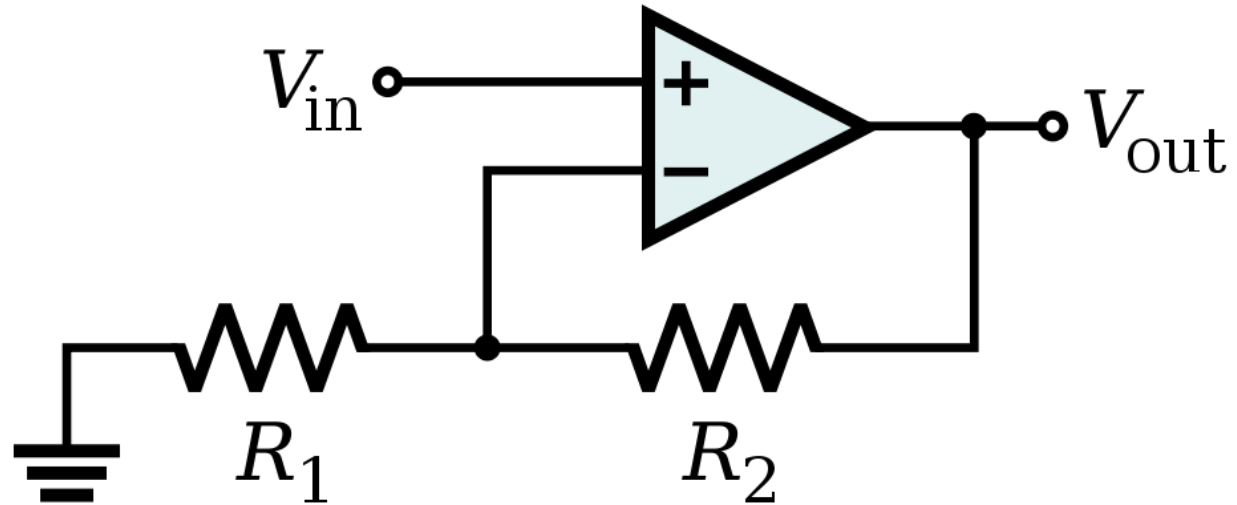


$$V_{out} = V_{in} \left( 1 + \frac{R_2}{R_1} \right)$$


# Op-Amp Buffer

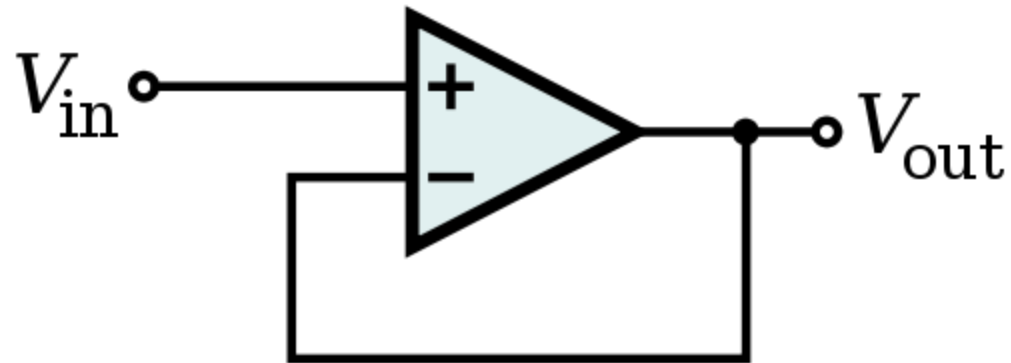

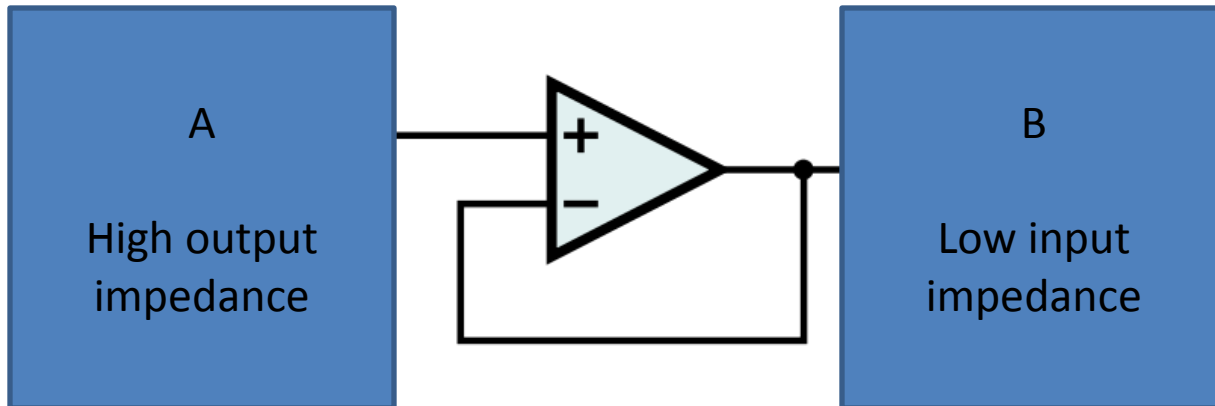$V_{out} = V_{in}$   
Isolates loading effects




# Op-Amp Differentiator

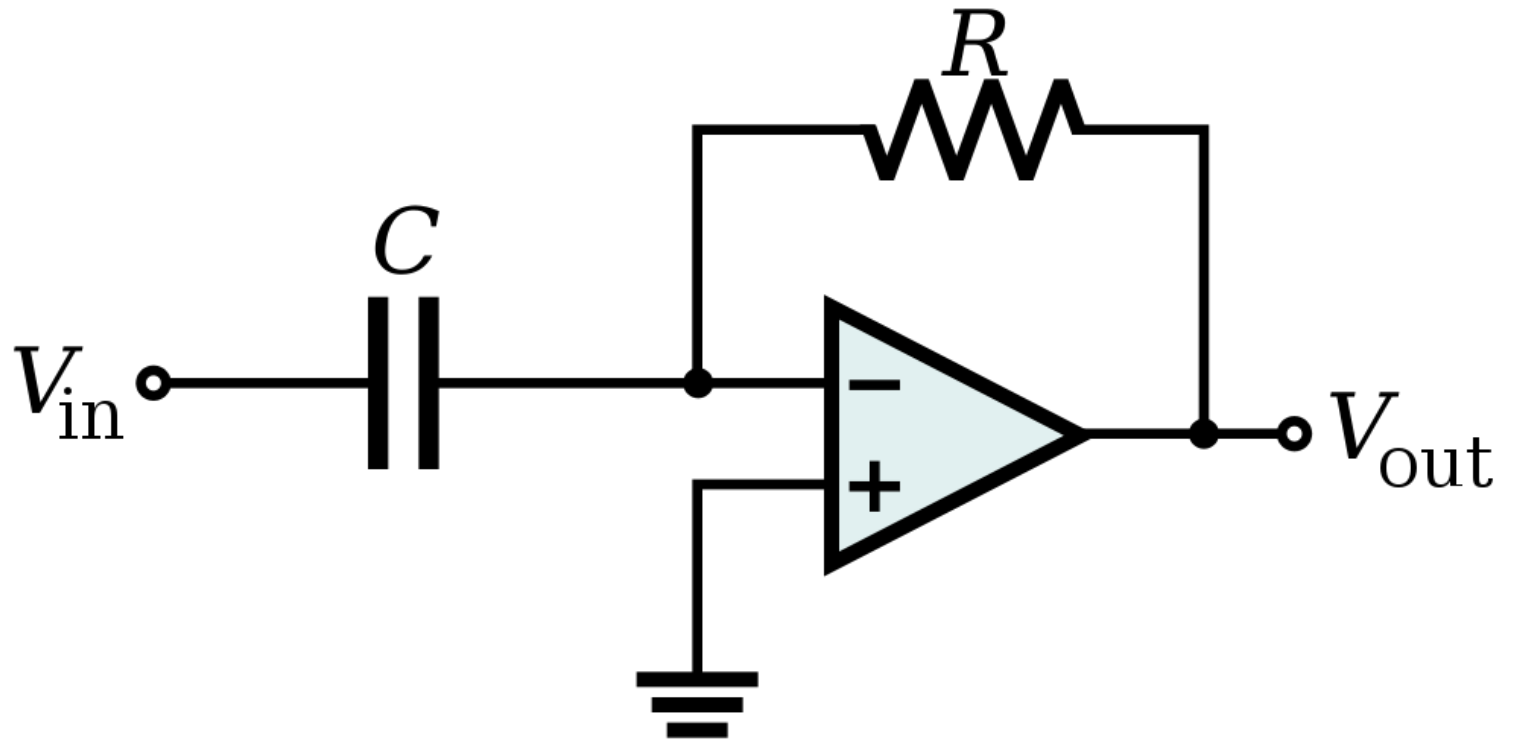


$$V_{out} = -RC \frac{dV_{in}}{dt}$$

# Op-Amp Integrator

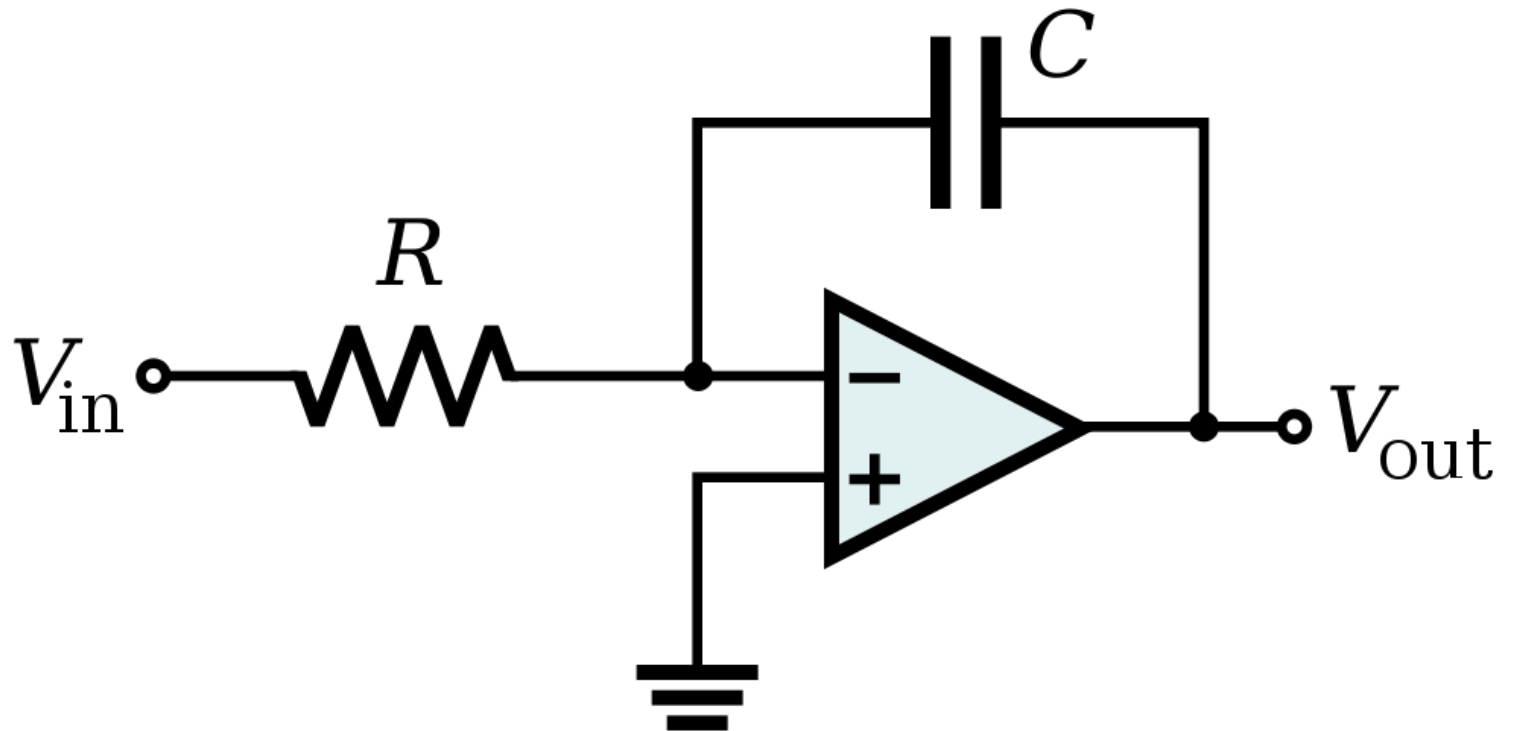


$$V_{out} = - \int_0^t \frac{V_{in}}{RC} dt + V_{initial}$$

# Op-Amp Summing Amplifier

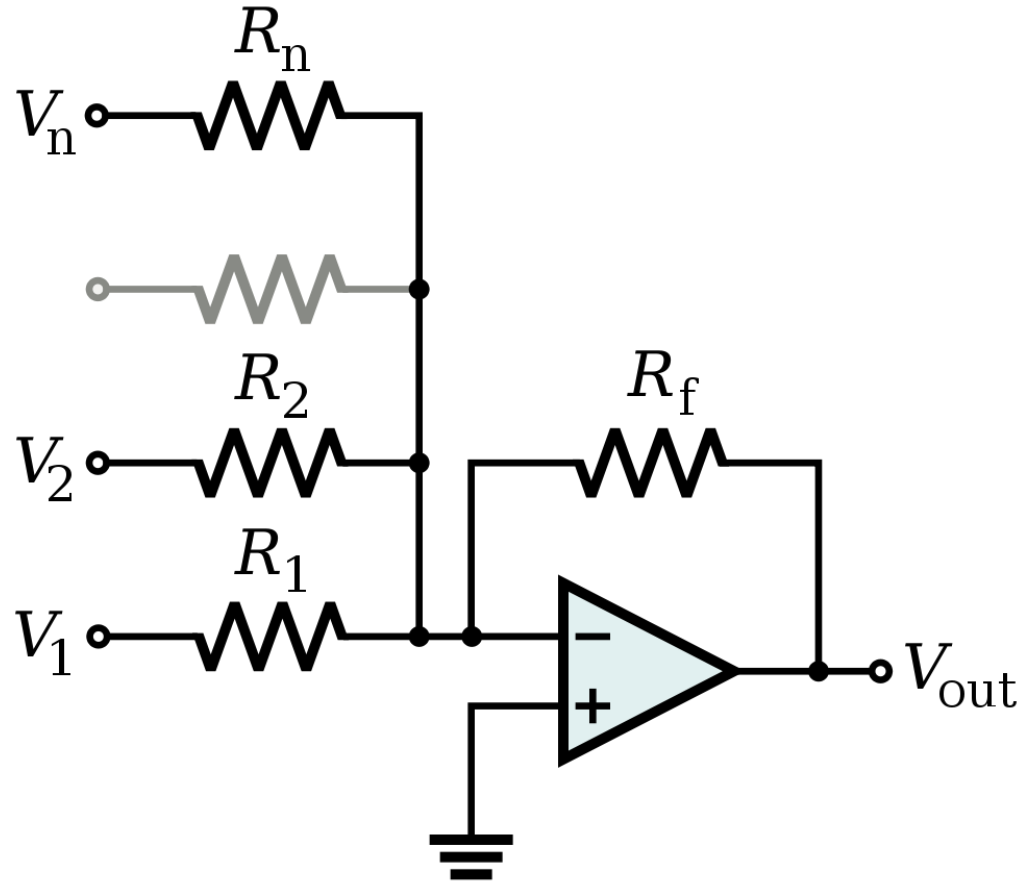

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

# Op-Amp Differential Amplifier

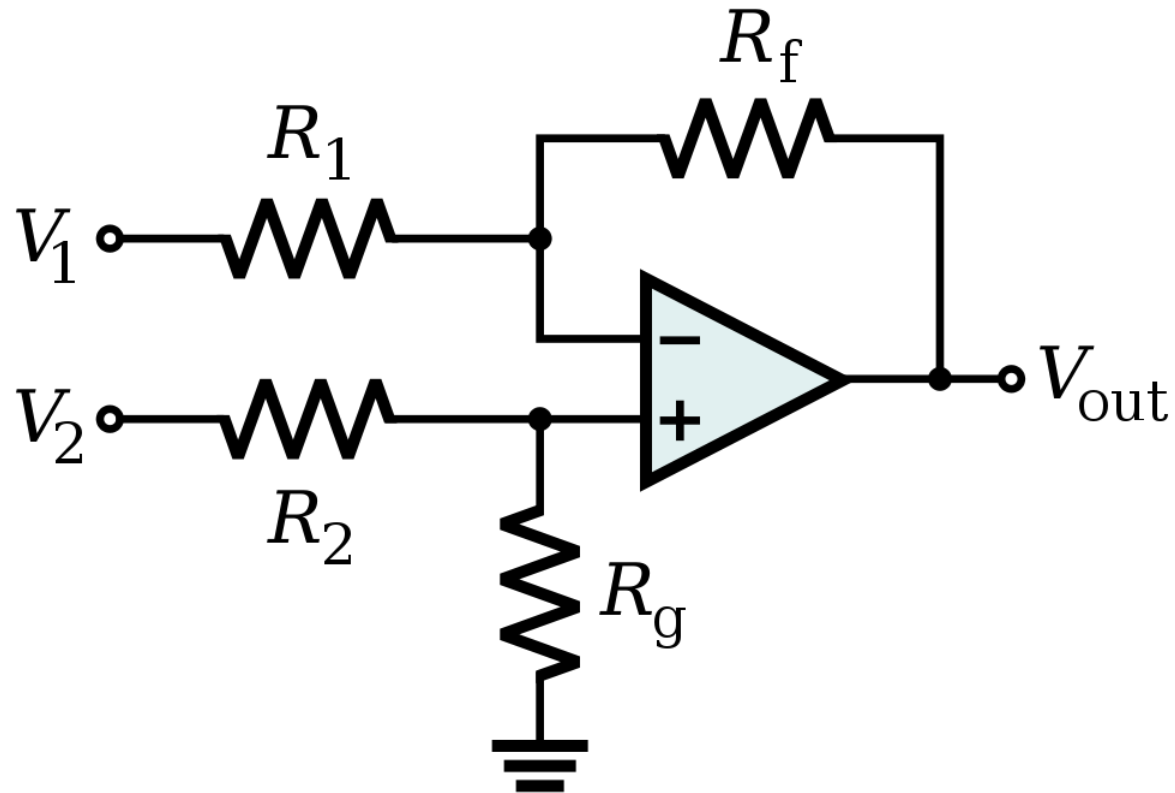

$$V_{\text{out}} = \frac{(R_f + R_1) R_g}{(R_g + R_2) R_1} V_2 - \frac{R_f}{R_1} V_1$$


If  $R_1 = R_2$  and  $R_f = R_g$ :

$$V_{\text{out}} = \frac{R_f}{R_1} (V_2 - V_1)$$

# Applications of Op-Amps

- Example of PI Control: Temperature Control

- Voltage Error Circuit:

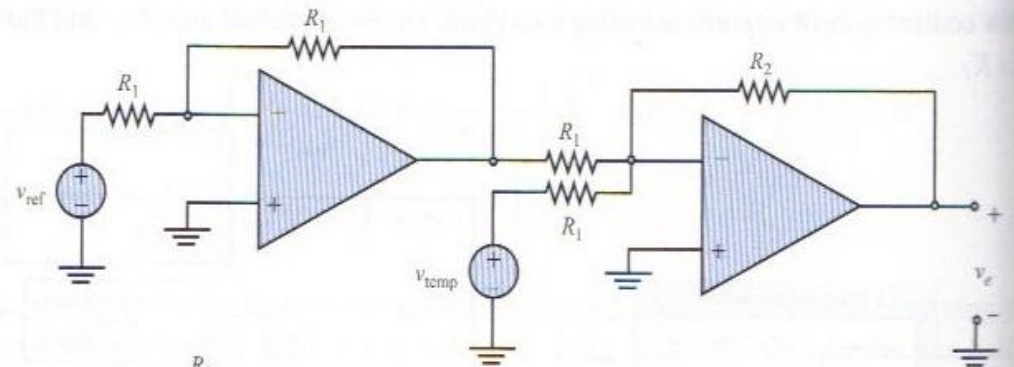

- Proportional-Integral Control Circuit:

