


# **NETWORK ANALYSIS AND SYNTHESIS**

Unit 1

# Graph Theory

# Matrices of Oriented Graphs

- Consider the following graph

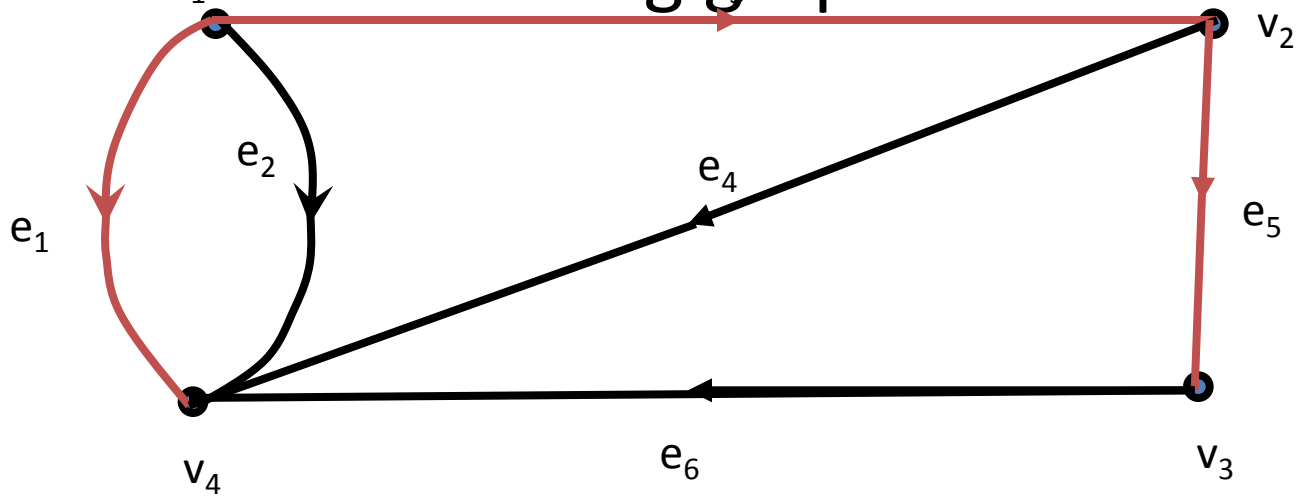

$$\mathbf{B}_f = \left[ \begin{array}{ccc|ccc} e_1 & e_3 & e_5 & e_2 & e_4 & e_6 \\ -1 & 0 & 0 & 1 & 0 & 0 \\ -1 & 1 & 0 & 0 & 1 & 0 \\ -1 & 1 & 1 & 0 & 0 & 1 \end{array} \right] \begin{matrix} (e_2) \\ (e_4) \\ (e_6) \end{matrix}$$

$$\mathbf{B}_f = [\mathbf{B} \quad \mathbf{U}]$$

# Matrices of Oriented Graphs

- **THEOREM:** If the column orderings of the circuit and incident matrices are identical then


$$\mathbf{B} \mathbf{\Pi}^T = \mathbf{0}$$

or

$$\mathbf{\Pi} \mathbf{B}^T = \mathbf{0}$$

# Matrices of Oriented Graphs

- Consider the following graph

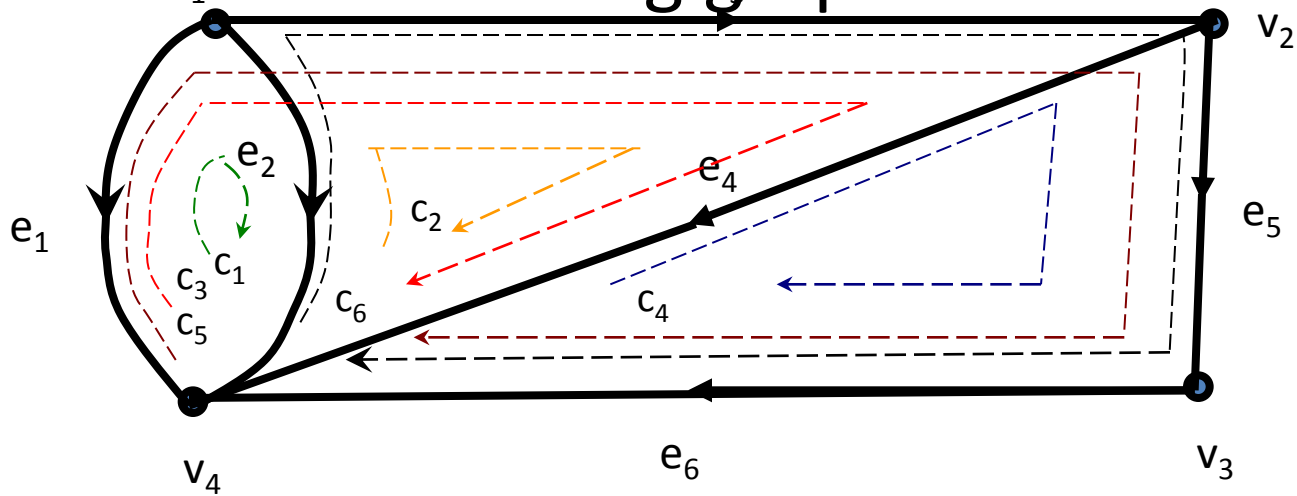

$$\mathbf{B} = \begin{array}{c|cccccc} & e_1 & e_2 & e_3 & e_4 & e_5 & e_6 \\ \hline c_1 & -1 & 1 & 0 & 0 & 0 & 0 \\ c_2 & 0 & -1 & 1 & 1 & 0 & 0 \\ c_3 & -1 & 0 & 1 & 1 & 0 & 0 \\ c_4 & 0 & 0 & 0 & -1 & 1 & 1 \\ c_5 & -1 & 0 & 1 & 0 & 1 & 1 \\ c_6 & 0 & -1 & 1 & 0 & 1 & 1 \end{array}$$

$$\mathbf{\Pi} = \begin{array}{c|cccccc} & e_1 & e_2 & e_3 & e_4 & e_5 & e_6 \\ \hline v_1 & 1 & 1 & 1 & 0 & 0 & 0 \\ v_2 & 0 & 0 & -1 & 1 & 1 & 0 \\ v_3 & 0 & 0 & 0 & 0 & -1 & 1 \\ v_4 & -1 & -1 & 0 & -1 & 0 & -1 \end{array}$$

**THANKS....**

Queries Please...