

NETWORK ANALYSIS AND SYNTHESIS


2.8 – Reciprocity Theorem

- ⌘ The reciprocity theorem is applicable only to single-source networks and states the following:
 - ⌘ The current I in any branch of a network, due to a single voltage source E anywhere in the network, will equal the current through the branch in which the source was originally located if the source is placed in the branch in which the current I was originally measured.
 - ⌘ The location of the voltage source and the resulting current may be interchanged without a change in current

Compensation Theorem

- In any linear bilateral active network, if any branch carrying a current I has its impedance Z
- changed by an amount ΔZ , the resulting changes that occur in the other branches are the same
- as those which would have been caused by the injection of a voltage source of $(-) I \cdot \Delta Z$ in the modified branch.


Circuit

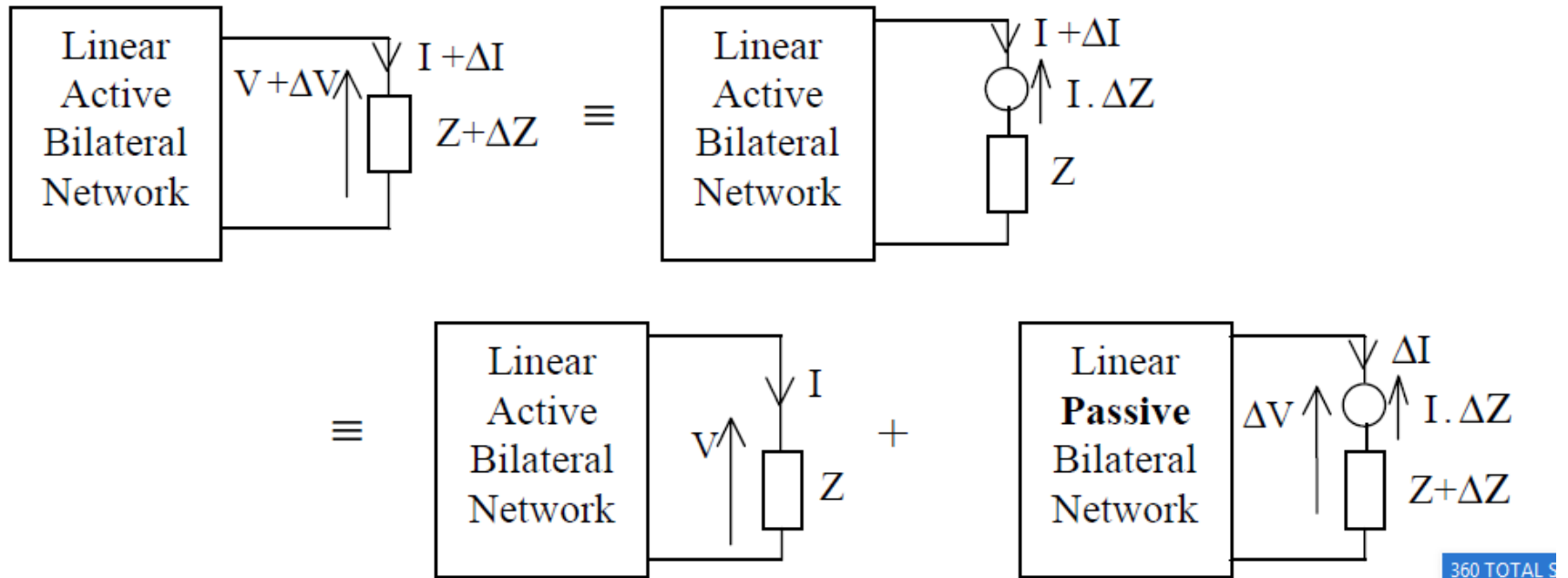

Verification

- Consider the voltage drop across the modified branch.
- $V + \Delta V = (Z + \Delta Z)(I + \Delta I) = Z \cdot I + \Delta Z \cdot I + (Z + \Delta Z) \cdot \Delta I$
from the original network, $V = Z \cdot I$
- $\therefore \Delta V = \Delta Z \cdot I + (Z + \Delta Z) \cdot \Delta I$

Example

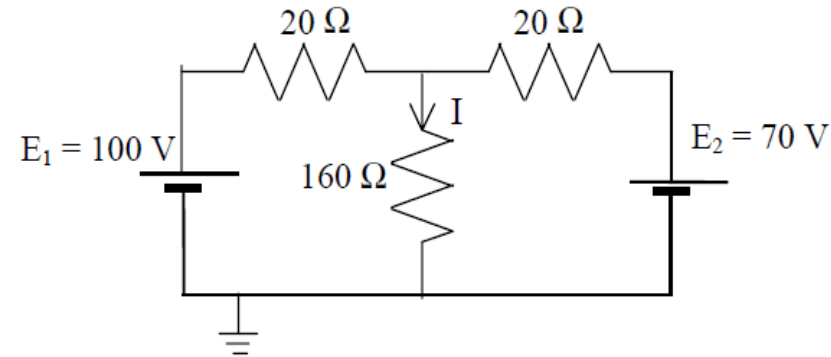

$$\Delta I = 0.6 - 0.5 = 0.1 \text{ A}$$

$$I = 0.5$$



$$\therefore \Delta I = \frac{(-)0.5 \times \Delta R}{160 + \Delta R + 20 // 20}$$

$$\text{i.e. } 0.1 = (-) \frac{0.5 \times \Delta R}{170 + \Delta R}$$

$$\therefore 17 + 0.1 \Delta R = (-) 0.5 \Delta R$$

$$\text{i.e. } \Delta R = (-)17/0.6 = (-) 28.333 \Omega$$

$$R = 160 - 28.333 = 131.67 \Omega$$

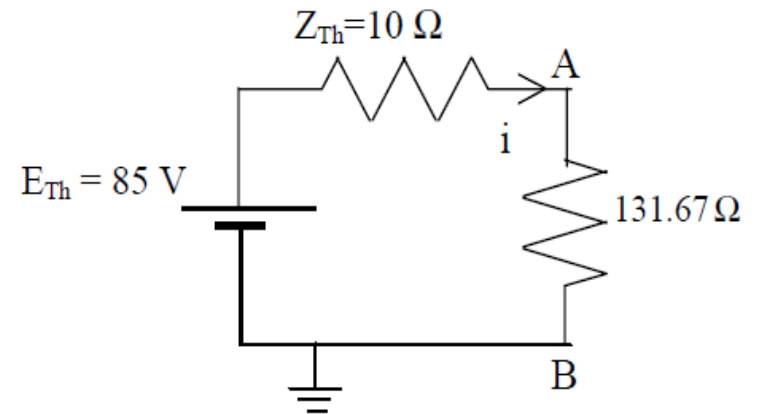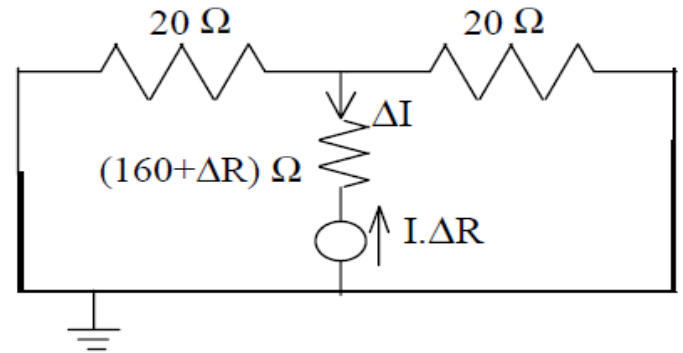

$$i = \frac{85}{10 + 131.667} = 0.6 \text{ A}$$

THANKS....

Queries Please...