


# **NETWORK ANALYSIS AND SYNTHESIS**

# Unit – III


## Transient Circuit Analysis

- Natural response and forced response,
- Transient response and steady state response for arbitrary inputs (DC and AC),
- Evaluation of time response both through classical and Laplace methods.

Circuit with switched DC excitation

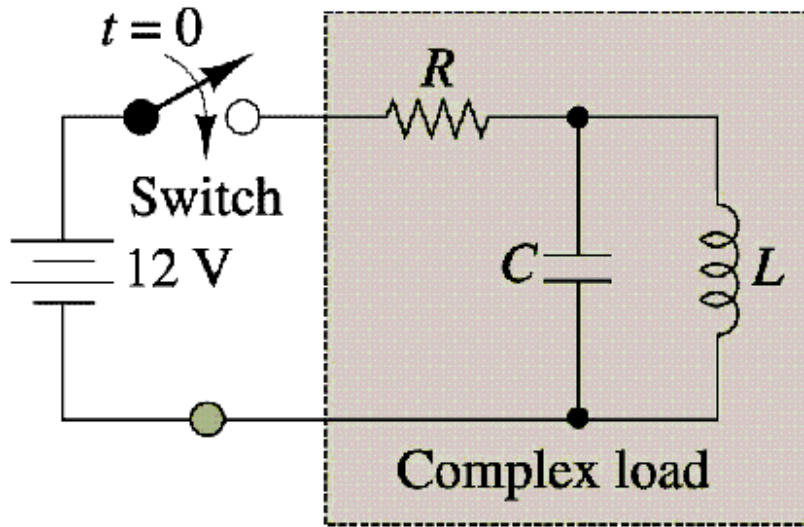


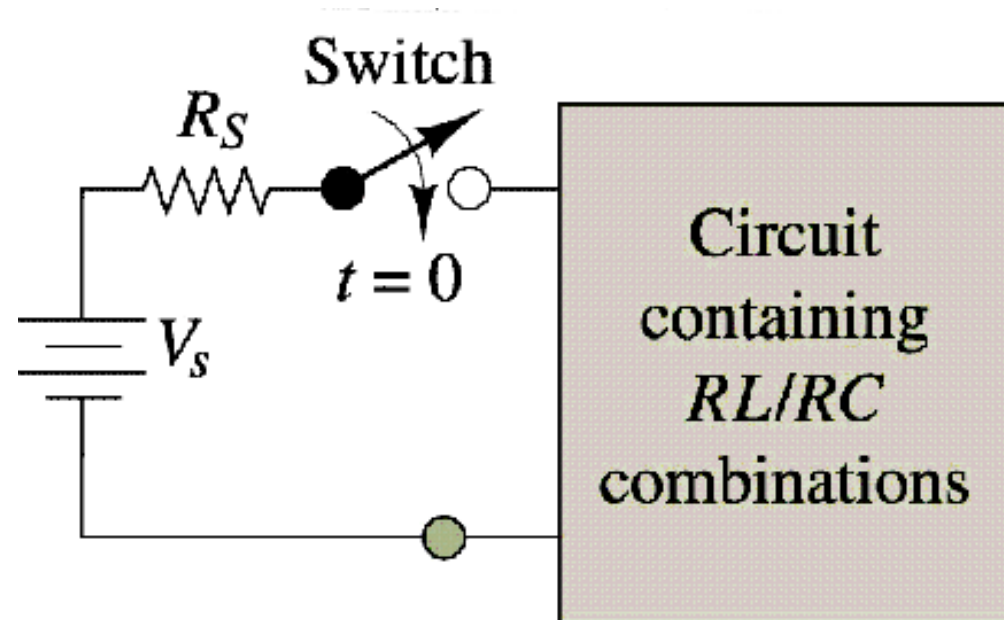
A general model of the transient analysis problem


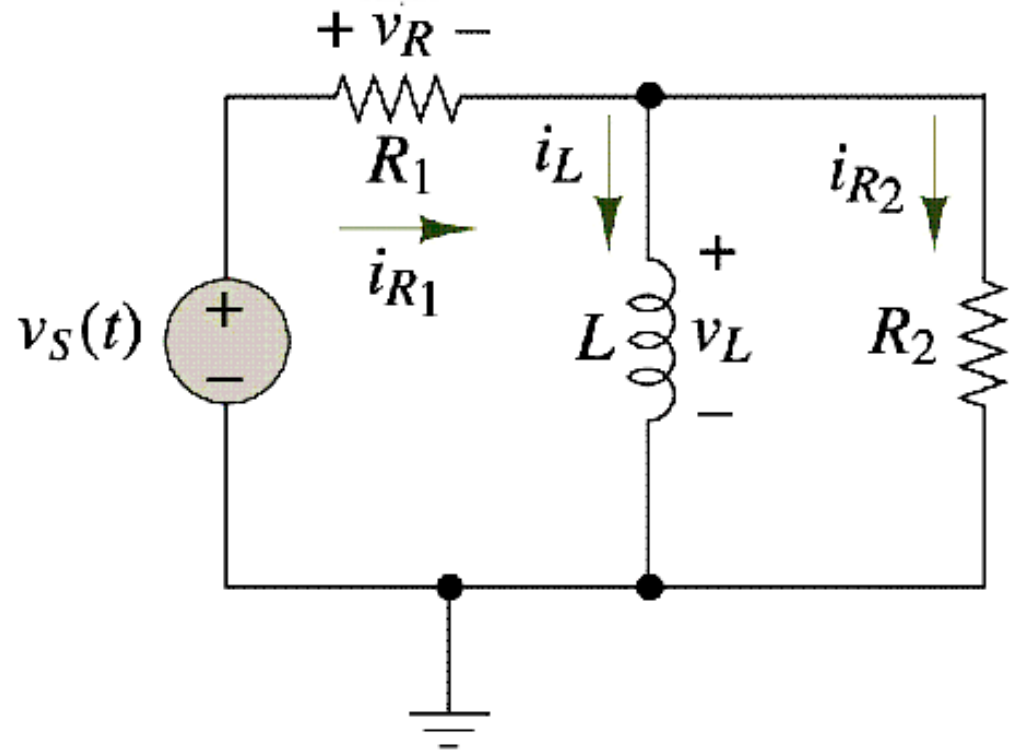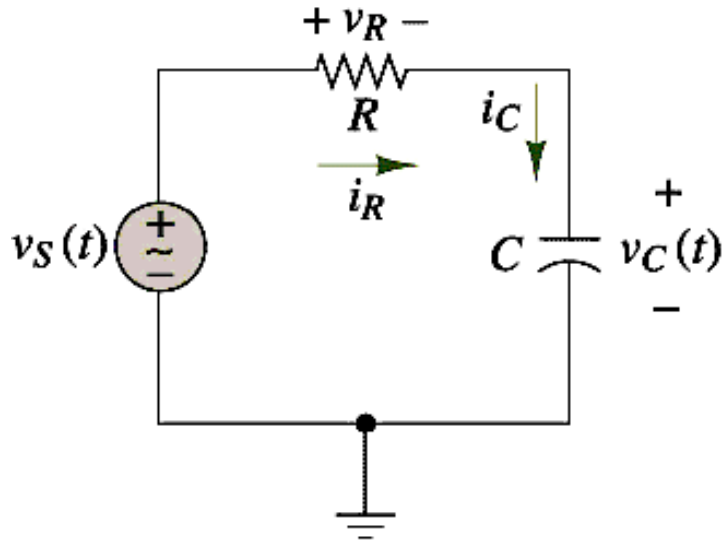
## In general, any circuit containing energy storage element


A circuit containing energy-storage elements is described by a differential equation. The differential equation describing the series  $RC$  circuit shown is

$$\frac{di_C}{dt} + \frac{1}{RC} i_C = \frac{dv_S}{dt}$$




(a) Circuit at  $t = 0$

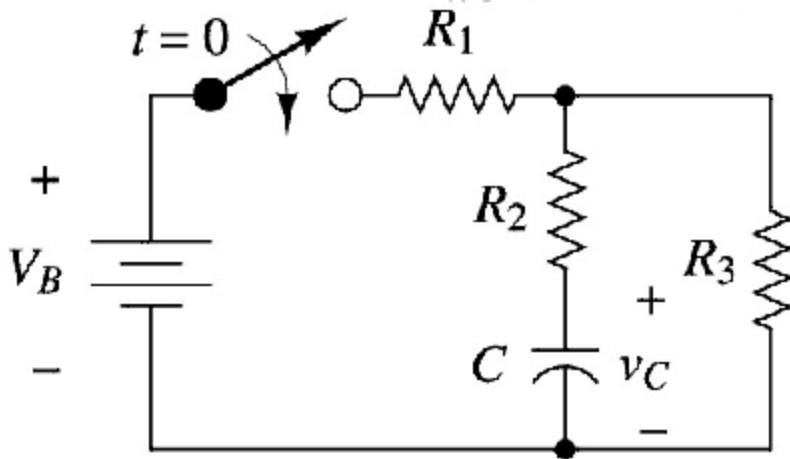(b) Same circuit a long time after the switch is closed



(a)

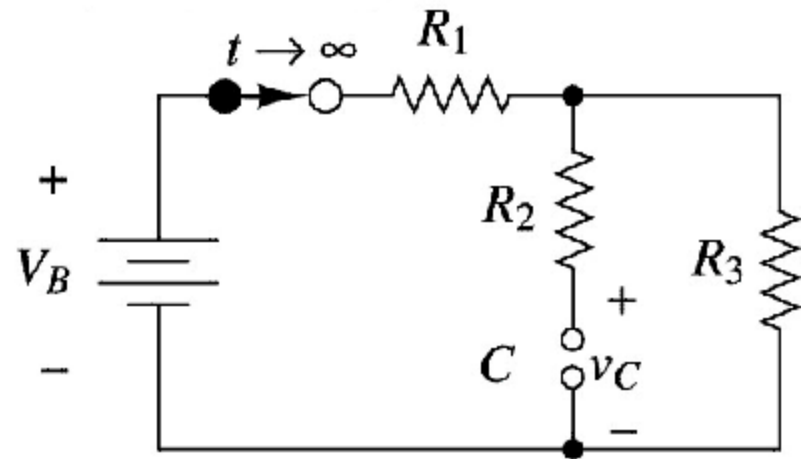


(b)


The capacitor acts as open circuit for the steady state condition (a long time after the switch is closed).

(a) Circuit for  $t = 0$

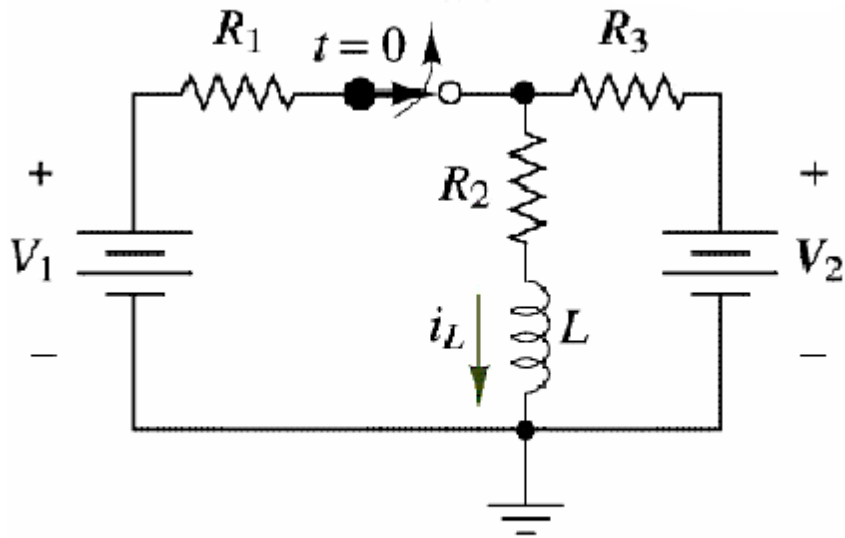(b) Same circuit a long time before the switch is opened



(a)

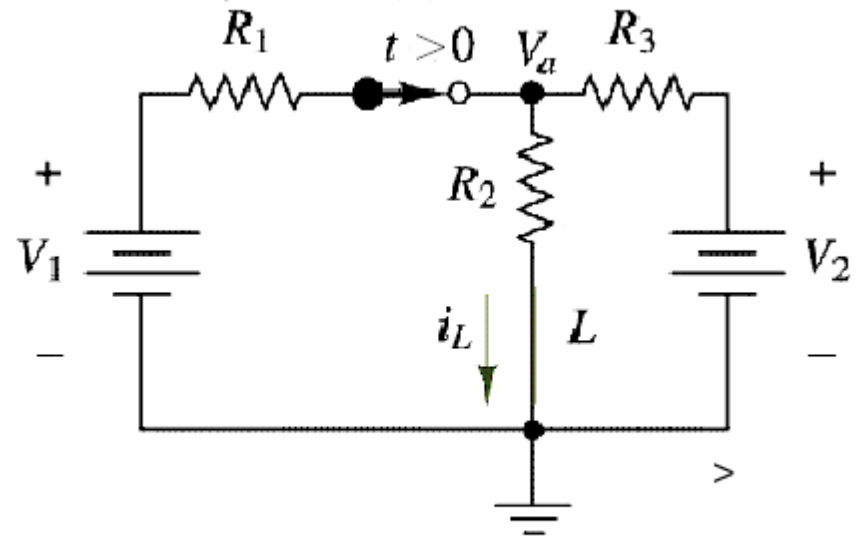

(b)

The inductor acts as short circuit for the steady state condition (a long time after the switch is closed).

**THANKS....**

Queries Please...