

NETWORK ANALYSIS AND SYNTHESIS

Unit – III

Transient Circuit Analysis

- Natural response and forced response,
- Transient response and steady state response for arbitrary inputs (DC and AC),
- Evaluation of time response both through classical and Laplace methods.

Discharge of a Capacitance through a Resistance

$$C \frac{dv_C(t)}{dt} + \frac{v_C(t)}{R} = 0$$

$$s = \frac{-1}{RC}$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 0$$

$$v_C(t) = Ke^{-t/RC}$$

$$v_C(0^+) = V_i$$


$$v_C(t) = Ke^{st}$$

$$= Ke^{0/RC}$$

$$= K$$

$$RCKse^{st} + Ke^{st} = 0$$

$$v_C(t) = V_i e^{-t/RC}$$

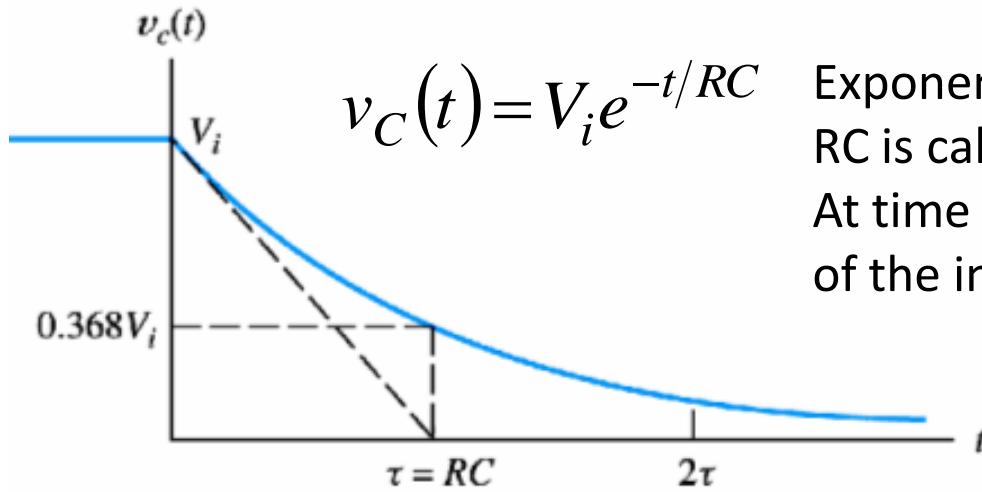


$$v_C(t) = V_i e^{-t/RC}$$

Exponential decay waveform

RC is called the time constant.

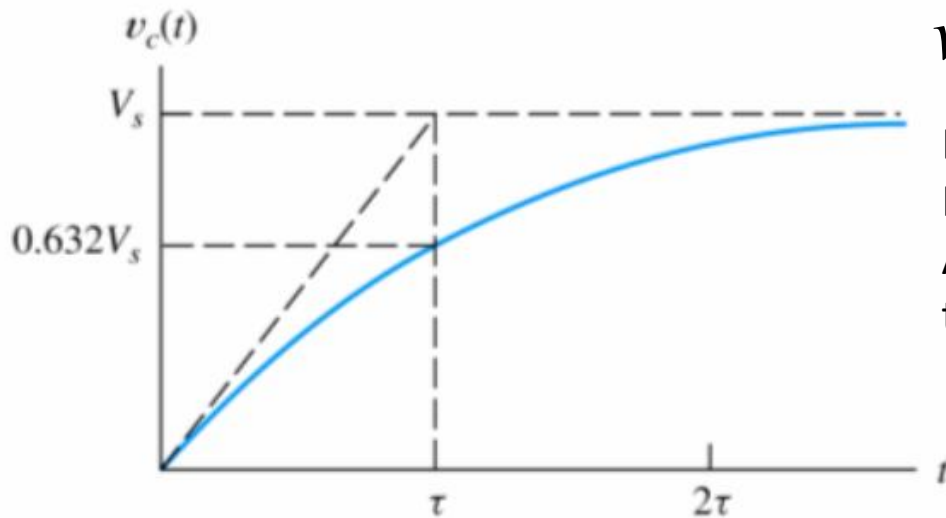At time constant, the voltage is 36.8% of the initial voltage.





$$v_C(t) = V_i (1 - e^{-t/RC})$$

Exponential rising waveform


RC is called the time constant.

At time constant, the voltage is 63.2% of the initial voltage.


RC CIRCUIT

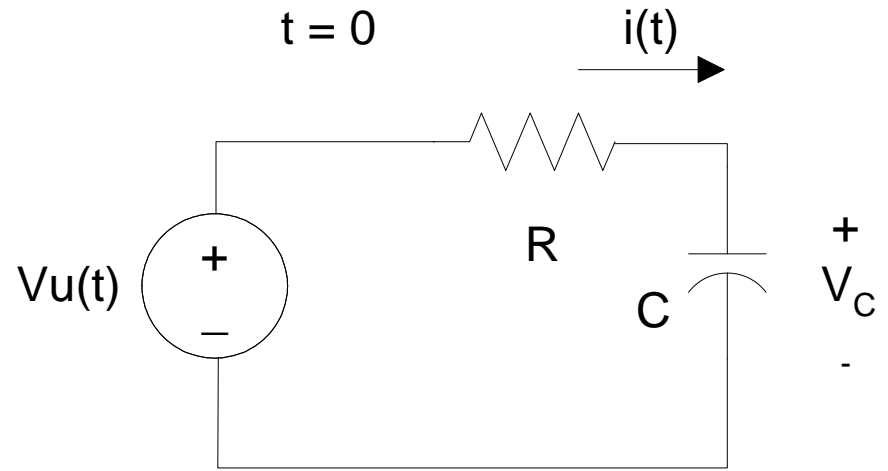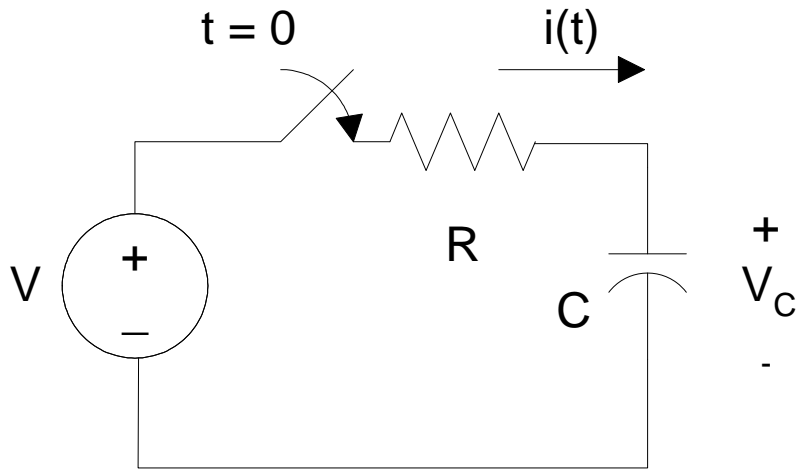

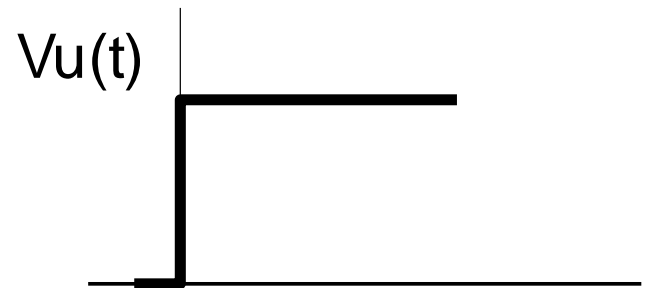for $t = 0^-$, $i(t) = 0$
 $u(t)$ is voltage-step function



RC CIRCUIT

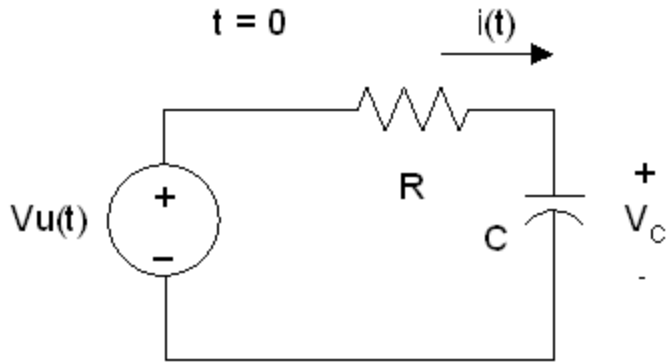


$$i_R = i_C$$

$$i_R = \frac{v_u(t) - v_C}{R}, \quad i_C = C \frac{dv_C}{dt}$$

$$RC \frac{dv_C}{dt} + v_C = V, \quad v_u(t) = V \text{ for } t \geq 0$$

Solving the differential equation

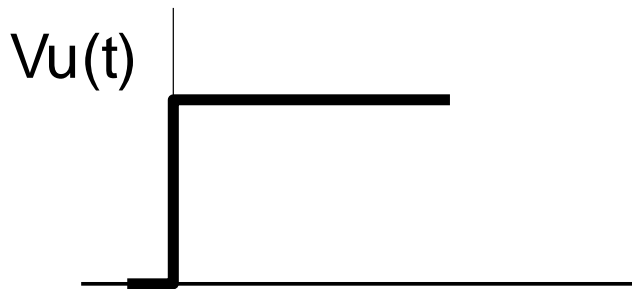


Complete Response



Complete response

= natural response + forced response

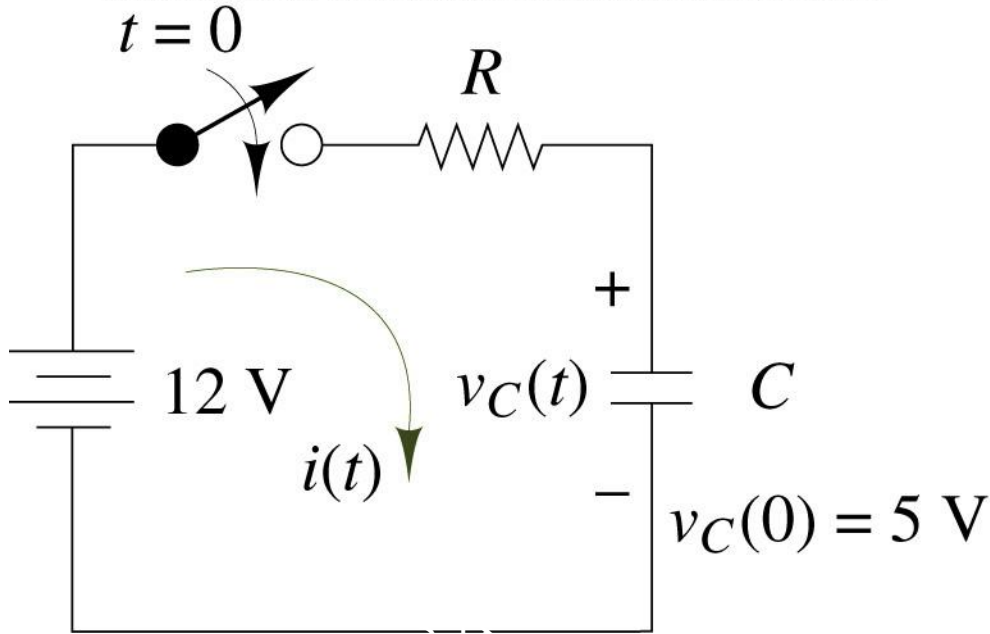- Natural response (source free response) is due to the initial condition
- Forced response is due to the external excitation.



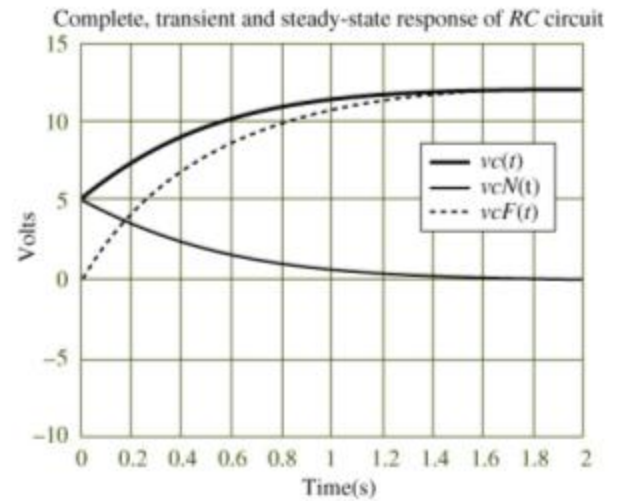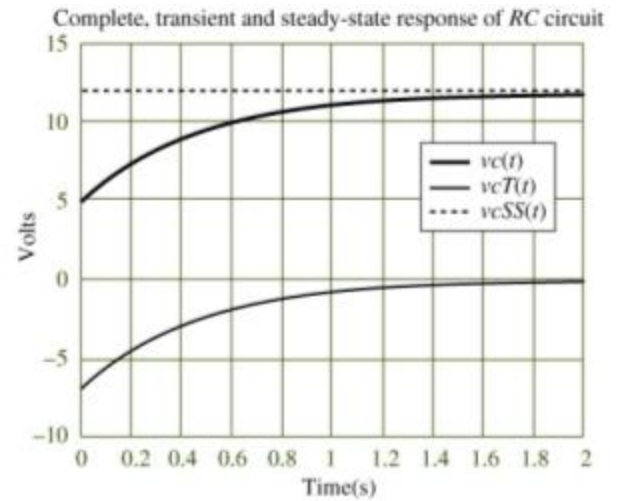- a). Complete, transient and steady state response
- b). Complete, natural, and forced responses of the circuit



THANKS....

Queries Please...