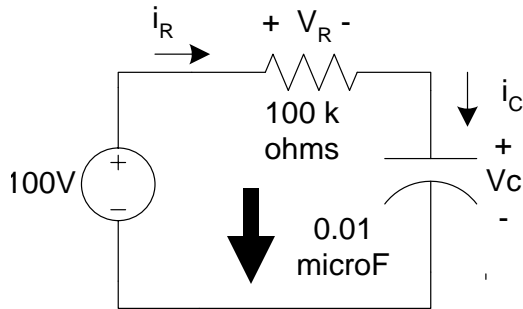


NETWORK ANALYSIS AND SYNTHESIS

Example



Initial condition $v_C(0) = 0V$

$$i_R = i_C$$


$$i_R = \frac{v_s - v_C}{R}, i_C = C \frac{dv_C}{dt}$$

$$RC \frac{dv_C}{dt} + v_C = v_s$$

$$10^5 \times 0.01 \times 10^{-6} \frac{dv_C}{dt} + v_C = 100$$

$$10^{-3} \frac{dv_C}{dt} + v_C = 100$$

Example

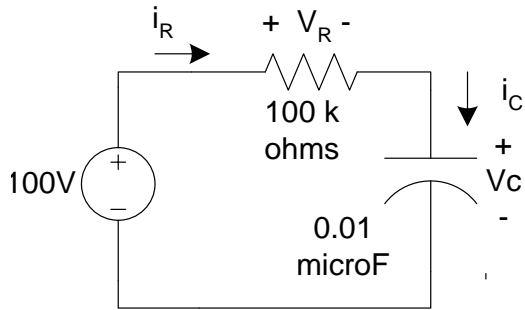

Initial condition $V_C(0) = 0V$

$$10^{-3} \frac{dv_C}{dt} + v_C = 100$$

$$\tau \frac{dx(t)}{dt} + x(t) = K_S f(t)$$

and

$$\begin{aligned} x &= x_N(t) + x_F(t) \\ &= \alpha e^{-t/\tau} + K_S F \\ &= \alpha e^{-t/\tau} + x(\infty) \end{aligned}$$

$$v_C = 100 + A e^{-\frac{t}{10^{-3}}}$$

$$\text{As } v_C(0) = 0, 0 = 100 + A$$

$$A = -100$$

$$v_C = 100 - 100 e^{-\frac{t}{10^{-3}}}$$

Energy stored in capacitor

$$p = vi = Cv \frac{dv}{dt}$$

$$\int_{t_o}^t p dt = \int_{t_o}^t Cv \frac{dv}{dt} dt = C \int_{t_o}^t v dv$$

$$= \frac{1}{2} C \left\{ [v(t)]^2 - [v(t_o)]^2 \right\}$$

If the zero-energy reference is selected at t_o , implying that the capacitor voltage is also zero at that instant, then

$$w_c(t) = \frac{1}{2} Cv^2$$

RC CIRCUIT

Power dissipation in the resistor is:


$$p_R = V^2/R = (V_o^2 / R) e^{-2t/RC}$$

Total energy turned into heat in the resistor

$$W_R = \int_0^{\infty} p_R dt = \frac{V_o^2 \int_0^{\infty} e^{-2t/RC} dt}{R}$$

$$= V_o^2 R \left(-\frac{1}{2RC} \right) e^{-2t/RC} \Big|_0^{\infty}$$

$$= \frac{1}{2} C V_o^2$$

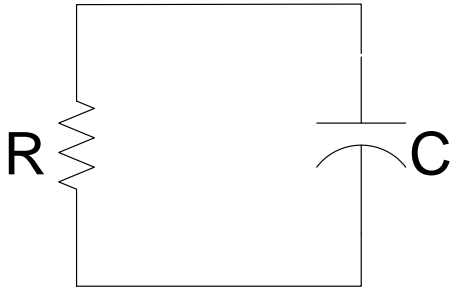

THANKS....

Queries Please...