

NETWORK ANALYSIS AND SYNTHESIS

Two Port Networks

Modifying the two port network:

We take a look at the original equations and the equations describing the new port conditions.

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 & 8 \\ 8 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_1 = 10 - 6I_1$$

$$V_2 = -4I_2$$

So we have,

$$10 - 6I_1 = 20I_1 + 8I_2$$

$$-4I_2 = 8I_1 + 12I_2$$

Two Port Networks

Modifying the two port network:

Rearranging the equations gives,

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} & \\ & \end{bmatrix}^{-1} \begin{bmatrix} \\ \end{bmatrix}$$


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \\ \end{bmatrix}$$



Two Port Networks

Y Parameters and Beyond:

Given the following network.

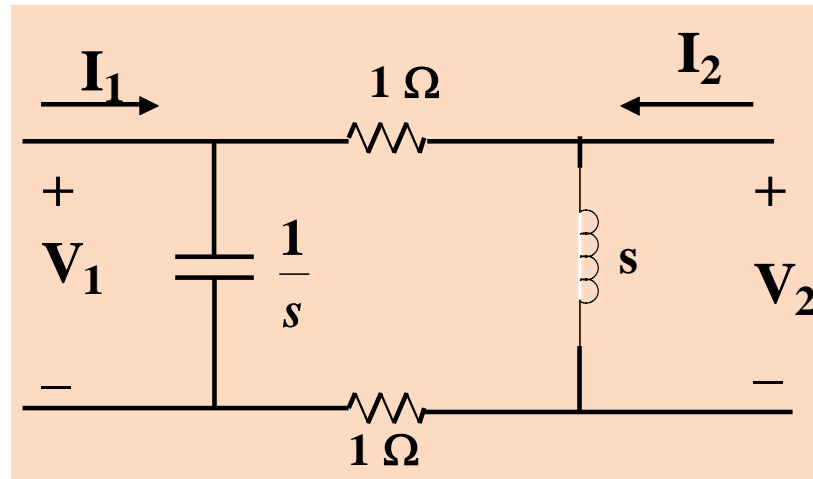


- Find the Y parameters for the network.
- From the Y parameters find the z parameters

Two Port Networks

Y Parameter Example

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

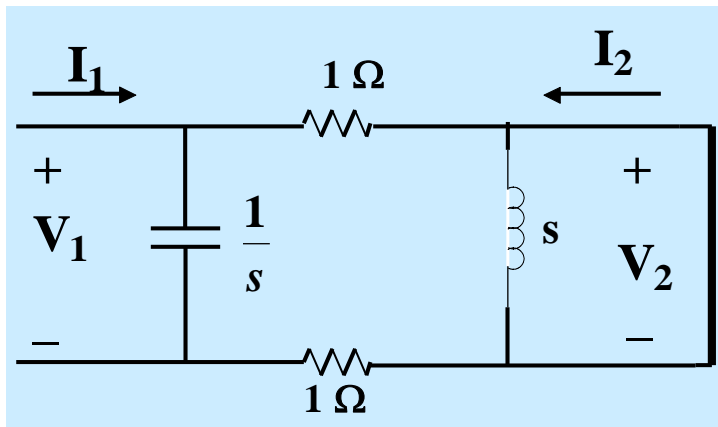

To find y_{11}

$$V_1 = I_1 \left(\frac{2/s}{2 + 1/s} \right) = I_1 \left[\frac{2}{2s + 1} \right]$$

so

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = s + 0.5$$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$


$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

We use the above equations to evaluate the parameters from the network.

Two Port Networks

Y Parameter Example

$$y_{21} = \frac{I_2}{V_1} \quad \Big| \quad V_2 = 0$$

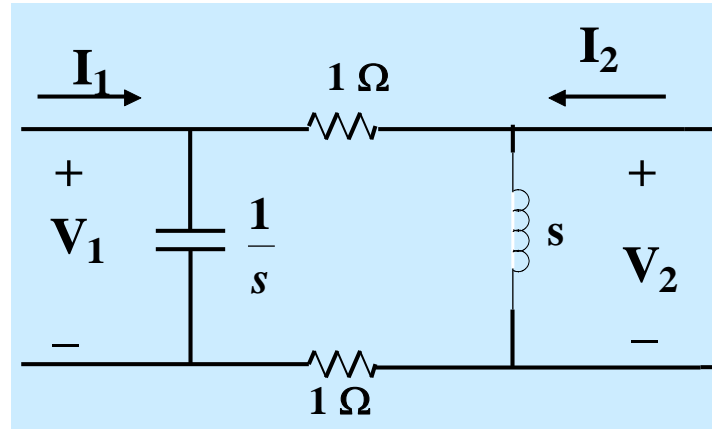

We see

$$V_1 = -2I_2$$

$$y_{21} = \frac{I_2}{V_1} = 0.5 \text{ S}$$

THANKS....

Queries Please...