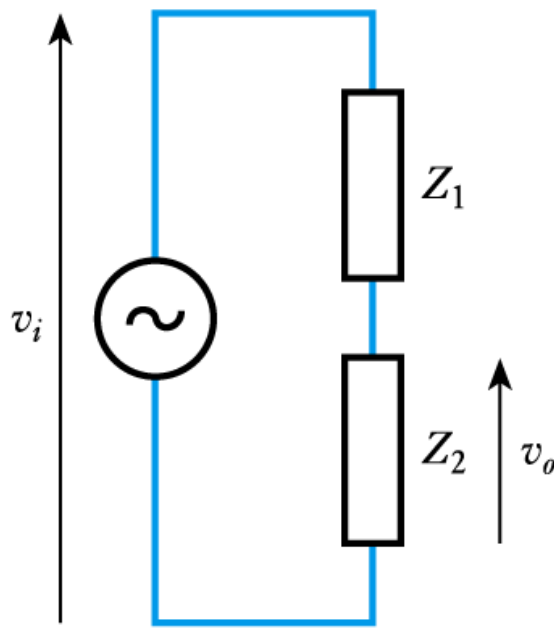


# **NETWORK ANALYSIS AND SYNTHESIS**

- We will start by considering very simple circuits
- Consider the potential divider shown here



- from our earlier consideration of the circuit

$$V_o = V_i \times \frac{Z_2}{Z_1 + Z_2}$$



- rearranging, the gain of the circuit is

$$\frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2}$$

- this is also called the **transfer function** of the circuit
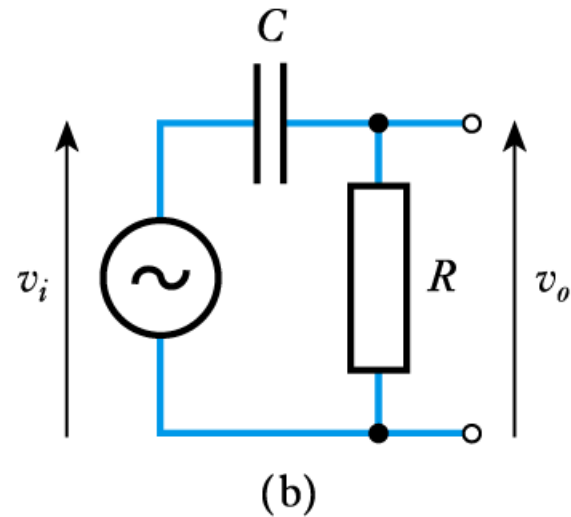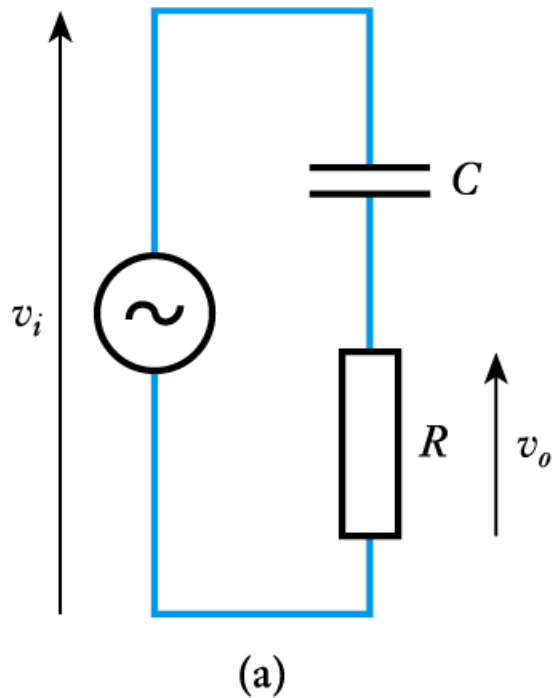
# A High-Pass $RC$ Network


- Consider the following circuit
  - which is shown re-drawn in a more usual form



- Clearly the transfer function is


$$\frac{v_o}{v_i} = \frac{\mathbf{Z}_R}{\mathbf{Z}_R + \mathbf{Z}_C} = \frac{R}{R - j\frac{1}{\omega C}} = \frac{1}{1 - j\frac{1}{\omega CR}}$$

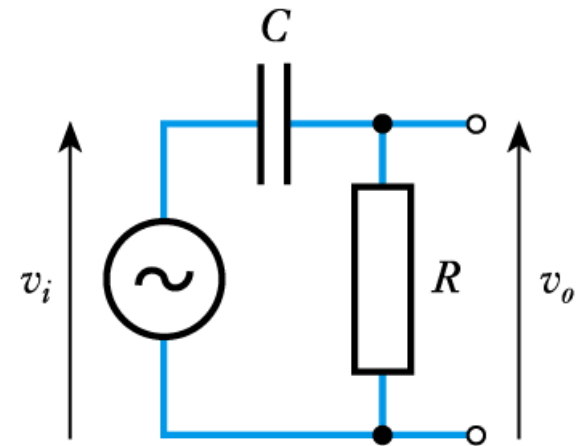- At high frequencies
  - $\omega$  is large, voltage gain  $\approx 1$
- At low frequencies
  - $\omega$  is small, voltage gain  $\rightarrow 0$



- Since the denominator has real and imaginary parts, the *magnitude* of the voltage gain is

$$|\text{Voltage gain}| = \frac{1}{\sqrt{1^2 + \left(\frac{1}{\omega CR}\right)^2}}$$

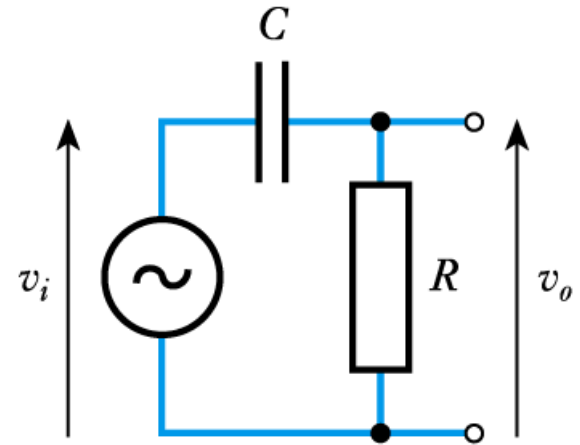

- When  $\frac{1}{\omega CR} = 1$   $|\text{Voltage gain}| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$

- This is a halving of power, or a fall in gain of 3 dB

- The half power point is the **cut-off frequency** of the circuit

- the angular frequency  $\omega_c$  at which this occurs is given by

$$\frac{1}{\omega_c CR} = 1$$

$$\omega_c = \frac{1}{CR} = \frac{1}{T} \text{ rad/s}$$

- where T is the time constant of the CR network. Also

$$f_c = \frac{\omega_c}{2\pi} = \frac{1}{2\pi CR} \text{ Hz}$$

**THANKS....**

Queries Please...