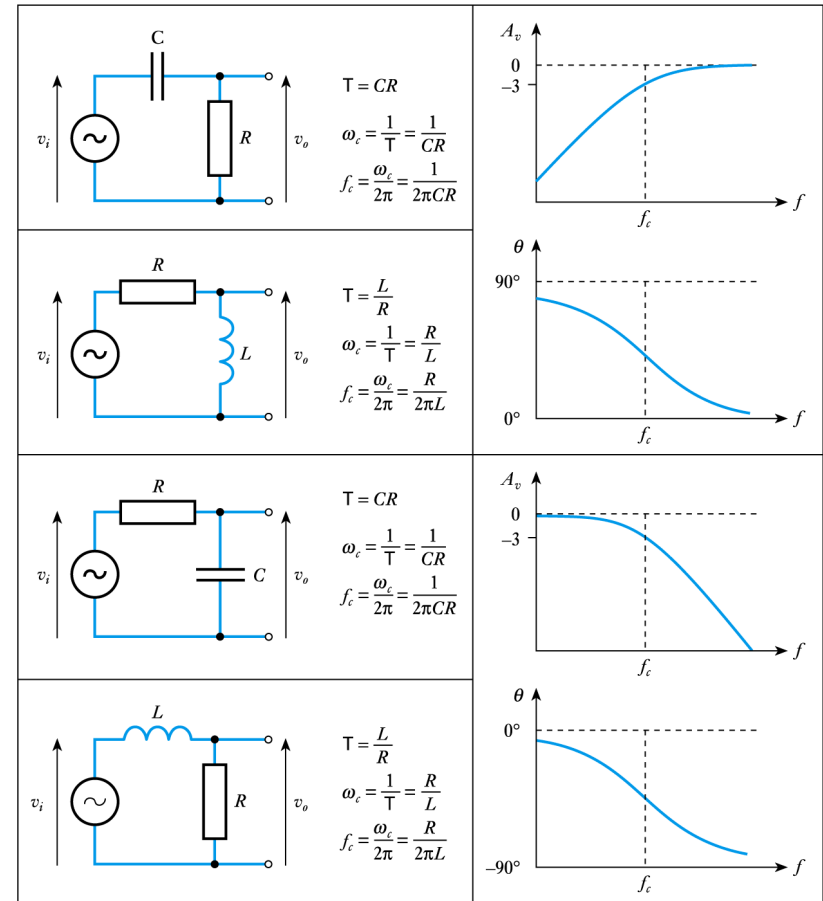


NETWORK ANALYSIS AND SYNTHESIS




A Comparison of RC and RL Networks

- Circuits using RC and RL techniques have similar characteristics
 - for a more detailed comparison, see **Figure 17.10** in the course text




Bode Diagrams

- Straight-line approximations

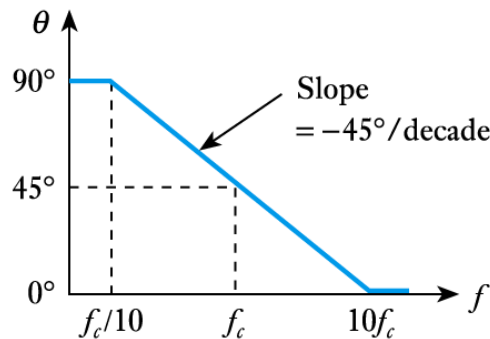
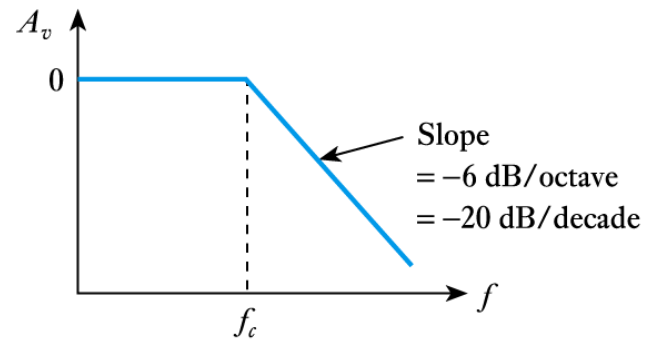
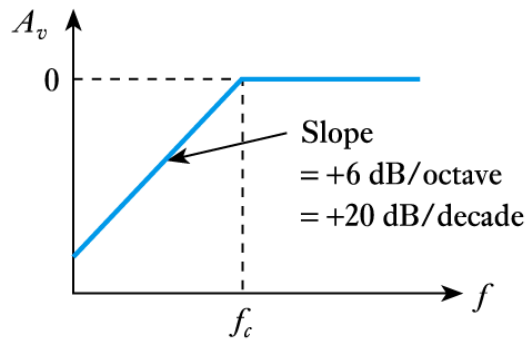


(a) High-pass circuit

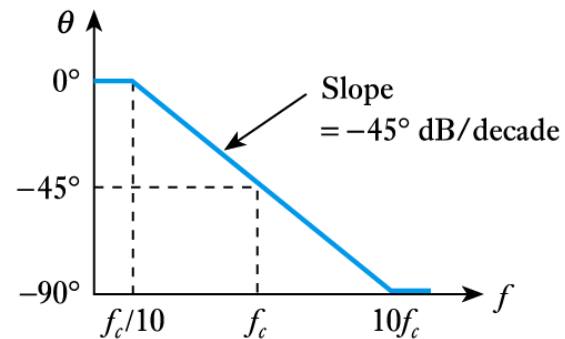


(b) Low-pass circuit

- Creating more detailed Bode diagrams

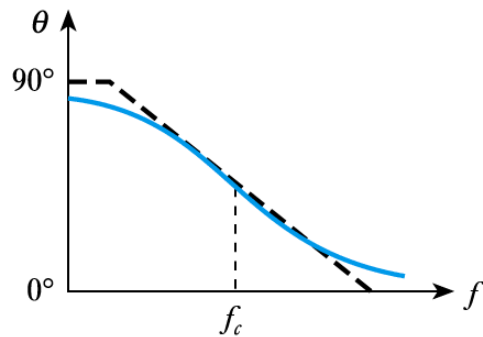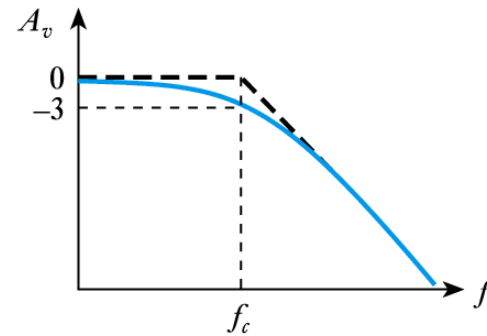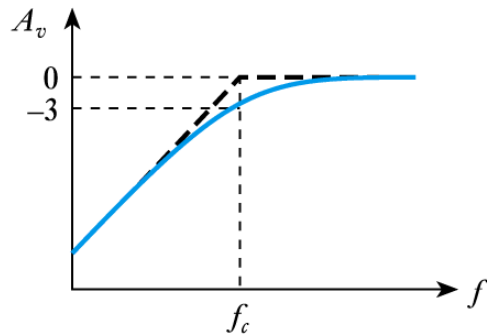


(a) High-pass circuit

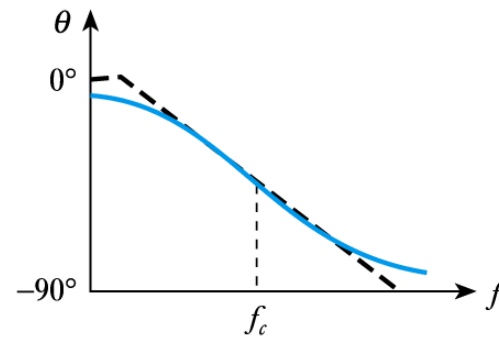

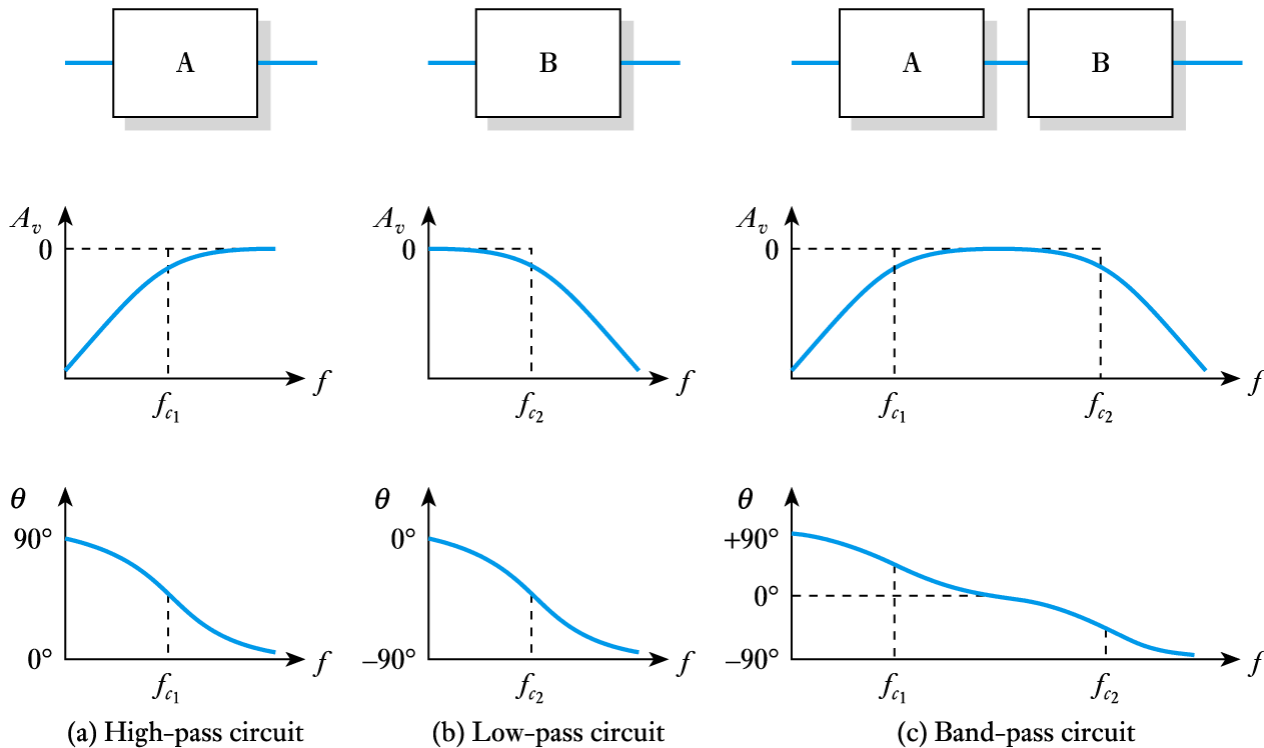
(b) Low-pass circuit

Combining the Effects of Several Stages

- The effects of several stages 'add' in bode diag



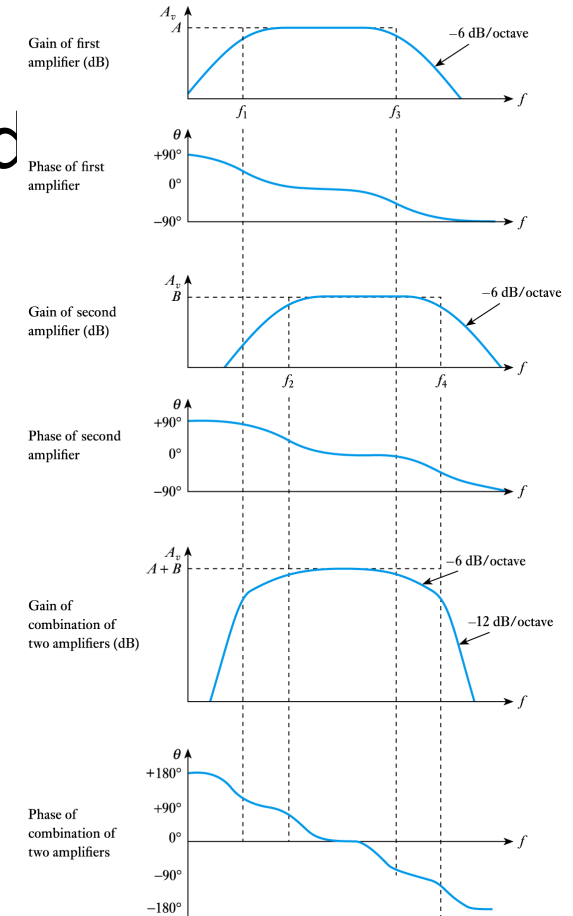- Multiple high- and low-pass elements may also be combined
 - this is illustrated in **Figure 17.14** in the course text



RLC Circuits and Resonance


- **Series RLC circuits**

- the impedance is given by

$$\mathbf{Z} = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

- if the magnitude of the reactance of the inductor and capacitor are equal, the imaginary part is zero and **the impedance is simply R**

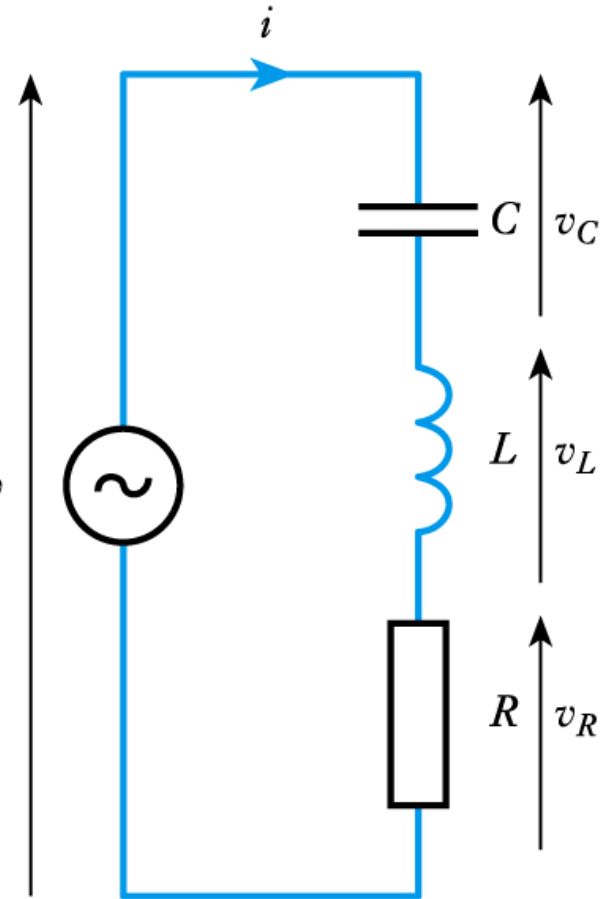
- this occurs when $\omega L = \frac{1}{\omega C}$ $\omega^2 = \frac{1}{LC}$ $\omega = \frac{1}{\sqrt{LC}}$



- This situation is referred to as **resonance**
 - the frequency at which it occurs is the **resonant frequency**

$$\omega_o = \frac{1}{\sqrt{LC}} \quad f_o = \frac{1}{2\pi\sqrt{LC}}$$

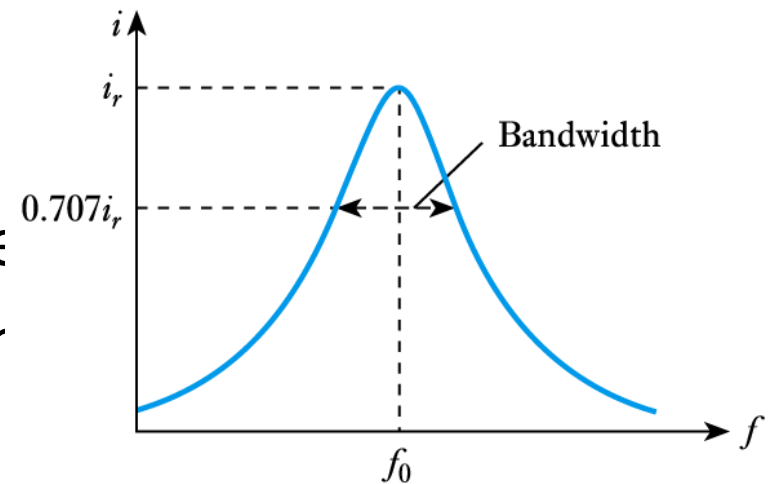- in the **series resonant circuit**, the *impedance* is at a minimum at resonance
- the *current* is at a maximum at resonance



- The resonant effect can be quantified by the **quality factor, Q**

- this is the ratio of the energy dissipated to the energy stored in each cycle

- it can be shown that

$$\text{Quality factor } Q = \frac{X_L}{R} = \frac{X_C}{R}$$

- and

$$Q = \frac{1}{R} \sqrt{\left(\frac{L}{C}\right)}$$

THANKS....

Queries Please...