


# **NETWORK ANALYSIS AND SYNTHESIS**

- The series *RLC* circuit is an **acceptor circuit**
  - the narrowness of bandwidth is determined by the  $Q$

$$\text{Quality factor } Q = \frac{\text{Resonant frequency}}{\text{Bandwidth}} = \frac{f_o}{B}$$

- combining this eqn  $B = \frac{R}{2\pi L} \text{ Hz}$  with the earlier one gives

- **Parallel *RLC* circuits**

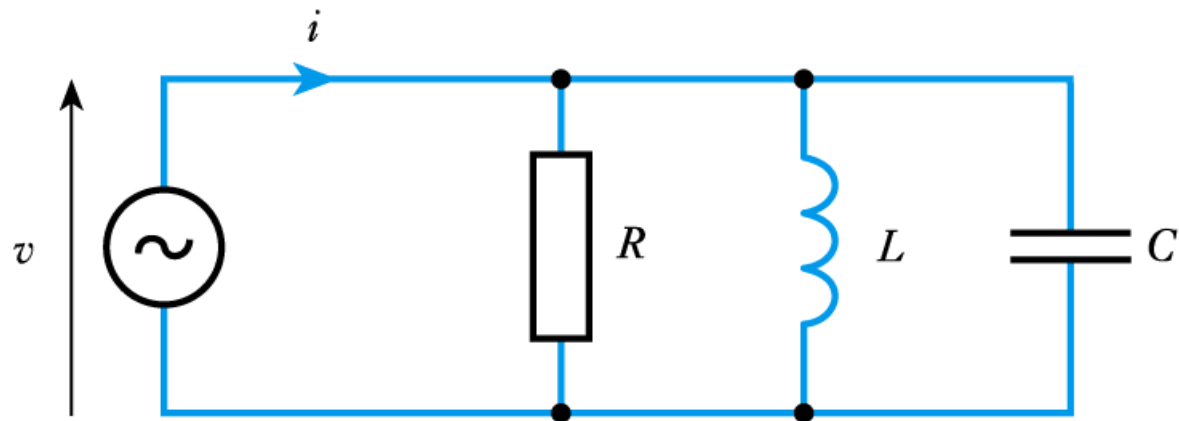

– as before

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$


- The parallel arrangement is a **rejector circuit**

- in the **parallel resonant circuit**, the *impedance* is at a maximum at resonance
- the *current* is at a minimum at resonance

- in this circuit

$$Q = R \sqrt{\left(\frac{C}{L}\right)}$$


$$B = \frac{1}{2\pi RC} \text{ Hz}$$

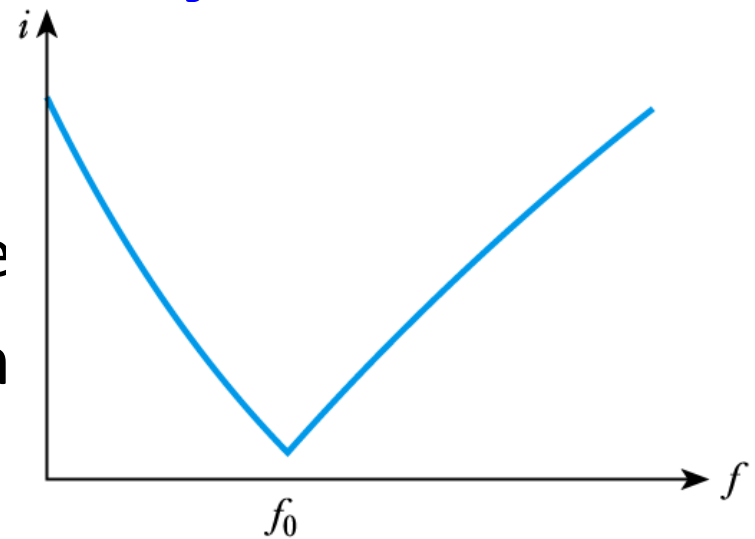

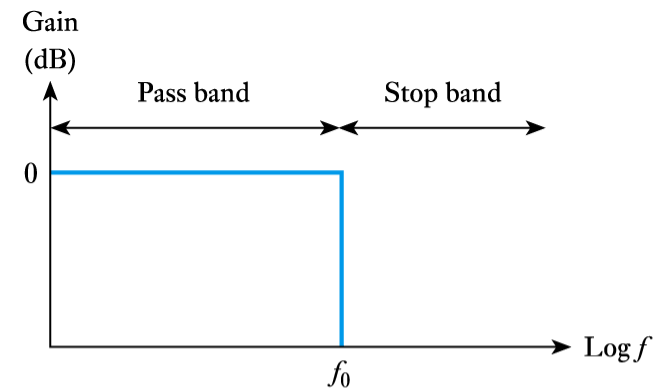
# Filters

- **RC Filters**
- The *RC* networks considered earlier are **first-order** or **single-pole** filters
  - these have a maximum roll-off of 6 dB/octave
  - they also produce a maximum of 90° phase shift
- Combining multiple stages can produce filters with a greater ultimate roll-off rates (12 dB, 18 dB, etc.) but such filters have a very soft ‘knee’

- An ideal filter would have constant gain and zero phase shift for frequencies within its **pass band**, and zero gain for frequencies outside this range (its **stop band**)
- Real filters do not have these idealised characteristics



(a) An ideal low-pass filter

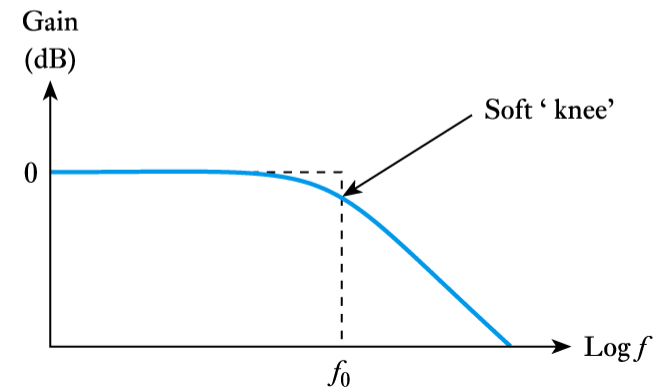

(b) A multi-stage RC filter

**THANKS....**

Queries Please...