


# **NETWORK ANALYSIS AND SYNTHESIS**

- **LC Filters**


- Simple LC filters can be produced using series or parallel tuned circuits

- these produce narrow-band filters with a centre

freq  $f_0 = \frac{1}{2\pi\sqrt{LC}}$

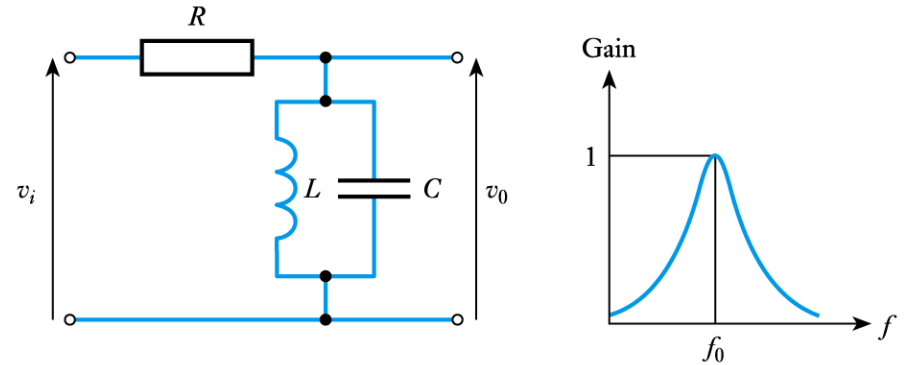


(a) A parallel LC network

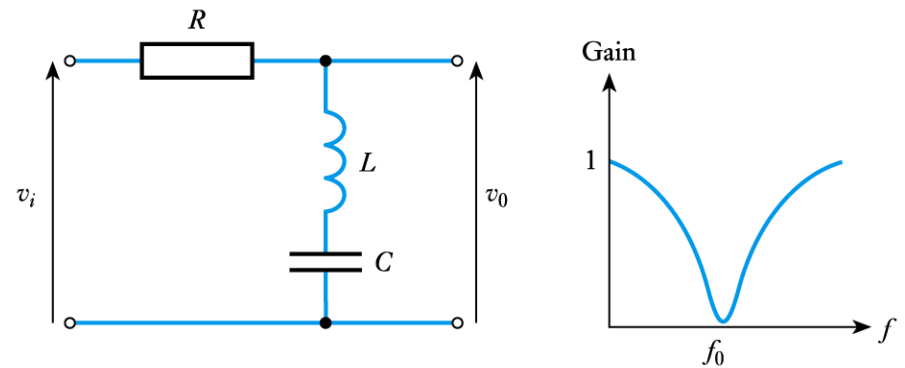



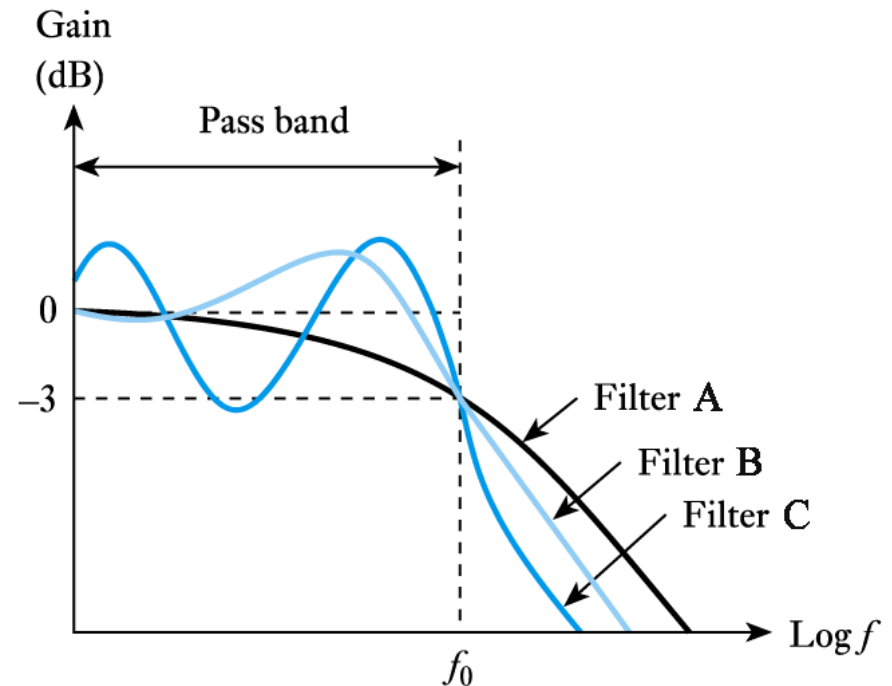
(b) A series LC network


- **Active filters**

- combining an op-amp with suitable resistors and capacitors can produce a range of filter characteristics
- these are termed **active filters**




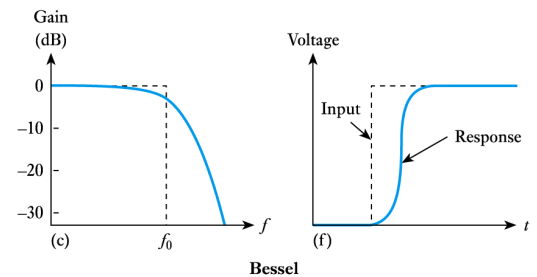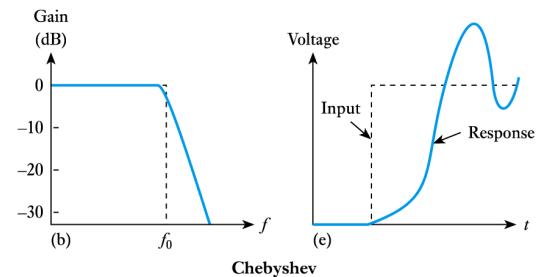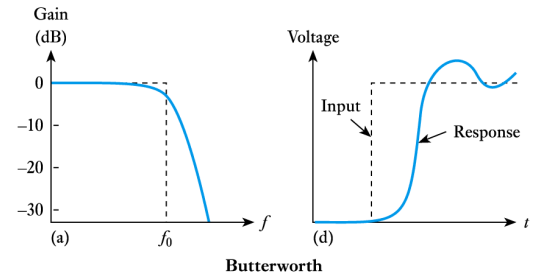- Common forms include:
  - **Butterworth**
    - optimised for a flat response
  - **Chebyshev**
    - optimised for a sharp ‘knee’
  - **Bessel**
    - optimised for its phase response
- see **Section 17.10.3** of the course text for more information on these




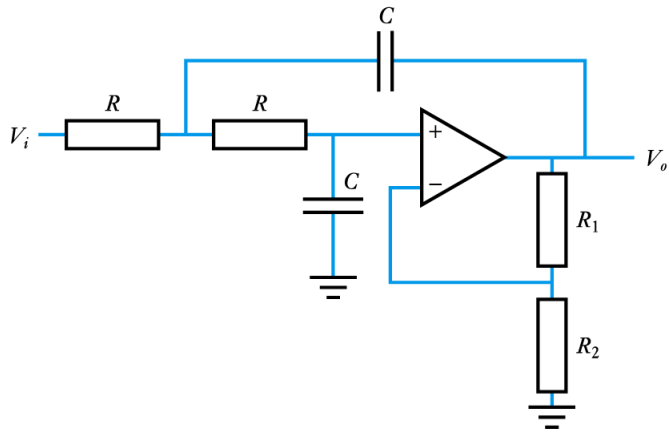


(a) A low-pass filter

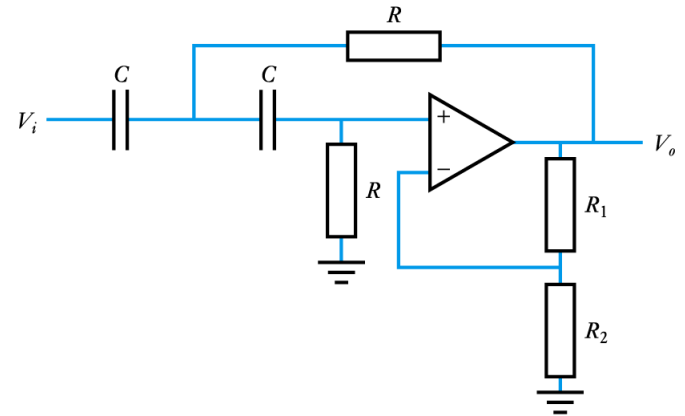

(b) A high-pass filter

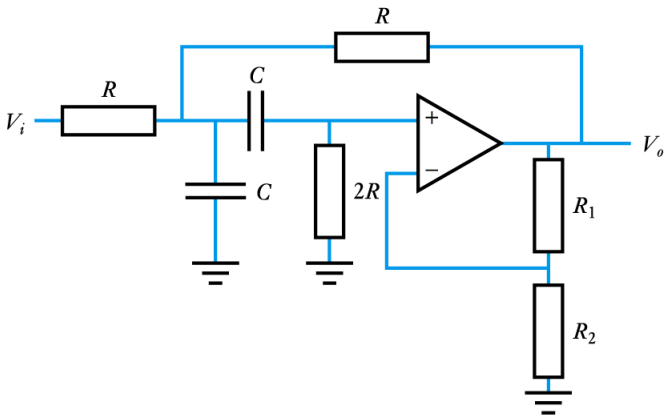


(c) A band-pass filter

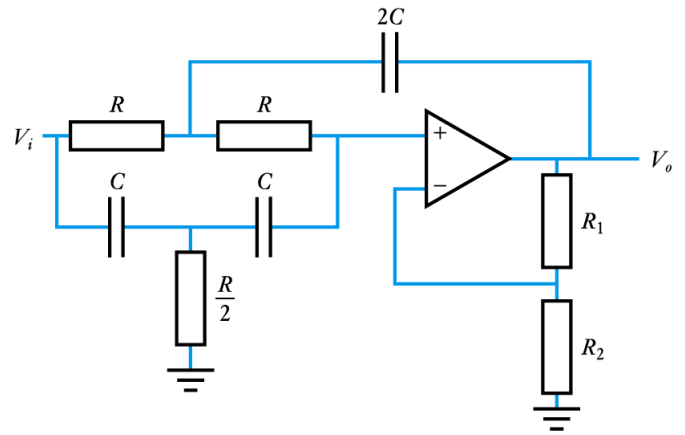


(d) A band-stop filter
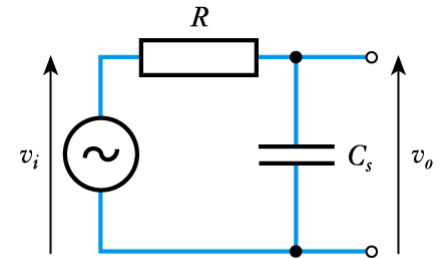
# Stray Capacitance and Inductance


- All circuits have stray capacitance and stray inductance
  - these unintended elements can dramatically affect circuit operation
  - for example:
    - (a)  $C_s$  adds an unintended low-pass filter
    - (b)  $L_s$  adds an unintended low-pass filter
    - (c)  $C_s$  produces an unintended resonant circuit and can produce instability



(a)

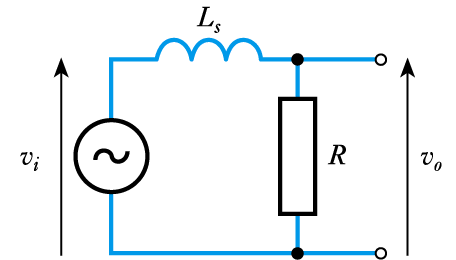

(b)

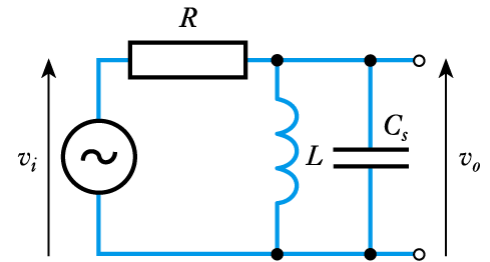

(c)

# Key Points

- The reactance of capacitors and inductors is dependent on frequency
- Single *RC* or *RL* networks can produce an arrangement with a single upper or lower cut-off frequency.
- In each case the angular cut-off frequency  $\omega_o$  is given by the reciprocal of the time constant  $T$
- For an *RC* circuit  $T = CR$ , for an *RL* circuit  $T = L/R$
- Resonance occurs when the reactance of the capacitive element cancels that of the inductive element
- Simple *RC* or *RL* networks represent single-pole filters
- Active filters produce high performance without inductors
- Stray capacitance and inductance are found in all circuits

**THANKS....**

Queries Please...