

# DC Choppers



# Introduction

- Chopper is a static device.
- A variable dc voltage is obtained from a constant dc voltage source.
- Also known as dc-to-dc converter.
- Widely used for motor control.
- Also used in regenerative braking.
- Thyristor converter offers greater efficiency, faster response, lower maintenance, smaller size and smooth control.




# Choppers are of Two Types

- Step-down choppers.
- Step-up choppers.
  - In step down chopper output voltage is less than input voltage.
  - In step up chopper output voltage is more than input voltage.





# Principle Of Step-down Chopper

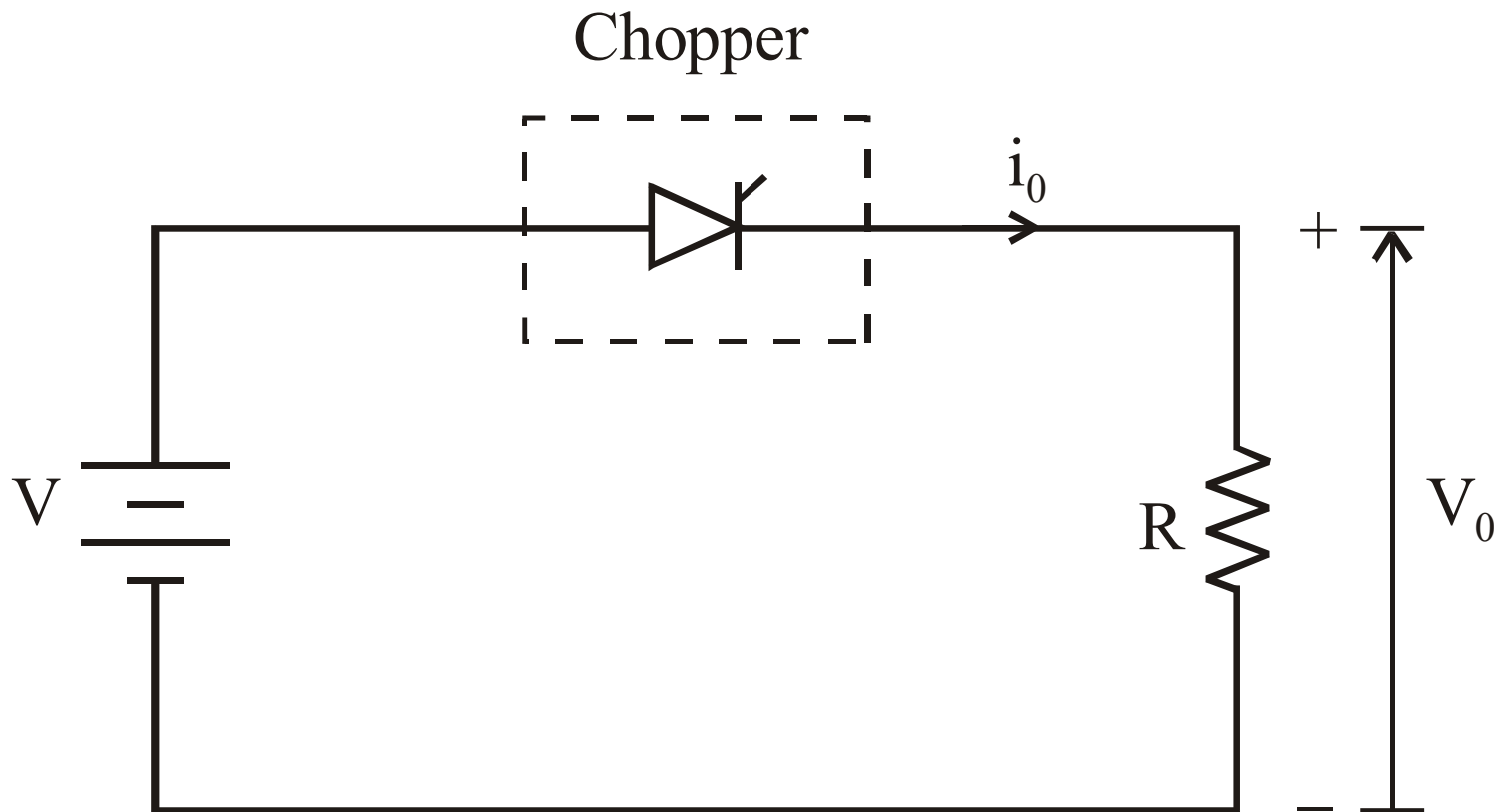

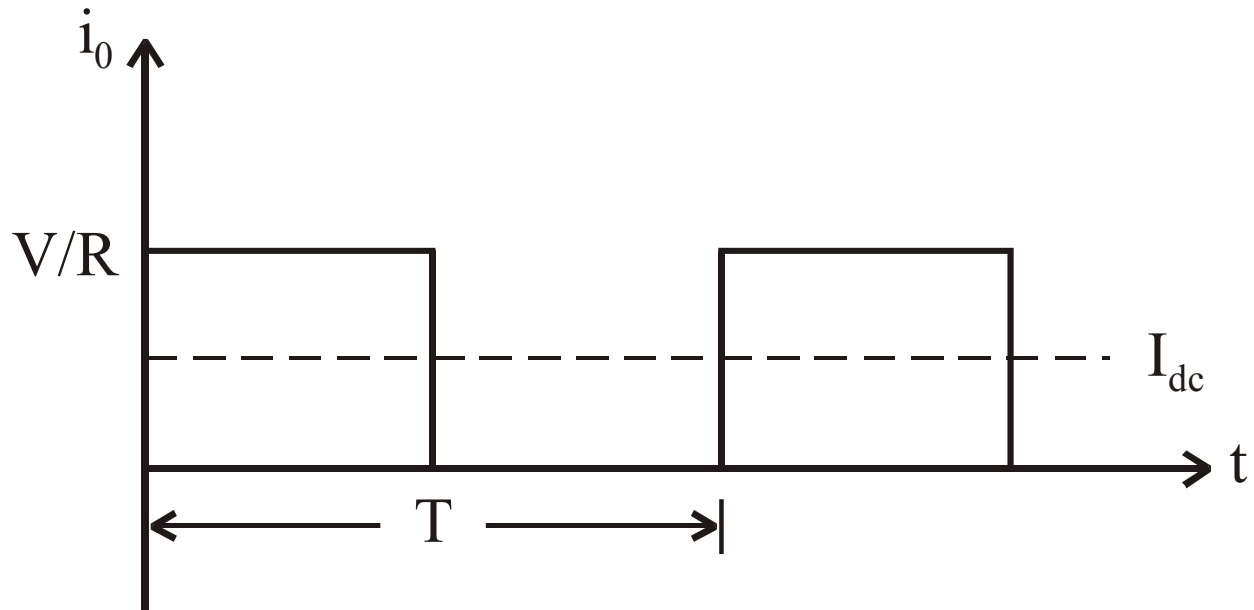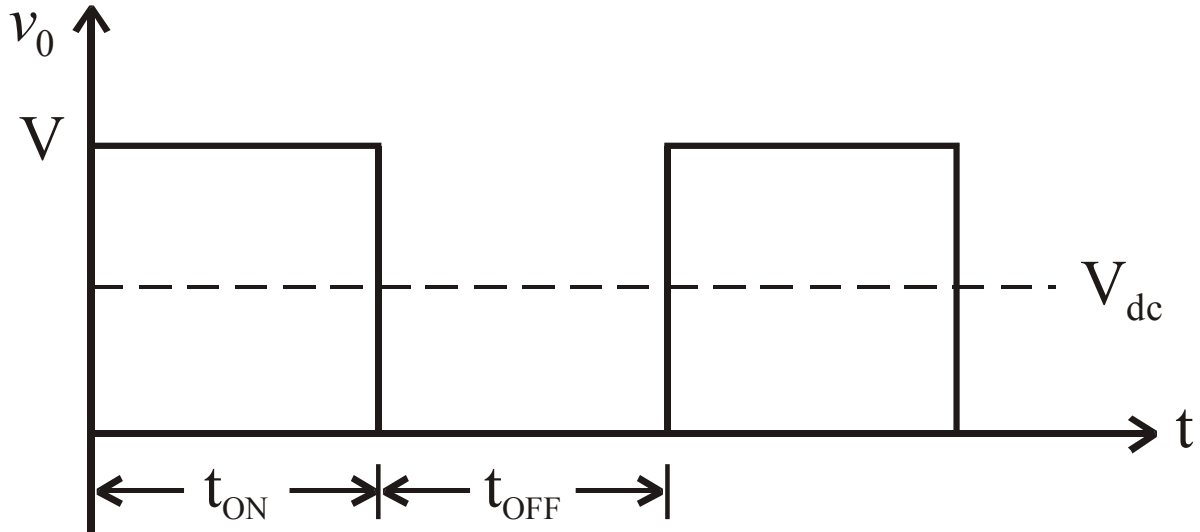- A step-down chopper with resistive load.
- The thyristor in the circuit acts as a switch.
- When thyristor is ON, supply voltage appears across the load
- When thyristor is OFF, the voltage across the load will be zero.





# Average Output Voltage

$$V_{dc} = V \left( \frac{t_{ON}}{t_{ON} + t_{OFF}} \right)$$

$$V_{dc} = V \left( \frac{t_{ON}}{T} \right) = V \cdot d$$

*but*  $\left( \frac{t_{ON}}{t} \right) = d = \text{duty cycle}$



# Average Output Current

$$I_{dc} = \frac{V_{dc}}{R}$$

$$I_{dc} = \frac{V}{R} \left( \frac{t_{ON}}{T} \right) = \frac{V}{R} d$$

RMS value of output voltage

$$V_o = \sqrt{\frac{1}{T} \int_0^{t_{ON}} v_o^2 dt}$$





But during  $t_{ON}$ ,  $v_o = V$

Therefore RMS output voltage

$$V_o = \sqrt{\frac{1}{T} \int_0^{t_{ON}} V^2 dt}$$

$$V_o = \sqrt{\frac{V^2}{T} t_{ON}} = \sqrt{\frac{t_{ON}}{T}} \cdot V$$

$$V_o = \sqrt{d} \cdot V$$



Output power  $P_o = V_o I_o$

But  $I_o = \frac{V_o}{R}$

$\therefore$  Output power

$$P_o = \frac{V_o^2}{R}$$

$$P_o = \frac{dV^2}{R}$$



# Effective input resistance of chopper

$$R_i = \frac{V}{I_{dc}}$$

$$R_i = \frac{R}{d}$$

The output voltage can be varied by varying the duty cycle.



# Methods Of Control

- The output dc voltage can be varied by the following methods.
  - Pulse width modulation control or constant frequency operation.
  - Variable frequency control.



# Pulse Width Modulation

- $t_{ON}$  is varied keeping chopping frequency ' $f$ ' & chopping period ' $T$ ' constant.
- Output voltage is varied by varying the ON time  $t_{ON}$



