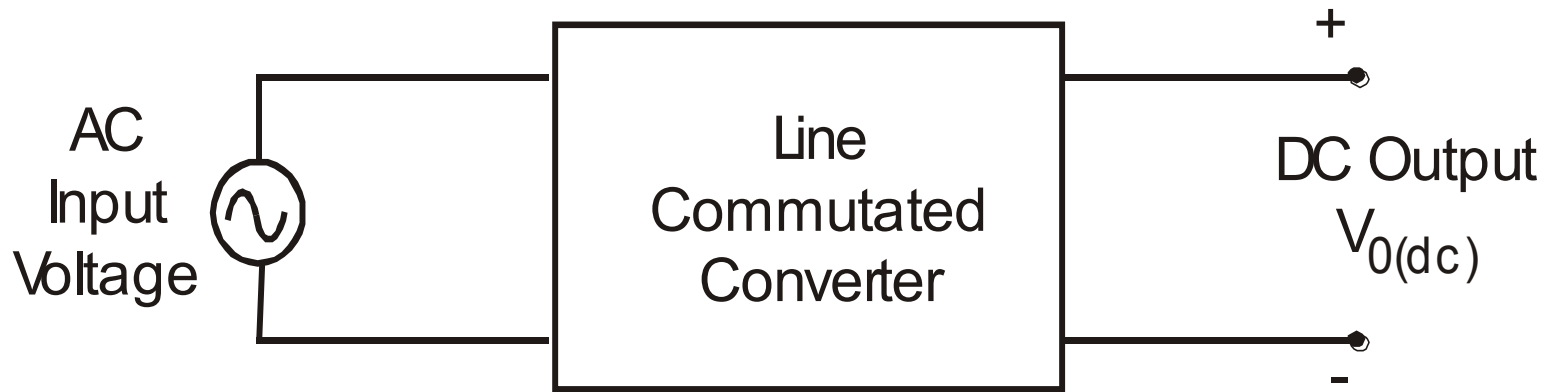


# Controlled Rectifiers

*(Line Commutated AC to DC converters)*



- Type of input: Fixed voltage, fixed frequency ac power supply.
- Type of output: Variable dc output voltage
- Type of commutation: Natural / AC line commutation.

# Different types of Line Commutated Converters

- AC to DC Converters (Phase controlled rectifiers)
- AC to AC converters (AC voltage controllers)
- AC to AC converters (Cyclo converters) at low output frequency.

# Differences Between Diode Rectifiers & Phase Controlled Rectifiers

- The diode rectifiers are referred to as uncontrolled rectifiers .
- The diode rectifiers give a fixed dc output voltage .
- Each diode conducts for one half cycle.
- Diode conduction angle =  $180^0$  or  $\pi$  radians.
- We can not control the dc output voltage or the average dc load current in a diode rectifier circuit.

Single phase half wave diode rectifier gives an

Average dc output voltage  $V_{O(dc)} = \frac{V_m}{\pi}$

Single phase full wave diode rectifier gives an

Average dc output voltage  $V_{O(dc)} = \frac{2V_m}{\pi}$

# Applications of Phase Controlled Rectifiers

- DC motor control in steel mills, paper and textile mills employing dc motor drives.
- AC fed traction system using dc traction motor.
- Electro-chemical and electro-metallurgical processes.
- Magnet power supplies.
- Portable hand tool drives.

# Classification of Phase Controlled Rectifiers

- Single Phase Controlled Rectifiers.
- Three Phase Controlled Rectifiers.




# Different types of Single Phase Controlled Rectifiers.


- Half wave controlled rectifiers.
- Full wave controlled rectifiers.
  - Using a center tapped transformer.
  - Full wave bridge circuit.
    - Semi converter.
    - Full converter.

# Different Types of Three Phase Controlled Rectifiers

- Half wave controlled rectifiers.
- Full wave controlled rectifiers.
  - Semi converter (half controlled bridge converter).
  - Full converter (fully controlled bridge converter).
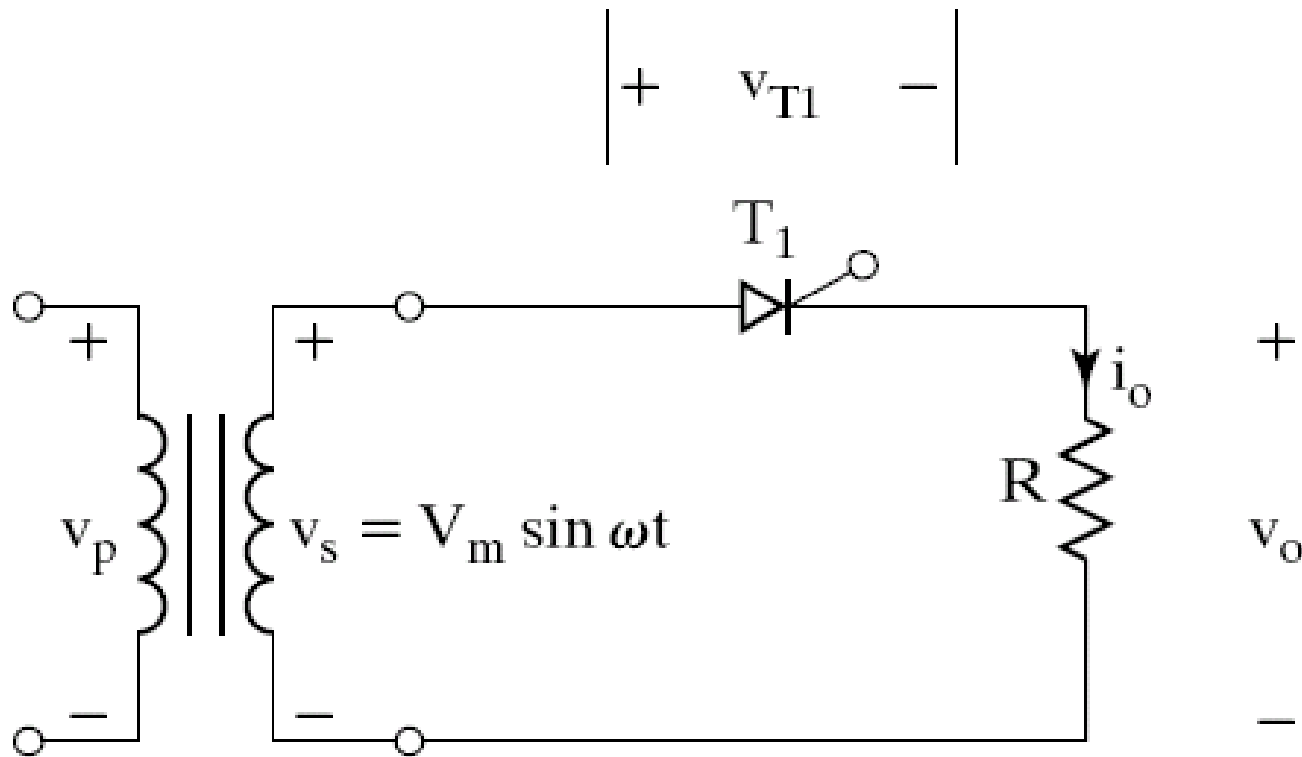
# Single Phase Half-Wave Thyristor Converter with a Resistive Load




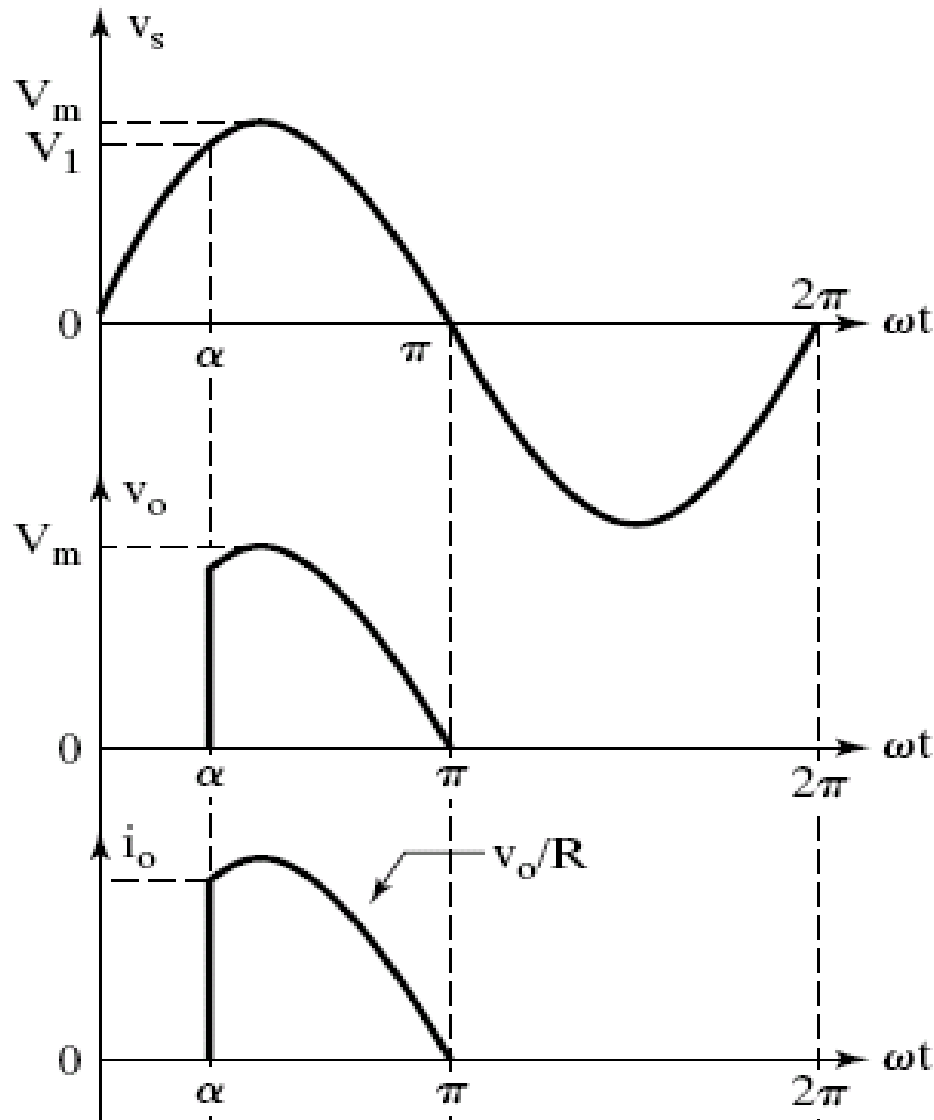


Supply Voltage

Output Voltage

Output (load)  
Current

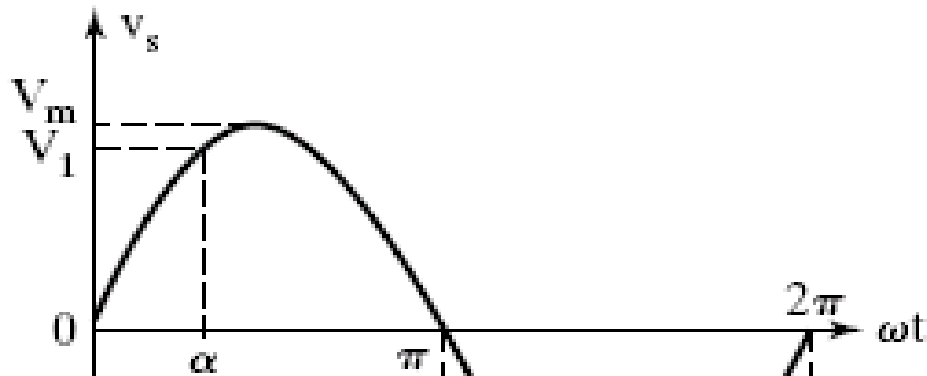

Supply Voltage

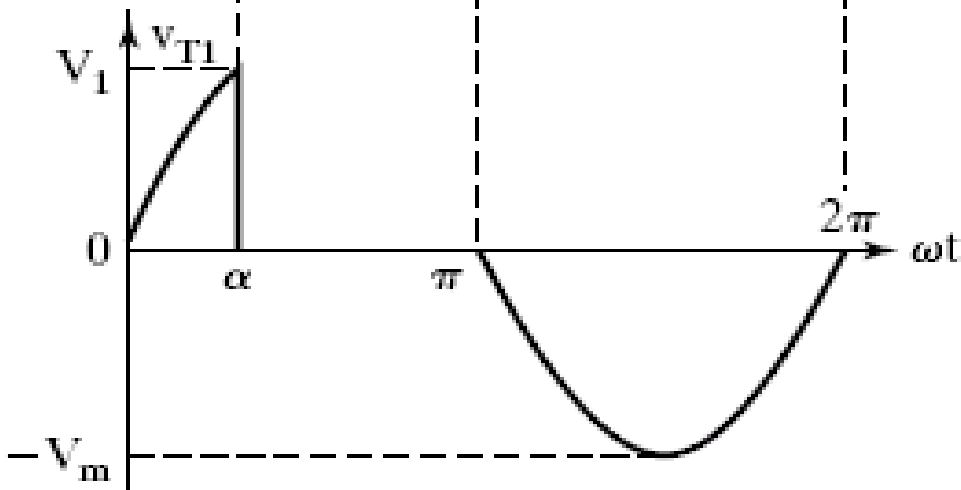

Thyristor Voltage

# Equations

$$v_s = V_m \sin \omega t = \text{i/p ac supply voltage}$$

$$V_m = \text{max. value of i/p ac supply voltage}$$

$$V_S = \frac{V_m}{\sqrt{2}} = \text{RMS value of i/p ac supply voltage}$$

$$v_O = v_L = \text{output voltage across the load}$$

When the thyristor is triggered at  $\omega t = \alpha$

$$v_O = v_L = V_m \sin \omega t; \omega t = \alpha \text{ to } \pi$$

$$i_O = i_L = \frac{v_O}{R} = \text{Load current}; \omega t = \alpha \text{ to } \pi$$

$$i_O = i_L = \frac{V_m \sin \omega t}{R} = I_m \sin \omega t; \omega t = \alpha \text{ to } \pi$$

Where  $I_m = \frac{V_m}{R} = \text{max. value of load current}$

To Derive an Expression for the  
Average (DC)  
Output Voltage Across The  
Load



$$V_{O(dc)} = V_{dc} = \frac{1}{2\pi} \int_0^{2\pi} v_o \cdot d(\omega t);$$

$$v_o = V_m \sin \omega t \text{ for } \omega t = \alpha \text{ to } \pi$$

$$V_{O(dc)} = V_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \int_{\alpha}^{\pi} \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \left[ -\cos \omega t \Big/_{\alpha}^{\pi} \right]$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \left[ -\cos \pi + \cos \alpha \right]; \quad \cos \pi = -1$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \left[ 1 + \cos \alpha \right]; \quad V_m = \sqrt{2}V_S$$

Maximum average (dc) o/p  
voltage is obtained when  $\alpha = 0$   
and the maximum dc output voltage

$$V_{dc(\max)} = V_{dm} = \frac{V_m}{2\pi} (1 + \cos 0); \quad \cos(0) = 1$$

$$\therefore V_{dc(\max)} = V_{dm} = \frac{V_m}{\pi}$$

$$V_{O(dc)} = \frac{V_m}{2\pi} [1 + \cos \alpha] ; V_m = \sqrt{2}V_s$$

The average dc output voltage can be varied by varying the trigger angle  $\alpha$  from 0 to a maximum of  $180^\circ$  ( $\pi$  radians)

We can plot the control characteristic ( $V_{O(dc)}$  vs  $\alpha$ ) by using the equation for  $V_{O(dc)}$

Control Characteristic  
of  
Single Phase Half Wave Phase  
Controlled Rectifier  
with  
Resistive Load

The average dc output voltage is given by the expression


$$V_{O(dc)} = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

We can obtain the control characteristic by plotting the expression for the dc output voltage as a function of trigger angle  $\alpha$

Trigger angle $\alpha$ in degrees	$V_{O(dc)}$	%
0	$V_{dm} = \frac{V_m}{\pi}$	100% $V_{dm}$
$30^\circ$	$0.933 V_{dm}$	93.3 % $V_{dm}$
$60^\circ$	$0.75 V_{dm}$	75 % $V_{dm}$
$90^\circ$	$0.5 V_{dm}$	50 % $V_{dm}$
$120^\circ$	$0.25 V_{dm}$	25 % $V_{dm}$
$150^\circ$	$0.06698 V_{dm}$	6.69 % $V_{dm}$
$180^\circ$	0	0

$$V_{dm} = \frac{V_m}{\pi} = V_{dc(max)}$$

# Control Characteristic

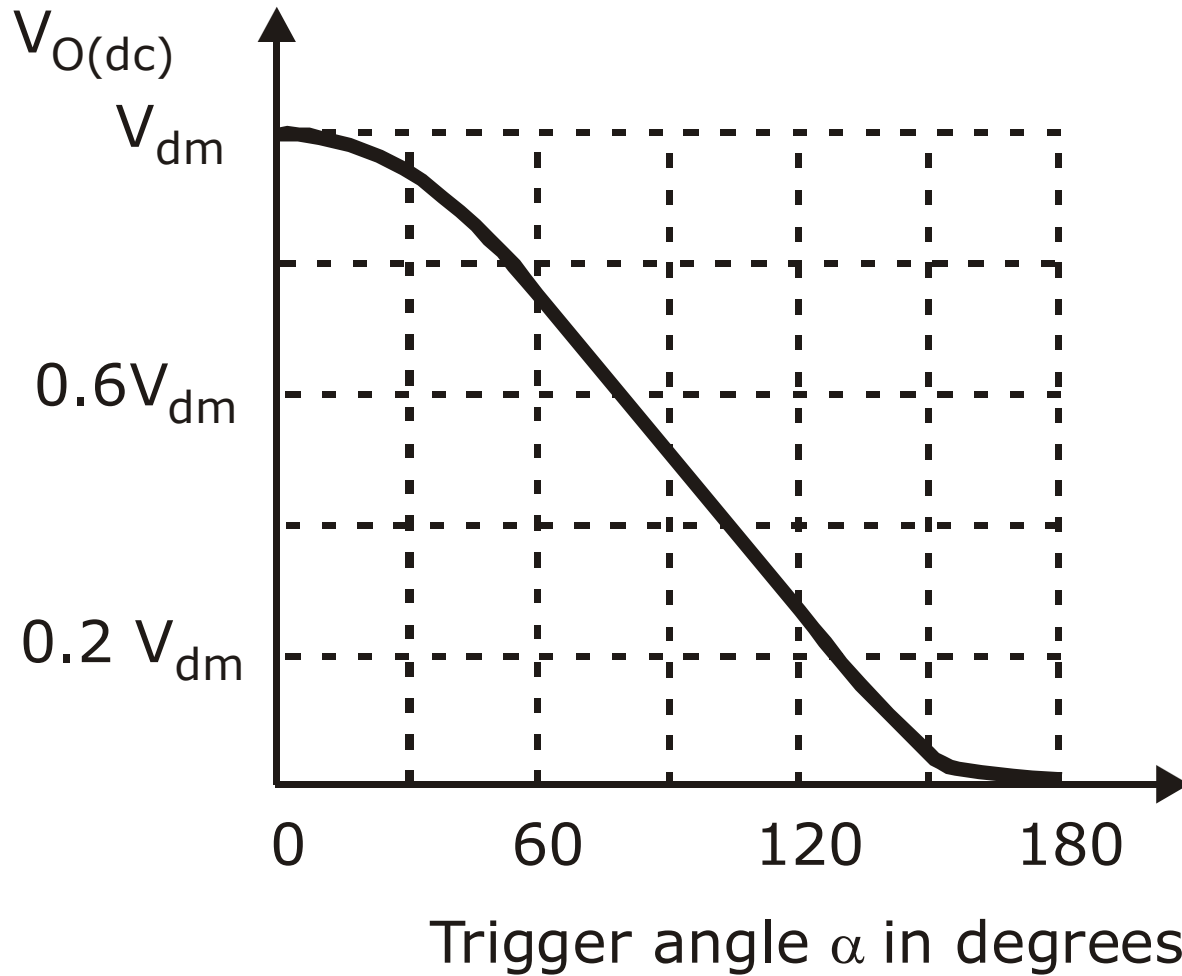



Normalizing the dc output  
voltage with respect to  $V_{dm}$ , the  
Normalized output voltage

$$V_n = \frac{V_{dc}}{V_{dm}} = \frac{\frac{V_m}{2\pi} (1 + \cos \alpha)}{\frac{V_m}{\pi}}$$

$$V_n = \frac{V_{dc}}{V_{dm}} = \frac{1}{2} (1 + \cos \alpha) = V_{dcn}$$

To Derive An  
Expression for the  
RMS Value of Output Voltage  
of a  
Single Phase Half Wave Controlled Rectifier With  
Resistive Load

The RMS output voltage is given by

$$V_{O(RMS)} = \left[ \frac{1}{2\pi} \int_0^{2\pi} v_o^2 \cdot d(\omega t) \right]$$

Output voltage  $v_o = V_m \sin \omega t$  ; for  $\omega t = \alpha$  to  $\pi$

$$V_{O(RMS)} = \left[ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{\frac{1}{2}}$$

By substituting  $\sin^2 \omega t = \frac{1 - \cos 2\omega t}{2}$ , we get

$$V_{O(RMS)} = \left[ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \frac{(1 - \cos 2\omega t)}{2} d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \left[ \frac{V_m^2}{4\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) d(\omega t) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \left[ \frac{V_m^2}{4\pi} \left\{ \int_{\alpha}^{\pi} d(\omega t) - \int_{\alpha}^{\pi} \cos 2\omega t d(\omega t) \right\} \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{2} \left[ \frac{1}{\pi} \left\{ (\omega t) \Big|_{\alpha}^{\pi} - \left( \frac{\sin 2\omega t}{2} \right) \Big|_{\alpha}^{\pi} \right\} \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{2} \left[ \frac{1}{\pi} \left( (\pi - \alpha) - \frac{(\sin 2\pi - \sin 2\alpha)}{2} \right) \right]^{\frac{1}{2}} ; \sin 2\pi = 0$$

$$V_{O(RMS)} = \frac{V_m}{2} \left[ \frac{1}{\pi} \left( (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right) \right]^{\frac{1}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \left( (\pi - \alpha) + \frac{\sin 2\alpha}{2} \right)^{\frac{1}{2}}$$