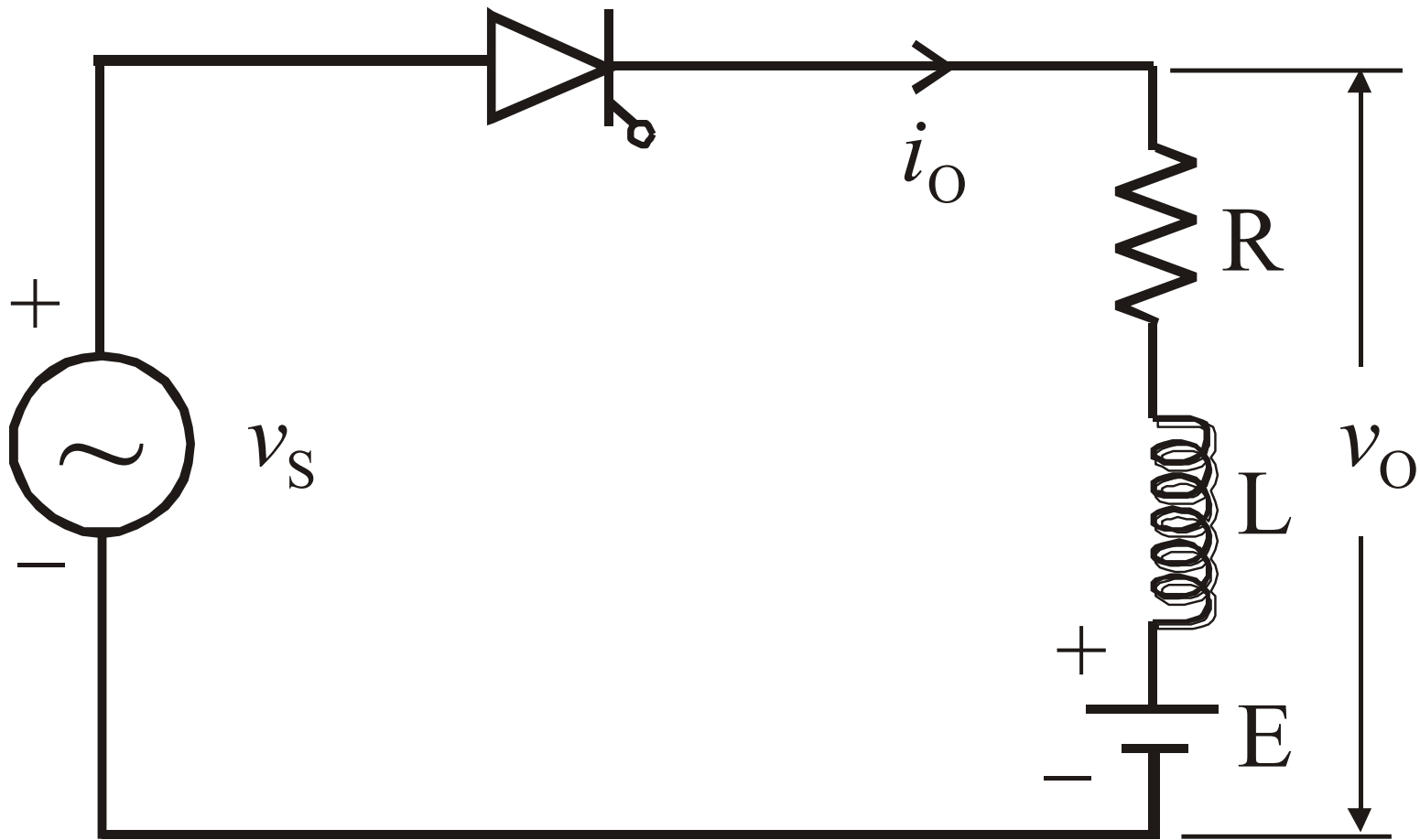


Single Phase Half Wave  
Controlled Rectifier With  
A  
General Load




$$\gamma = \sin^{-1} \left( \frac{E}{V_m} \right)$$

For trigger angle  $\alpha < \gamma$ ,

the Thyristor conducts from  $\omega t = \gamma$  to  $\beta$

For trigger angle  $\alpha > \gamma$ ,

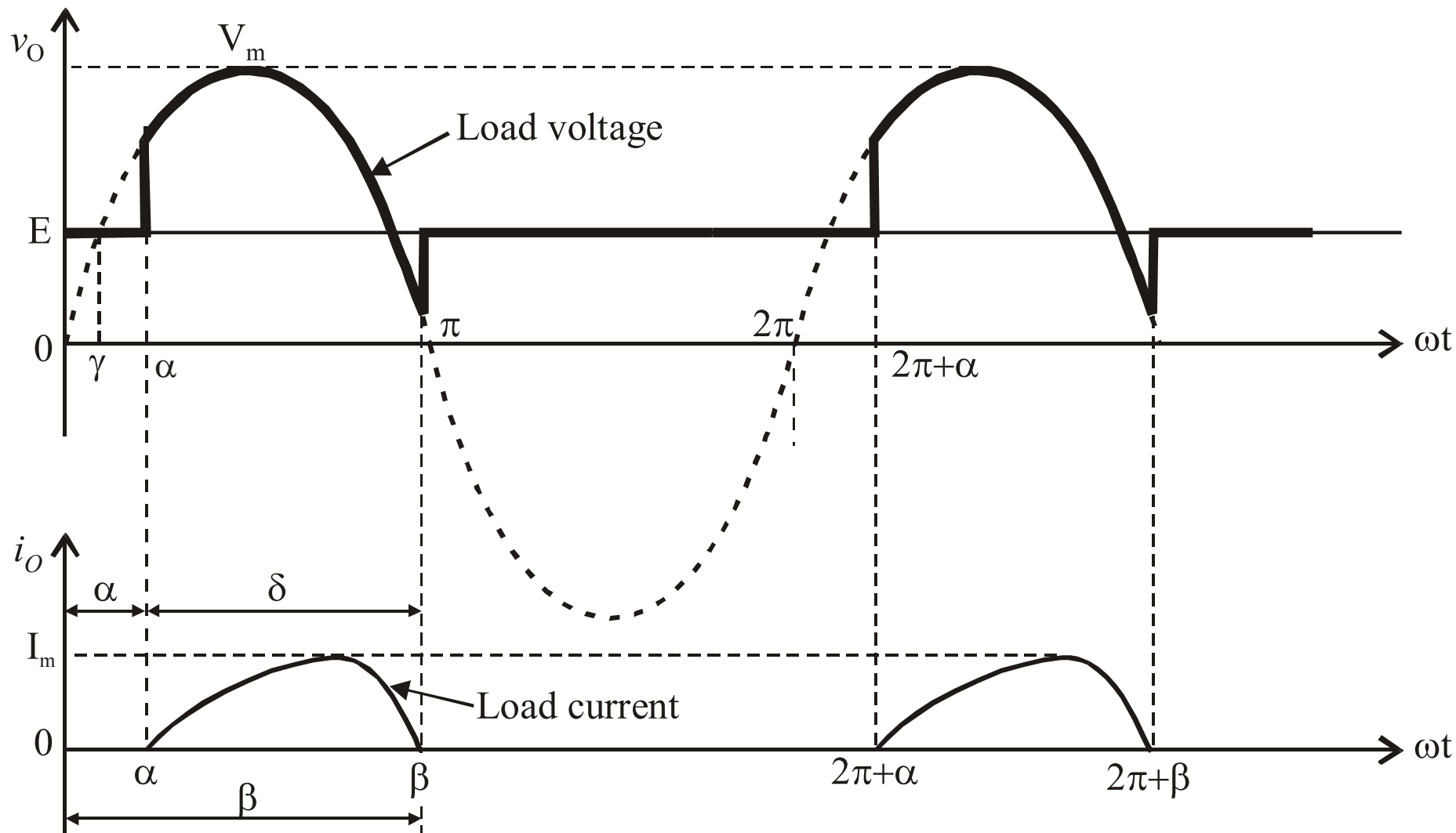the Thyristor conducts from  $\omega t = \alpha$  to  $\beta$



# Equations

$$v_S = V_m \sin \omega t = \text{Input supply voltage.}$$

$$v_O = V_m \sin \omega t = \text{o/p (load) voltage}$$

$$\text{for } \omega t = \alpha \text{ to } \beta.$$

$$v_O = E \text{ for } \omega t = 0 \text{ to } \alpha \text{ \&}$$

$$\text{for } \omega t = \beta \text{ to } 2\pi.$$

# Expression for the Load Current

When the thyristor is triggered at a delay angle of  $\alpha > \gamma$ , the eqn. for the circuit can be written as

$$V_m \sin \omega t = i_o \times R + L \left( \frac{di_o}{dt} \right) + E ; \alpha \leq \omega t \leq \beta$$

The general expression for the output load current can be written as

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + A e^{\frac{-t}{\tau}}$$

Where

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load Impedance.}$$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right) = \text{Load impedance angle.}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

The general expression for the o/p current can

be written as

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + Ae^{\frac{-R}{L}t}$$

To find the value of the constant 'A' apply the initial conditions at  $\omega t = \alpha$ , load current  $i_o = 0$ , Equating the general expression for the load current to zero at  $\omega t = \alpha$ , we get

$$i_o = 0 = \frac{V_m}{Z} \sin(\alpha - \phi) - \frac{E}{R} + A e^{\frac{-R}{L} \times \frac{\alpha}{\omega}}$$



We obtain the value of constant 'A' as

$$A = \left[ \frac{E}{R} - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{\frac{R}{\omega L} \alpha}$$

Substituting the value of the constant 'A' in the expression for the load current; we get the complete expression for the output load current as

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + \left[ \frac{E}{R} - \frac{V_m}{Z} \sin(\alpha - \phi) \right] e^{\frac{-R}{\omega L}(\omega t - \alpha)}$$

To Derive  
An  
Expression For The Average  
Or  
DC Load Voltage

$$V_{O(dc)} = \frac{1}{2\pi} \int_0^{2\pi} v_O \cdot d(\omega t)$$

$$V_{O(dc)} = \frac{1}{2\pi} \left[ \int_0^{\alpha} v_O \cdot d(\omega t) + \int_{\alpha}^{\beta} v_O \cdot d(\omega t) + \int_{\beta}^{2\pi} v_O \cdot d(\omega t) \right]$$

$v_O = V_m \sin \omega t =$  Output load voltage for  $\omega t = \alpha$  to  $\beta$

$v_O = E$  for  $\omega t = 0$  to  $\alpha$  & for  $\omega t = \beta$  to  $2\pi$

$$V_{O(dc)} = \frac{1}{2\pi} \left[ \int_0^{\alpha} E \cdot d(\omega t) + \int_{\alpha}^{\beta} V_m \sin \omega t + \int_{\beta}^{2\pi} E \cdot d(\omega t) \right]$$

$$V_{O(dc)} = \frac{1}{2\pi} \left[ E(\omega t) \Big|_0^\alpha + V_m (-\cos \omega t) \Big|_\alpha^\beta + E(\omega t) \Big|_\beta^{2\pi} \right]$$

$$V_{O(dc)} = \frac{1}{2\pi} \left[ E(\alpha - 0) - V_m (\cos \beta - \cos \alpha) + E(2\pi - \beta) \right]$$

$$V_{O(dc)} = \frac{V_m}{2\pi} \left[ (\cos \alpha - \cos \beta) \right] + \frac{E}{2\pi} \left[ (2\pi - \beta + \alpha) \right]$$


$$V_{O(dc)} = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta) + \left[ \frac{2\pi - (\beta - \alpha)}{2\pi} \right] E$$

Conduction angle of thyristor  $\delta = (\beta - \alpha)$

RMS Output Voltage can be calculated  
by using the expression

$$V_{O(RMS)} = \sqrt{\frac{1}{2\pi} \left[ \int_0^{2\pi} v_o^2 \cdot d(\omega t) \right]}$$

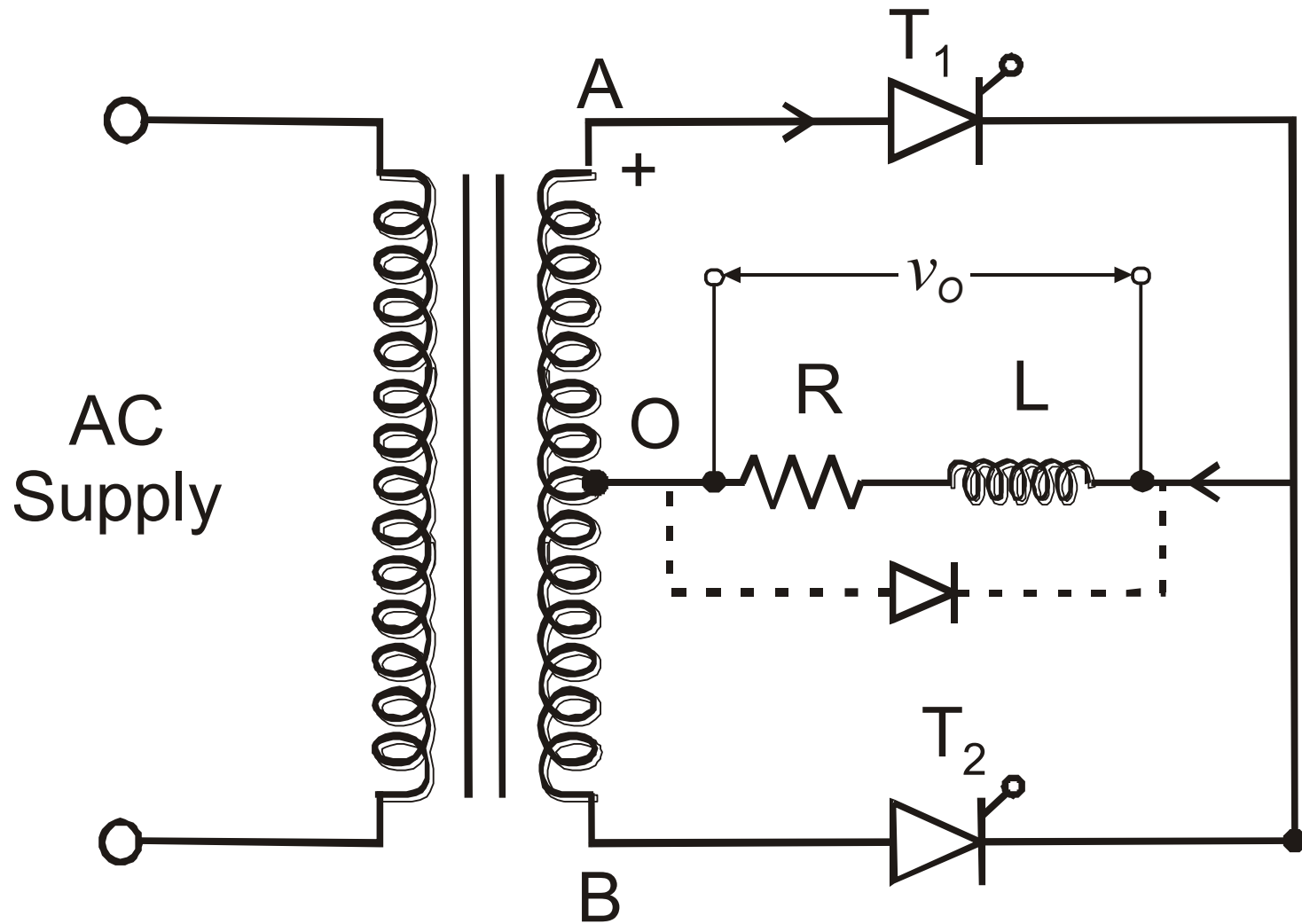
Single Phase  
Full Wave Controlled Rectifier Using  
A  
Center Tapped Transformer



Discontinuous  
Load Current Operation  
without FWD  
for

$$\pi < \beta < (\pi + \alpha)$$



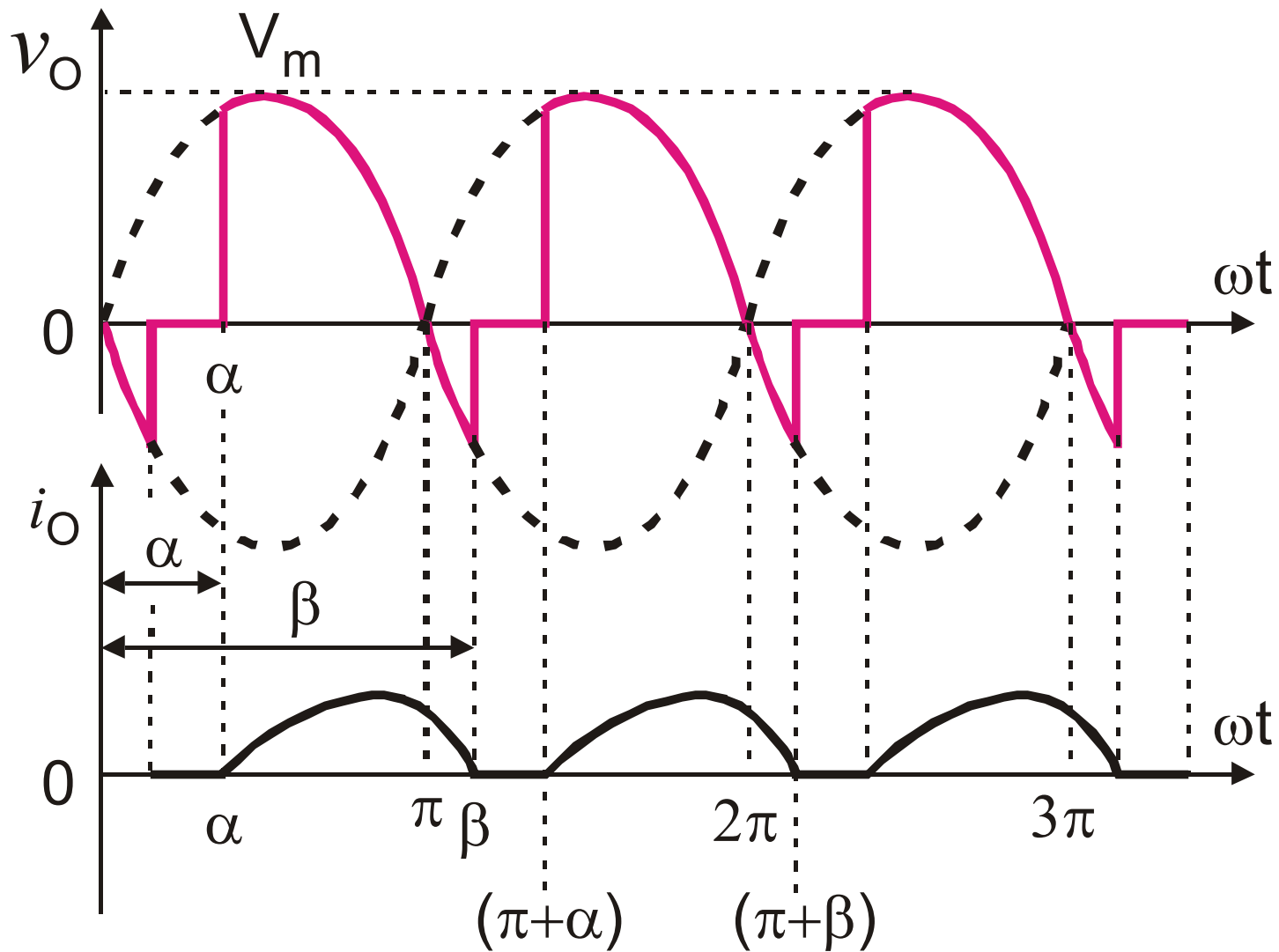

To Derive An Expression For  
The Output  
(Load) Current, During  $\omega t = \alpha$  to  $\beta$   
When Thyristor  $T_1$  Conducts

Assuming  $T_1$  is triggered  $\omega t = \alpha$ ,  
we can write the equation,

$$L \left( \frac{di_o}{dt} \right) + Ri_o = V_m \sin \omega t ; \alpha \leq \omega t \leq \beta$$

General expression for the output current,

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-t}{\tau}}$$

$$V_m = \sqrt{2}V_s = \text{maximum supply voltage.}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \text{Load impedance.}$$

$$\phi = \tan^{-1} \left( \frac{\omega L}{R} \right) = \text{Load impedance angle.}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$

$\therefore$  general expression for the output load current

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{\frac{-R}{L} t}$$

Constant  $A_1$  is calculated from

initial condition  $i_o = 0$  at  $\omega t = \alpha$  ;  $t = \left( \frac{\alpha}{\omega} \right)$

$$i_o = 0 = \frac{V_m}{Z} \sin(\alpha - \phi) + A_1 e^{\frac{-R}{L} t}$$

$$\therefore A_1 e^{\frac{-R}{L} t} = \frac{-V_m}{Z} \sin(\alpha - \phi)$$

We get the value of constant  $A_1$  as

$$A_1 = e^{\frac{R(\alpha)}{\omega L}} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

Substituting the value of constant  $A_1$  in the general expression for  $i_o$

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + e^{\frac{-R}{\omega L}(\omega t - \alpha)} \left[ \frac{-V_m}{Z} \sin(\alpha - \phi) \right]$$

$\therefore$  we obtain the final expression for the inductive load current

$$i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right];$$

Where  $\alpha \leq \omega t \leq \beta$

Extinction angle  $\beta$  can be calculated by using the condition that  $i_o = 0$  at  $\omega t = \beta$


$$i_o = \frac{V_m}{Z} \left[ \sin(\omega t - \phi) - \sin(\alpha - \phi) e^{\frac{-R}{\omega L}(\omega t - \alpha)} \right] = 0$$

$$\therefore \sin(\beta - \phi) = e^{\frac{-R}{\omega L}(\beta - \alpha)} \times \sin(\alpha - \phi)$$

$\beta$  can be calculated by solving the above eqn.

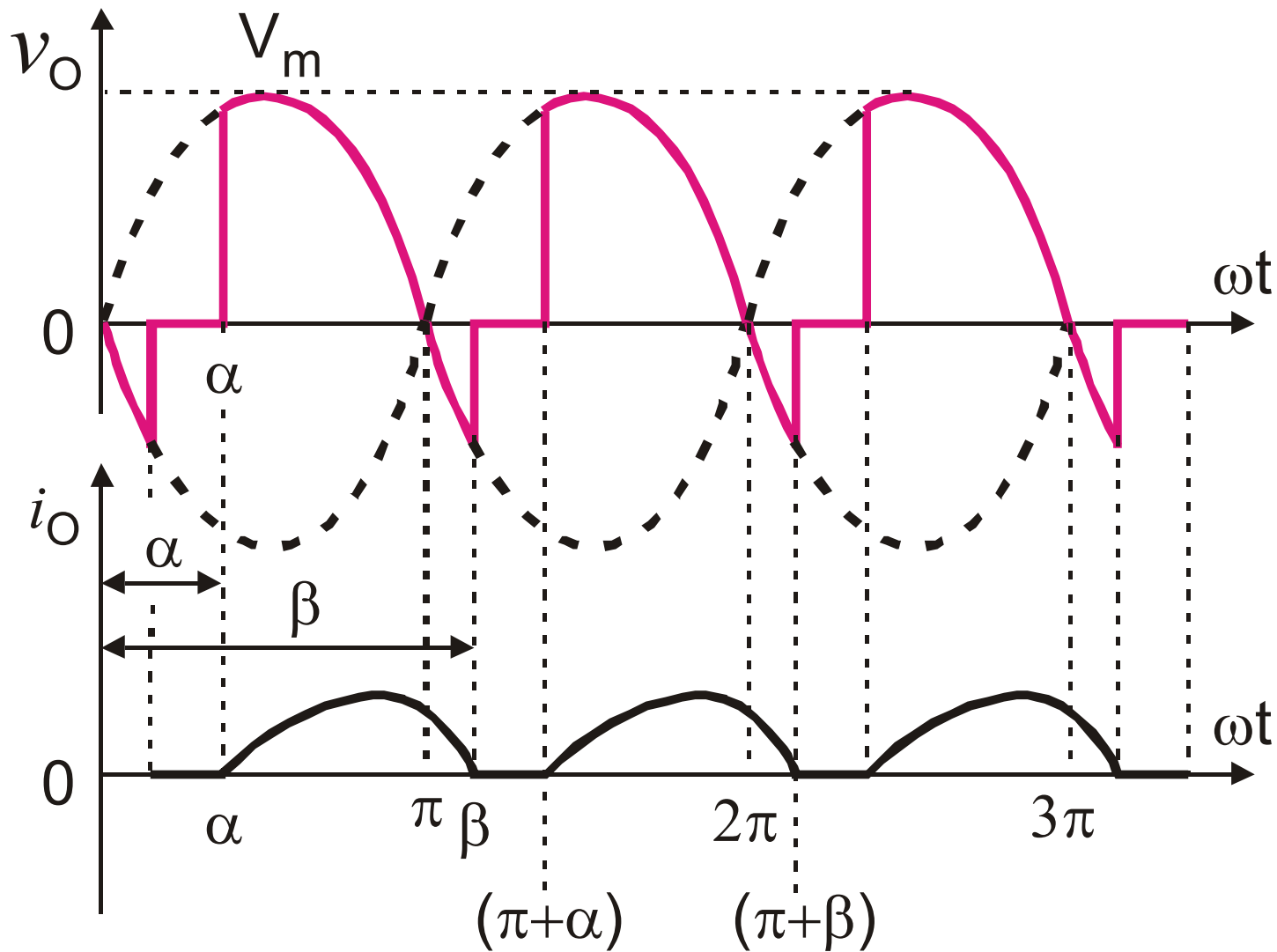To Derive An Expression For The DC Output  
Voltage Of  
A Single Phase Full Wave Controlled Rectifier  
With RL Load  
*(Without FWD)*





$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t = \alpha}^{\beta} v_o \cdot d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \left[ \int_{\alpha}^{\beta} V_m \sin \omega t \cdot d(\omega t) \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \omega t \Big|_{\alpha}^{\beta} \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} (\cos \alpha - \cos \beta)$$

When the load inductance is negligible ( i.e.,  $L \approx 0$  )

Extinction angle  $\beta = \pi$  radians

Hence the average or dc output voltage for R load

$$V_{O(dc)} = \frac{V_m}{\pi} (\cos \alpha - \cos \pi)$$


$$V_{O(dc)} = \frac{V_m}{\pi} (\cos \alpha - (-1))$$

$$V_{O(dc)} = \frac{V_m}{\pi} (1 + \cos \alpha); \text{ for R load, when } \beta = \pi$$

To calculate the RMS output voltage we use the expression

$$V_{O(RMS)} = \sqrt{\frac{1}{\pi} \left[ \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]}$$
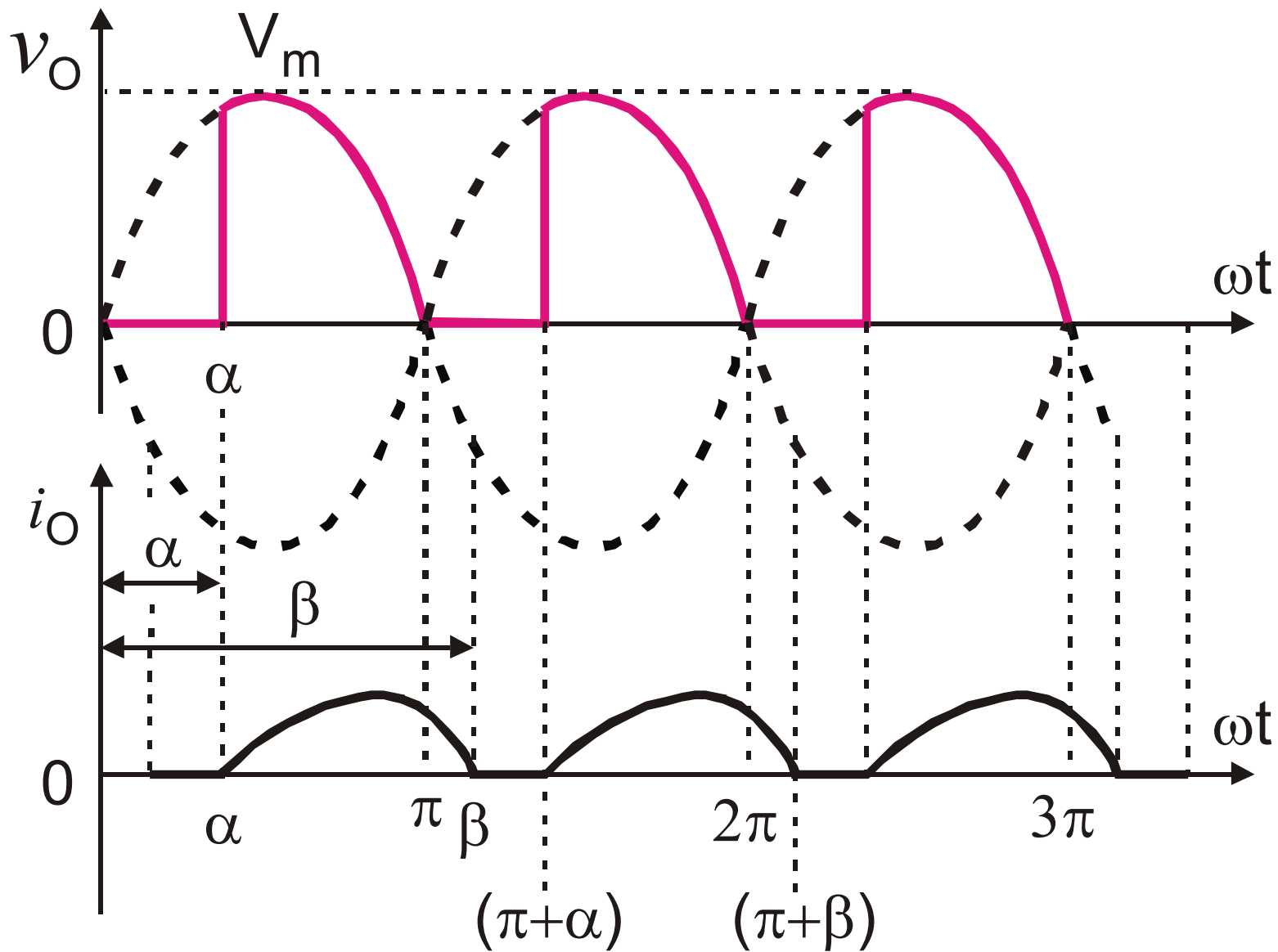
# Discontinuous Load Current Operation with FWD



Thyristor  $T_1$  is triggered at  $\omega t = \alpha$ ;

$T_1$  conducts from  $\omega t = \alpha$  to  $\pi$

Thyristor  $T_2$  is triggered at  $\omega t = (\pi + \alpha)$ ;

$T_2$  conducts from  $\omega t = (\pi + \alpha)$  to  $2\pi$

FWD conducts from  $\omega t = \pi$  to  $\beta$  &

$v_o \approx 0$  during discontinuous load current.

To Derive an Expression  
For The  
DC Output Voltage For  
A  
Single Phase Full Wave Controlled  
Rectifier  
With RL Load & FWD



$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t=0}^{\pi} v_o \cdot d(\omega t)$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \omega t \Big|_{\alpha}^{\pi} \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[ -\cos \pi + \cos \alpha \right] \quad ; \quad \cos \pi = -1$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

- The load current is discontinuous for low values of load inductance and for large values of trigger angles.
- For large values of load inductance the load current flows continuously without falling to zero.
- Generally the load current is continuous for large load inductance and for low trigger angles.