
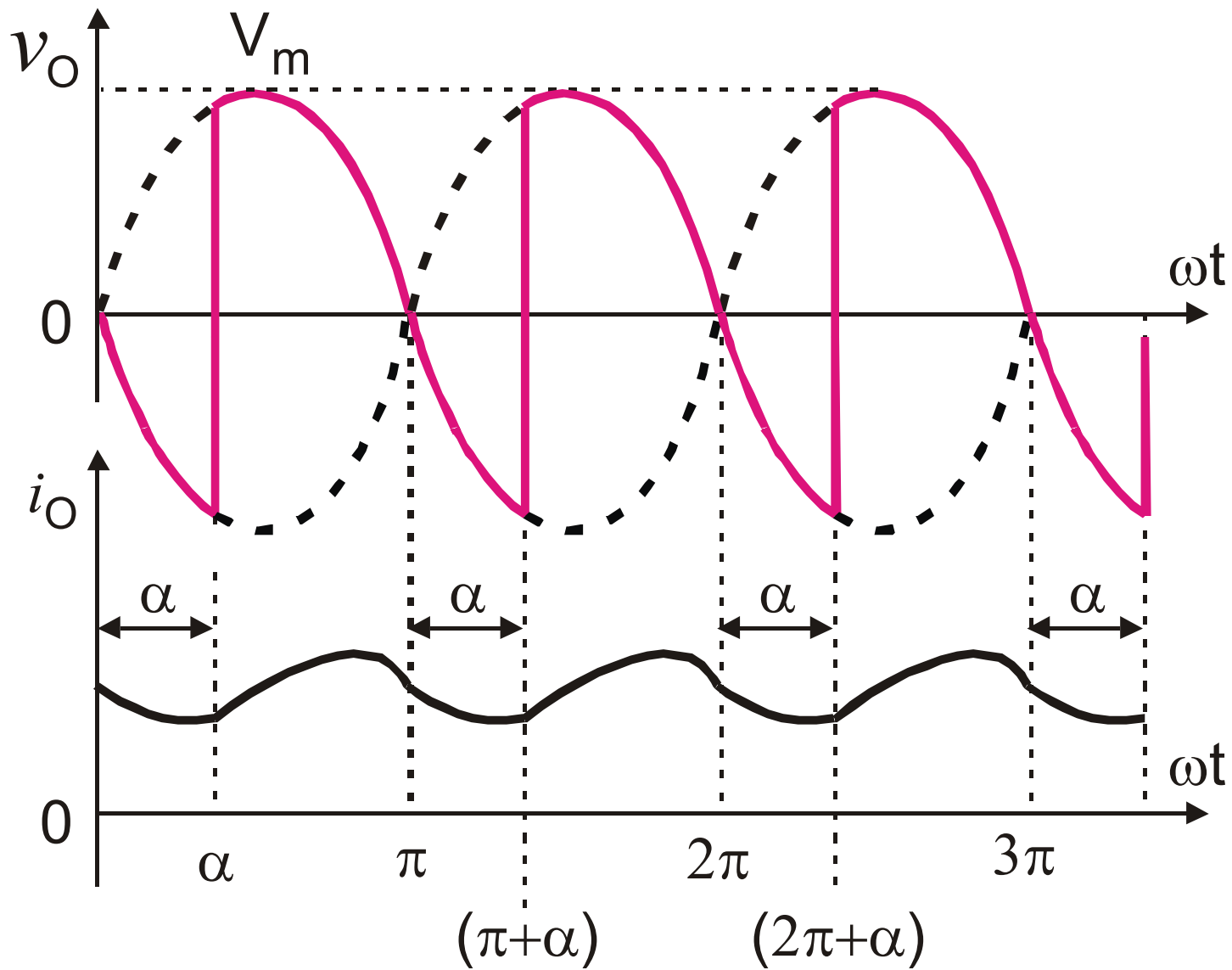


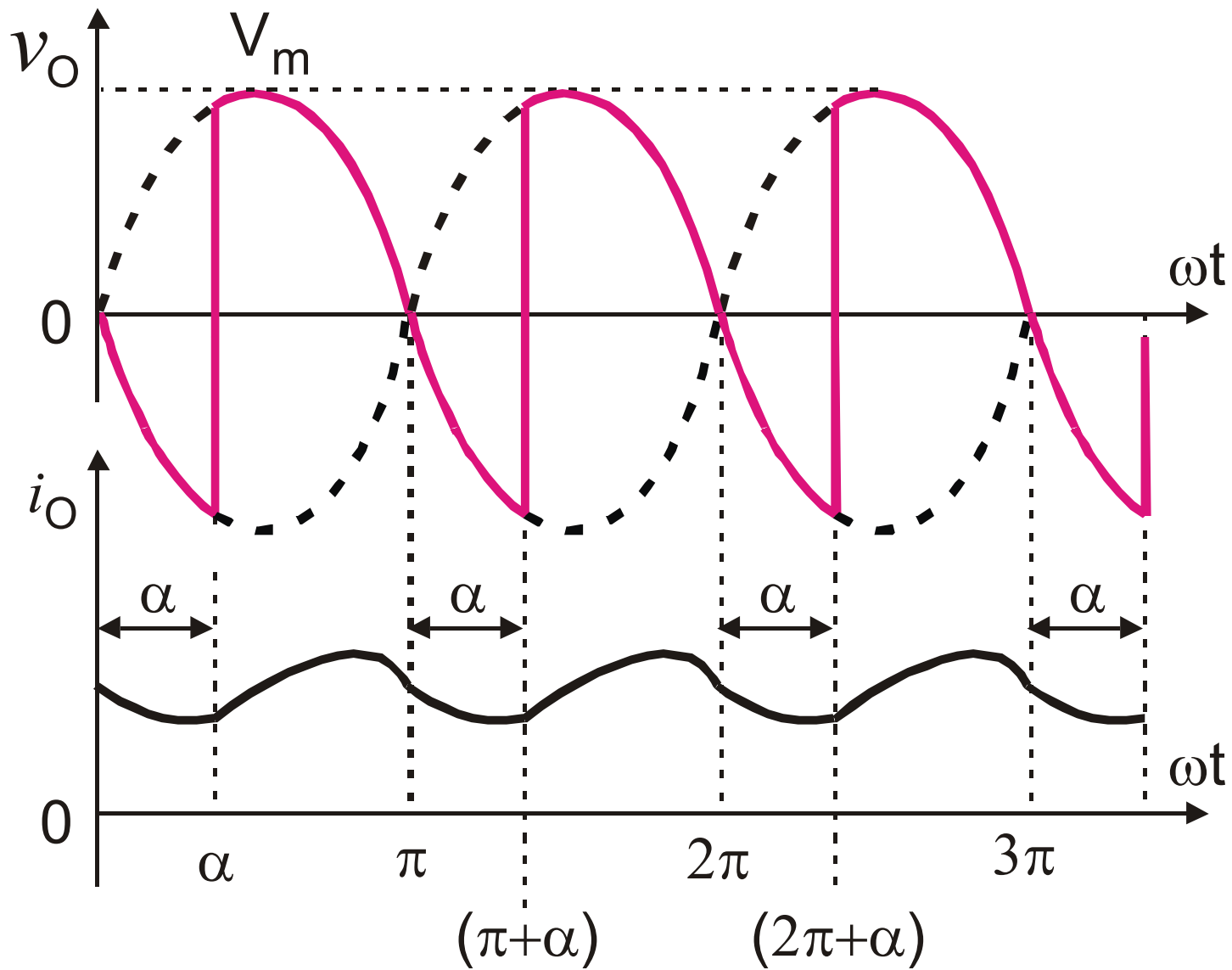Continuous Load Current Operation (Without FWD)



To Derive
An Expression For
Average / DC Output Voltage
Of

Single Phase Full Wave Controlled Rectifier For
Continuous Current Operation without FWD



$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t = \alpha}^{(\pi + \alpha)} v_o \cdot d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \left[\int_{\alpha}^{(\pi + \alpha)} V_m \sin \omega t \cdot d(\omega t) \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[-\cos \omega t \Big|_{\alpha}^{(\pi + \alpha)} \right]$$

$$V_{O(dc)} = V_{dc}$$

$$= \frac{V_m}{\pi} \left[\cos \alpha - \cos(\pi + \alpha) \right];$$

$$\cos(\pi + \alpha) = -\cos \alpha$$


$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[\cos \alpha + \cos \alpha \right]$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$

- By plotting $V_{O(dc)}$ *versus* α , we obtain the control characteristic of a single phase full wave controlled rectifier with RL load for continuous load current operation without FWD

| Trigger angle α in degrees | $V_{O(dc)}$ | Remarks |
|--------------------------------------|--|---|
| 0 | $V_{dm} = \left(\frac{2V_m}{\pi} \right)$ | Maximum dc output voltage $V_{dc(max)} = V_{dm} = \left(\frac{2V_m}{\pi} \right)$ |
| 30° | $0.866 V_{dm}$ | $V_{dc} = V_{dm} \times \cos \alpha$ |
| 60° | $0.5 V_{dm}$ | |
| 90° | $0 V_{dm}$ | |
| 120° | $-0.5 V_{dm}$ | |
| 150° | $-0.866 V_{dm}$ | |
| 180° | $-V_{dm} = -\left(\frac{2V_m}{\pi} \right)$ | |

$$V_{dc} = V_{dm} \times \cos \alpha$$

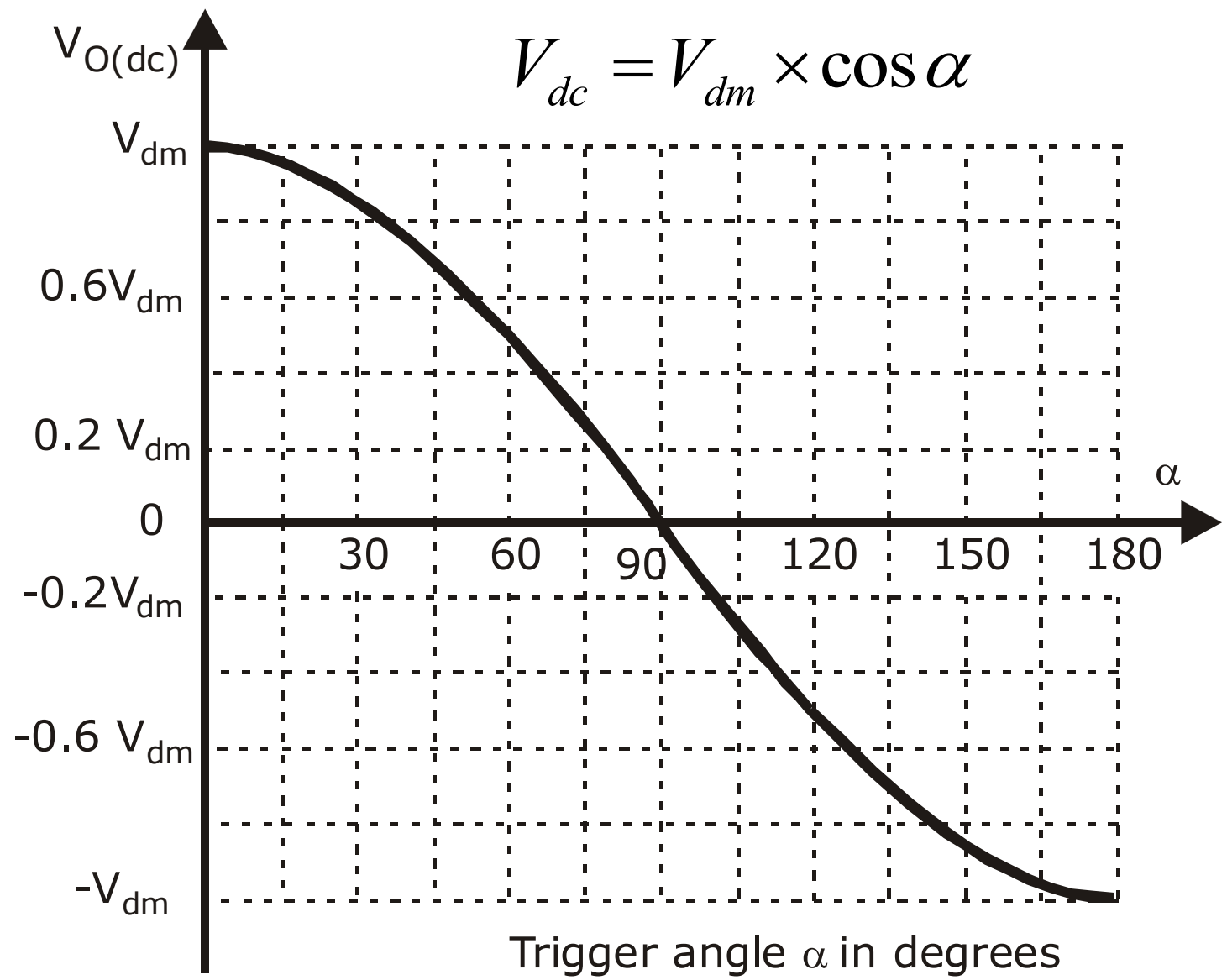

Trigger angle α in degrees

By varying the trigger angle we can vary the output dc voltage across the load. Hence we can control the dc output power flow to the load.

For trigger angle α , 0 to 90° (*i.e.*, $0 \leq \alpha \leq 90^\circ$);

$\cos \alpha$ is positive and hence V_{dc} is positive

V_{dc} & I_{dc} are positive ; $P_{dc} = (V_{dc} \times I_{dc})$ is positive

Converter operates as a **Controlled Rectifier**.

Power flow is from the ac source to the load.

For trigger angle α , 90° to 180°

$$(i.e., 90^\circ \leq \alpha \leq 180^\circ),$$

$\cos\alpha$ is negative and hence

V_{dc} is negative; I_{dc} is positive ;

$$P_{dc} = (V_{dc} \times I_{dc}) \text{ is negative.}$$

In this case the converter operates

as a **Line Commutated Inverter**.

Power flows from the load ckt. to the i/p ac source.

The inductive load energy is fed back to the
i/p source.

Drawbacks Of Full Wave Controlled Rectifier With Centre Tapped Transformer

- We require a centre tapped transformer which is quite heavier and bulky.
- Cost of the transformer is higher for the required dc output voltage & output power.
- Hence full wave bridge converters are preferred.

Single Phase


Full Wave Bridge Controlled Rectifier

2 types of FW Bridge Controlled Rectifiers are

- Half Controlled Bridge Converter
(Semi-Converter)
- Fully Controlled Bridge Converter
(Full Converter)

The bridge full wave controlled rectifier does not require a centre tapped transformer

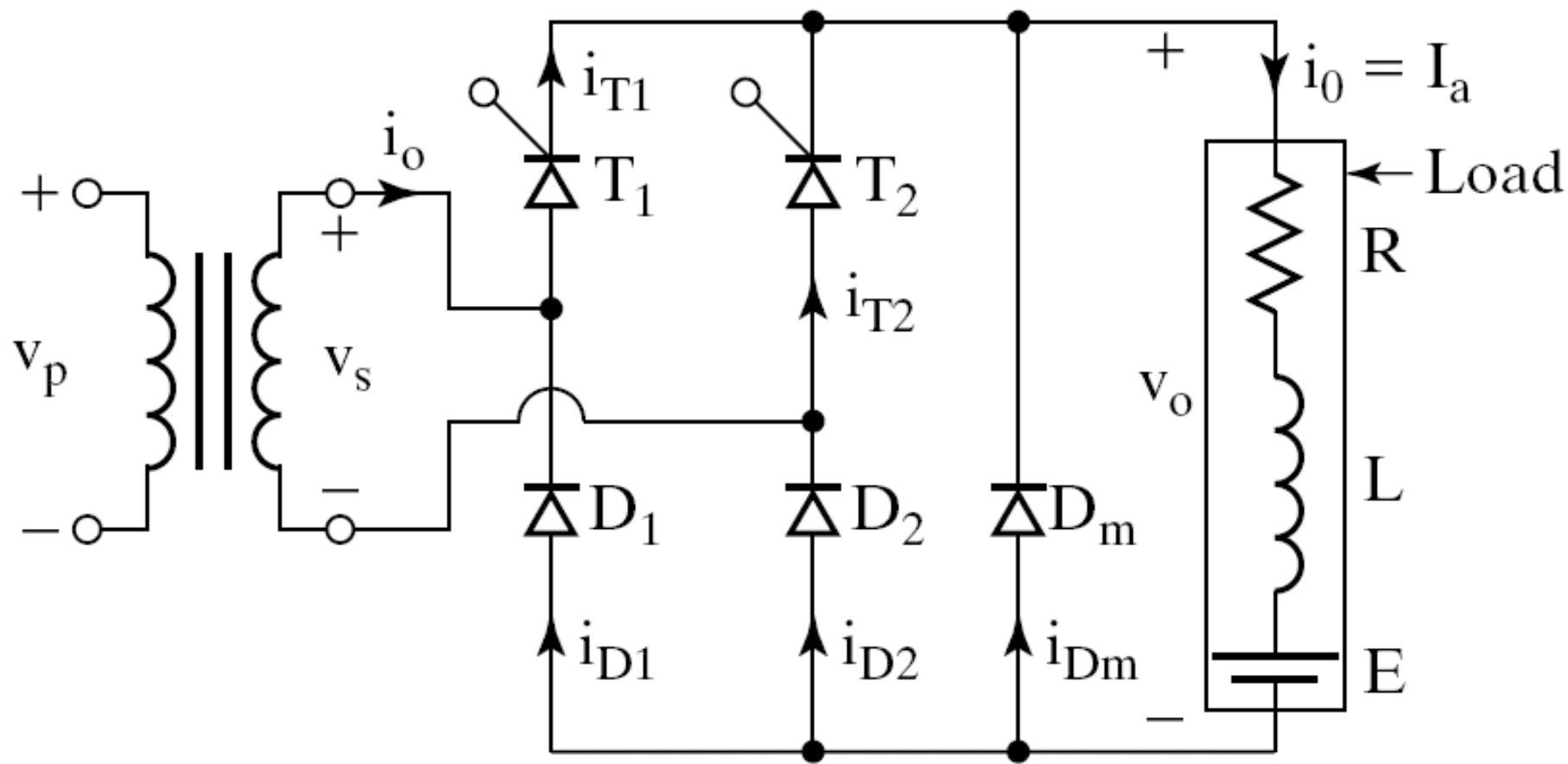Single Phase
Full Wave Half Controlled Bridge
Converter
(Single Phase Semi Converter)



Trigger Pattern of Thyristors

Thyristor T_1 is triggered at

$$\omega t = \alpha, \text{ at } \omega t = (2\pi + \alpha), \dots$$



Thyristor T_2 is triggered at

$$\omega t = (\pi + \alpha), \text{ at } \omega t = (3\pi + \alpha), \dots$$


The time delay between the gating


signals of T_1 & $T_2 = \pi$ radians or 180°

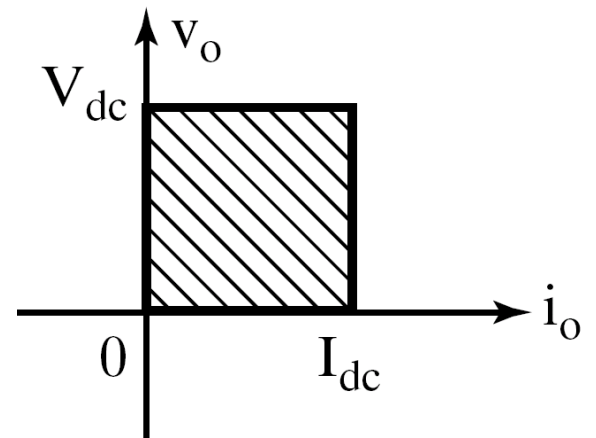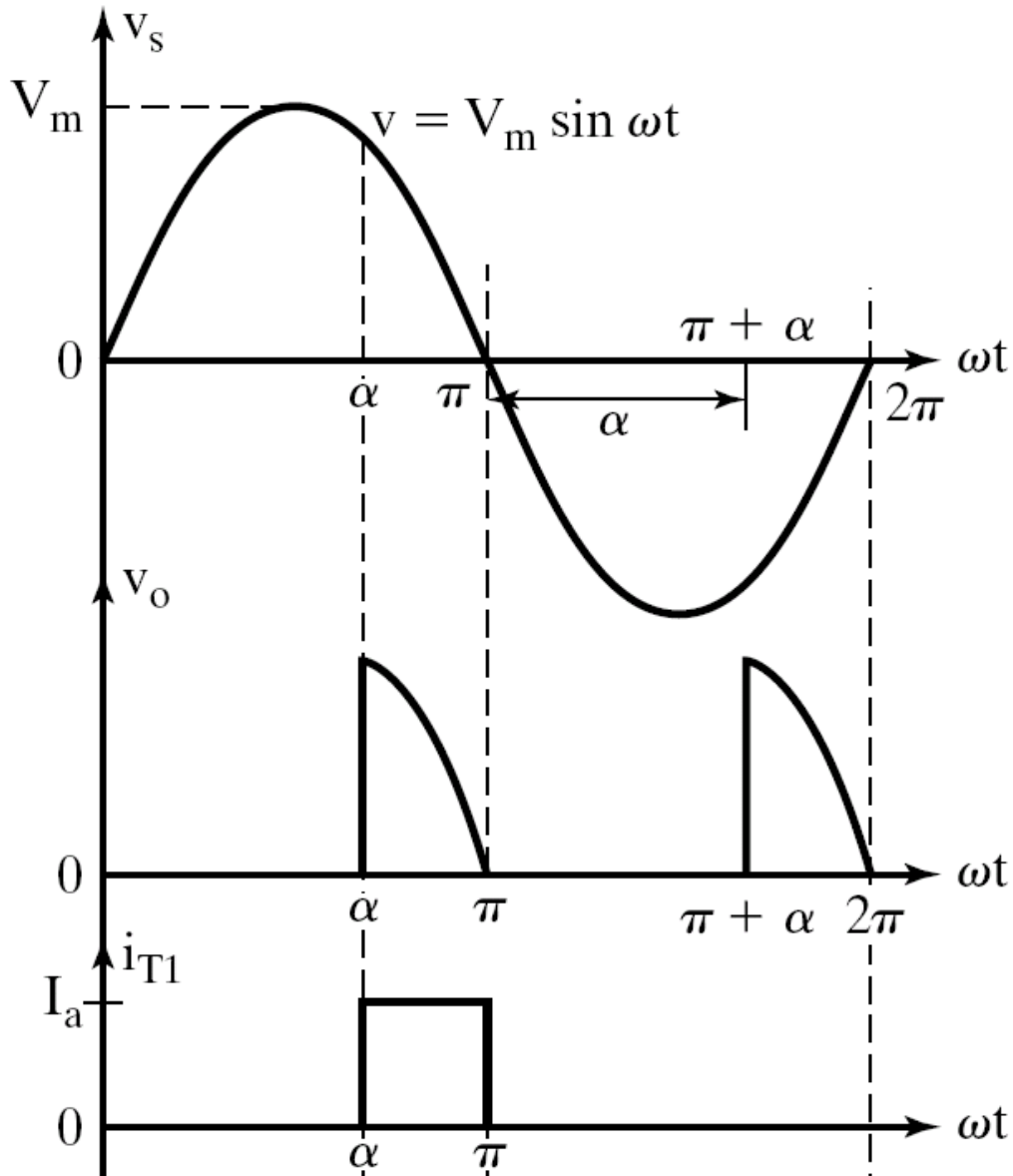Waveforms of
single phase semi-converter
with general load & FWD
for $\alpha > 90^{\circ}$



Single Quadrant
Operation

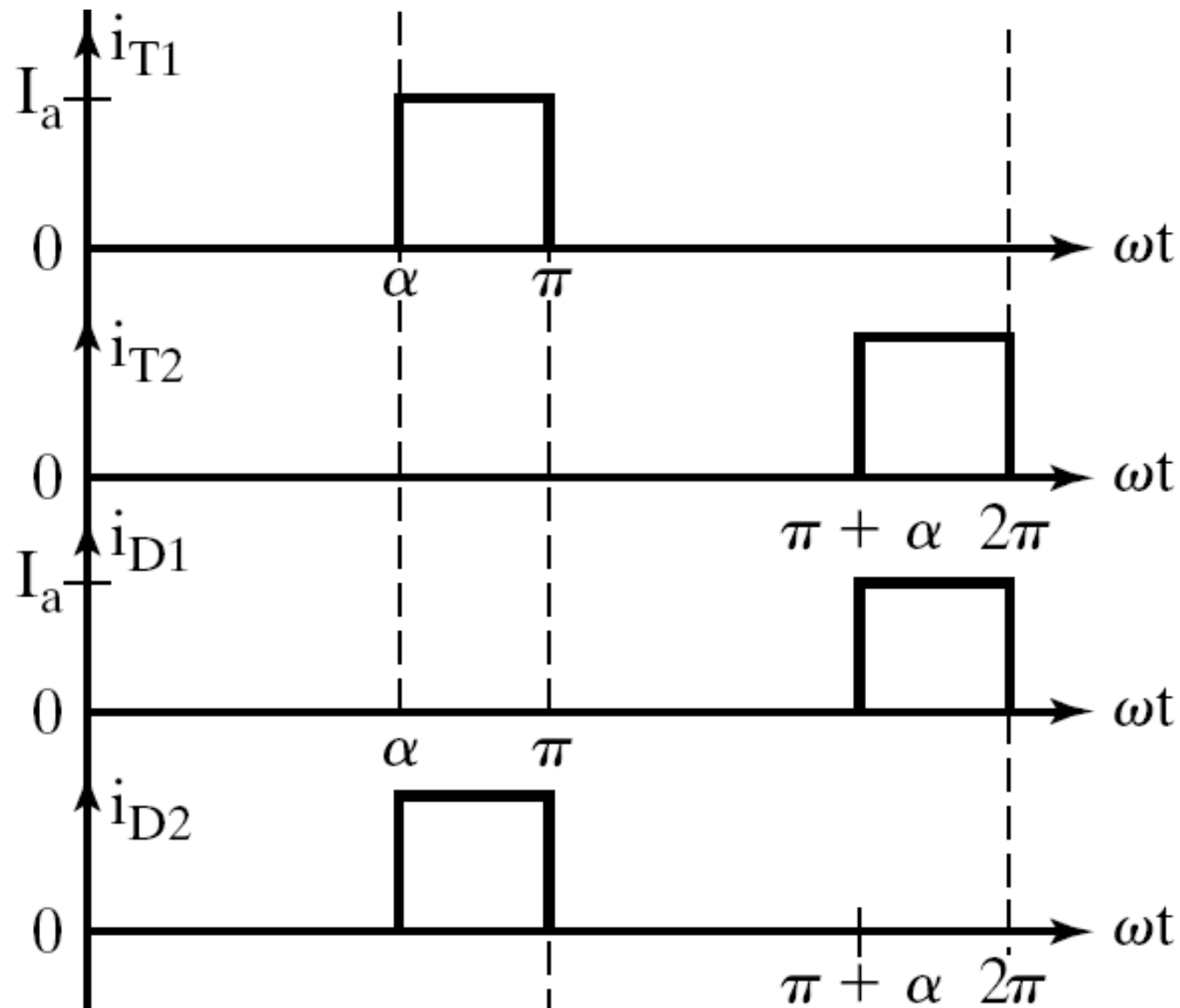

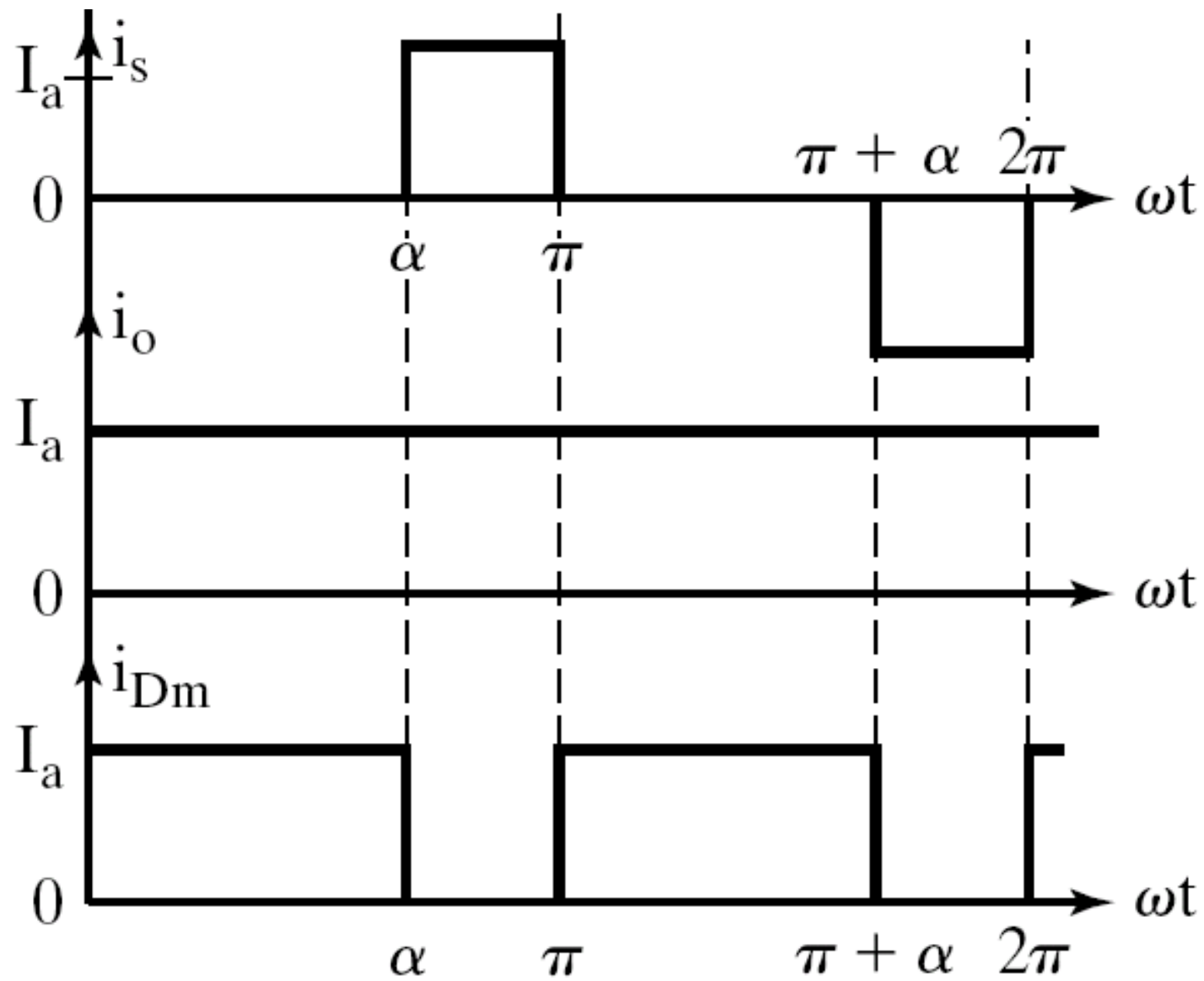

Thyristor T_1 & D_1 conduct

from $\omega t = \alpha$ to π


Thyristor T_2 & D_2 conduct

from $\omega t = (\pi + \alpha)$ to 2π

FWD conducts during

$\omega t = 0$ to α , π to $(\pi + \alpha)$, ...

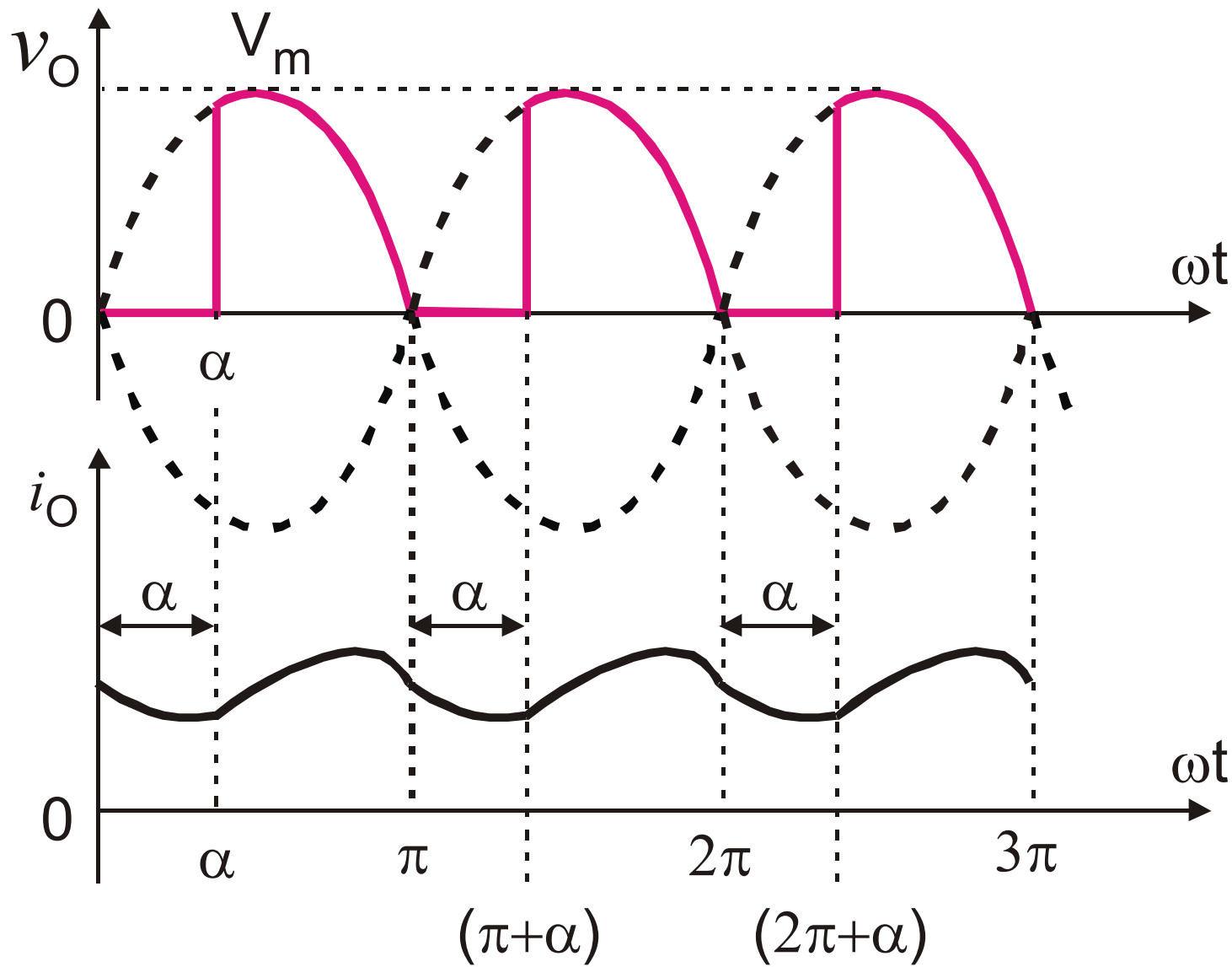Load Voltage & Load Current Waveform of
Single Phase Semi Converter for
 $\alpha < 90^\circ$
& Continuous load current operation



To Derive an Expression
For The
DC Output Voltage of
A
Single Phase Semi-Converter With R,L,
& E Load & FWD
For Continuous, Ripple Free Load
Current Operation

$$V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\omega t=0}^{\pi} v_o \cdot d(\omega t)$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[-\cos \omega t \Big|_{\alpha}^{\pi} \right]$$

$$V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} \left[-\cos \pi + \cos \alpha \right] \quad ; \quad \cos \pi = -1$$

$$\therefore V_{O(dc)} = V_{dc} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

V_{dc} can be varied from a max.

value of $\frac{2V_m}{\pi}$ to 0 by varying α from 0 to π .

For $\alpha = 0$, The max. dc o/p voltage obtained is

$$V_{dc(\max)} = V_{dm} = \frac{2V_m}{\pi}$$

Normalized dc o/p voltage is

$$V_{dcn} = V_n = \frac{V_{dc}}{V_{dn}} = \frac{V_m (1 + \cos \alpha)}{\pi \left(\frac{2V_m}{\pi} \right)} = \frac{1}{2} (1 + \cos \alpha)$$


RMS O/P Voltage $V_{O(RMS)}$

$$V_{O(RMS)} = \left[\frac{2}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right]^{\frac{1}{2}}$$


$$V_{O(RMS)} = \left[\frac{V_m^2}{2\pi} \int_{\alpha}^{\pi} (1 - \cos 2\omega t) \cdot d(\omega t) \right]^{\frac{1}{2}}$$


$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{\frac{1}{2}}$$

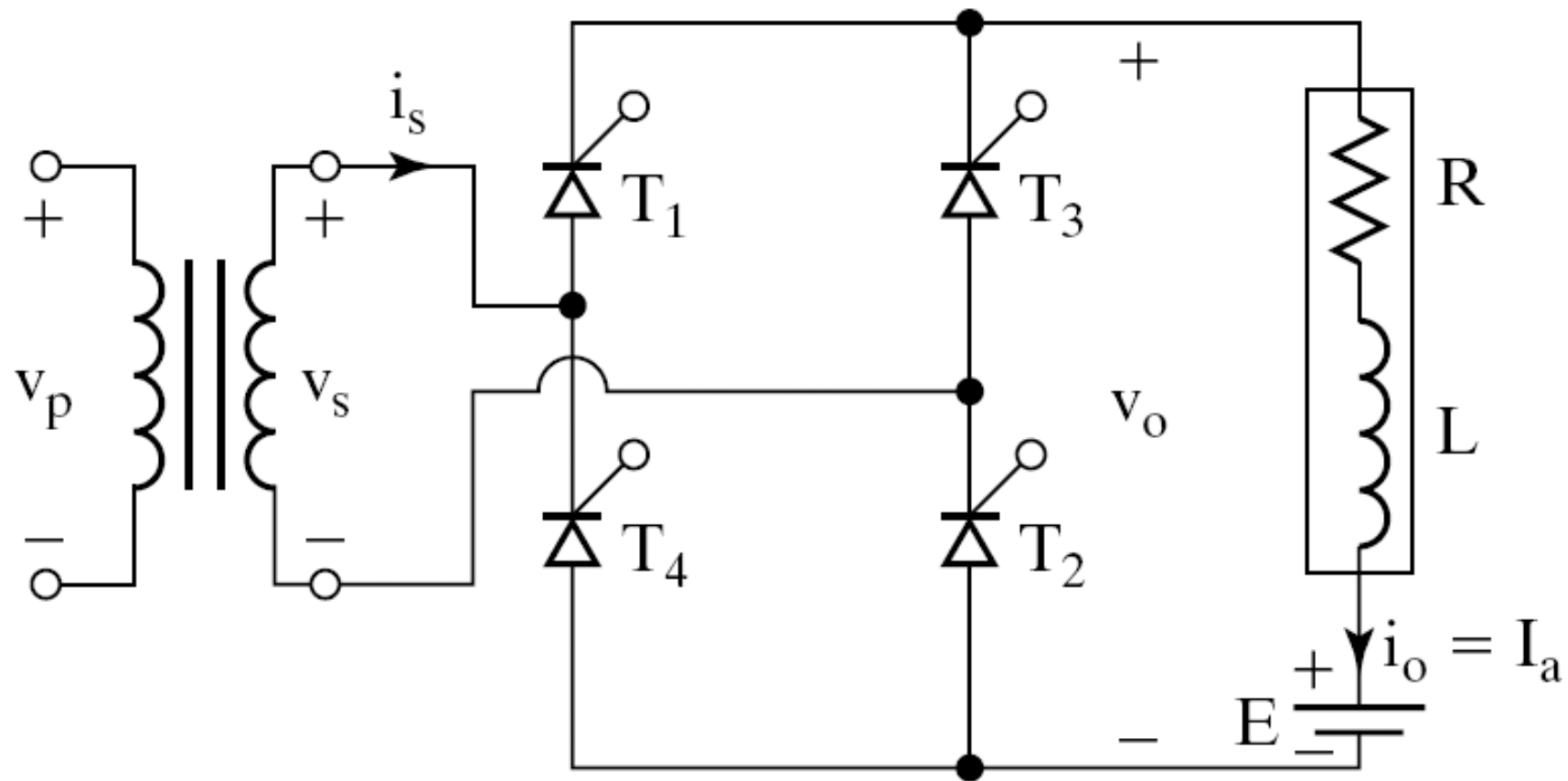
Single Phase Full Wave
Full Converter
(Fully Controlled Bridge Converter)
With R,L, & E Load



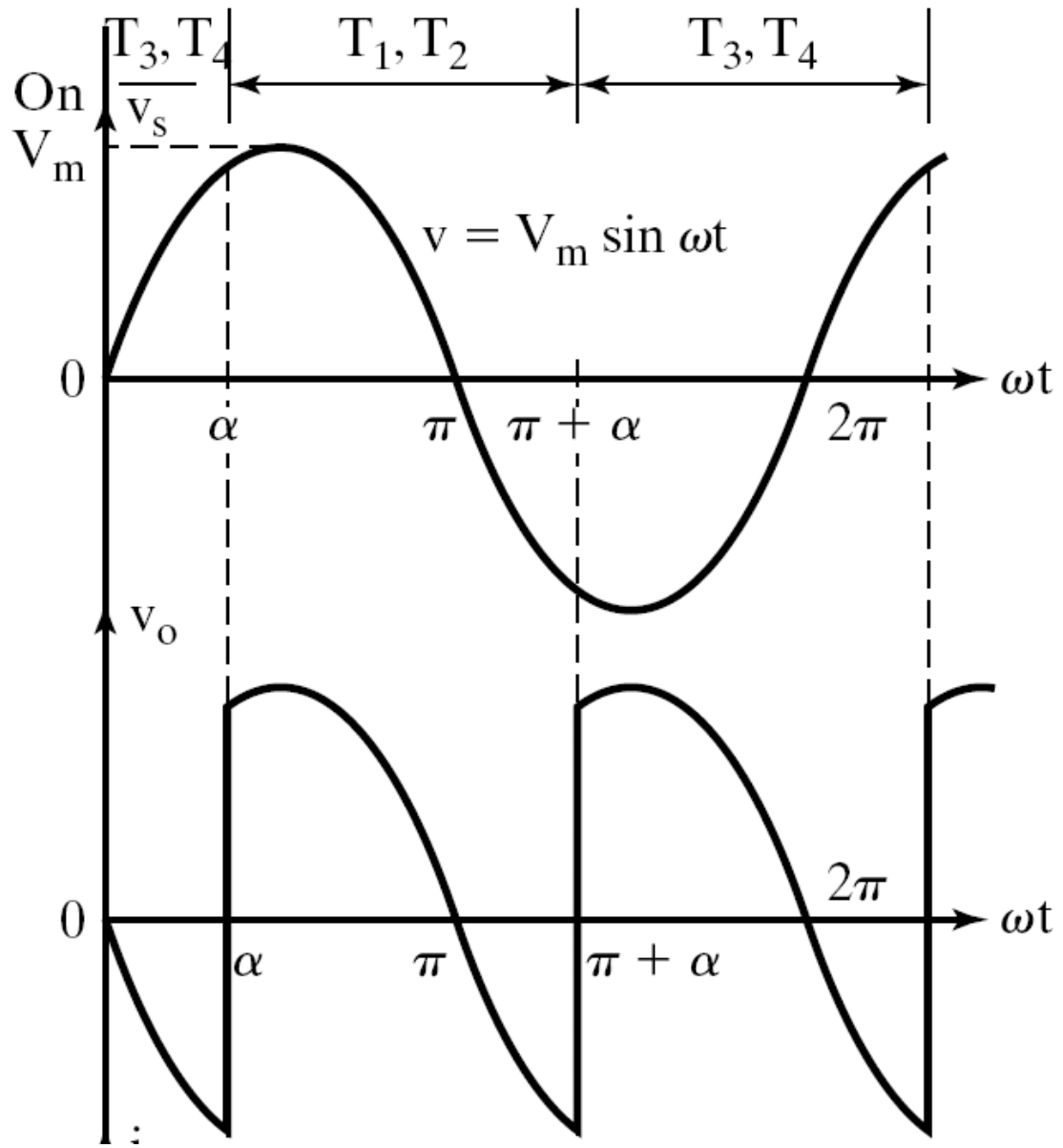Waveforms of
Single Phase Full Converter
Assuming Continuous (Constant Load
Current)
&
Ripple Free Load Current



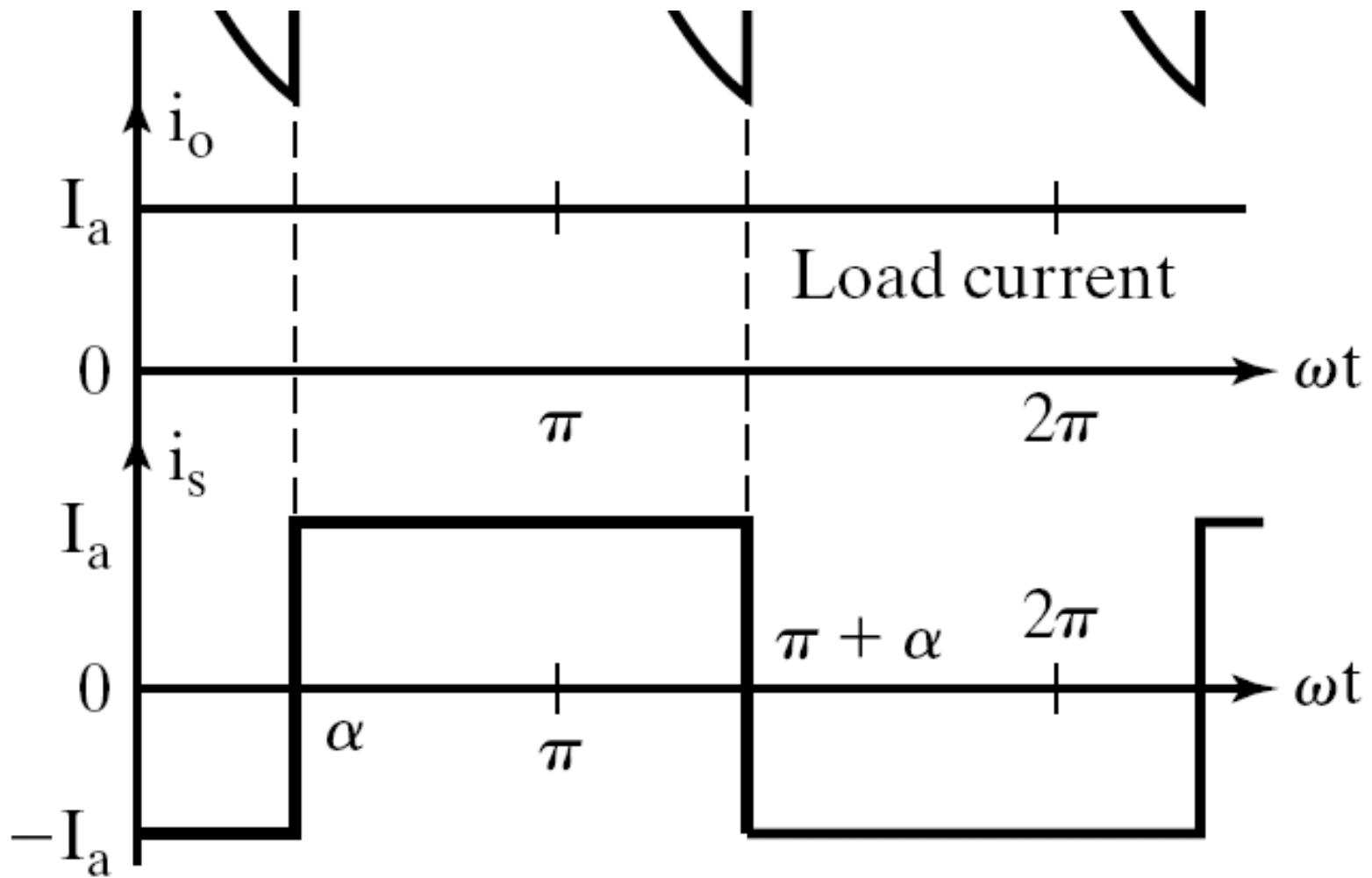

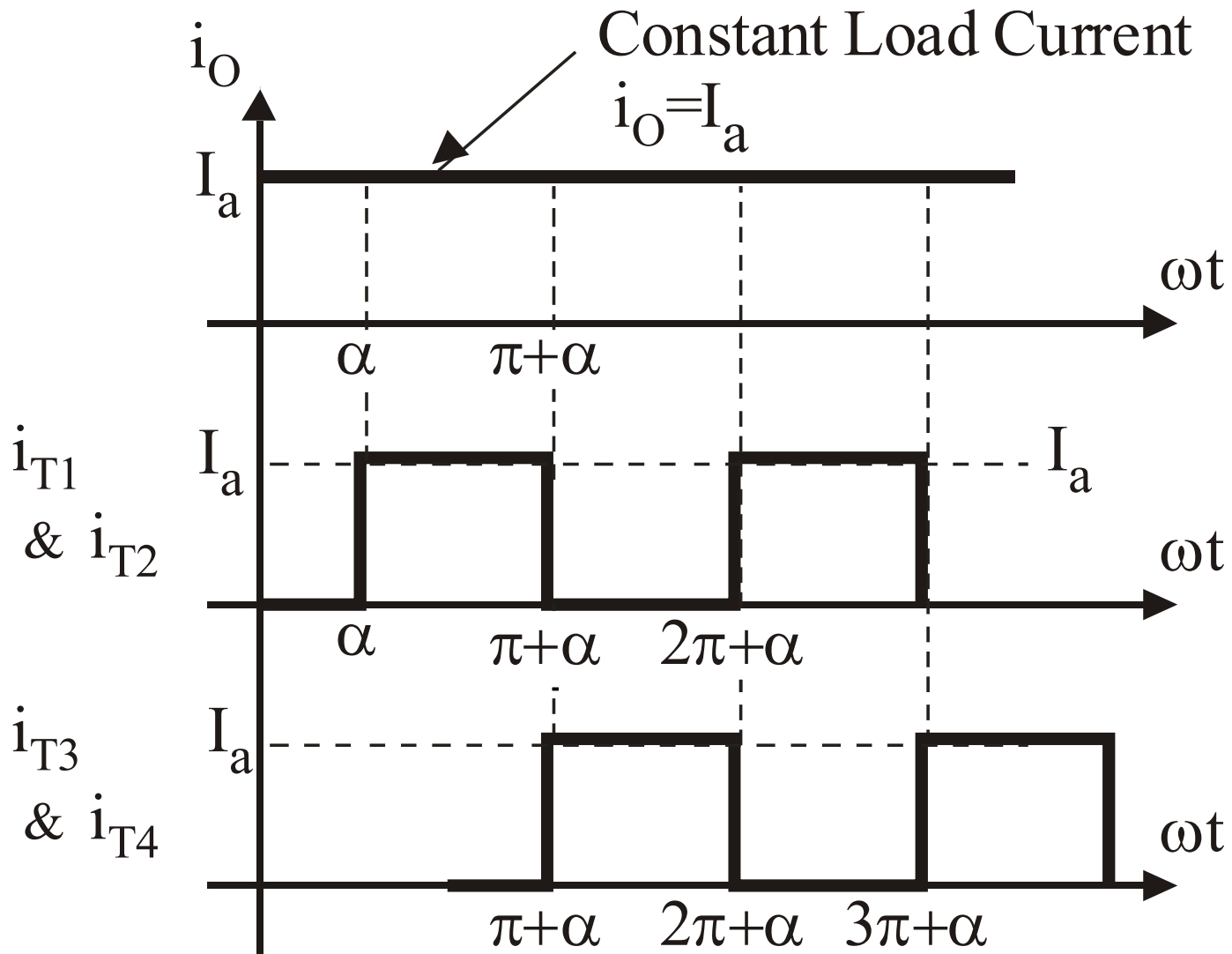

To Derive
An Expression For
The Average DC Output Voltage of a Single
Phase Full Converter
assuming
Continuous & Constant Load Current

The average dc output voltage can be determined by using the expression

$$V_{O(dc)} = V_{dc} = \frac{1}{2\pi} \left[\int_0^{2\pi} v_o \cdot d(\omega t) \right];$$

The o/p voltage waveform consists of two o/p pulses during the input supply time period of 0 to 2π radians. Hence the Average or dc o/p voltage can be calculated as

$$V_{O(dc)} = V_{dc} = \frac{2}{2\pi} \left[\int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \cdot d(\omega t) \right]$$

$$V_{O(dc)} = V_{dc} = \frac{2V_m}{2\pi} \left[-\cos \omega t \right]_{\alpha}^{\pi+\alpha}$$

$$V_{O(dc)} = V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$

Maximum average dc output voltage is calculated for a trigger angle $\alpha = 0^\circ$ and is obtained as

$$V_{dc(\max)} = V_{dm} = \frac{2V_m}{\pi} \times \cos(0) = \frac{2V_m}{\pi}$$

$$\therefore V_{dc(\max)} = V_{dm} = \frac{2V_m}{\pi}$$

The normalized average output voltage is given by

$$V_{dcn} = V_n = \frac{V_{O(dc)}}{V_{dc(max)}} = \frac{V_{dc}}{V_{dm}}$$
$$\therefore V_{dcn} = V_n = \frac{\frac{2V_m}{\pi} \cos \alpha}{\frac{2V_m}{\pi}} = \cos \alpha$$

By plotting $V_{O(dc)}$ *versus* α ,
we obtain the control characteristic of a
single phase full wave fully controlled bridge
converter
(single phase full converter)
for constant & continuous
load current operation.

To plot the control characteristic of a Single Phase Full Converter for constant & continuous load current operation.

We use the equation for the average/ dc output voltage

$$V_{O(dc)} = V_{dc} = \frac{2V_m}{\pi} \cos \alpha$$

| Trigger angle α in degrees | $V_{O(dc)}$ | Remarks |
|--------------------------------------|--|---|
| 0 | $V_{dm} = \left(\frac{2V_m}{\pi} \right)$ | Maximum dc output voltage $V_{dc(max)} = V_{dm} = \left(\frac{2V_m}{\pi} \right)$ |
| 30° | $0.866 V_{dm}$ | |
| 60° | $0.5 V_{dm}$ | |
| 90° | $0 V_{dm}$ | |
| 120° | $-0.5 V_{dm}$ | |
| 150° | $-0.866 V_{dm}$ | |
| 180° | $-V_{dm} = -\left(\frac{2V_m}{\pi} \right)$ | |