
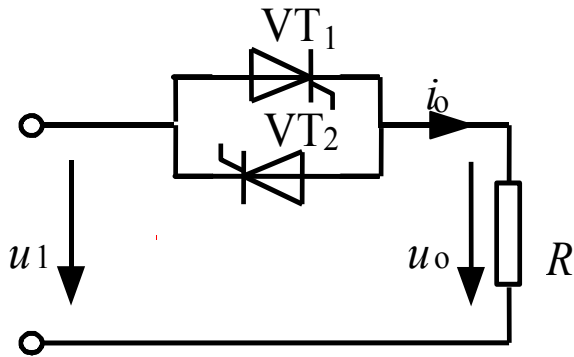


Single-phase AC voltage controller

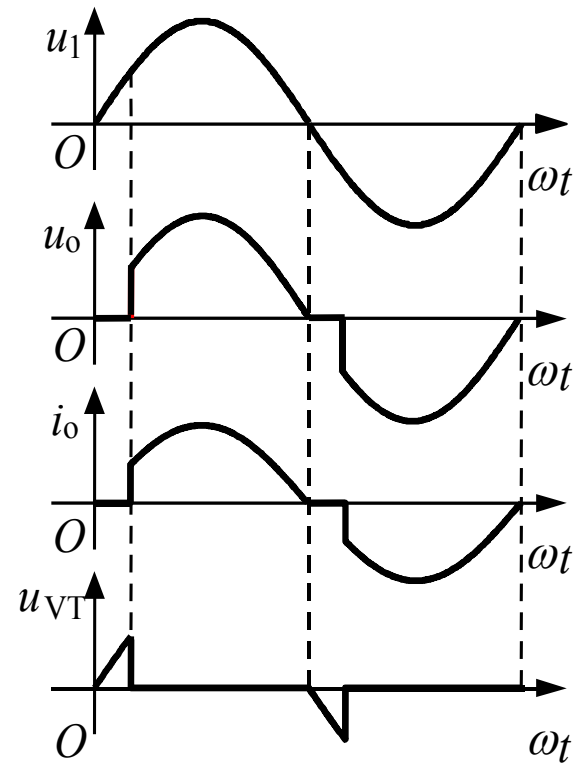

The phase shift range
(operation range of phase
delay angle):

$$0 \leq \alpha \leq \pi$$



- **Resistive load, quantitative analysis**

RMS value of output voltage

$$U_o = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} (\sqrt{2}U_1 \sin \omega t)^2 d(\omega t)} = U_1 \sqrt{\frac{1}{2\pi} \sin 2\alpha + \frac{\pi - \alpha}{\pi}} \quad (4-1)$$

RMS value of output current

$$I_o = \frac{U_o}{R} \quad (4-2)$$


RMS value of thyristor current

$$I_T = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} \left(\frac{\sqrt{2}U_1 \sin \omega t}{R} \right)^2 d(\omega t)} = \frac{U_1}{R} \sqrt{\frac{1}{2} \left(1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi} \right)} \quad (4-3)$$

Power factor of the circuit


$$\lambda = \frac{P}{S} = \frac{U_o I_o}{U_1 I_o} = \frac{U_o}{U_1} = \sqrt{\frac{1}{2\pi} \sin 2\alpha + \frac{\pi - \alpha}{\pi}} \quad (4-4)$$

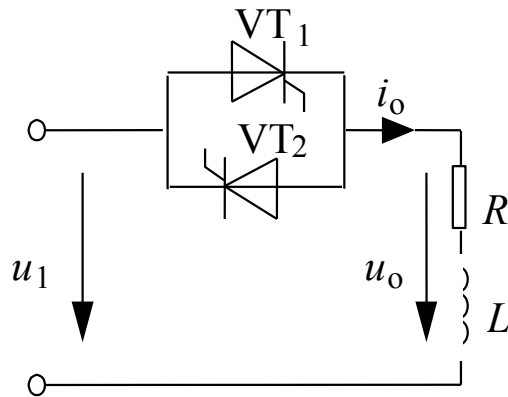Inductive (Inductor- resistor) load , operation principle



The phase shift range:

$$\varphi \leq \alpha \leq \pi$$

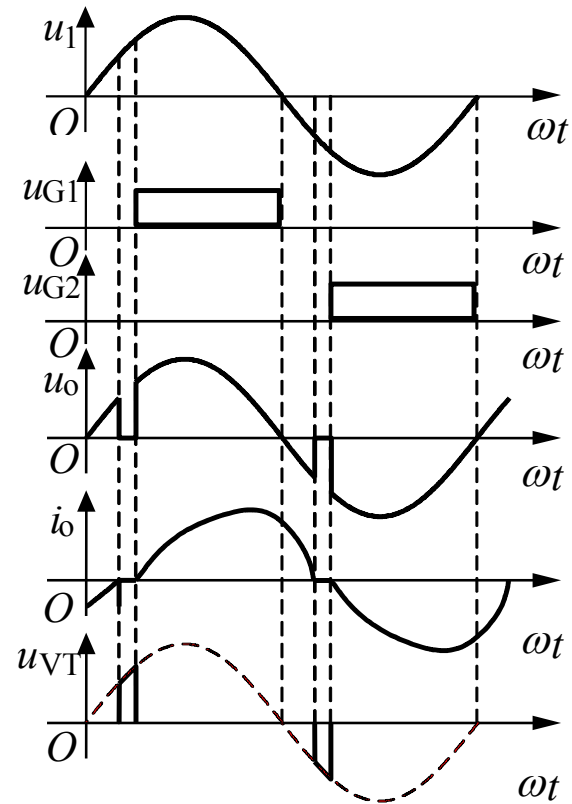

Inductive load, quantitative analysis

Differential equation

$$L \frac{di_o}{dt} + Ri_o = \sqrt{2}U_1 \sin \omega t$$

$$i_o \Big|_{\omega t = \alpha} = 0 \quad (4-5)$$

Solution


$$i_o = \frac{\sqrt{2}U_1}{Z} \left[\sin(\omega t - \varphi) - \sin(\alpha - \varphi) e^{\frac{\alpha - \omega t}{\text{tg} \varphi}} \right] \quad \alpha \leq \omega t \leq \alpha + \theta \quad (4-6)$$

Considering $i_o = 0$ when $\omega t = \alpha + \theta$

We have


$$\sin(\alpha + \theta - \varphi) = \sin(\alpha - \varphi) e^{\frac{-\theta}{\text{tg} \varphi}} \quad (4-7)$$

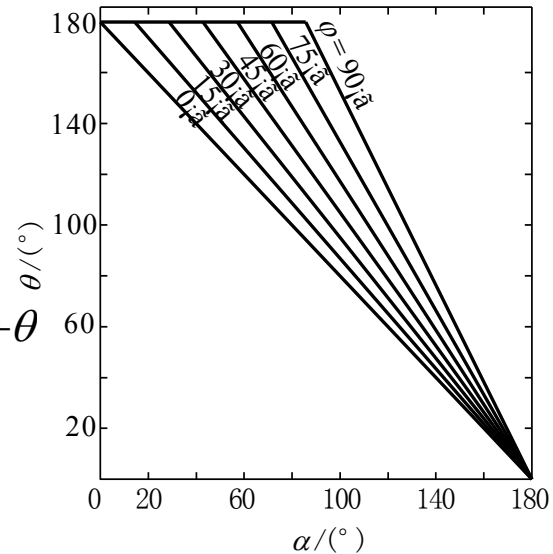The RMS value of output voltage, output current, and thyristor current can then be calculated.




4.1.2 Three-phase AC voltage controller


Classification of three-phase circuits

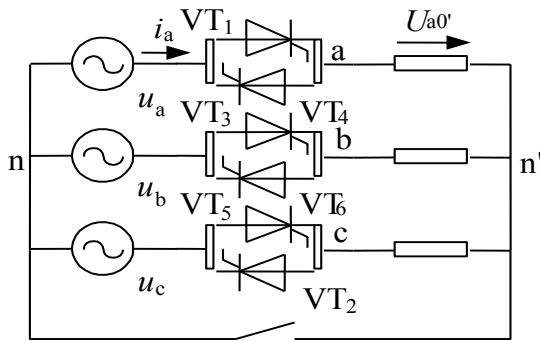


Y connection

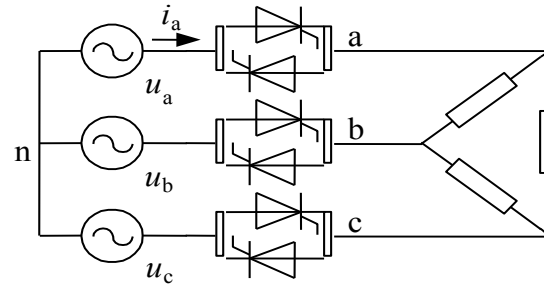

Line-controlled Δ connection

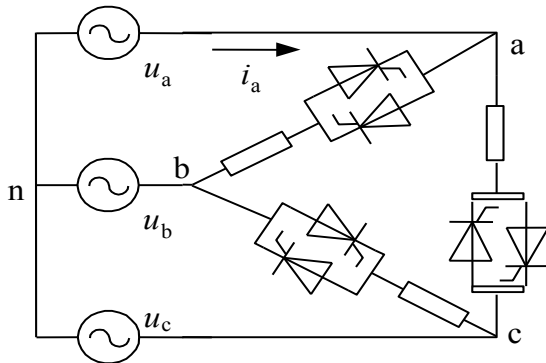


Branch-controlled Δ connection

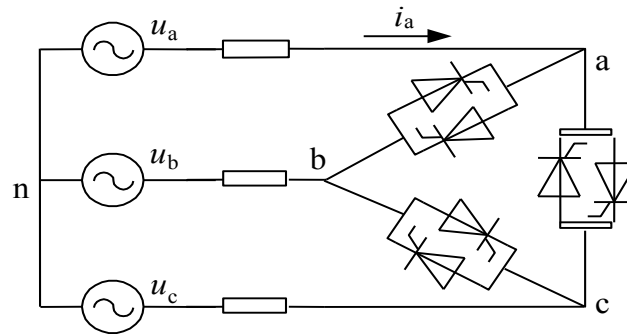

Neutral-point controlled Δ connection

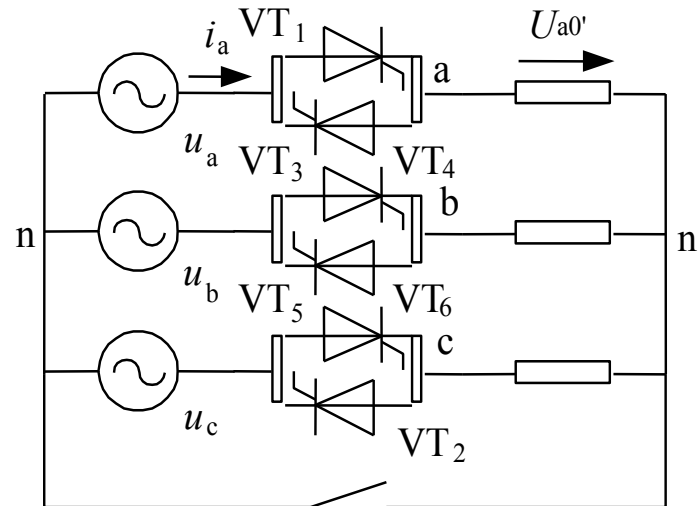- **3- phase 3- wire Y connection AC voltage controller**



For a time instant, there are 2 possible conduction states:

- Each phase has a thyristor conducting. Load voltages are the same as the source voltages.
- There are only 2 thyristors conducting, each from a phase. The load voltages of the two conducting phases are half of the corresponding line to line voltage, while the load voltage of the other phase is 0.