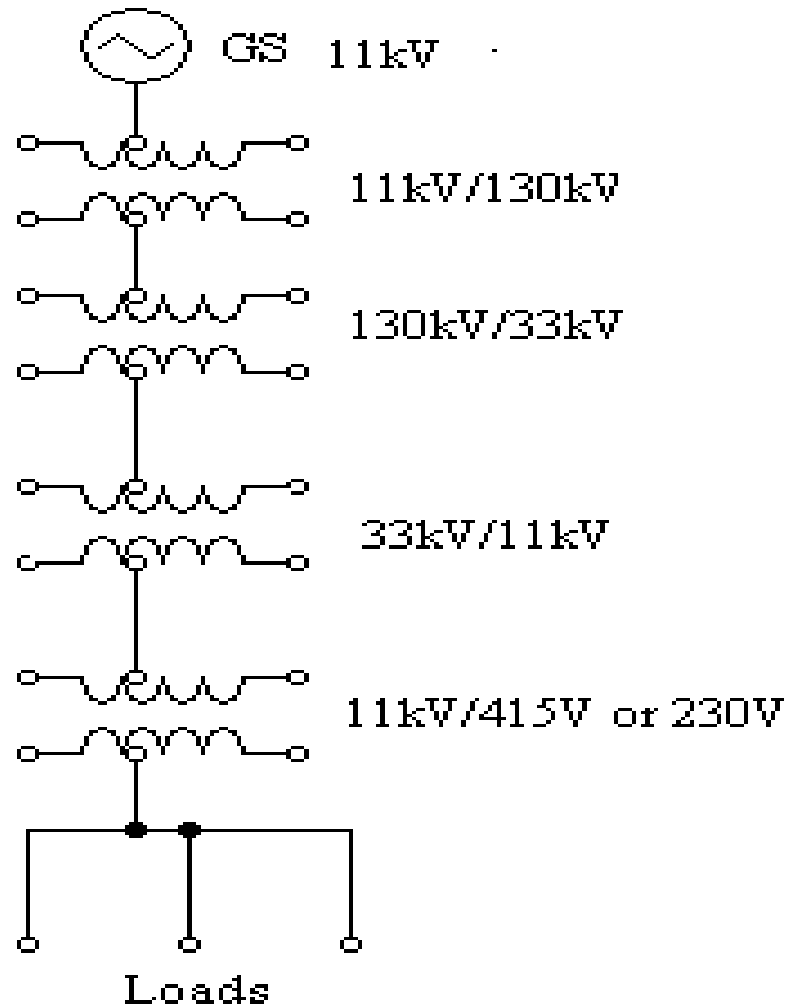



EEE- 601  
POWER SYSTEM ANALYSIS  
Unit-1

# Power system network


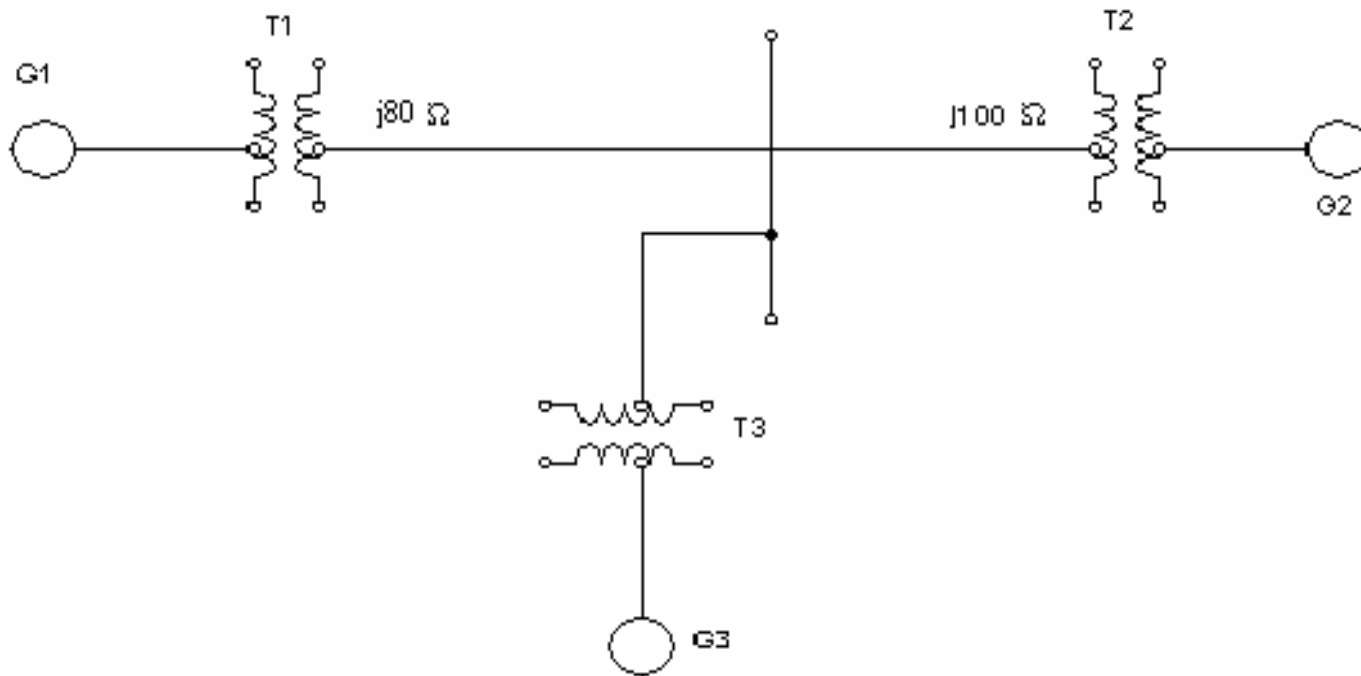
# ONE LINE DIAGRAM


It is a diagrammatic representation of a power system in which the components are represented by their symbols.




# COMPONENTS OF A POWER SYSTEM

1. Alternator
2. Power transformer
3. Transmission lines
4. Substation transformer
5. Distribution transformer
6. Loads
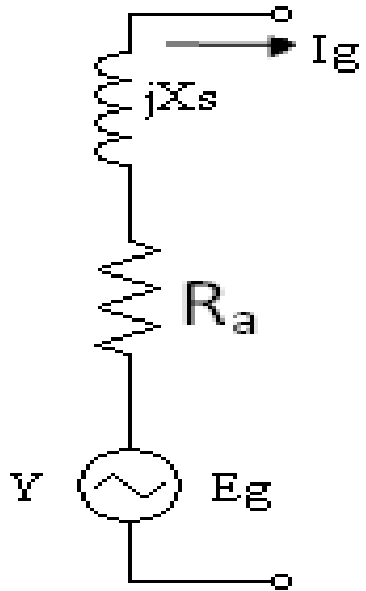
# MODELLING OF GENERATOR AND SYNCHRONOUS MOTOR




1Φ equivalent circuit of generator

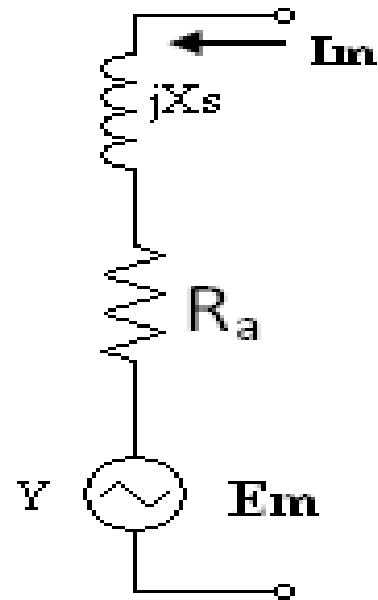

1Φ equivalent circuit of synchronous motor

# MODELLING OF TRANSFORMER

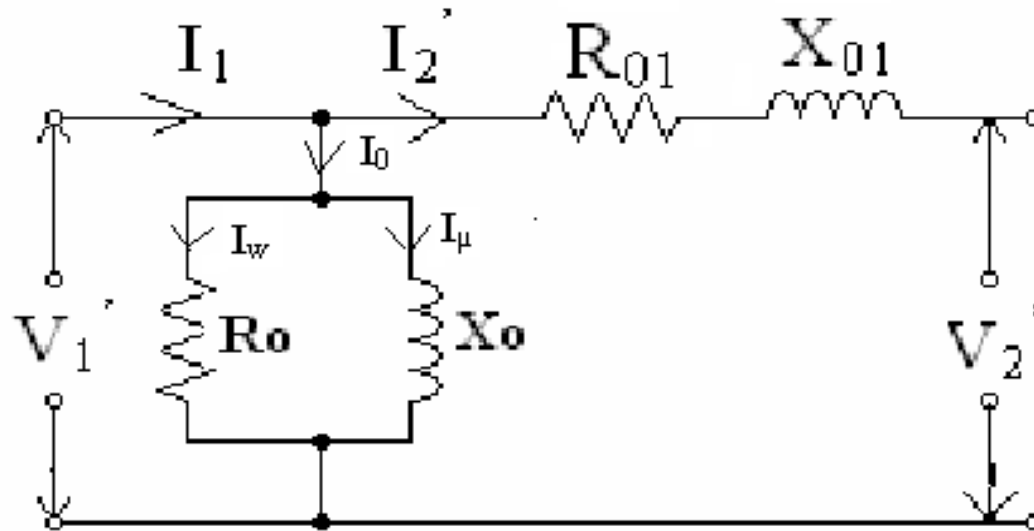


$$K = \frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$


$$R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2} \quad \text{=Equivalent resistance referred to } 1^\circ$$

$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2} \quad \text{=Equivalent reactance referred to } 1^\circ$$

# MODELLING OF TRANSMISSION LINE

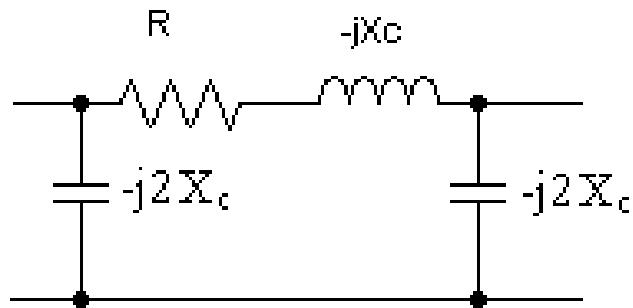

Π type

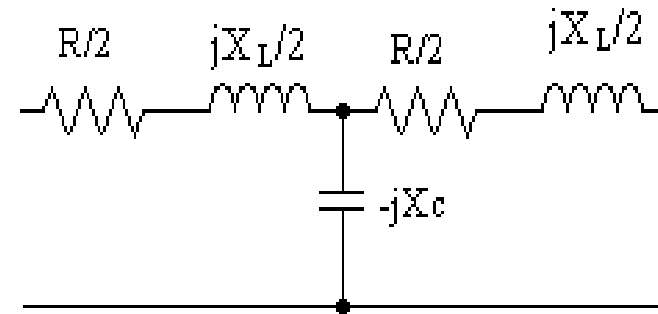

T type

**Thank you**