

EEE- 601  
POWER SYSTEM ANALYSIS  
Unit-1

# Per Unit

per unit=actual value/base value

Let  $KVA_b$ =Base KVA

$kV_b$ =Base voltage

$Z_b$ =Base impedance in  $\Omega$

$$Z_b = \frac{(kV_b)^2}{MVA_b} = \frac{(kV_b)^2}{\frac{KVA_b}{1000}}$$

# Changing the base of per unit quantities

Let  $z$  = actual impedance( $\Omega$ )

$Z_b$  = base impedance ( $\Omega$ )

$$Z_{p.u} = \frac{Z}{Z_b} = \frac{Z}{\frac{(kV_b)^2}{MVA_b}} = \frac{Z * MVA_b}{(kV_b)^2}$$

Let  $kV_{b,old}$  &  $MVA_{b,old}$  represent old base values

$kV_{b,new}$  &  $MVA_{b,new}$  represent new base values

$$Z_{p.u.,old} = \frac{Z * MVA_{b,old}}{(kV_{b,old})^2} \rightarrow (1)$$

$$Z = \frac{Z_{p.u.,old} * MVA_{b,old}}{(kV_{b,old})^2} \rightarrow (2)$$

$$Z_{p.u.,new} = \frac{Z * MVA_{b,new}}{(kV_{b,new})^2} \rightarrow (3)$$

$$Z_{p.u.,new} = Z_{p.u.,old} * \frac{(kV_{b,old})^2}{(kV_{b,new})^2} * \frac{MVA_{b,new}}{MVA_{b,old}}$$

## ADVANTAGES OF PER UNIT CALCULATIONS

- ❖ The p.u impedance referred to either side of a  $1\Phi$  transformer is same
- ❖ The manufacturers provide the impedance value in p.u
- ❖ The p.u impedance referred to either side of a  $3\Phi$  transformer is same regardless of the  $3\Phi$  connections Y-Y,  $\Delta$ -Y
- ❖ p.u value always less than unity.

# IMPEDANCE DIAGRAM

- This diagram obtained by replacing each component by their  $1\Phi$  equivalent circuit.


Following approximations are made to draw impedance diagram

1. The impedance b/w neutral and ground omitted.
2. Shunt branches of the transformer equivalent circuit neglected.

# REACTANCE DIAGRAM

- ❖ It is the equivalent circuit of the power system in which the various components are represented by their respective equivalent circuit.
- ❖ Reactance diagram can be obtained after omitting all resistances & capacitances of the transmission line from impedance diagram.
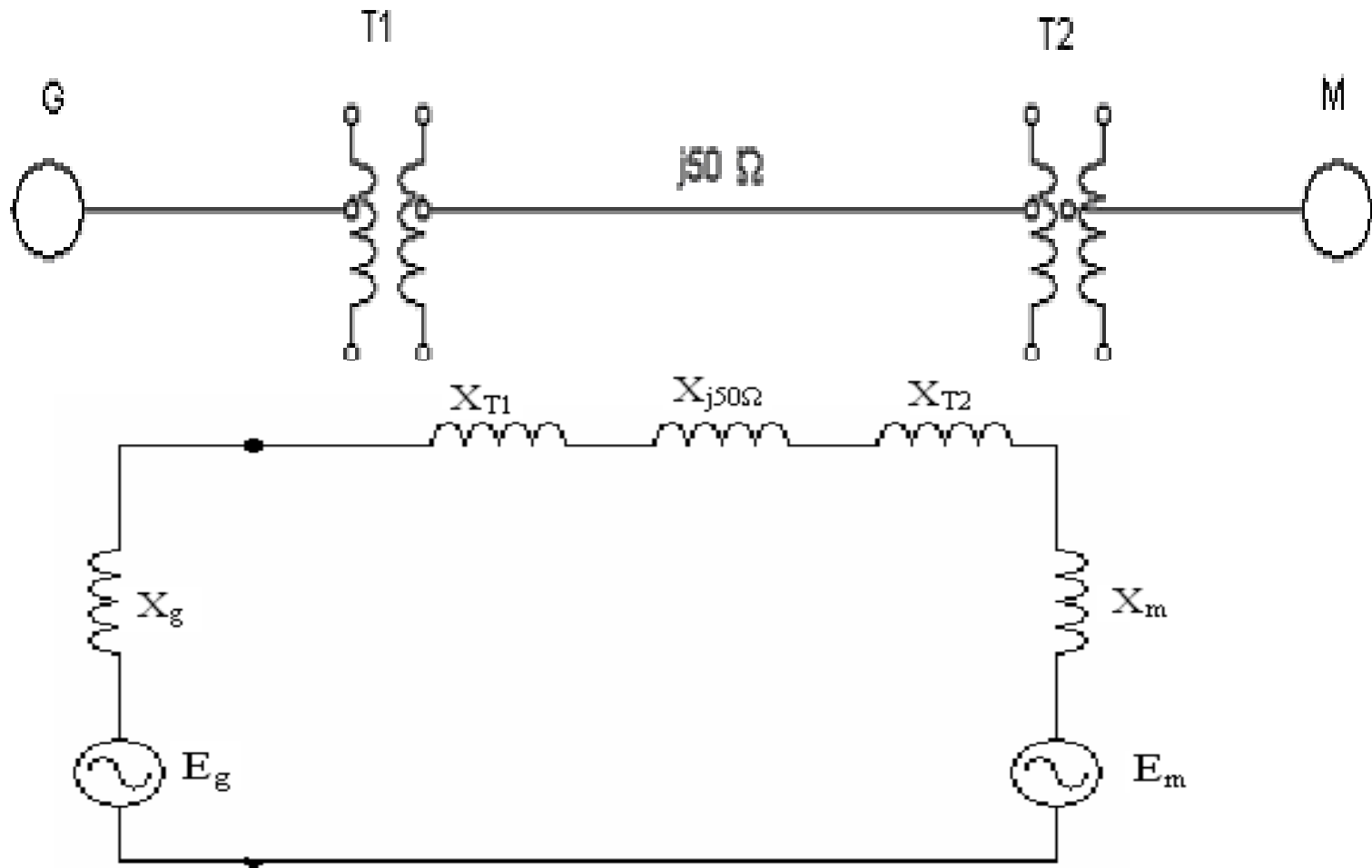
# REACTANCE DIAGRAM FOR THE GIVEN POWER SYSTEM NETWORK





## PROCEDURE TO FORM REACTANCE DIAGRAM FROM SINGLE DIAGRAM

1. Select a base power  $kVA_b$  or  $MVA_b$
2. Select a base voltage  $kV_b$
3. The voltage conversion is achieved by means of transformer  $kV_b$  on LT section =  $kV_b$  on HT section x LT voltage rating / HT voltage rating
4. When specified reactance of a component is in ohms  
p.u reactance = actual reactance / base reactance

$$X_{p.u,new} = X_{p.u,old} * \frac{\left(kV_{b,old}\right)^2}{\left(kV_{b,new}\right)^2} * \frac{MVA_{b,new}}{MVA_{b,old}}$$

**Thank you**