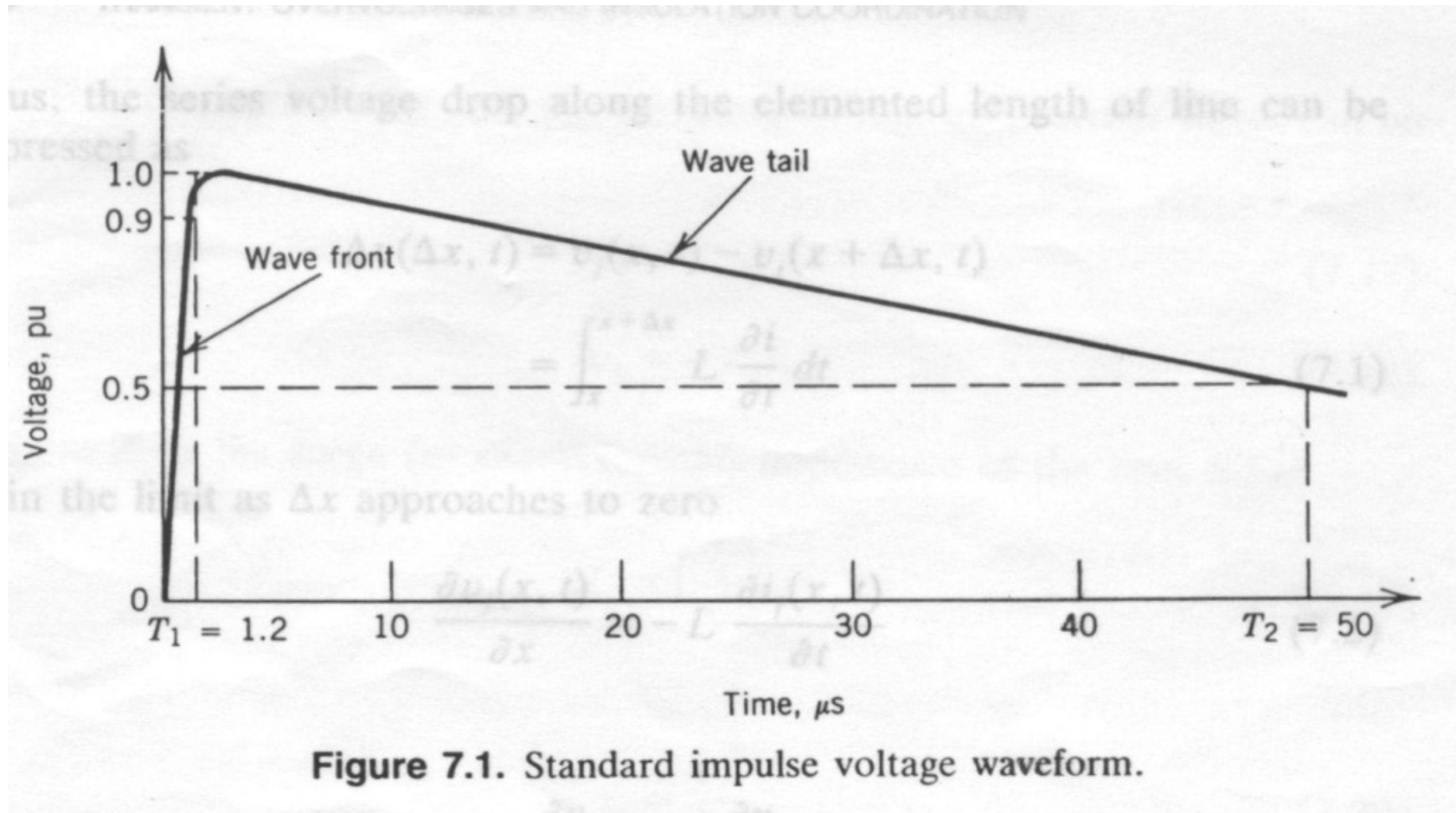


UNIT V
TRAVELLING WAVE

Introduction

- Transient Phenomenon :
 - Aperiodic function of time
 - Short duration
- Example : Voltage & Current Surge :
(The current surge are made up of charging or discharging capacitive currents that introduced by the change in voltages across the shunt capacitances of the transmission system)
 - Lightning Surge
 - Switching Surge

Impulse Voltage Waveform



Travelling Wave

- Disturbance represented by closing or opening the switch S.
- If Switch S closed, the line suddenly connected to the source.
- The whole line is not energized instantaneously.
- Processed :
 - When Switch S closed
 - The first capacitor becomes charged immediately
 - Because of the first series inductor (acts as open circuit), the second capacitor is delayed
- This gradual buildup of voltage over the line conductor can be regarded as a voltage wave is traveling from one end to the other end

Travelling Wave

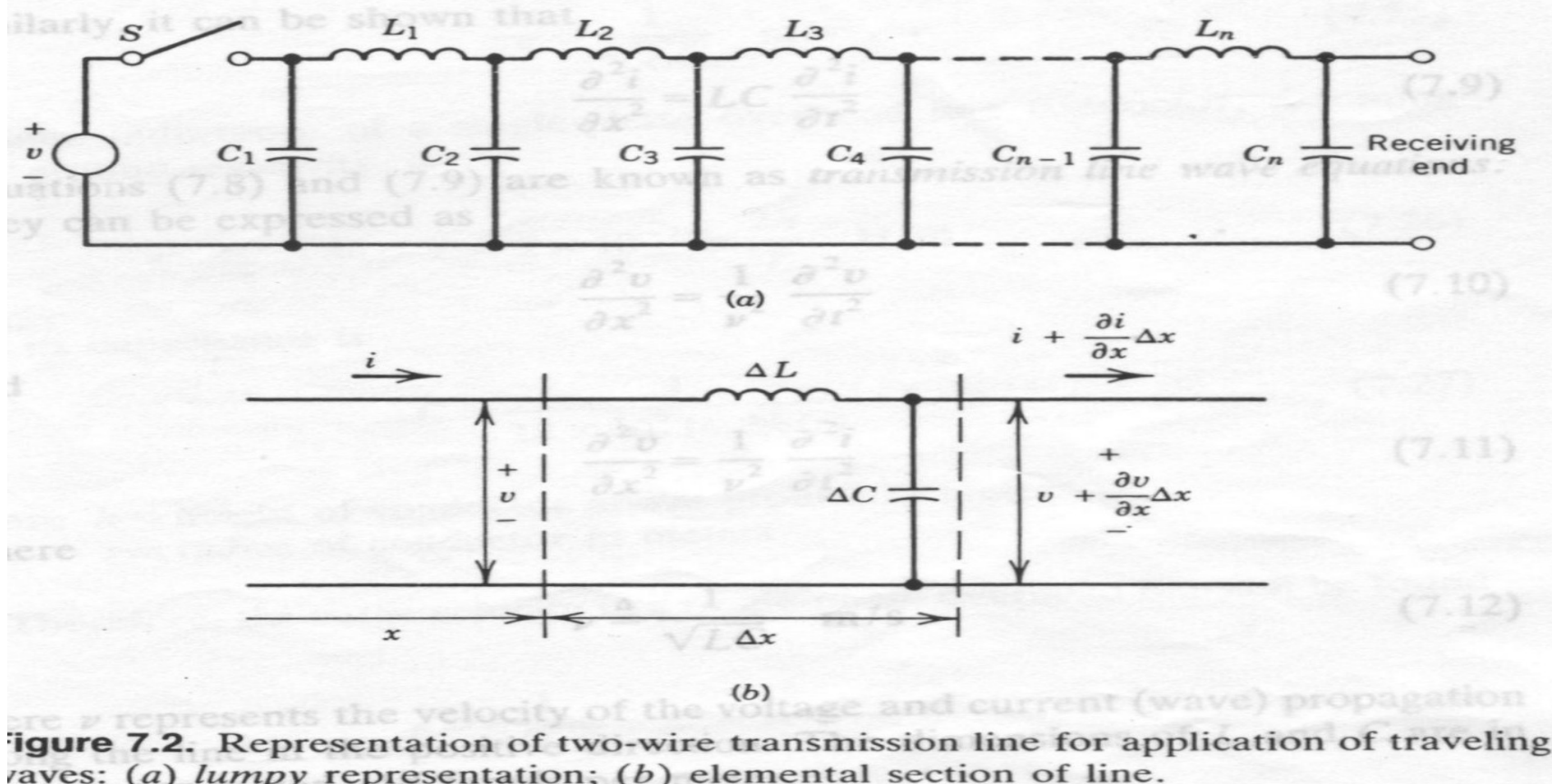


Figure 7.2. Representation of two-wire transmission line for application of traveling waves: (a) *lumpy* representation; (b) elemental section of line.

Voltage Function

- $v_f = v_1(x - vt)$
- $v_b = v_2(x + vt)$
- $v = 1/\sqrt{LC}$
- $v(x, t) = v_f + v_b$
- $v_f = Z_c i_f$
- $v_b = Z_c i_b$

Current Function

- $v_f = v_1(x - vt)$
- $v_b = v_2(x + vt)$
- $v = 1/\sqrt{LC}$
- $v(x, t) = v_f + v_b$
- $v_f = Z_c i_f$
- $v_b = Z_c i_b$

Velocity of Surge Propagation

- In the air = 300 000 km/s
- $v = 1/\sqrt{LC}$ m/s
- Inductance single conductor Overhead Line
(assuming zero ground resistivity) :
 $L = 2 \times 10^{-7} \ln(2h/r)$ H/m
 $C = 1/[18 \times 10^9 \ln(2h/r)]$ F/m

-

Velocity of Surge Propagation

- In the cable : $v = 1/\sqrt{LC} = 3 \times 10^8 \sqrt{K}$ m/s
K=dielectric constant (2.5 to 4.0)

$$v = \frac{1}{\sqrt{LC}} = \left[\left(\frac{2 \times 10^{-7} \ln(2h/r)}{18 \times 10^9 \ln(2h/r)} \right)^{1/2} \right]^{-1}$$

Surge Power Input & Energy Storage

- $P=vi$ Watt
- $W_s = \frac{1}{2} C v^2$; $W_m = \frac{1}{2} L i^2$
- $W=W_s+W_m = 2 W_s = 2 W_m = C v^2 = L i^2$
- $P=W \omega = L i^2 / \sqrt{LC} = i^2 Z_c = v^2 / Z_c$

Superposition of Forward and Backward-Travelling Wave

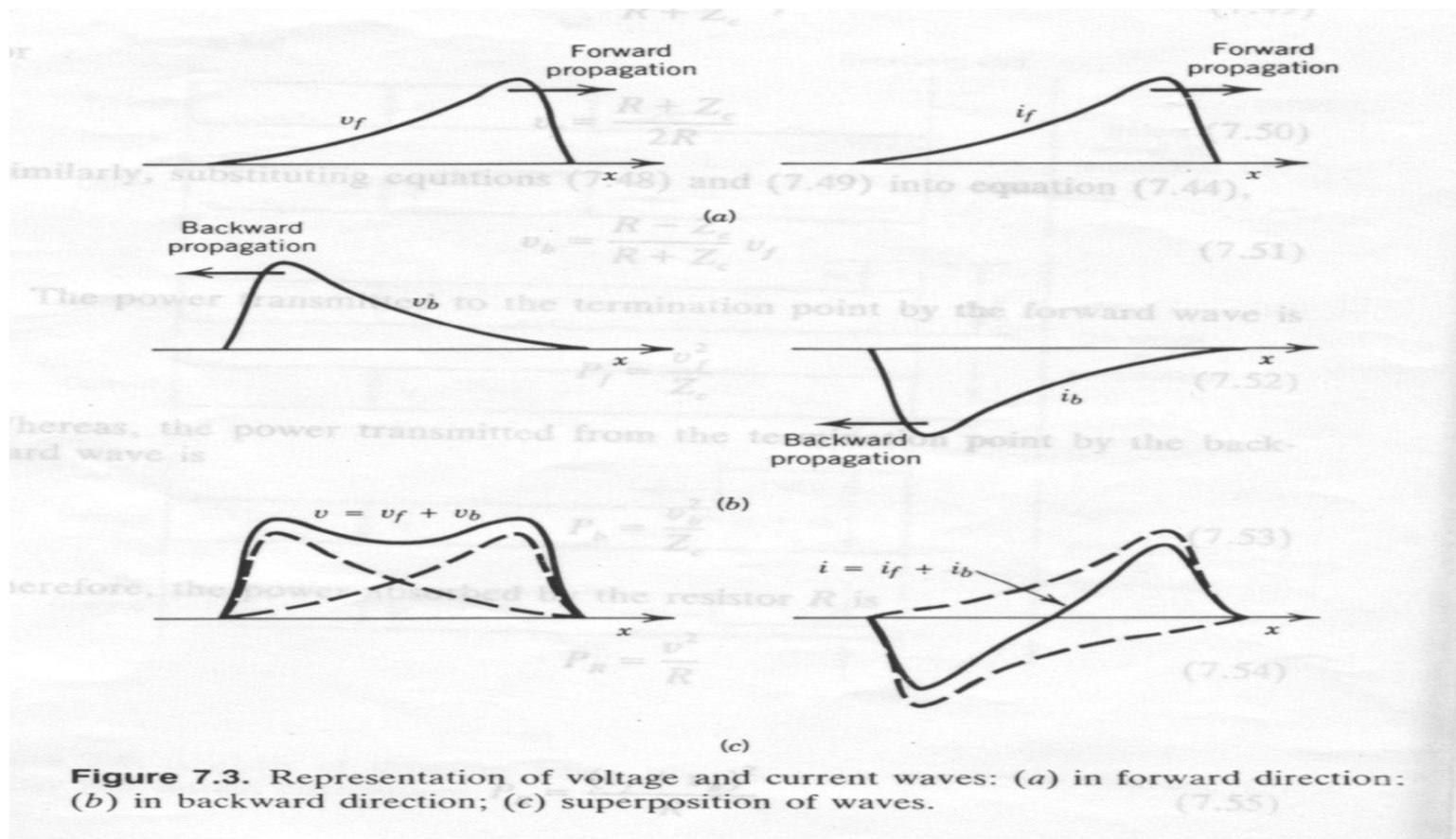


Figure 7.3. Representation of voltage and current waves: (a) in forward direction; (b) in backward direction; (c) superposition of waves.

Thank you