

Unit-V

Travelling Wave

Effects of Line Termination

- Assuming v_f , i_f , v_b and i_b are the instantaneous voltage and current.

Hence the instantaneous voltage and current at the point discontinuity are :

- $v(x,t) = v_f + v_b$ and $i(x,t) = i_f + i_b$

Effects of Line Termination

- $I = v_f / Z_c - v_b / Z_c$
and $iZ_c = v_f - v_b$
- $v + iZ_c = 2v_f$
so $v = 2v_f - iZ_c$
- $v_f = \frac{1}{2} (v + iZ_c)$
and $v_b = \frac{1}{2} (v - iZ_c)$
or $v_b = v_f - iZ_c$

Line Termination in Resistance

$$v = iR$$

$$i = \frac{2}{R + Z_c} v_f$$

$$v_f = \frac{R + Z_c}{2R}$$

$$v_b = \frac{R - Z_c}{R + Z_c} v_f$$

Line Termination in Resistance

$$P_f = \frac{v_f^2}{Z_c}$$

$$P_b = \frac{v_b^2}{Z_c}$$

$$P_R = \frac{v^2}{R} = \frac{(v_f + v_b)^2}{R}$$

$$P_f = P_b + P_R$$

Line Termination in Impedance (Z)

$$i = \frac{2}{Z + Z_c} i_f$$

$$v = \frac{2Z}{Z + Z_c} v_f$$

$$v = \tau v_f$$

$$\tau \cong \frac{2Z}{Z + Z_c}$$

Line Termination in Impedance (Z)

$$v_f = \frac{Z + Z_c}{2R} v$$

$$v_b = \frac{Z - Z_c}{Z + Z_c} v_f$$

$$v_b = \rho v_f$$

$$\rho \cong \frac{Z - Z_c}{Z + Z_c}$$

- Line is terminated with its characteristic impedance :
 - $Z=Z_c$
 - $\rho =0$, no reflection (infinitely long)

- $Z>Z_c$
 - v_b is positive
 - I_b is negative
 - Reflected surges increased voltage and reduced current

- $Z < Z_c$
 - v_b is negative
 - I_b is positive
 - Reflected surges reduced voltage and increased current

- Z_s and Z_R are defined as the sending-end and receiving end.

$$\rho_s = \frac{Z_s - Z_c}{Z_s + Z_c}; \rho_R = \frac{Z_R - Z_c}{Z_R + Z_c}$$

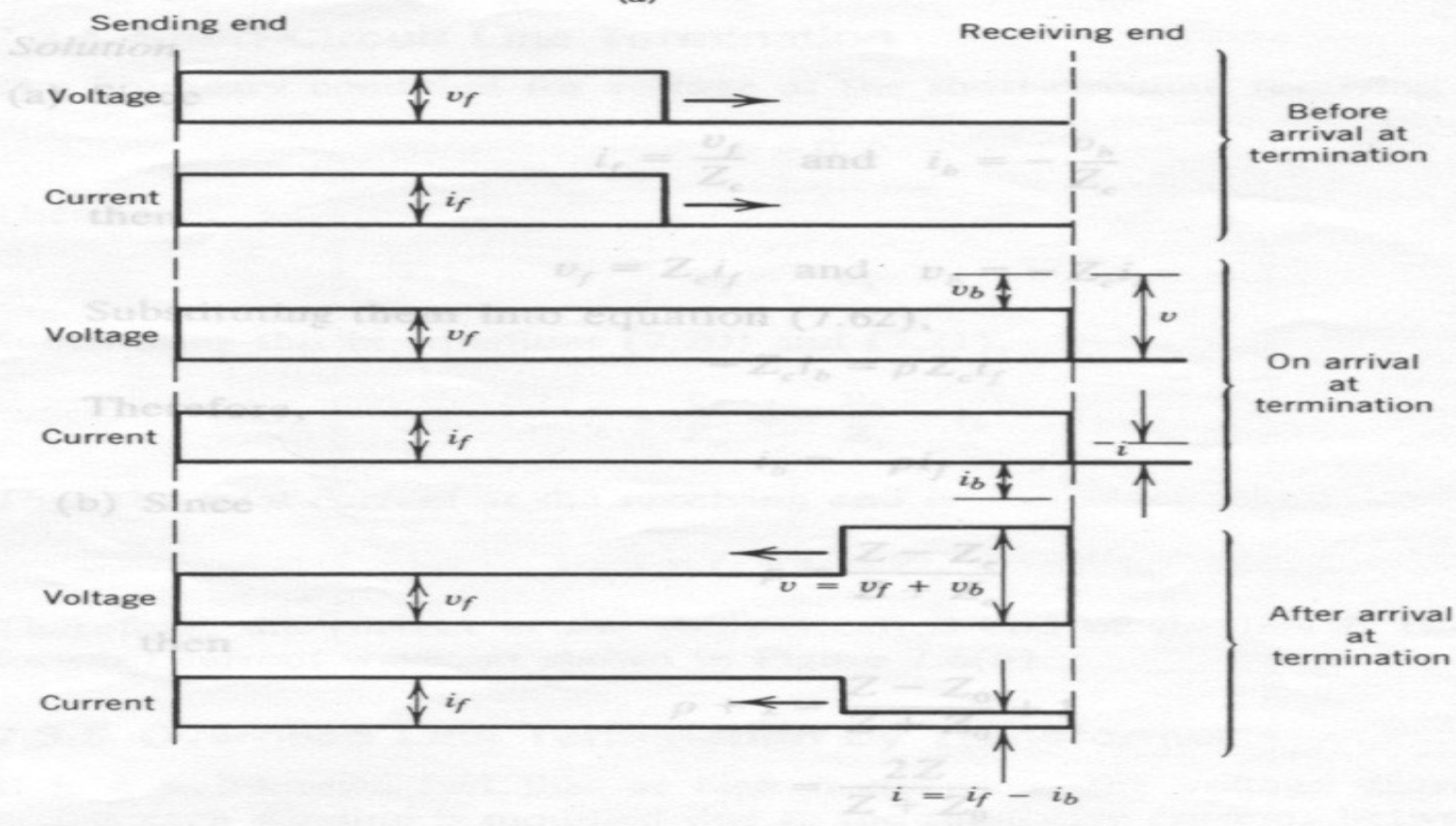
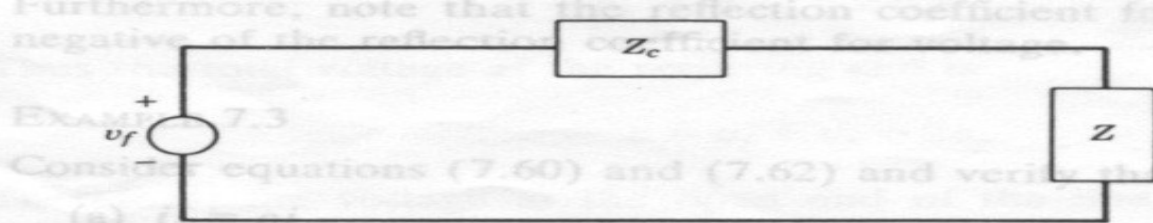


Figure 7.4. Analysis of traveling waves when $Z > Z_c$: (a) circuit diagram; (b) voltage and current distributions.

$$\rho_s = \frac{Z_s - Z_c}{Z_s + Z_c} \quad (7.65)$$

- (b) Reflection coefficient of voltage wave.
- (c) Backward-traveling voltage wave.
- (d) Voltage at end of line.
- (e) Reflection coefficient of current wave.
- (f) Backward-traveling current wave.
- (g) Current flowing through resistor.
- (h) Reflection coefficient of current wave.

Solution

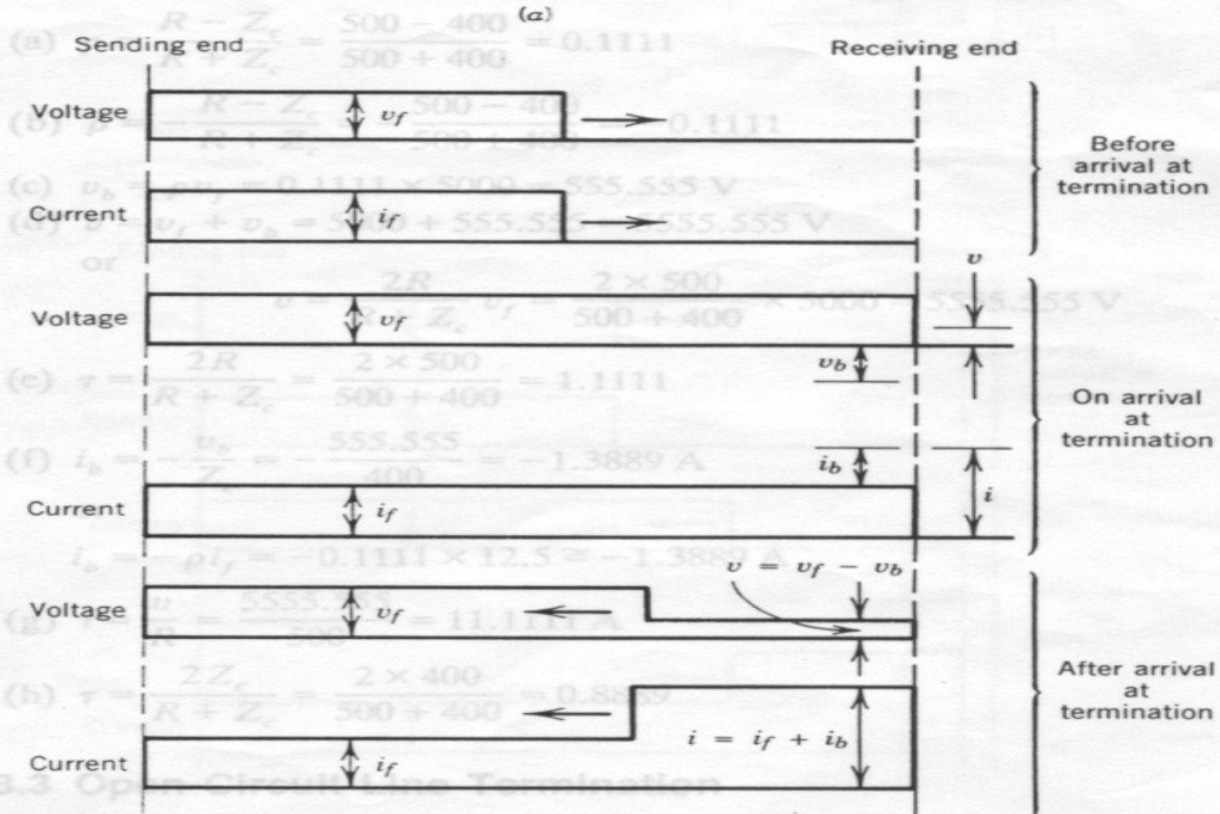


Figure 7.5. Analysis of traveling waves when $Z < Z_c$: (a) circuit diagram; (b) voltage and current distributions.



Thanks