

Unit-V

Travelling Wave


Open-Circuit Line Termination

- Open circuit at receiving $Z_t = \infty$
- Boundary condition for current $i=0$
- Therefore $i_f = -i_b$
- $V_b = Z_c i_b = Z_c (-i_f) = -Z_c i_f = -v_f$
- Thus total voltage at the receiving end
 $v = v_f + v_b = 2v_f$
- Voltage at the open end is twice the forward voltage wave


Systems

Sending end


Receiving end

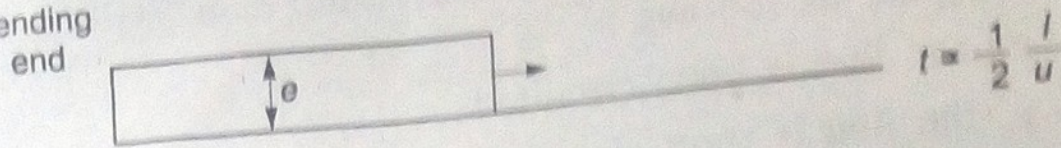


(a)

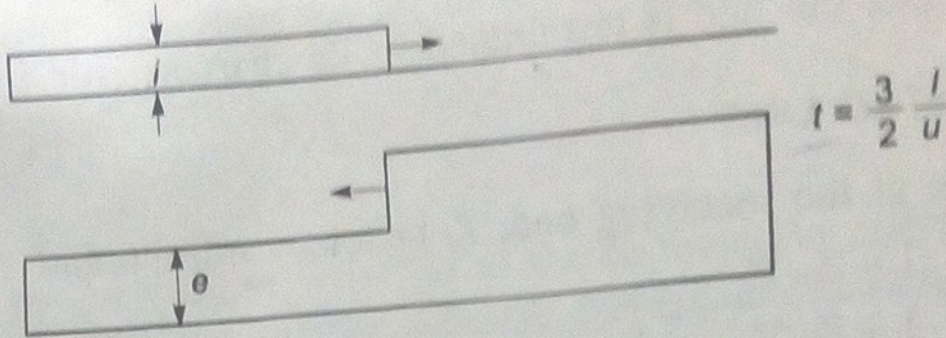

(b)

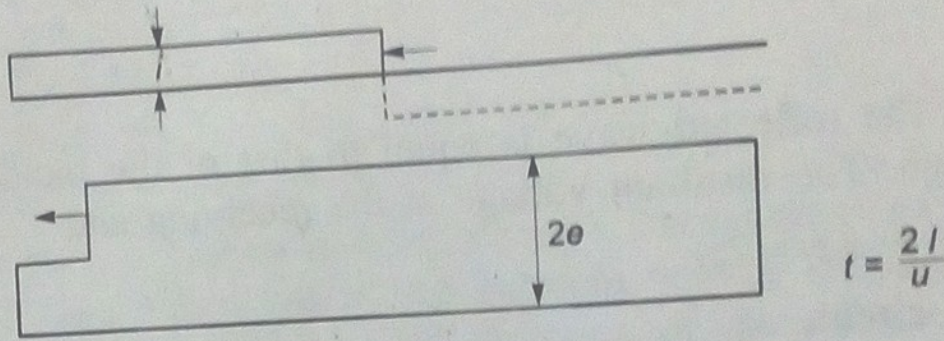

(c)

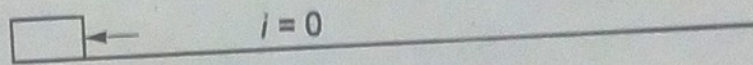


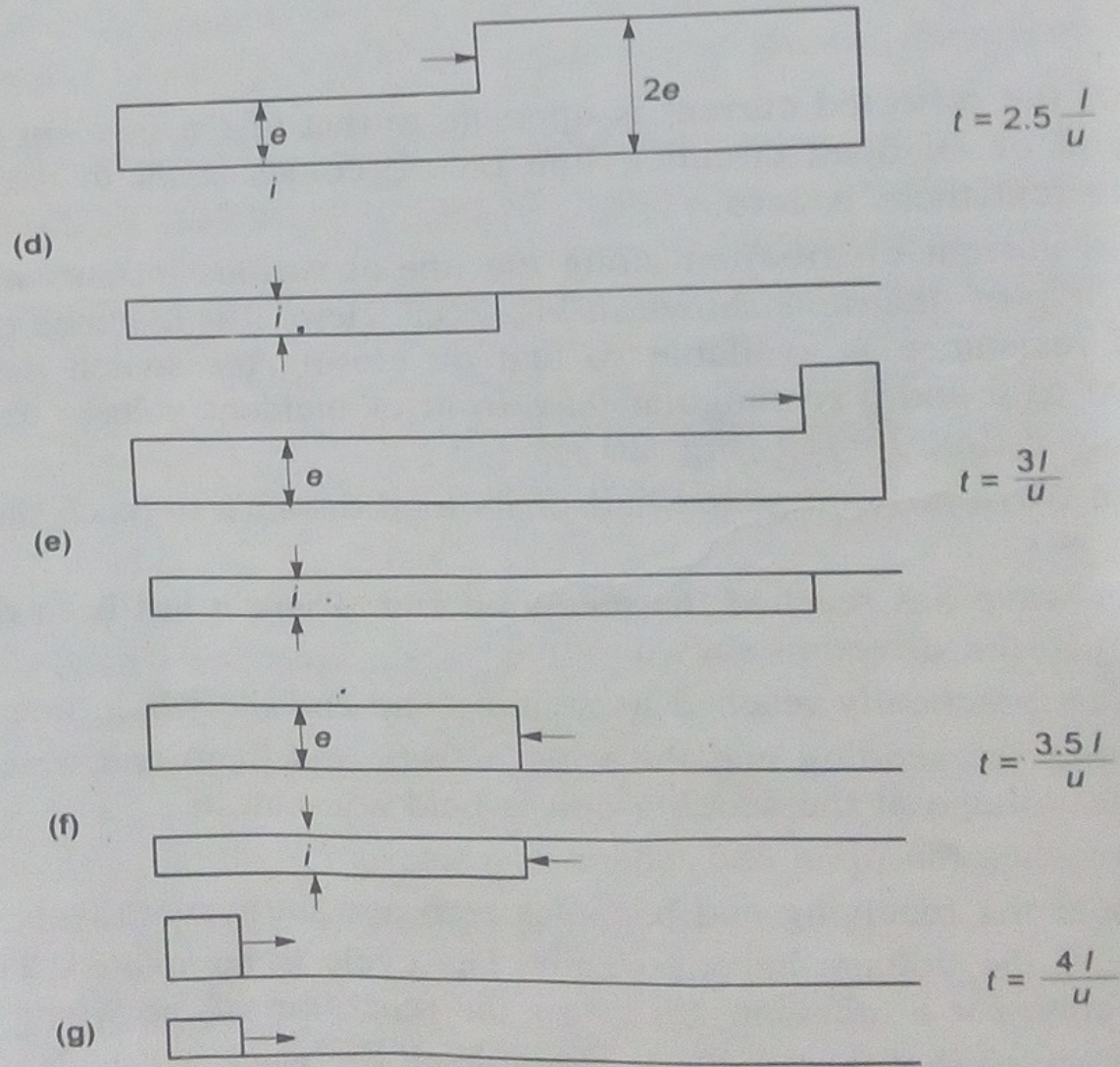
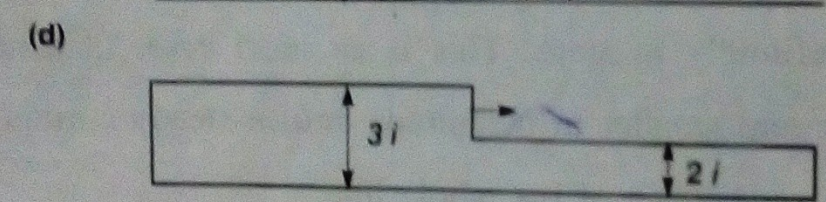
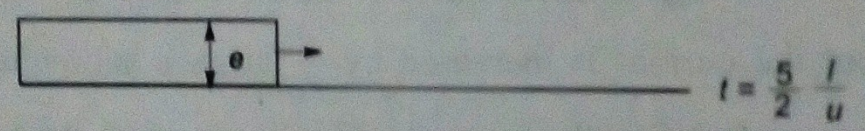
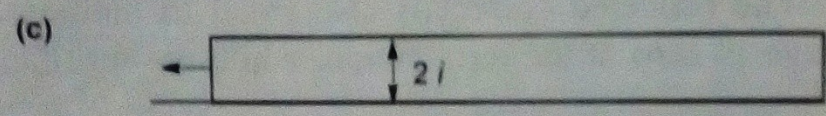
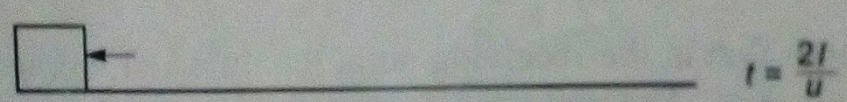
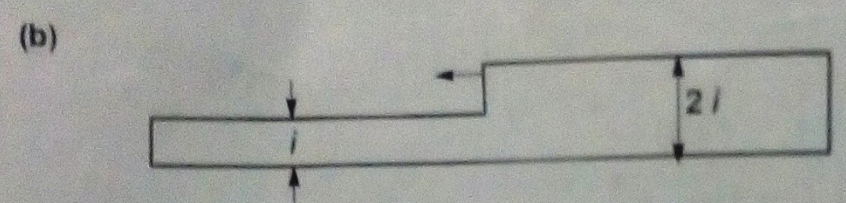
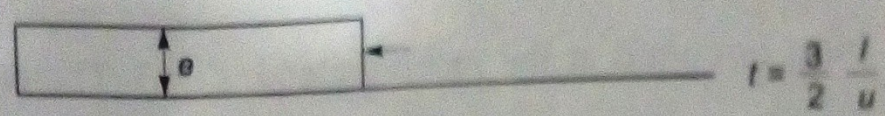
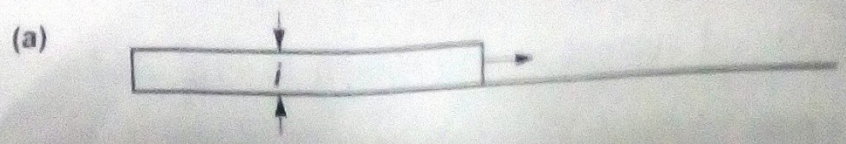


Fig. 20.3. Voltage and current distributions in an open-circuited line.

Short Circuit Line Termination

- Boundary condition for current $v=0$
- Therefore $v_f = -v_b$
- $i_f = v_f / Z_c = -(v_b / Z_c) = i_b$
- Thus total voltage at the receiving end
 $v = i_f + i_b = 2i_f$
- Current at the open end is twice the forward current wave

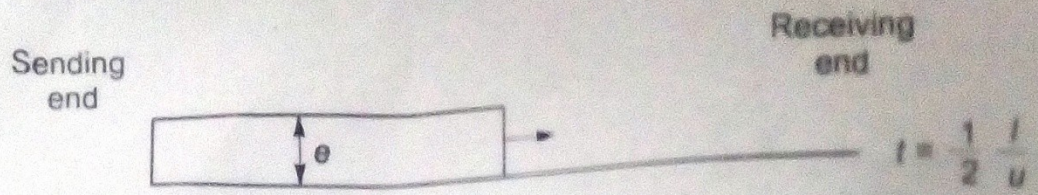

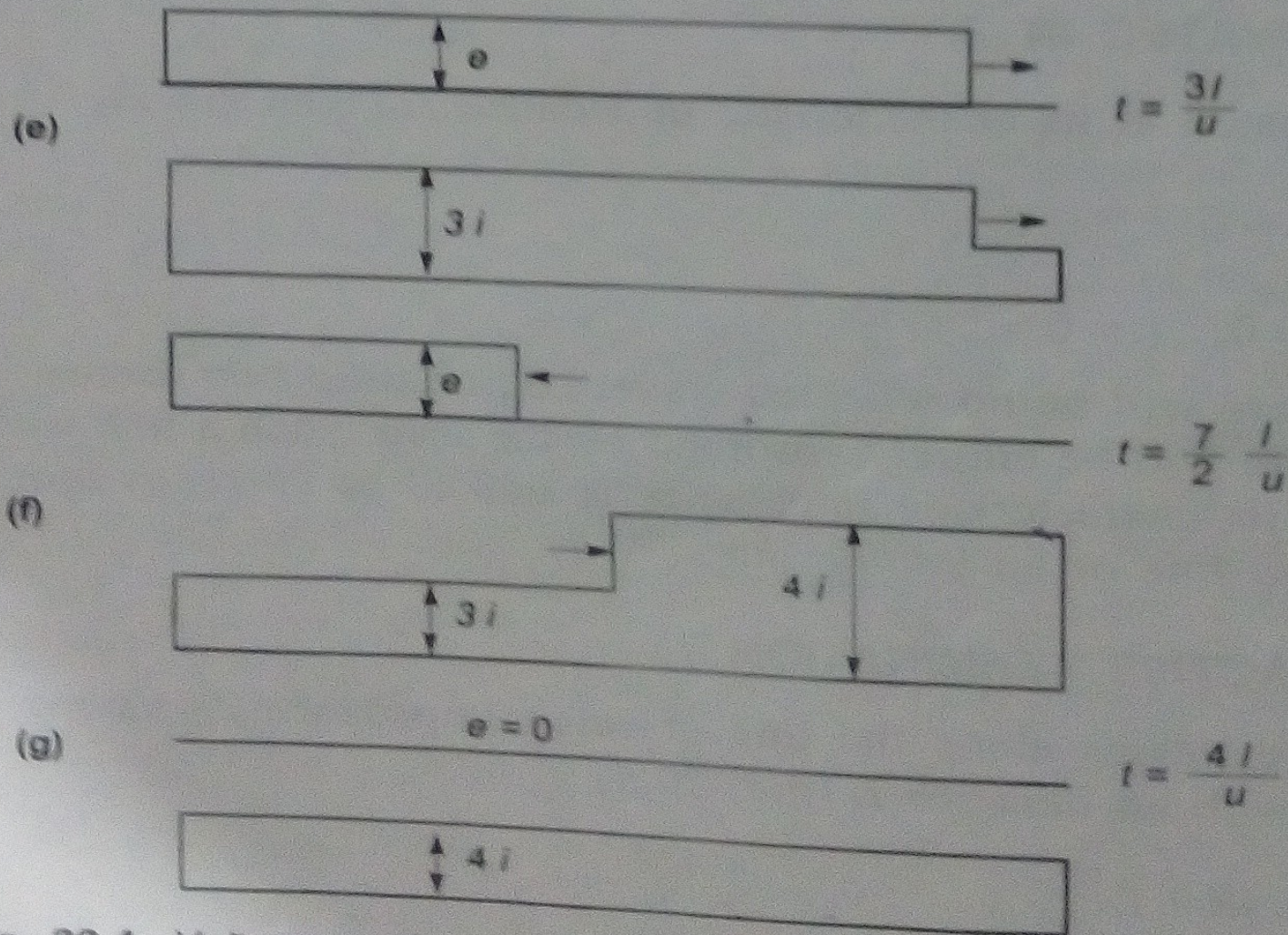


Fig. 20.4. Voltage and current distributions in a short-circuited line.



Thanks