

Unit-V

Travelling Wave



Junction of Several Line

Example:


$$v = \frac{2v_f}{Z_{c1} + Z_{c2}/2} \frac{Z_{c2}}{2}$$

$$v = \frac{2Z_{c1}}{Z_{c1} + Z_{c2}/2} i_f$$

$$i_f = \frac{2v_f}{Z_{c1} + Z_{c2}/2}$$

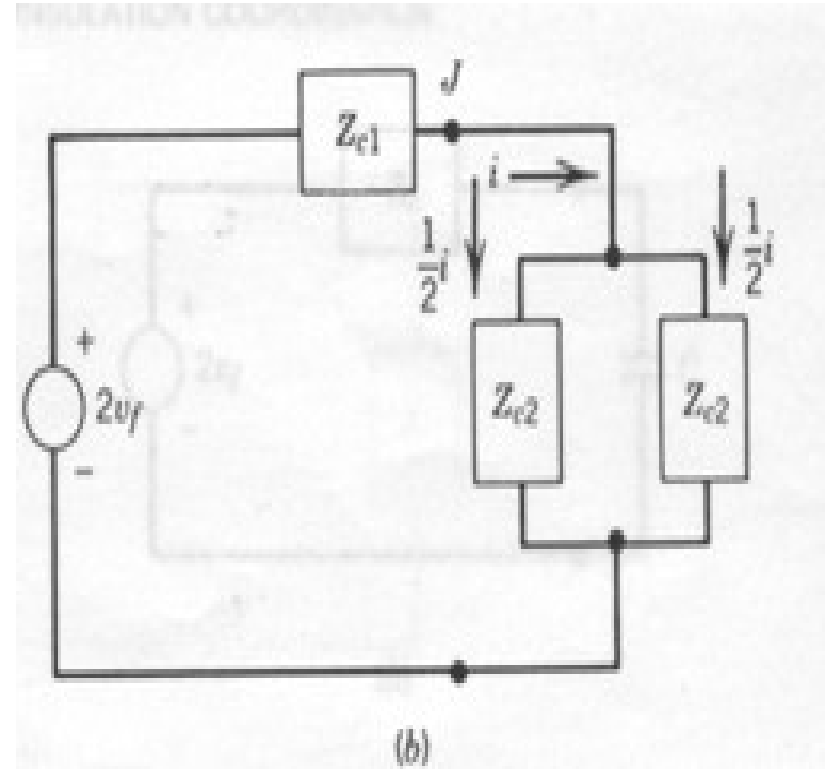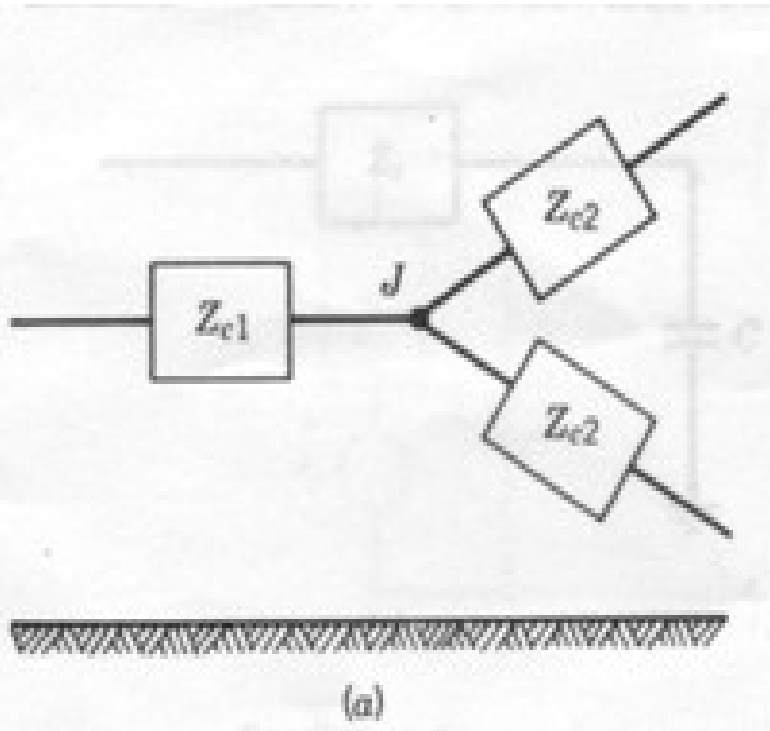

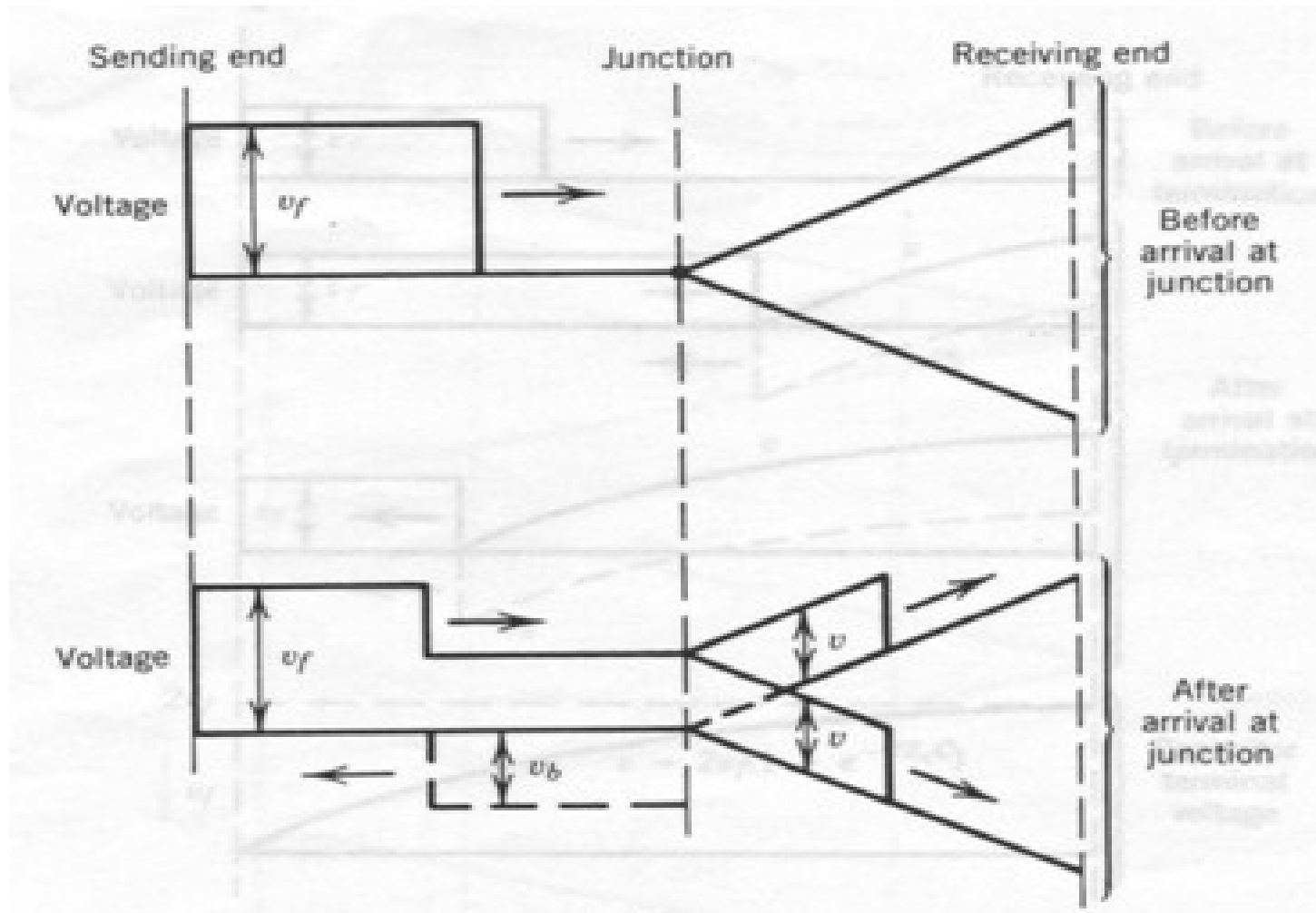Travelling voltage wave encountering line bifurcation (a) system,
 (b) Equivalent circuit



Travelling voltage wave reflected and transmitted at junction of three lines

Effect of cable on Surge

- The reflected wave at a junction

$$e_r = \frac{2Z_2}{Z_1 + Z_2} e_f$$

- Characteristics Impedance of a line $Z_1 = 200-500$ ohm
- Characteristics Impedance of a cable $Z_2 = 30-50$ ohm

Contd...

- If line is terminated with cable


$$e_t = 60/330 * e_f$$

- If line is terminated with line

$$e_t = 600/330 * e_f$$

- The transmitted wave is much lesser than in case of line terminated with cable.


Bewley Lattice Diagram

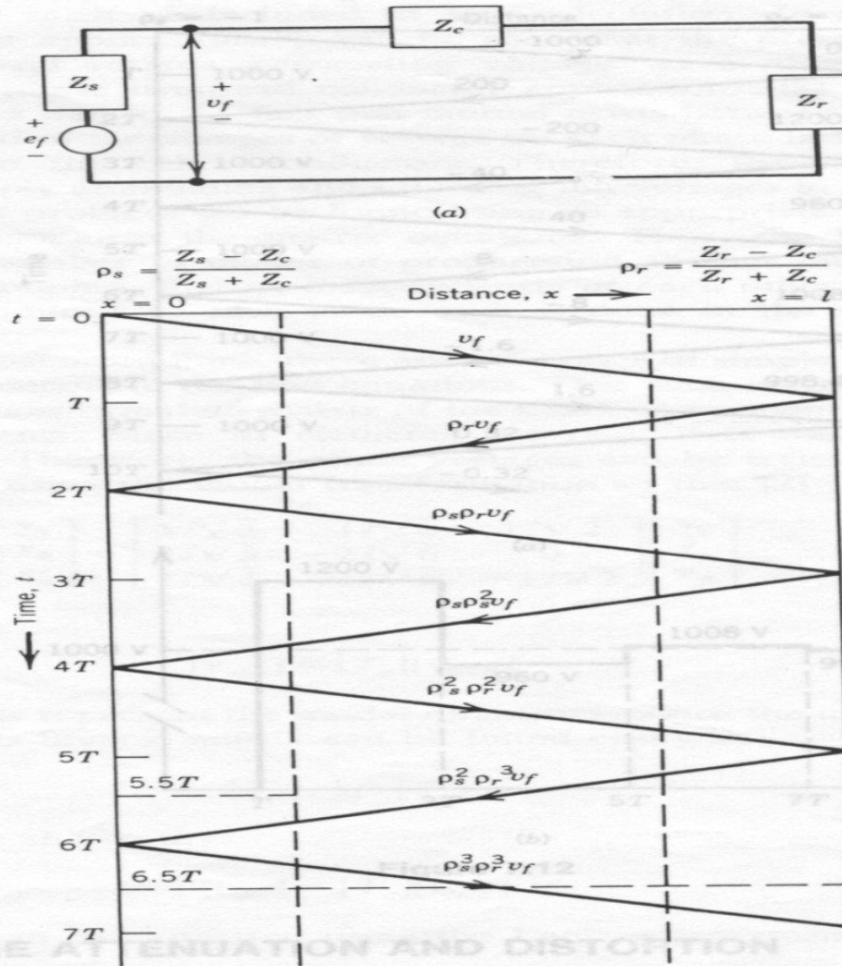


7.8 SURGE ATTENUATION AND DISTORTION

In general, in addition to the effects of reflections at transition points, traveling waves are also subject to both attenuation (decrease in magnitude) and distortion (change in shape) as they propagate along the line. They are

Figure 7.11. Bewley lattice diagram: (a) circuit diagram; (b) lattice diagram.

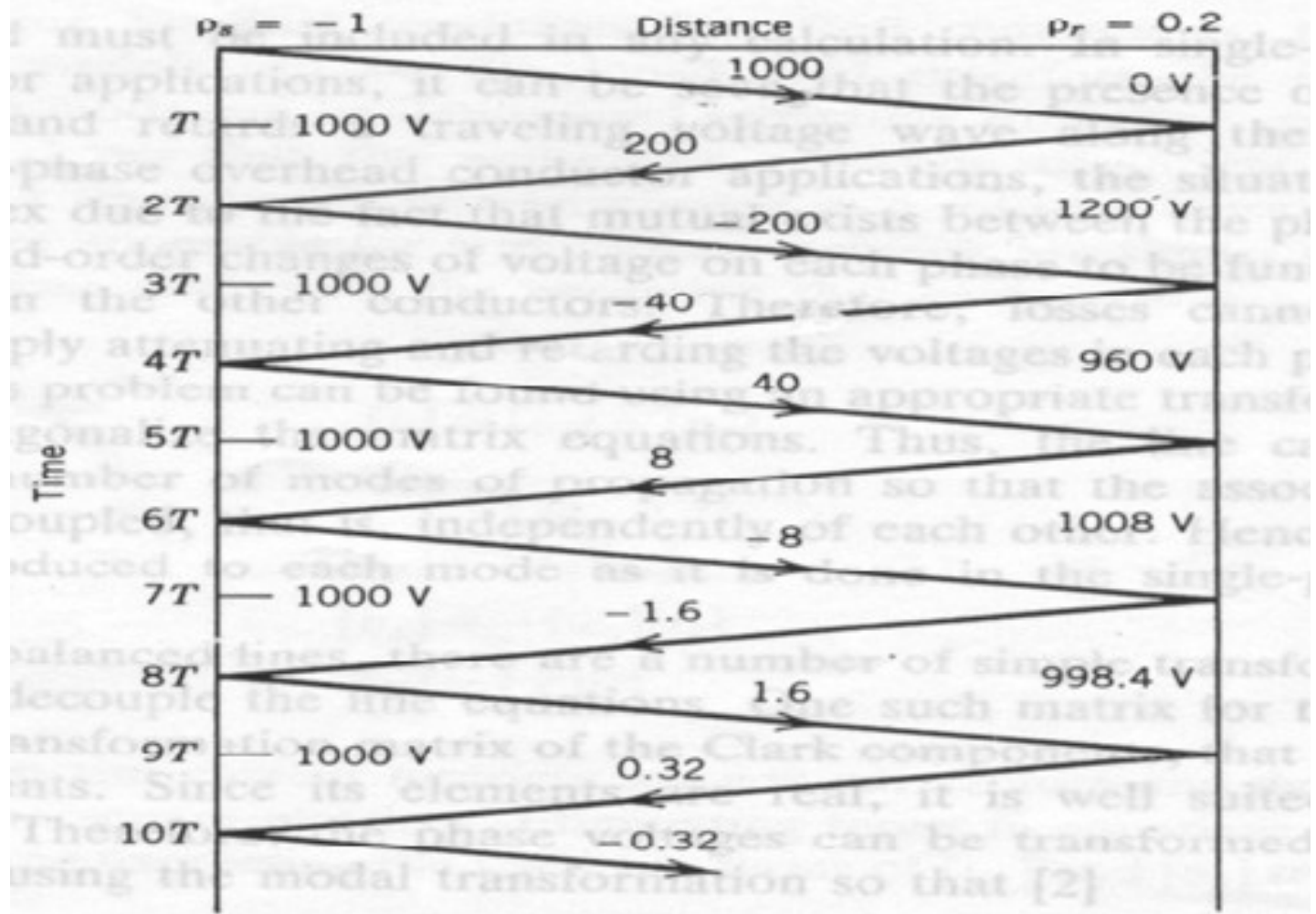

(a)

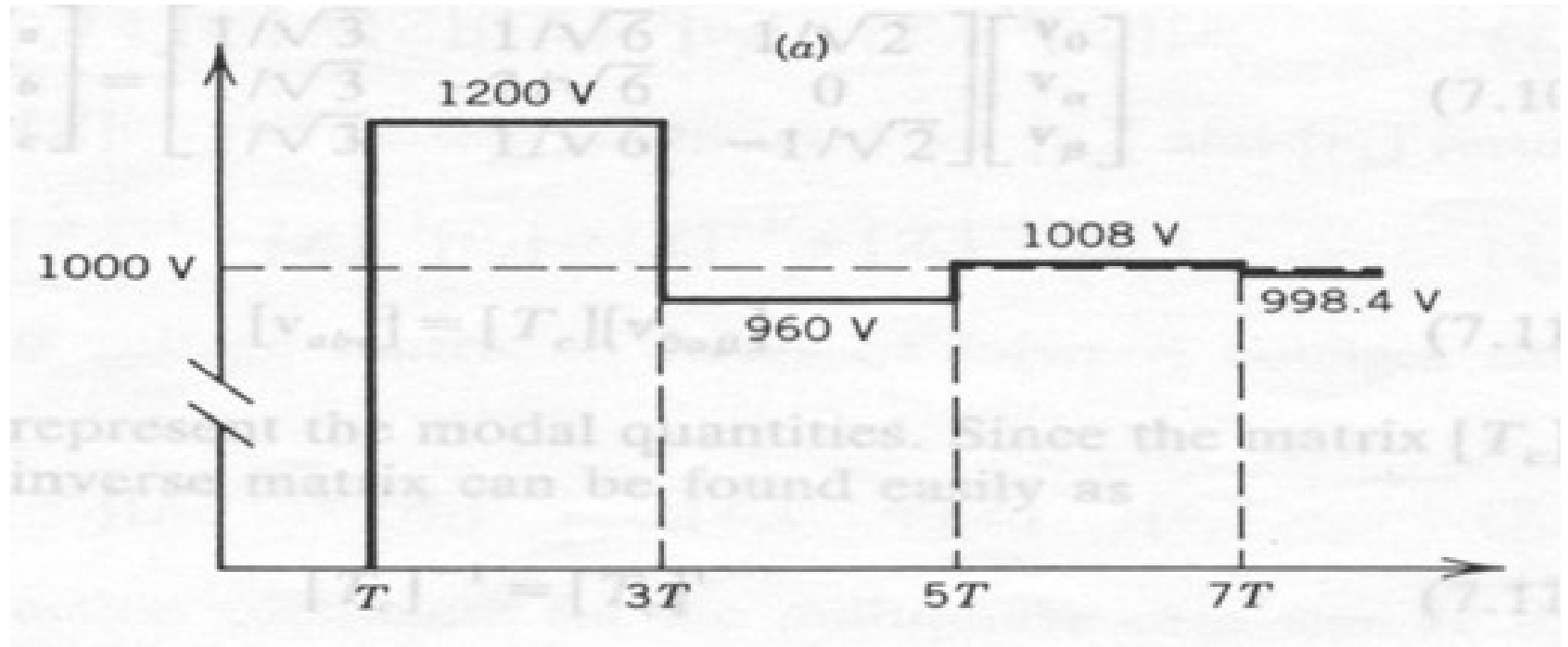



Thanks