

DC Motor

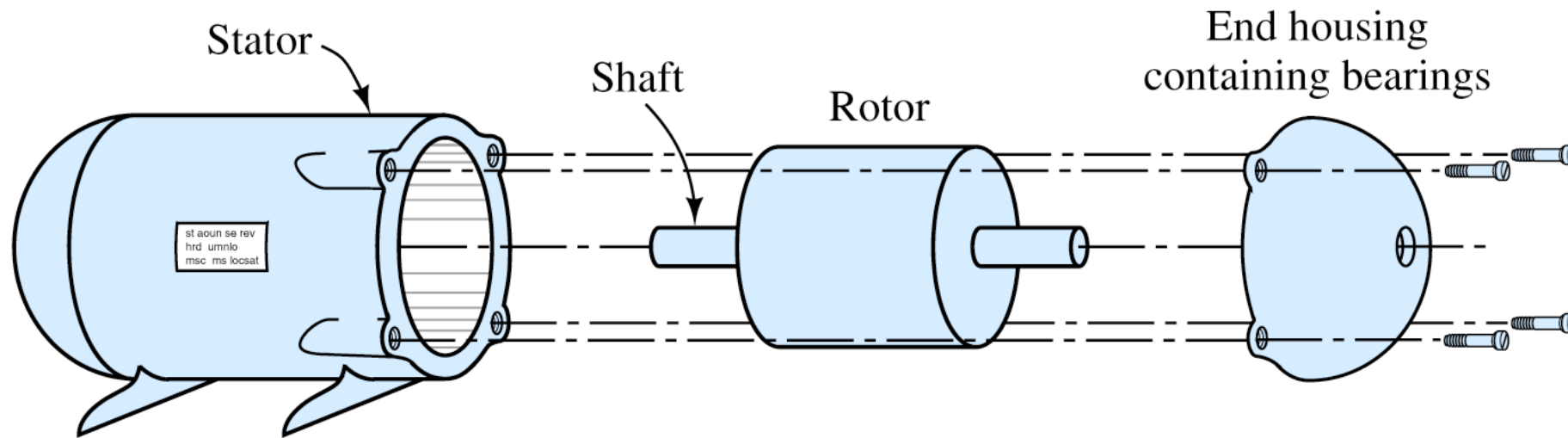


Figure 16.1 An electrical motor consists of a cylindrical rotor that spins inside a stator.

A Two Pole DC Motor

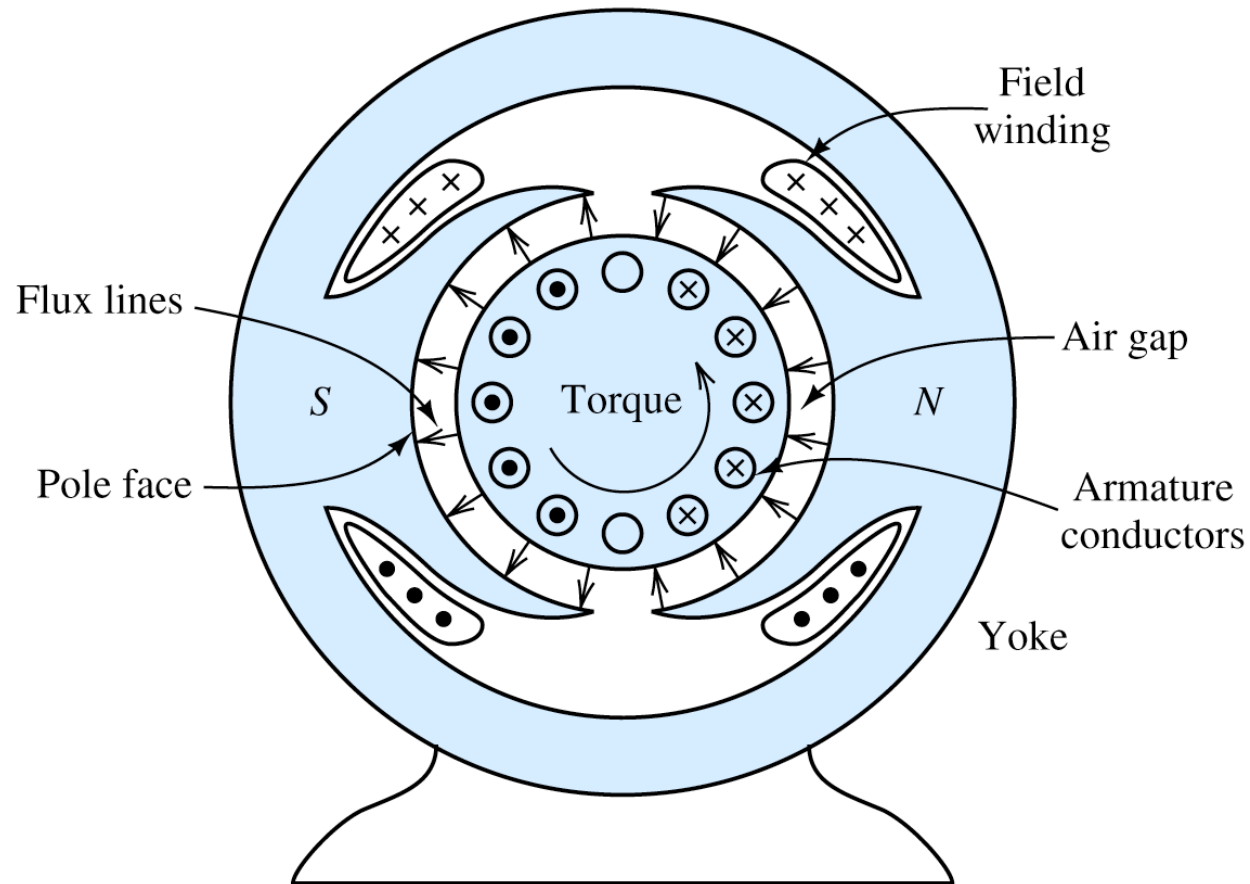


Figure 16.10 Cross section of a two-pole dc machine.

A Four Pole DC Motor

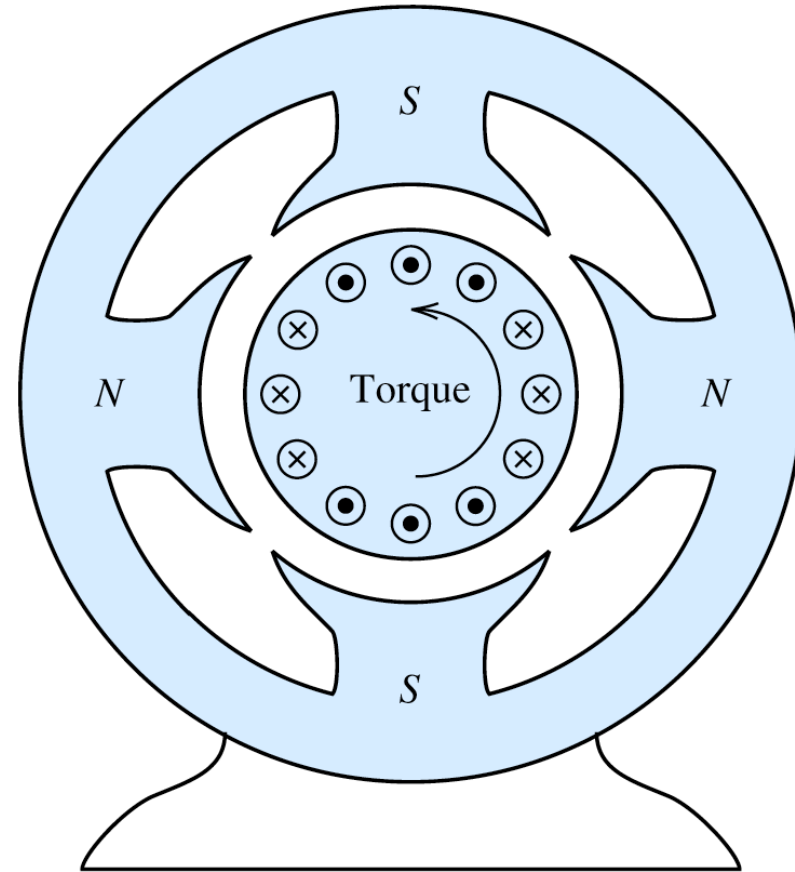


Figure 16.11 Cross section of a four-pole dc machine.

Operating Principle of a DC Machine



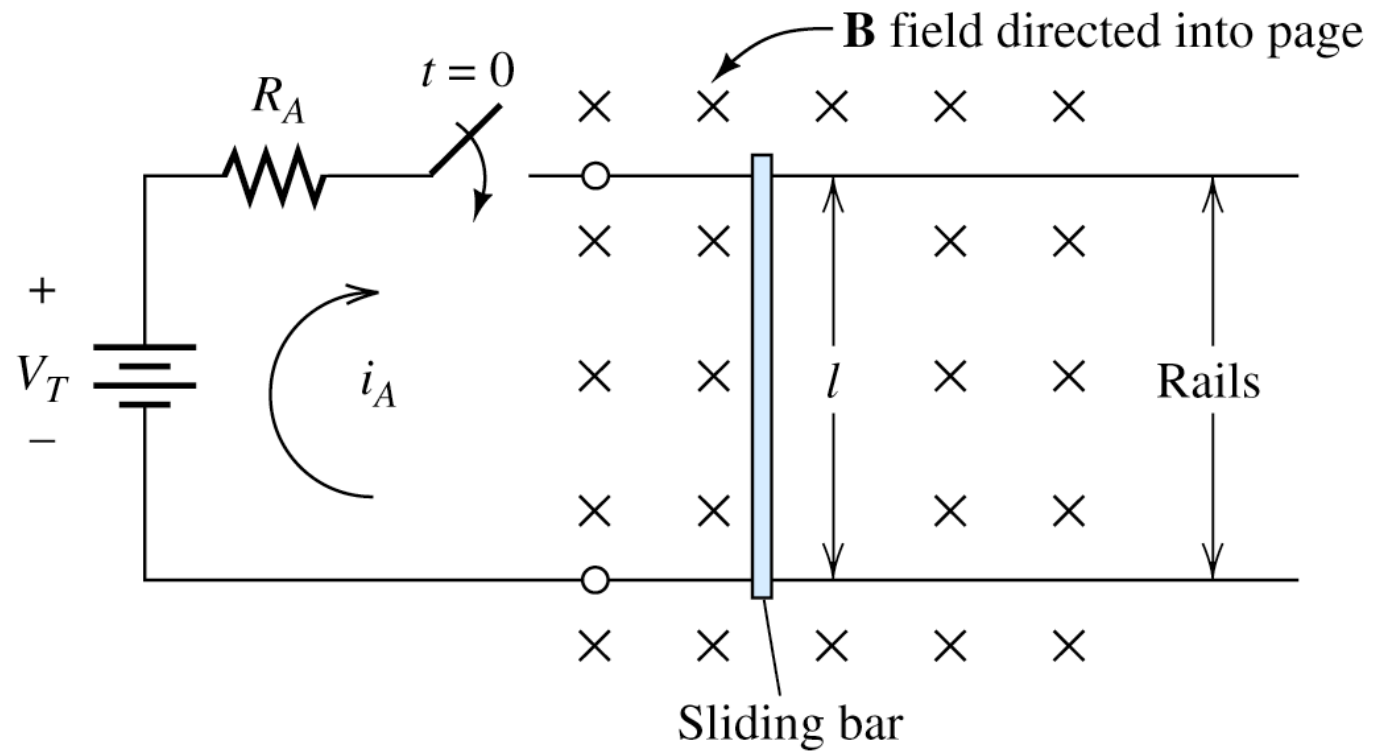


Figure 16.6 A simple dc machine consisting of a conducting bar sliding on conducting rails.

Fleming's Left Hand Rule Or Motor Rule

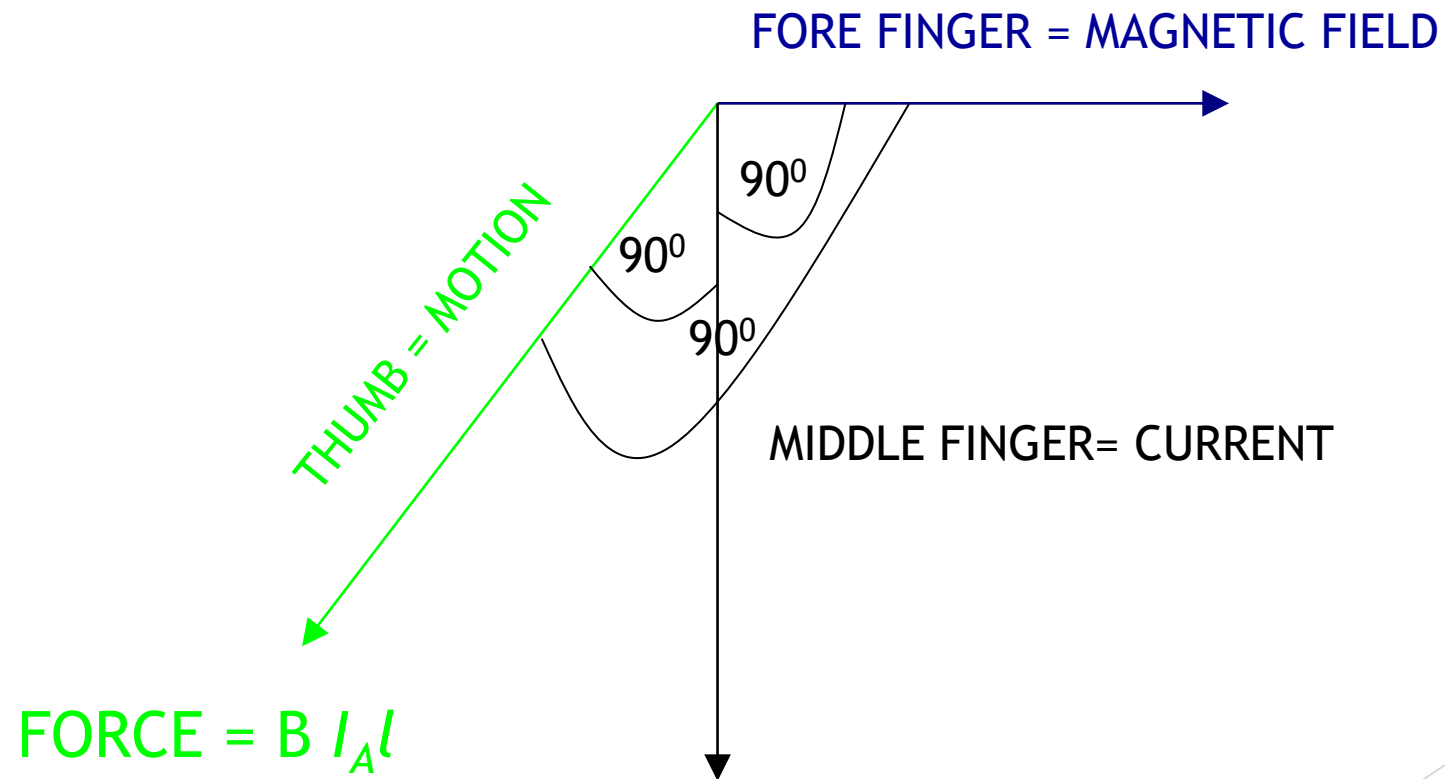

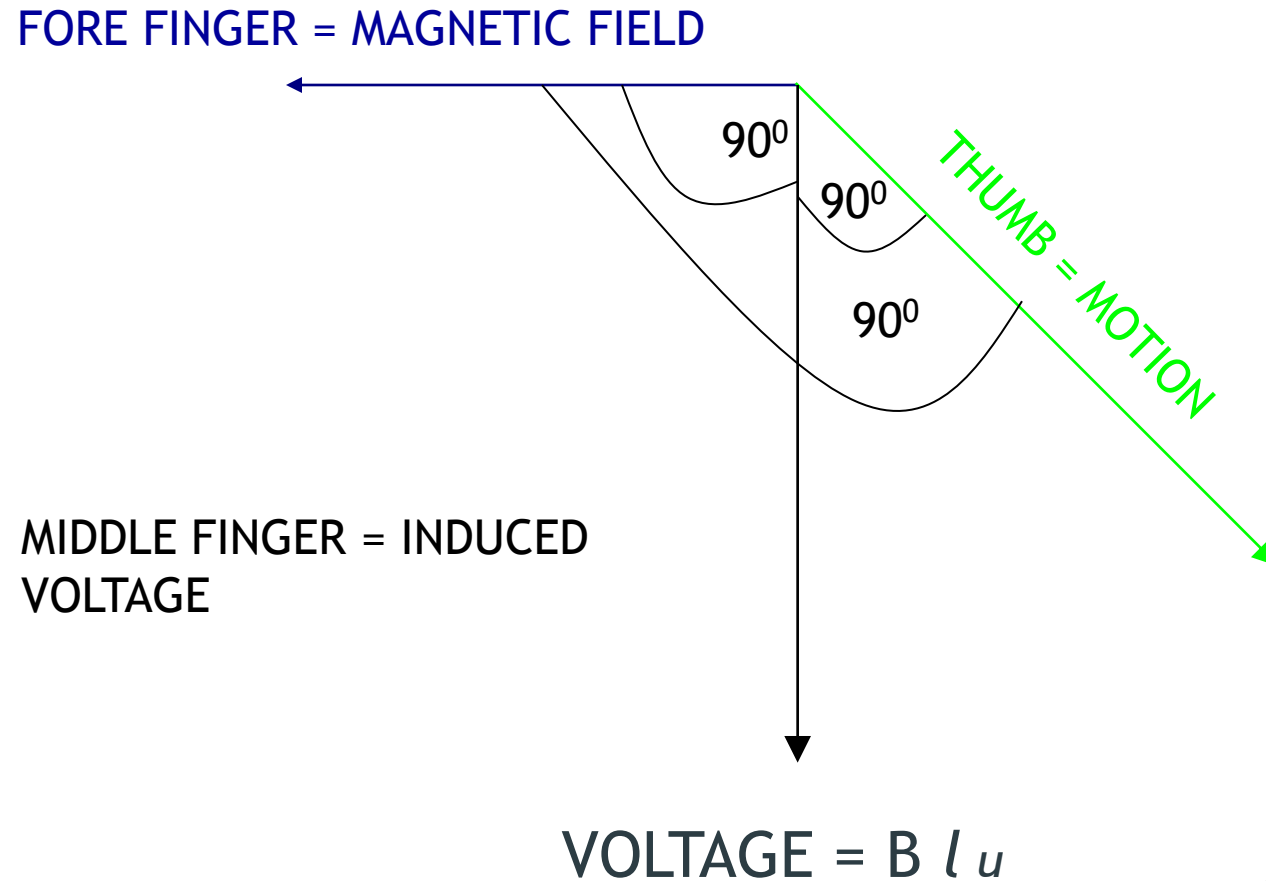Fleming's Right Hand Rule Or Generator Rule



Action of a Commutator

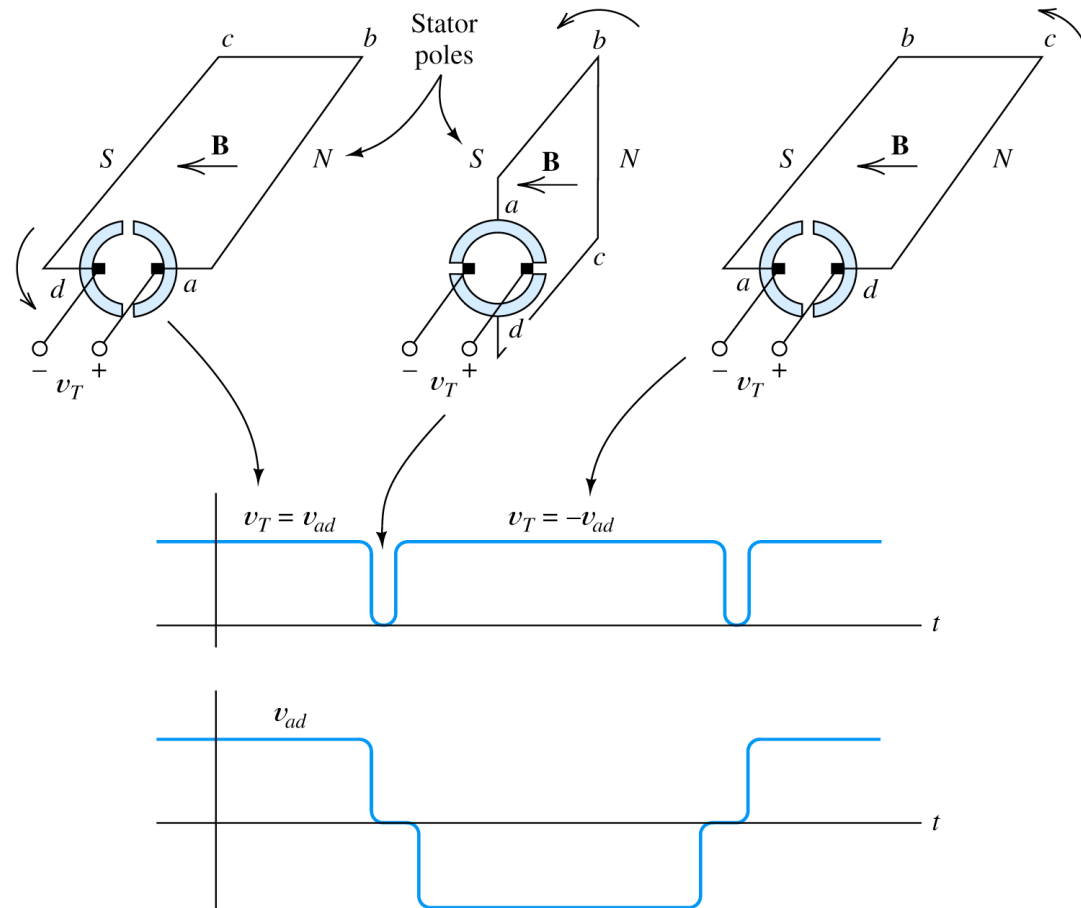


Figure 16.12 Commutation for a single armature winding.

Armature of a DC Motor

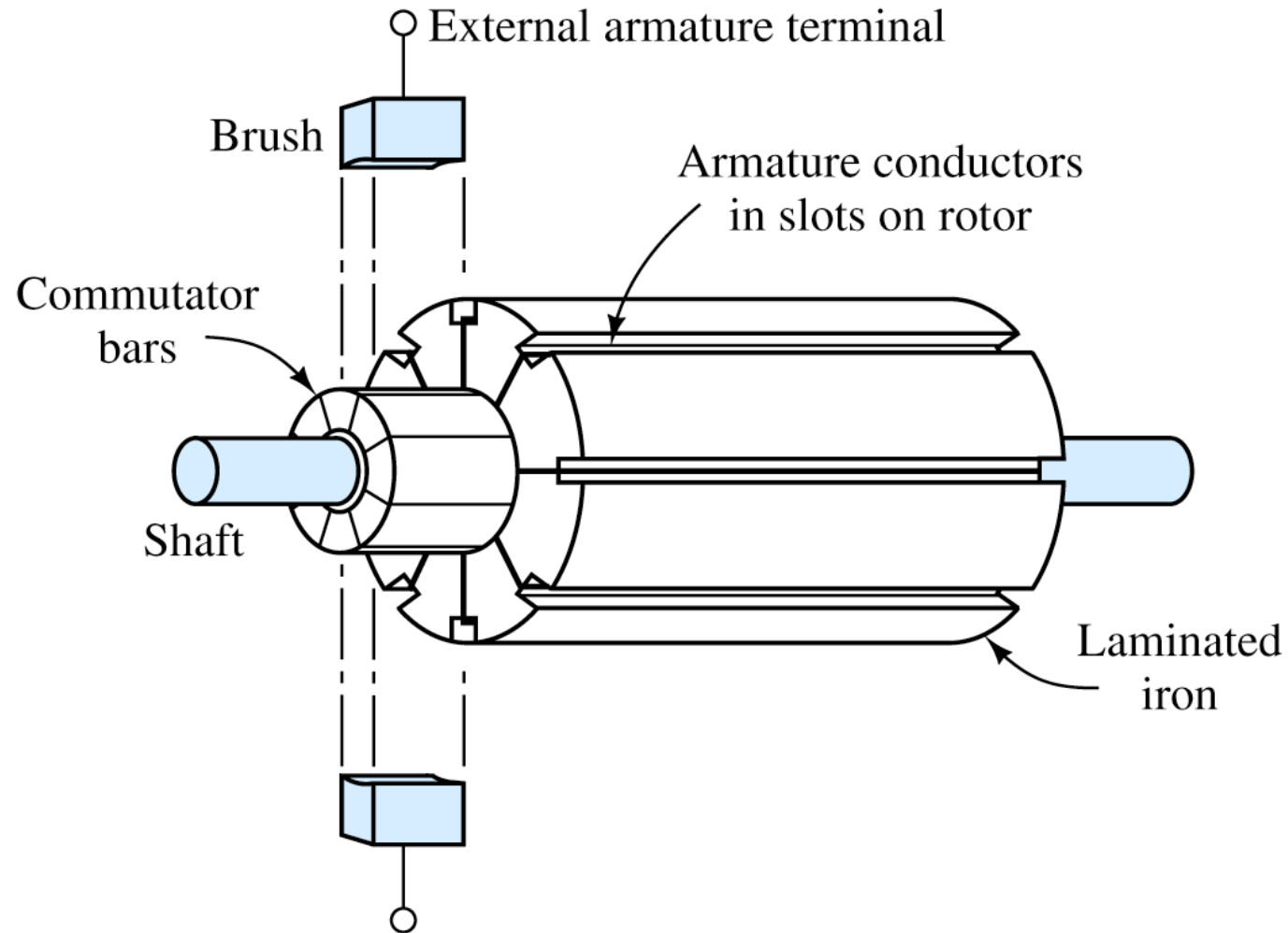


Figure 16.9 Rotor assembly of a dc machine.

Generated Voltage in a DC Machine


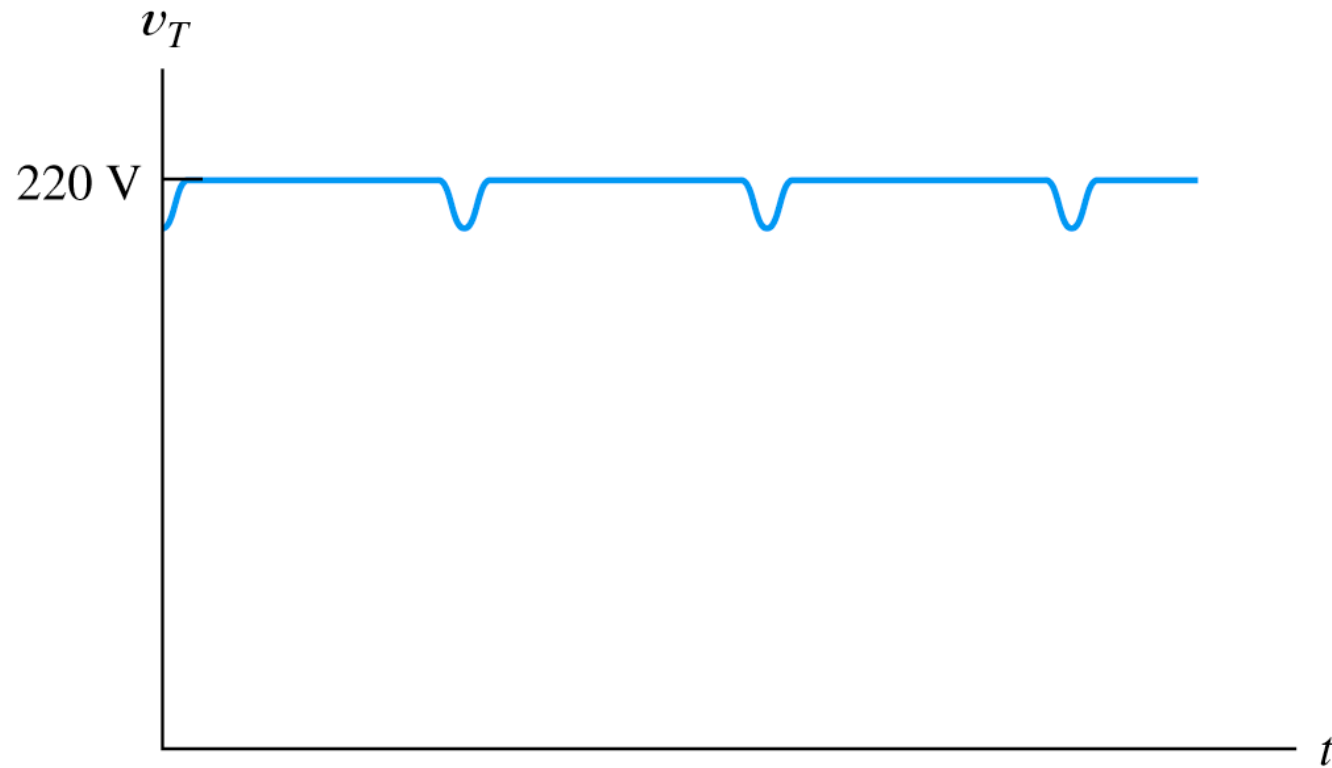


Figure 16.13 Voltage produced by a practical dc machine. Because only a few (out of many) conductors are commutated (switched) at a time, the voltage fluctuations are less pronounced than in the single-loop case illustrated in Figure 16.12.

Armature Winding in a DC Machine

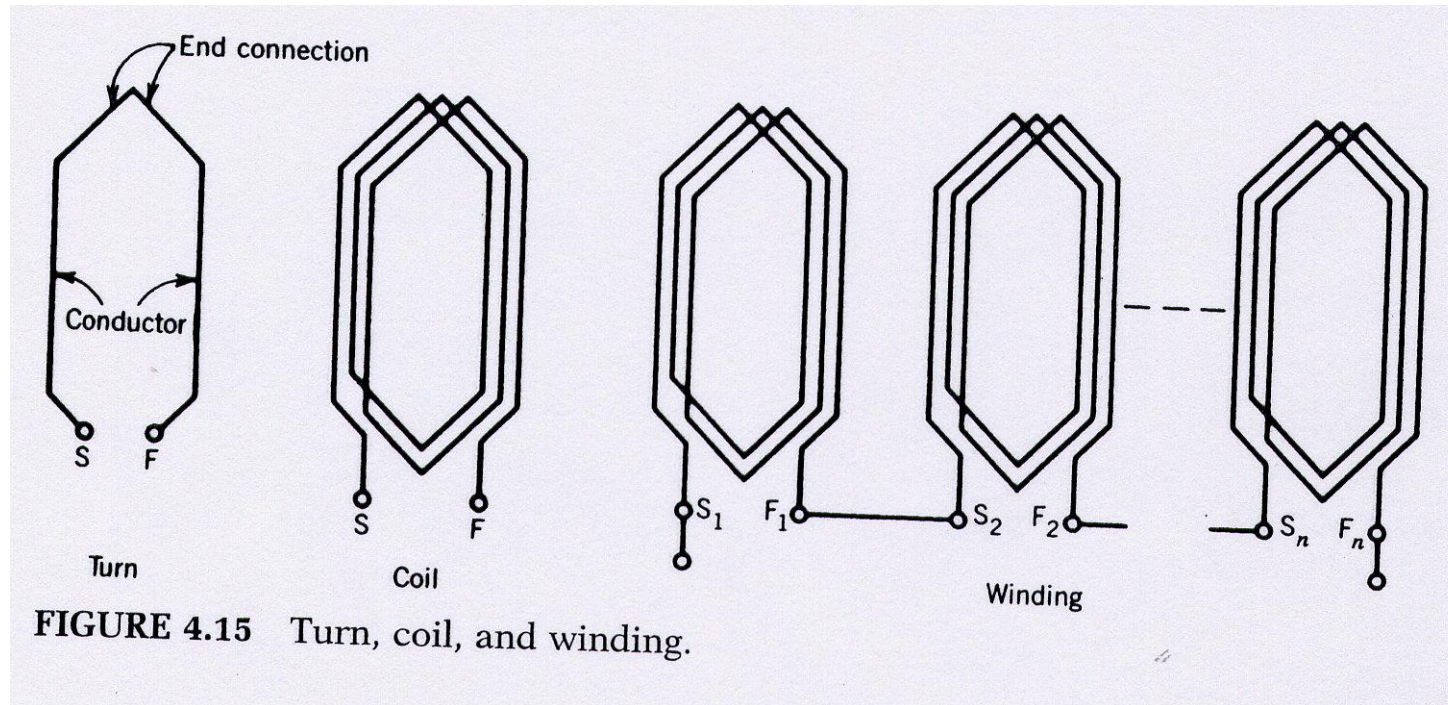

Lap Winding of a DC Machine

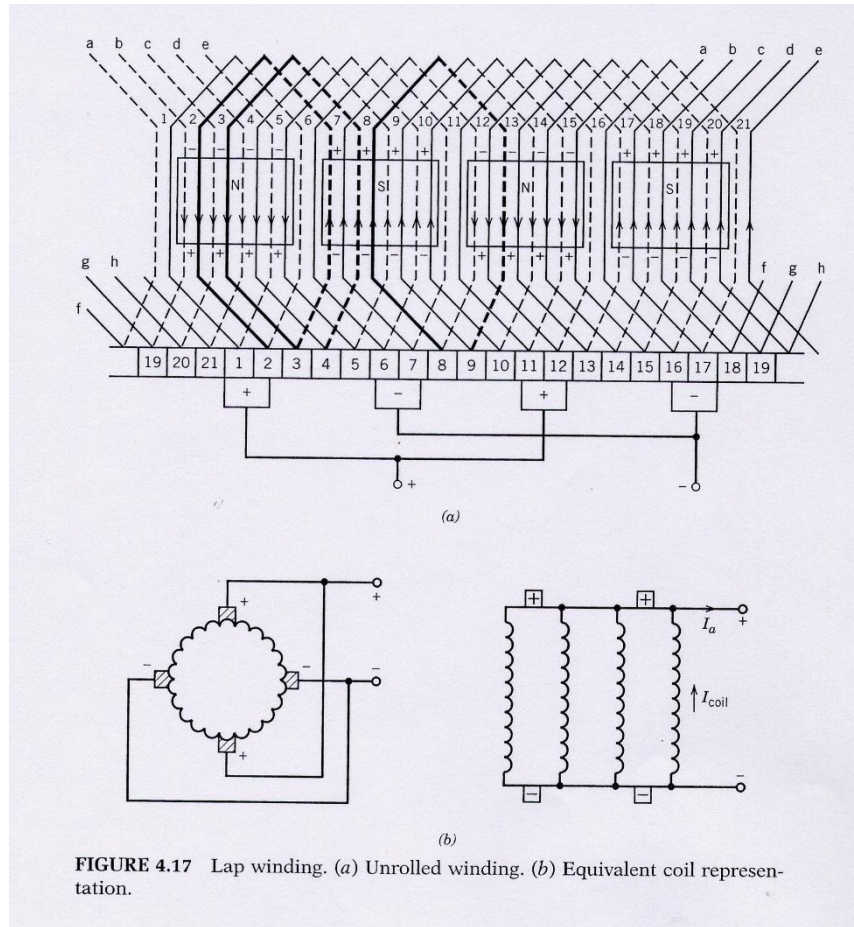


FIGURE 4.17 Lap winding. (a) Unrolled winding. (b) Equivalent coil representation.

- Used in high current low voltage circuits

- Number of parallel paths equals number of brushes or poles

Wave Winding of a DC Machine

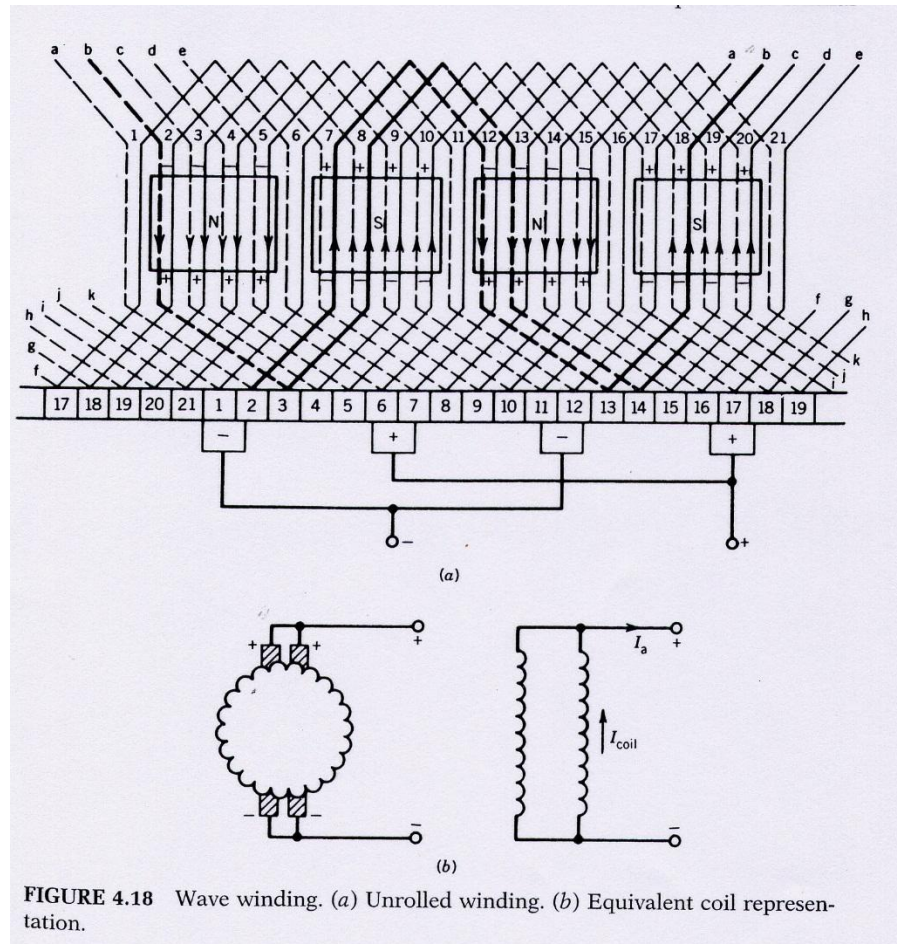


FIGURE 4.18 Wave winding. (a) Unrolled winding. (b) Equivalent coil representation.

- Used in high voltage low current circuits
- Number of parallel paths always equals 2


Magnetic circuit of a 4 pole DC Machine

θ_{md} = mechanical degrees or angular measure in space


θ_{ed} = electrical degrees or angular measure in cycles

then, for a p -pole machine,
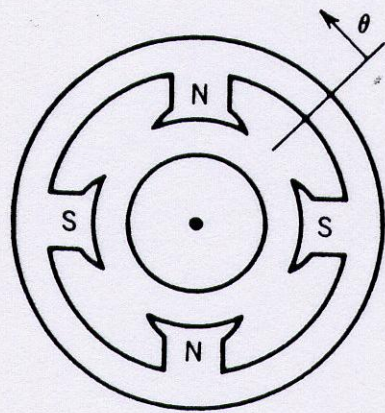
$$\theta_{ed} = \frac{p}{2} \theta_{md} \quad (4.3)$$




(a)

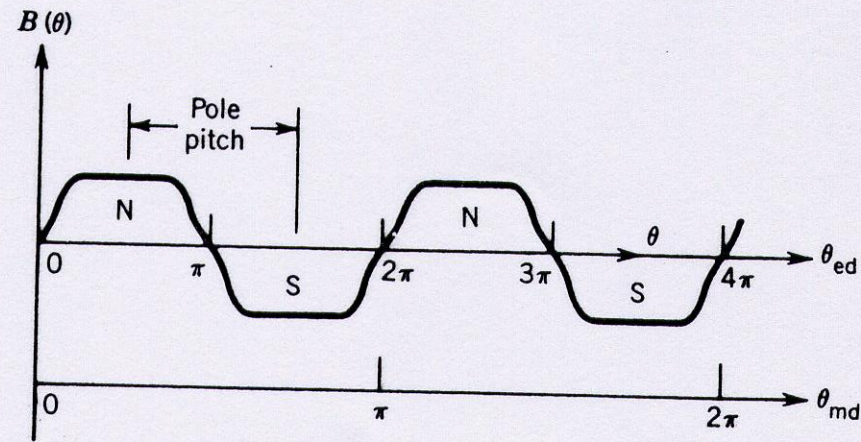

(b)

FIGURE 4.16 Mechanical and electrical degrees. (a) Four-pole dc machine. (b) Flux density distribution.


Magnetic circuit of a 2 pole DC Machine

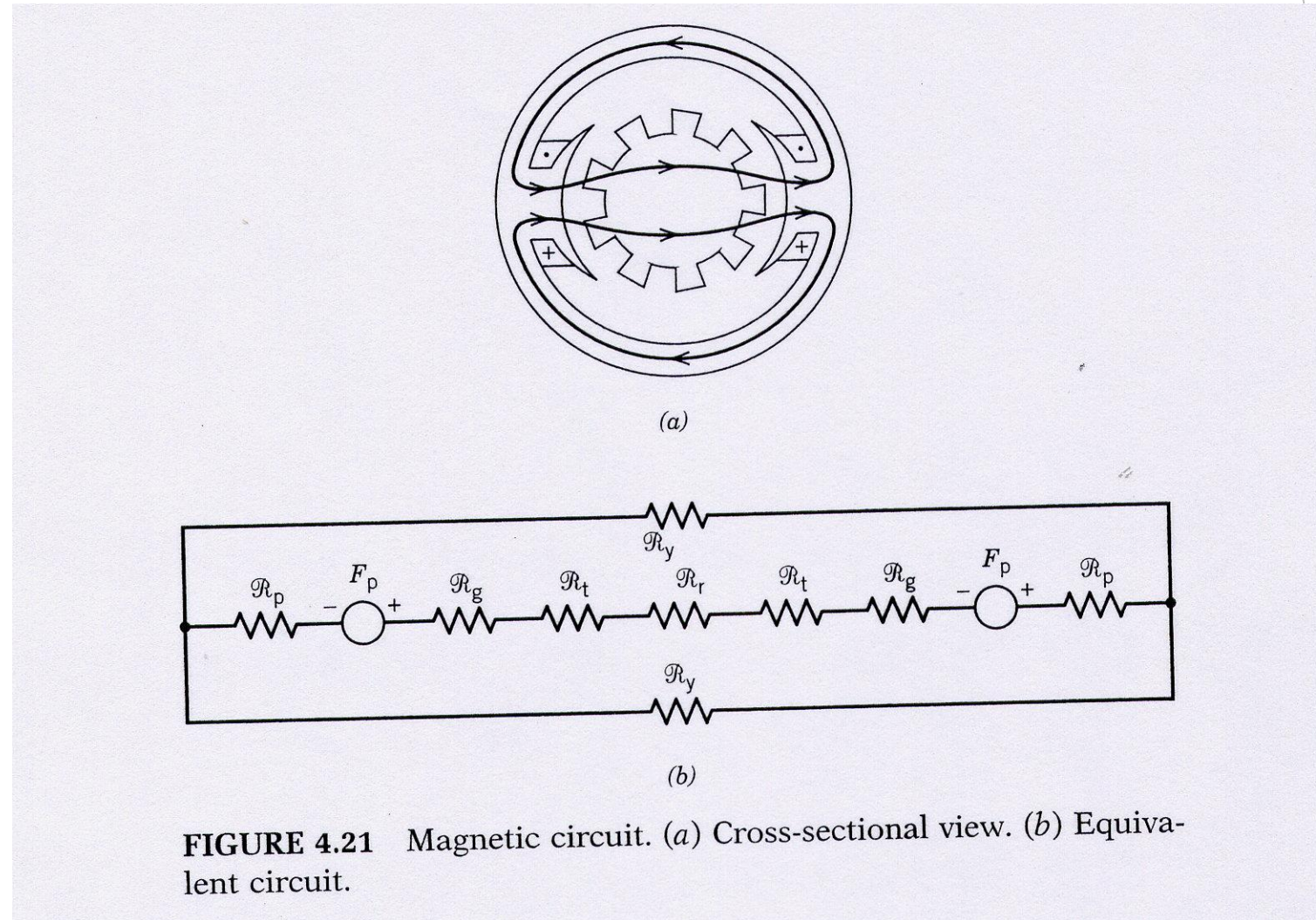

Summary of a DC Machine

- Basically consists of
 1. An electromagnetic or permanent magnetic structure called field which is static
 2. An Armature which rotates
- The Field produces a magnetic medium
- The Armature produces voltage and torque under the action of the magnetic field

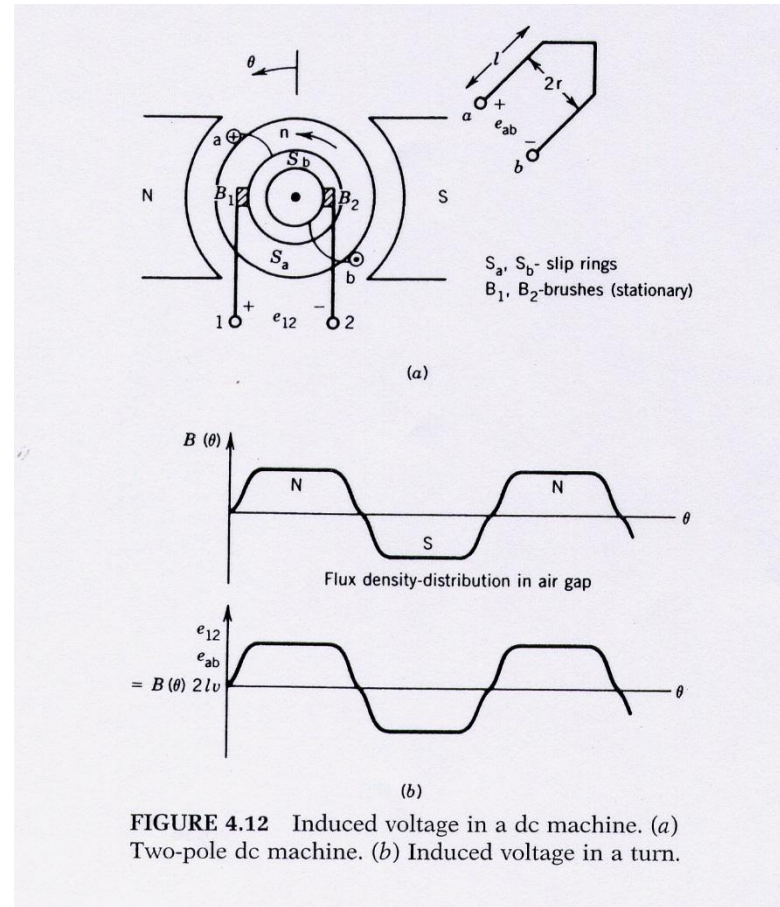Deriving the induced voltage in a DC Machine



Deriving the electromagnetic torque in a DC Machine

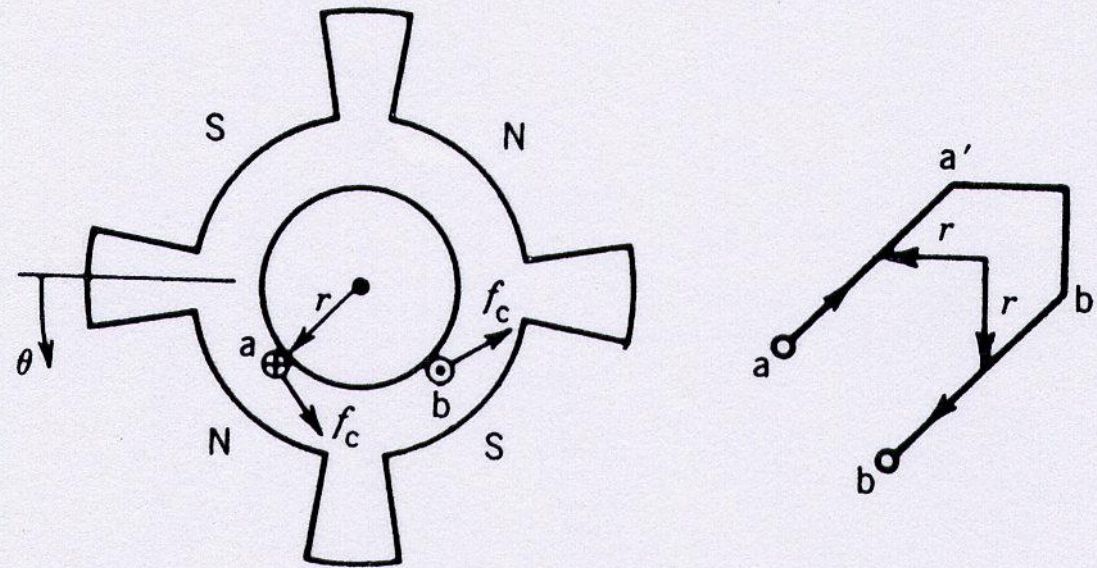


FIGURE 4.19 Torque production in dc machine.

Voltage and Torque developed in a DC Machine


- Induced EMF, $E_a = K_a \Phi \omega_m$ (volts)
- Developed Torque, $T_{dev} = K_a \Phi I_a$ (Newton-meter or Nm)

where ω_m is the speed of the armature in rad/sec., Φ is the flux per pole in weber (Wb)

I_a is the Armature current

K_a is the machine constant

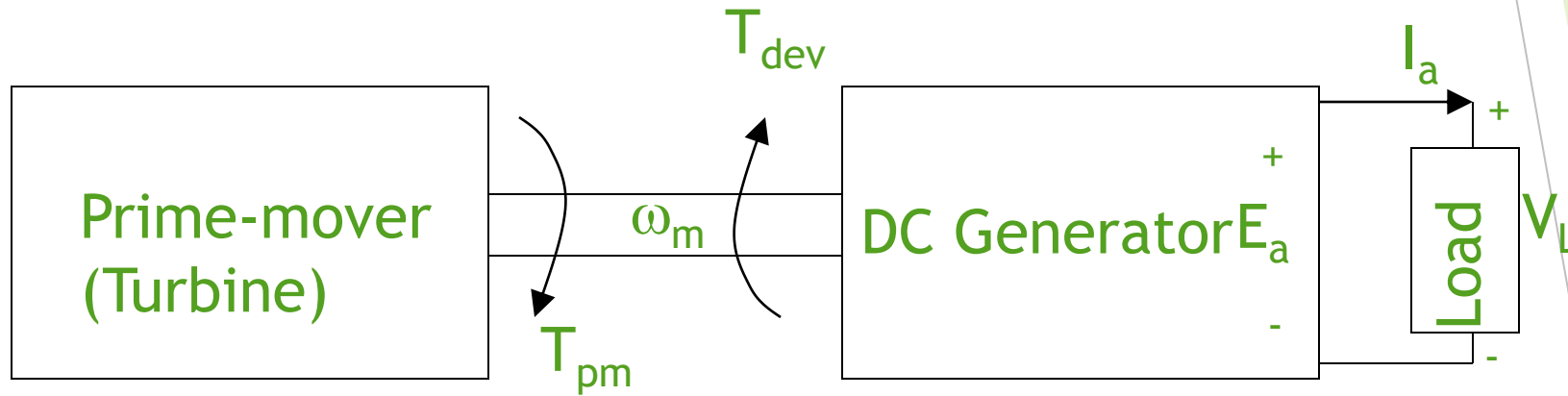Interaction of Prime-mover DC Generator and Load




E_a is Generated voltage

V_L is Load voltage

T_{pm} is the Torque generated by Prime Mover

T_{dev} is the opposing generator torque

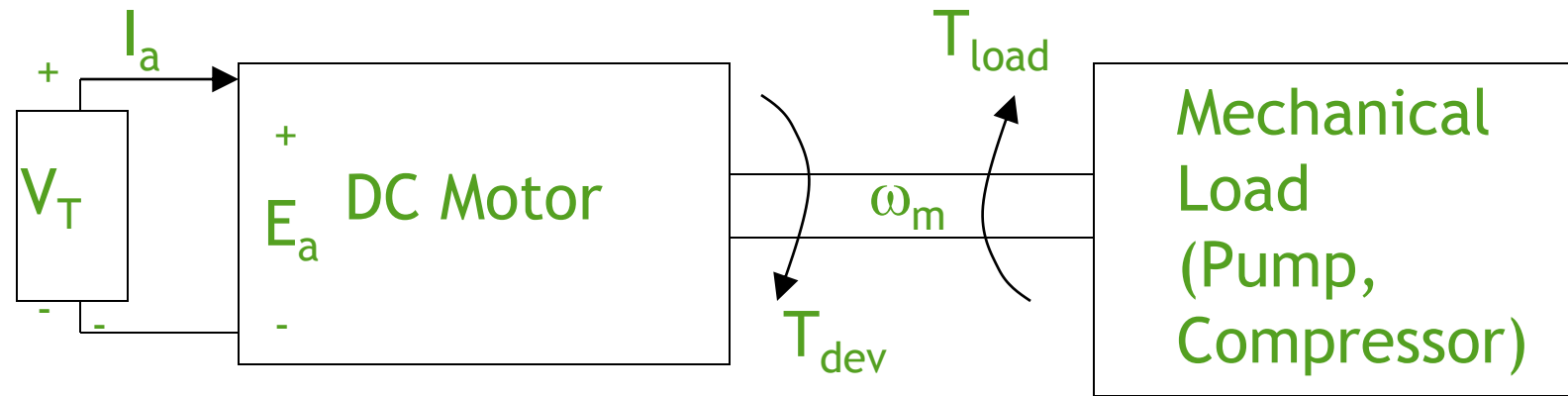Interaction of the DC Motor and Mechanical Load



E_a is Back EMF

V_T is Applied voltage

T_{dev} is the Torque developed by DC Motor

T_{load} is the opposing load torque

Power Developed in a DC Machine

Neglecting Losses,

• *Input mechanical power* to dc generator

$$\begin{aligned} &= T_{\text{dev}} \omega_m = K_a \Phi I_a \omega_m = E_a I_a \\ &= \textit{Output electric power} \text{ to load} \end{aligned}$$

• *Input electrical power* to dc motor

$$\begin{aligned} &= E_a I_a = K_a \Phi \omega_m I_a = T_{\text{dev}} \omega_m \\ &= \textit{Output mechanical power} \text{ to load} \end{aligned}$$


Equivalence of motor and generator

- In every generator there is a motor (T_{dev} opposes T_{pm})
- In every motor there is a generator (E_a opposes V_T)

Example of winding specific motor and generator

Worked out on greenboard

Magnetization Curve

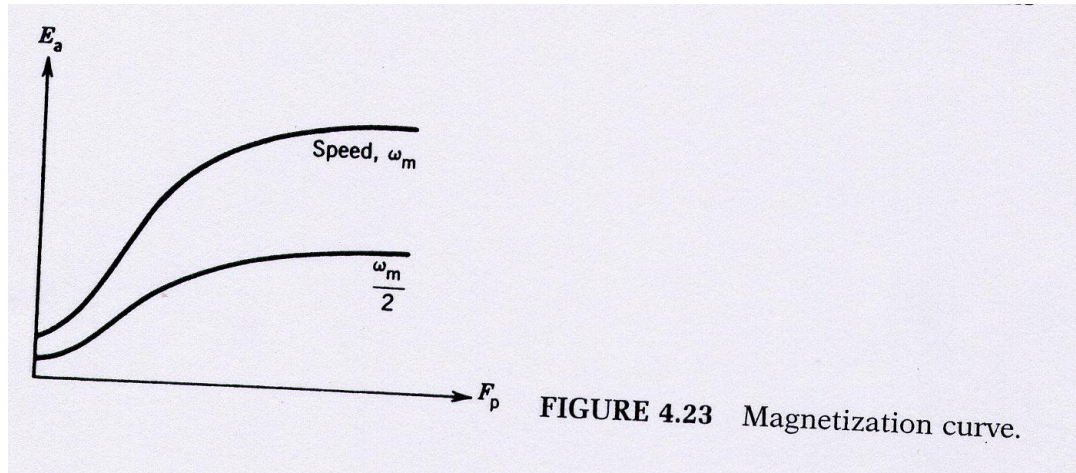


$$E_a = K_a \Phi \omega_m$$


- Flux is a non-linear function of field current and

hence E_a is a non-linear function of field current

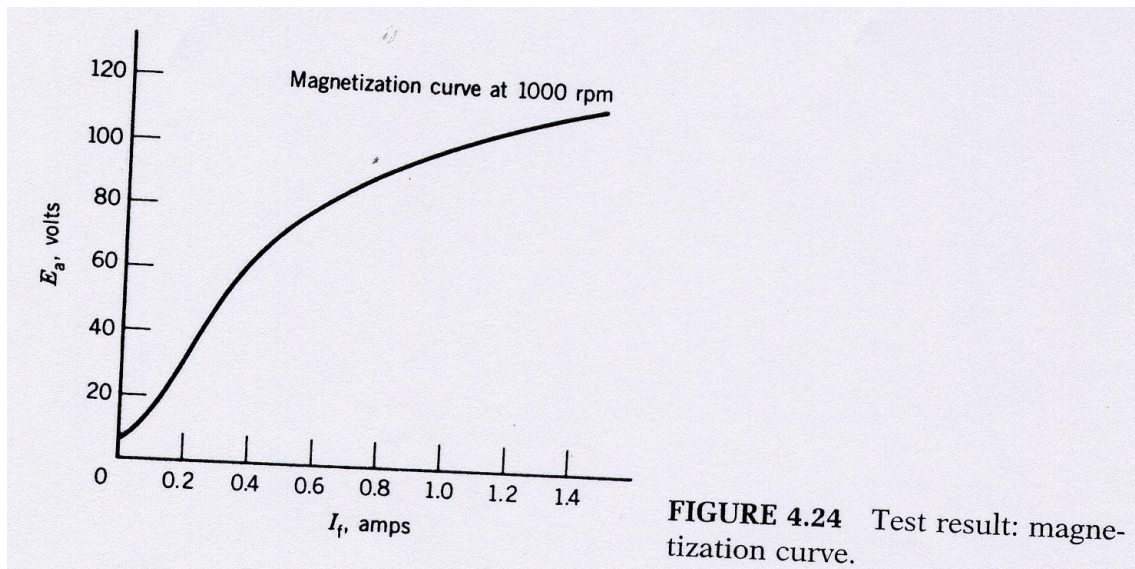
- For a given value of flux E_a is directly proportional to ω_m




Separately Excited DC Machine

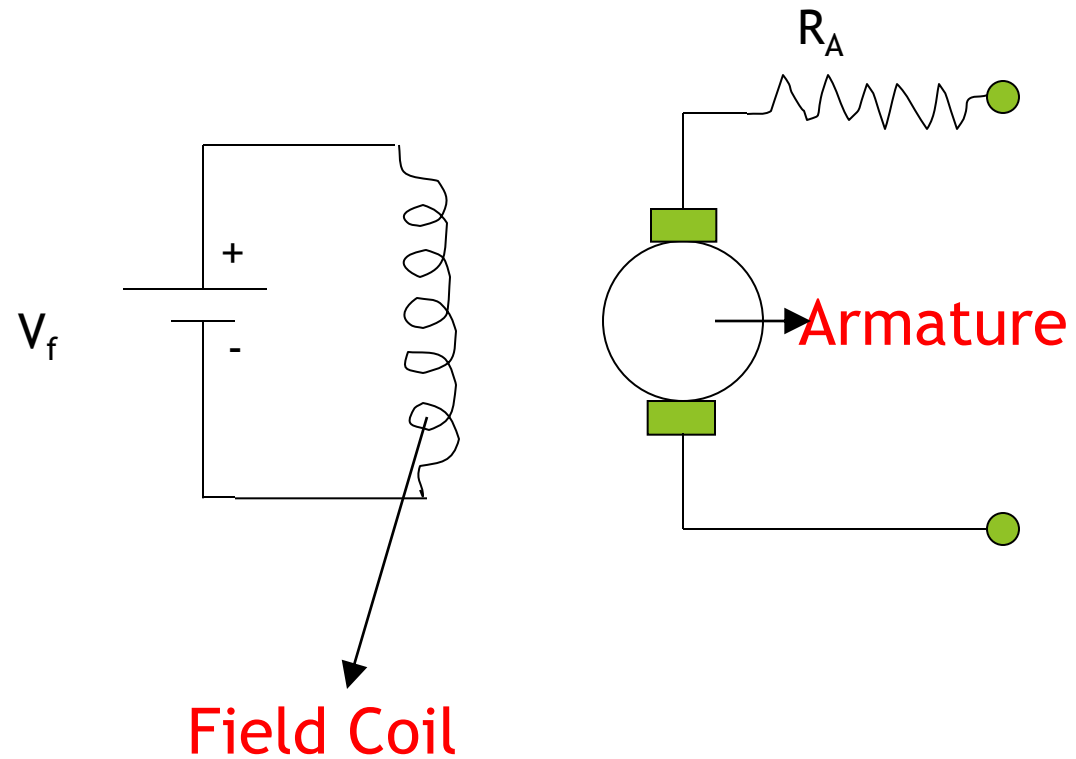


Shunt Excited DC Machine

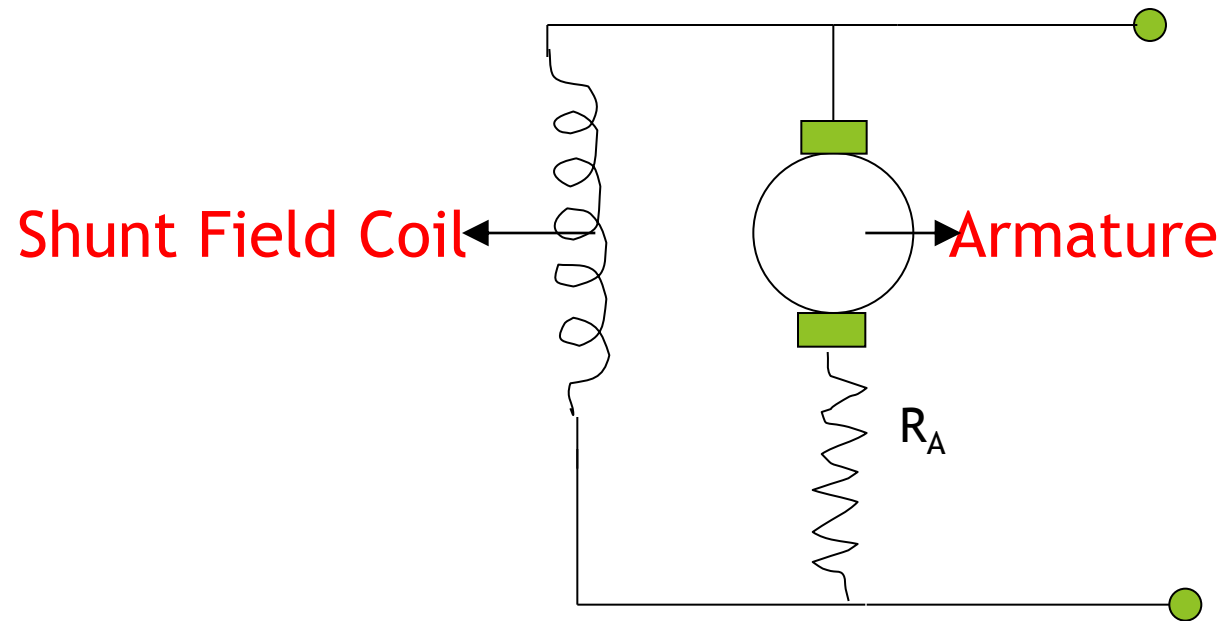

Series Excited DC Machine

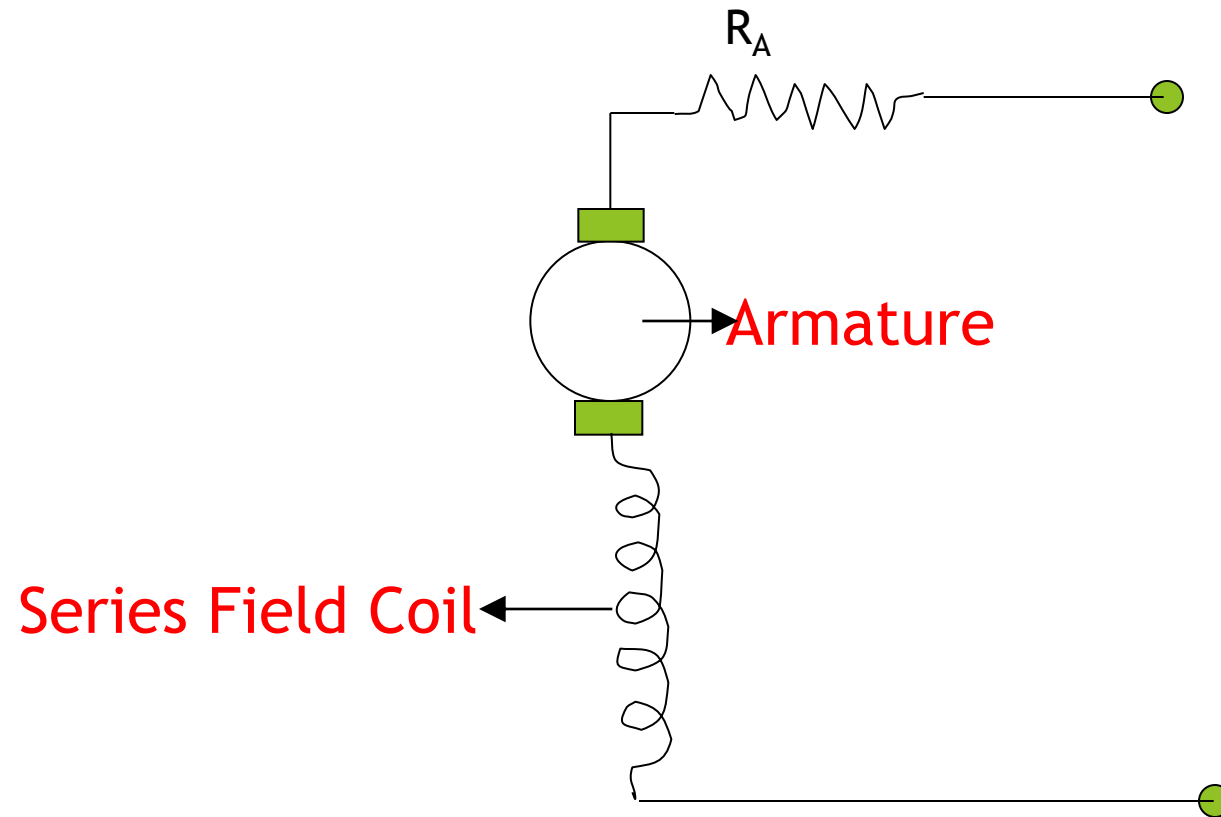


Compound Excited DC Machine

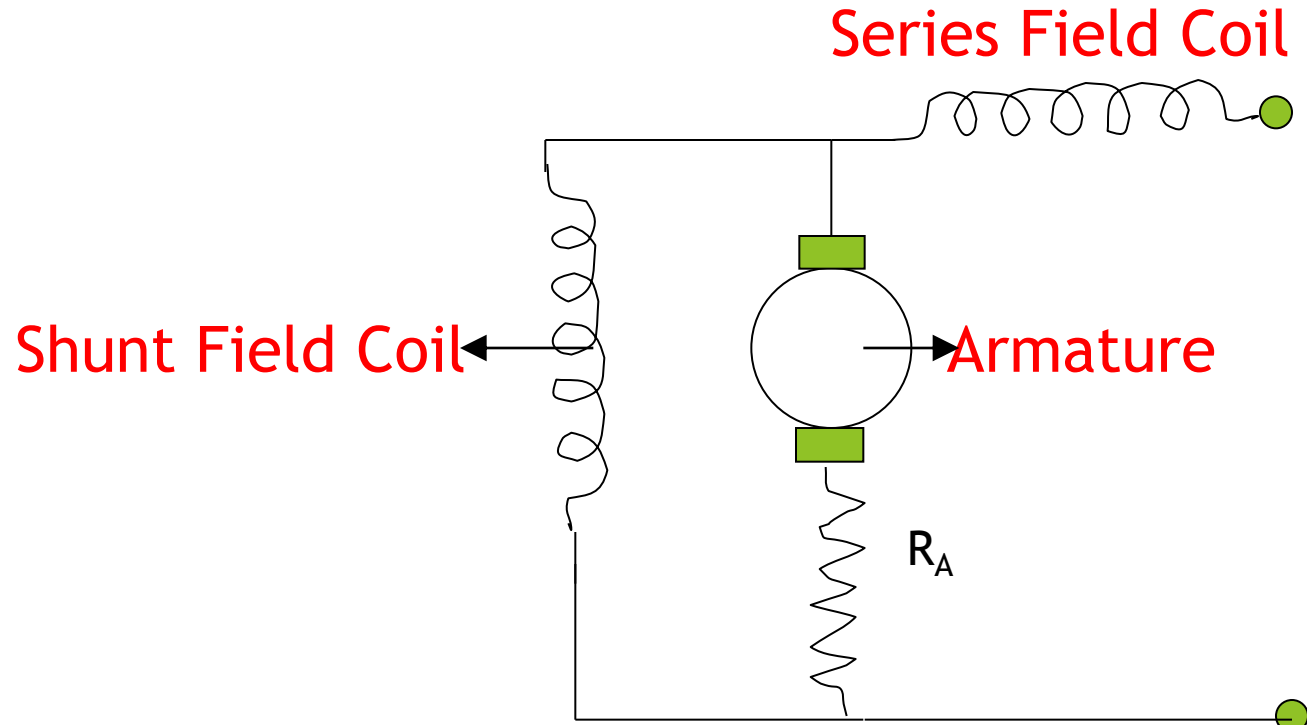


- If the shunt and series field aid each other it is called a cumulatively excited machine
- If the shunt and series field oppose each other it is called a differentially excited machine


Armature Reaction(AR)

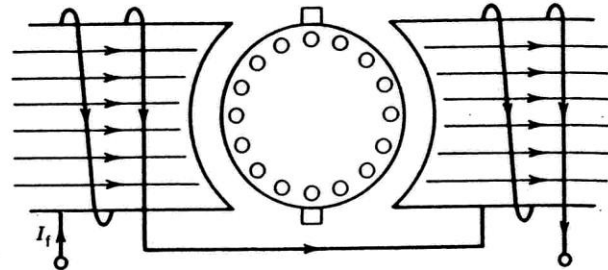

(a)

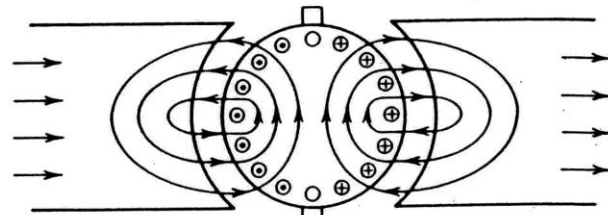

(b)

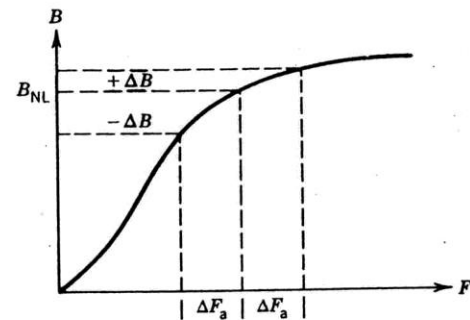

(c)

FIGURE 4.30 Armature reaction effects.

- AR is the magnetic field produced by the armature current

- AR aids the main flux in one half of the pole and opposes the main flux in the other half of the pole

- However due to saturation of the pole faces the net effect of AR is demagnetizing

Effects of Armature Reaction


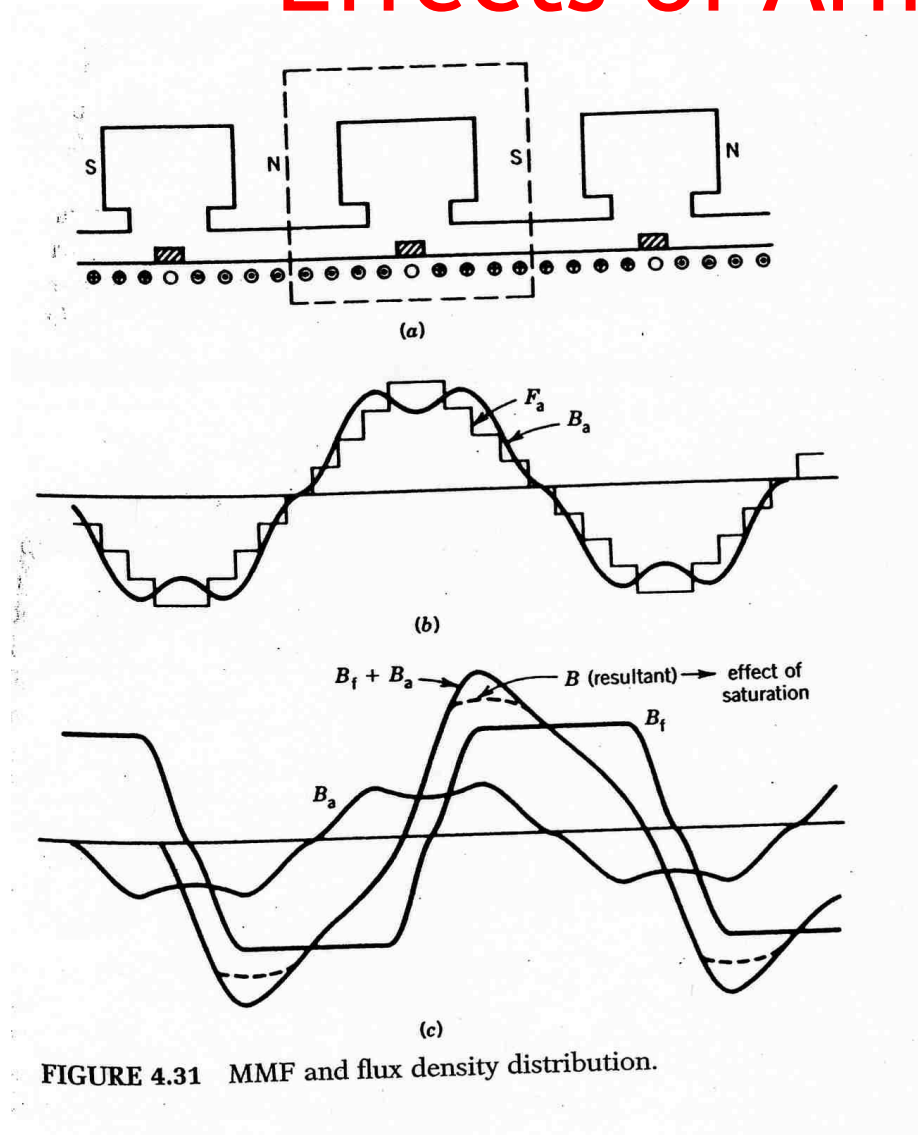


FIGURE 4.31 MMF and flux density distribution.

- The magnetic axis of the AR is 90° electrical (cross) out-of-phase with the main flux. This causes commutation problems as zero of the flux axis is changed from the interpolar position.

Minimizing Armature Reaction

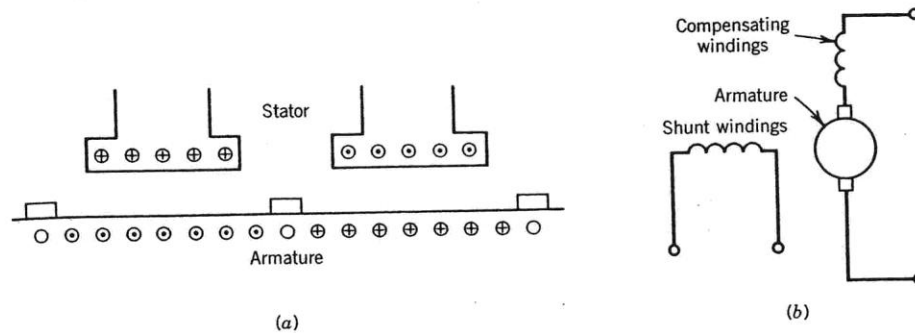

- Since AR reduces main flux, voltage in generators and torque in motors reduces with it. This is particularly objectionable in steel rolling mills that require sudden torque increase.

- **Compensating windings** put on pole faces can effectively negate the effect of AR. These windings are connected in series with armature winding.

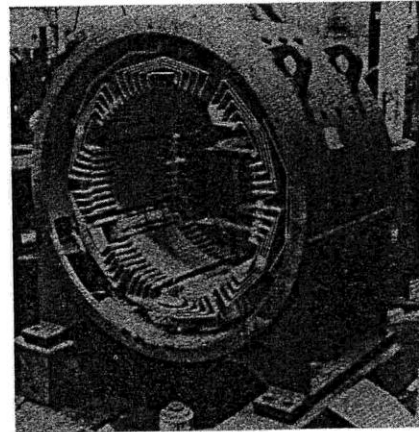


FIGURE 4.33 Compensating winding. (a) Developed diagram. (b) Schematic diagram. (c) Photograph. (Courtesy of General Electric Canada Inc.)

Minimizing commutation problems

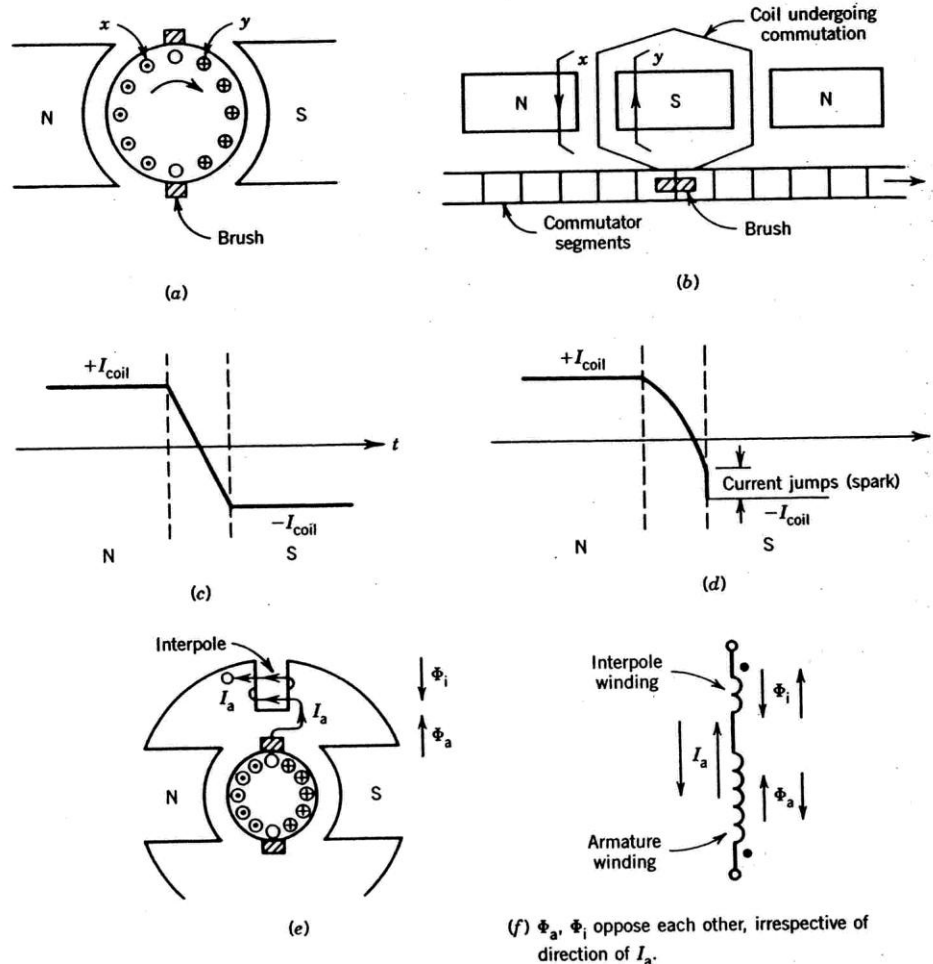


FIGURE 4.46 Current communication in dc machine.

- Smooth transfer of current during commutation is hampered by
 - a) coil inductance and
 - b) voltage due to AR flux in the interpolar axis. This voltage is called reactance voltage.

- Can be minimized using interpoles. They produce an opposing field that cancels out the AR in the interpolar region. Thus this winding is also connected in series with the armature winding.


Note: The UVic lab motors have interpoles in them. This should be connected in series with the armature winding for experiments.

Question:


Can interpoles be replaced by compensating windings and vice-versa?

Why or why not?

Separately Excited DC Generator

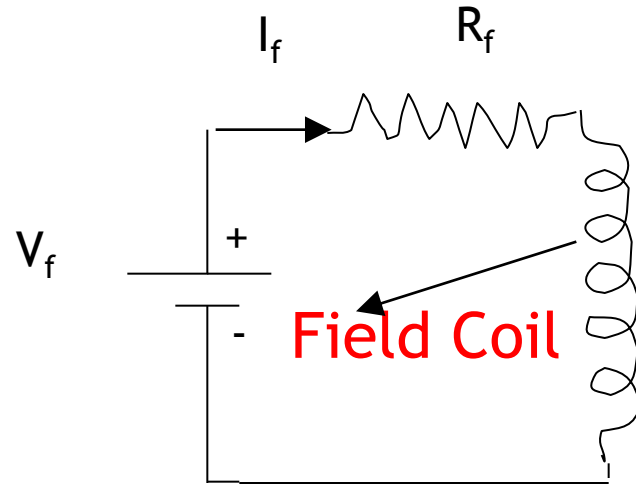

Field equation: $V_f = R_f I_f$

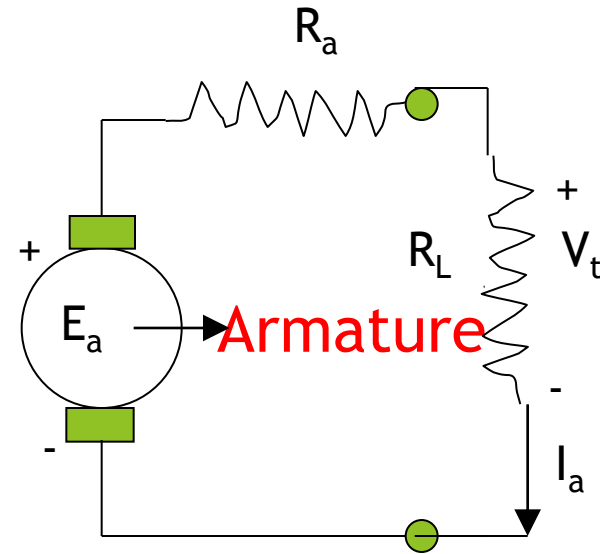


Armature equation: $V_t = E_a - I_a R_a$

$V_t = I_a R_L, E_a = K_a \Phi \omega_m$

Shunt Generators

Shunt Field Coil

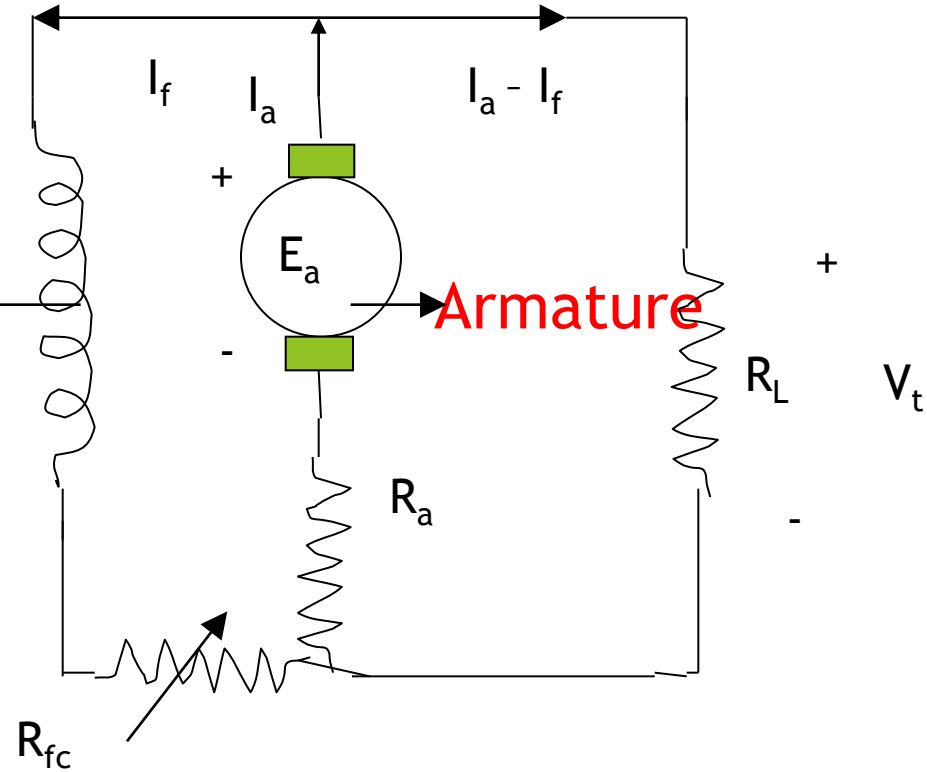Field coil has R_{fw} :
Implicit field resistance





Field equation: $V_t = R_f I_f$

$R_f = R_{fw} + R_{fc}$


Armature equation: $V_t = E_a - I_a R_a$

$V_t = (I_a - I_f) R_L$, $E_a = K_a \Phi \omega_m$

Voltage build-up of shunt generators

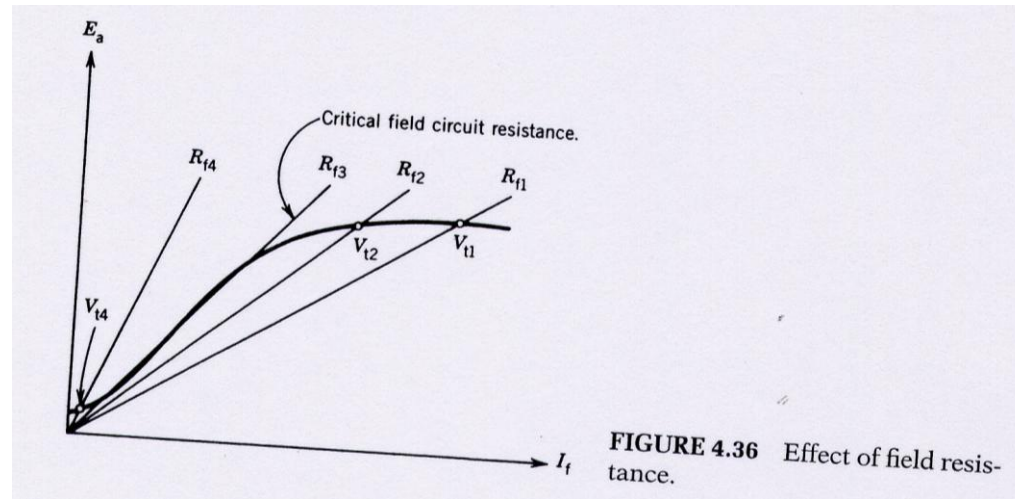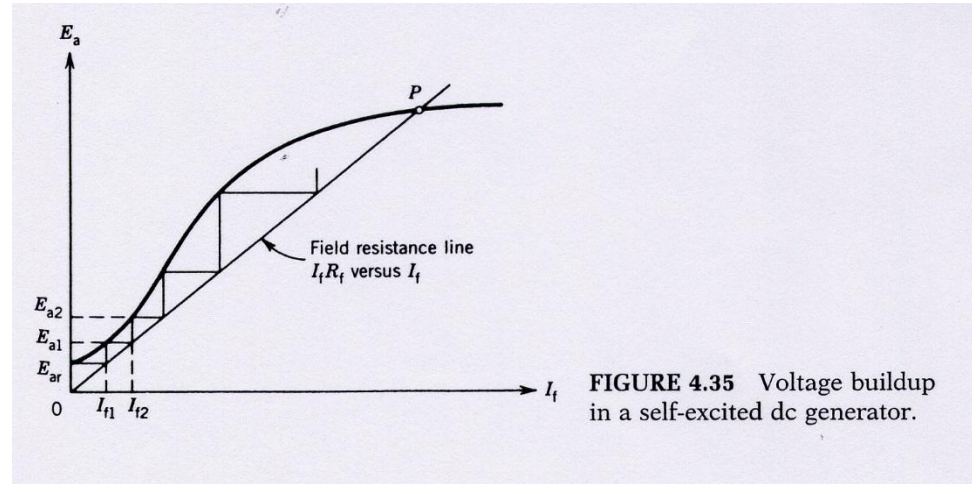


Example on shunt generators' buildup

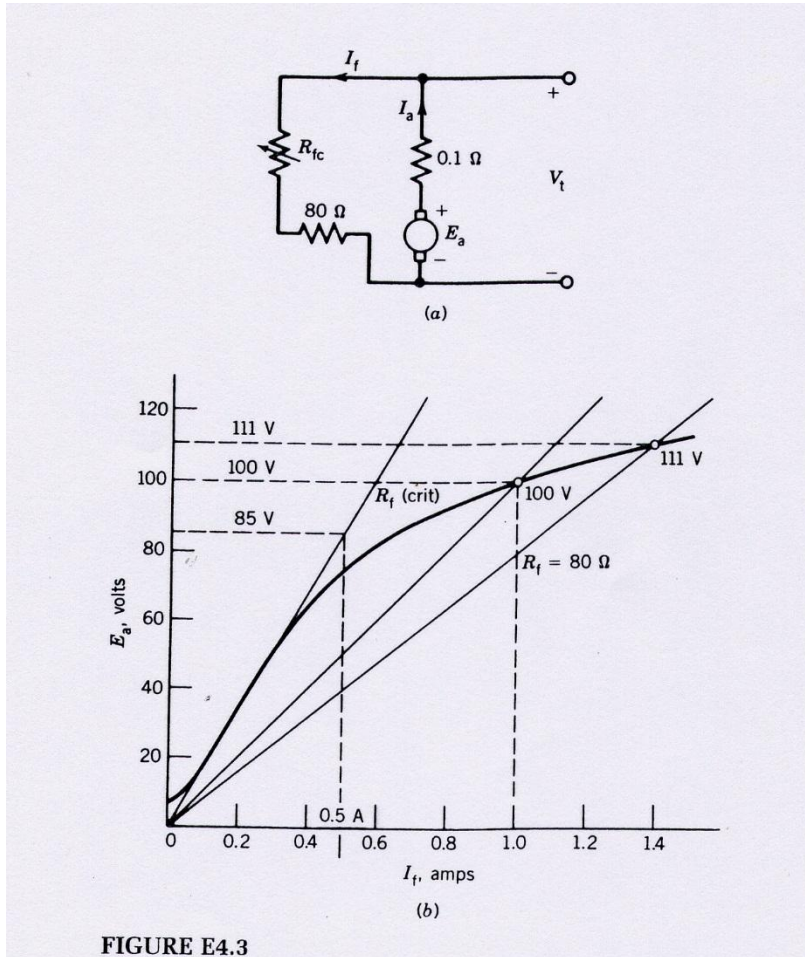


For proper voltage build-up the following are required:

- Residual magnetism
- Field MMF should aid residual magnetism
- Field circuit resistance should be less than critical field circuit resistance

Separately Excited DC Motor

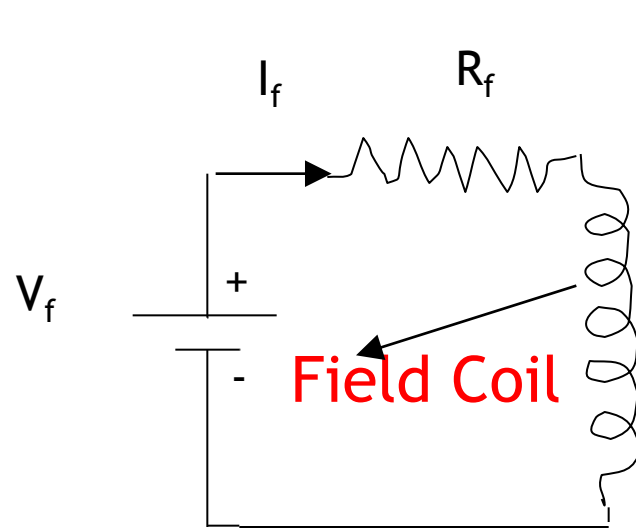



Field equation: $V_f = R_f I_f$

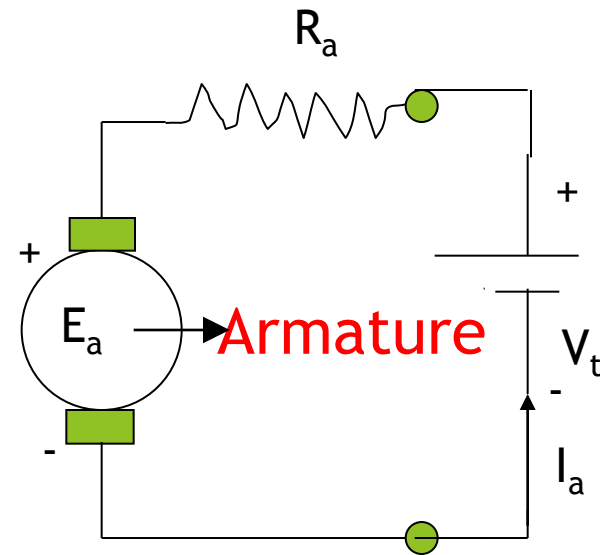

Armature equation: $E_a = V_t - I_a R_a$

$$E_a = K_a \Phi \omega_m$$

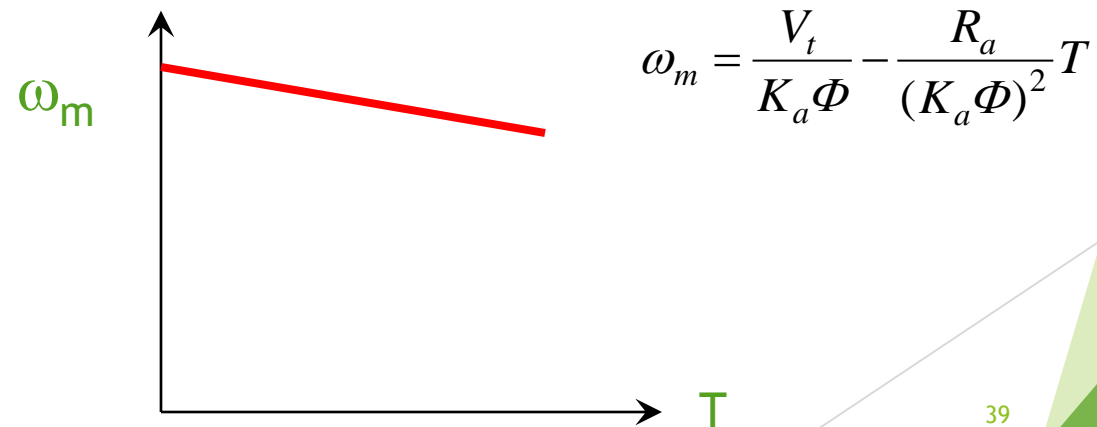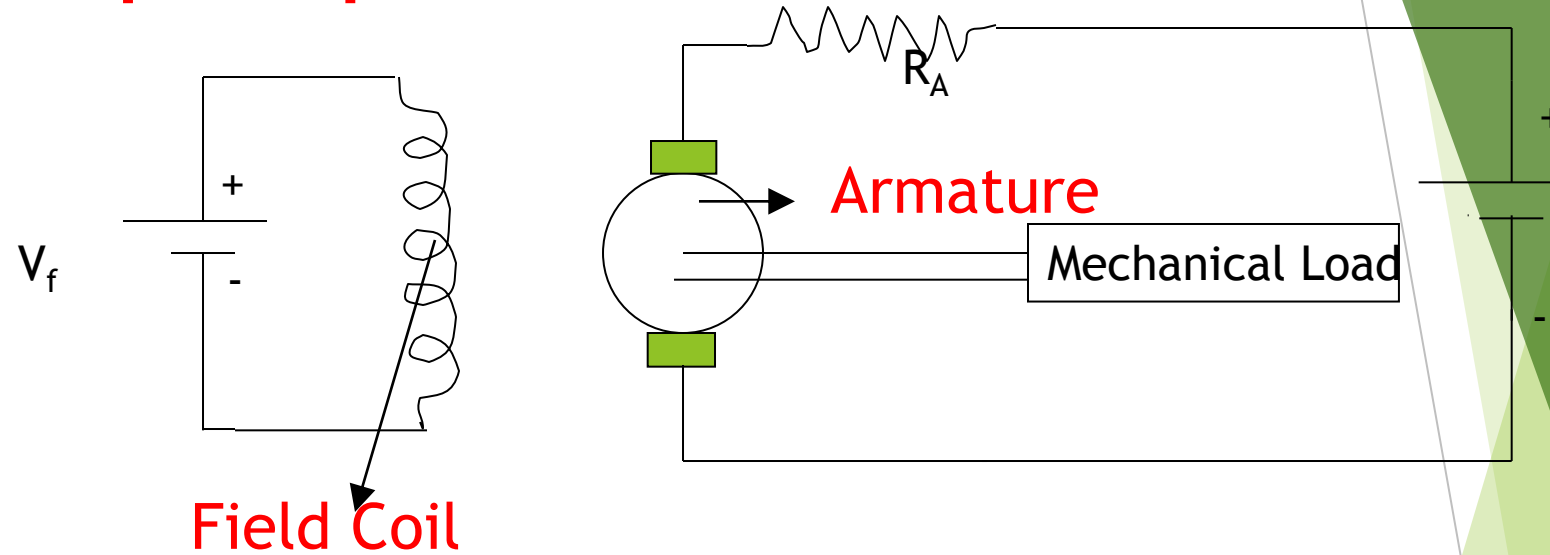Separately Excited DC Motor Torque-speed Characteristics




Separately excited DC Motor-Example 1

A dc motor has $R_a = 2 \Omega$, $I_a = 5 \text{ A}$, $E_a = 220 \text{ V}$, $N_m = 1200 \text{ rpm}$. Determine i) voltage applied to the armature, developed torque, developed power . ii) Repeat with $N_m = 1500 \text{ rpm}$. Assume same I_a .

Solution on Greenboard


Speed Control of Separately Excited DC Motor(2)

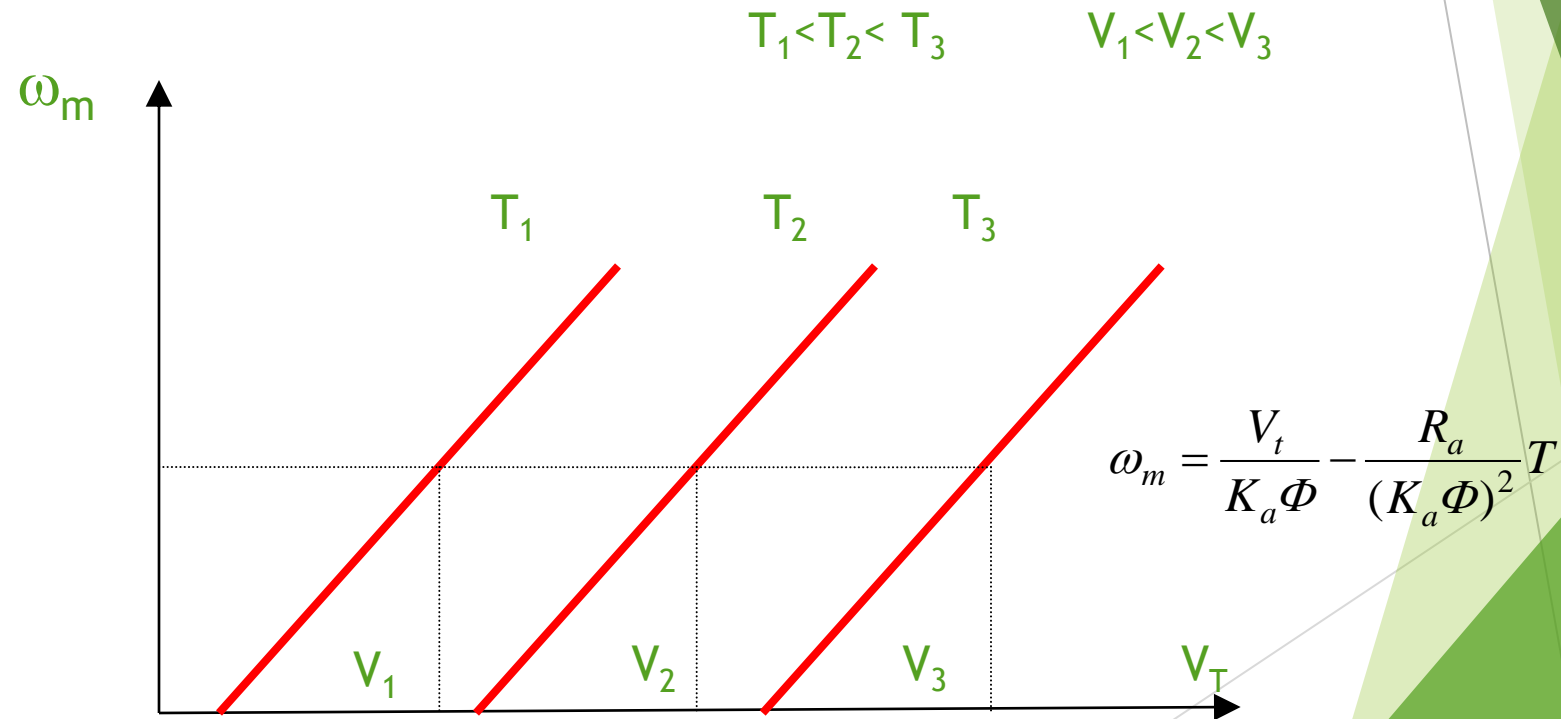- By *Controlling* Terminal Voltage V_t and keeping I_f or Φ constant at rated value. This method of speed control is applicable for speeds below rated or base speed.




Speed Control of Separately Excited DC Motor

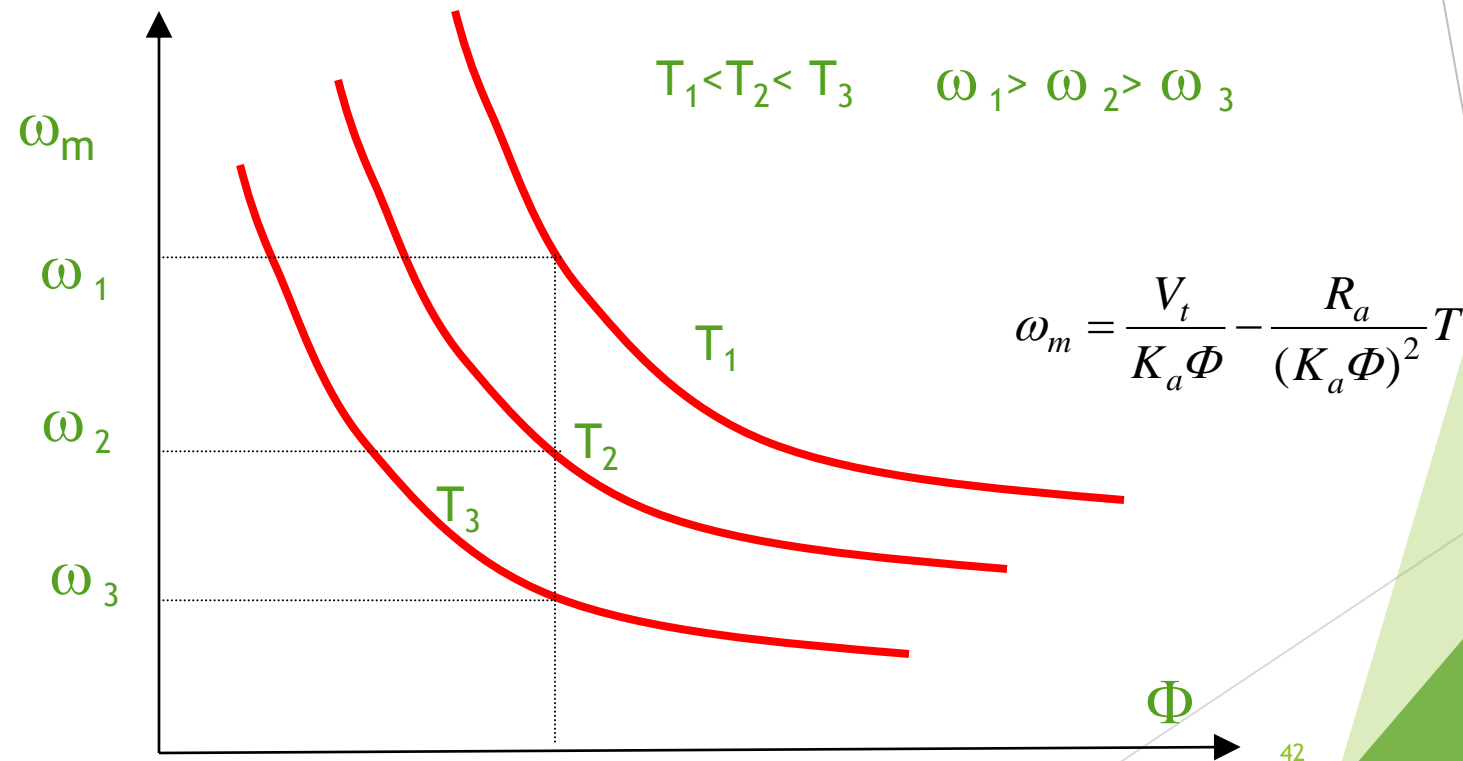- By *Controlling* (reducing) Field Current I_f or Φ and keeping V_t at rated value. This method of speed control is applicable for speeds above rated speed.



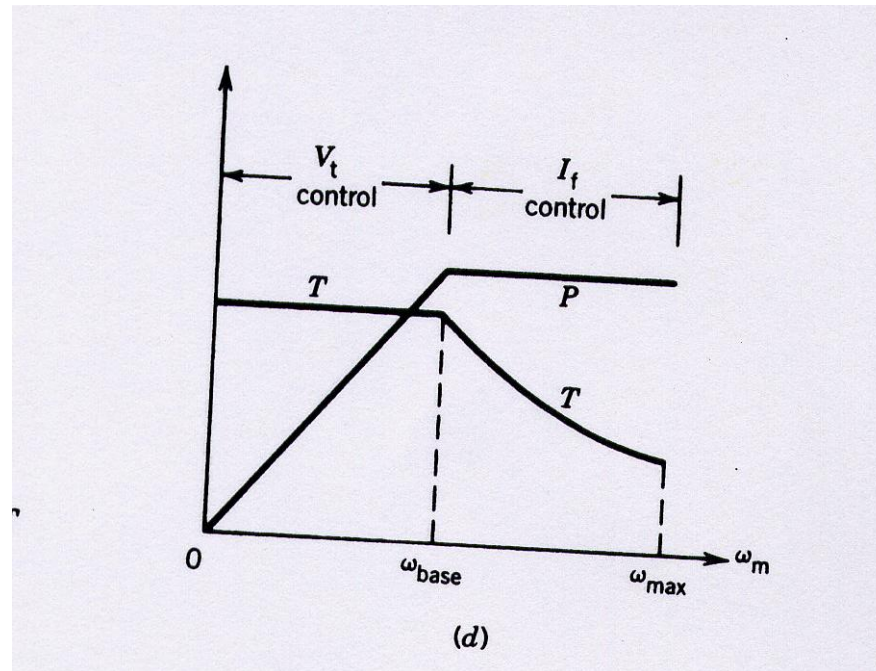Regions of operation of a Separately Excited DC Motor





Separately excited dc motor -Example 2

A separately excited dc motor with negligible armature resistance operates at 1800 rpm under no-load with $V_t = 240\text{V}$ (rated voltage). The rated speed of the motor is 1750 rpm.

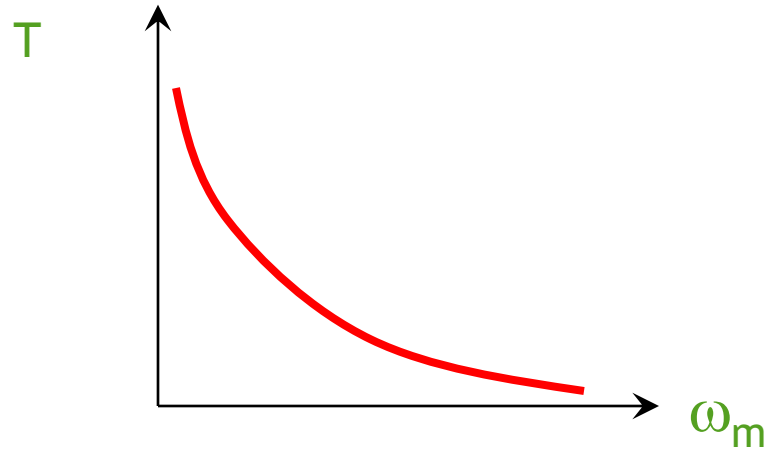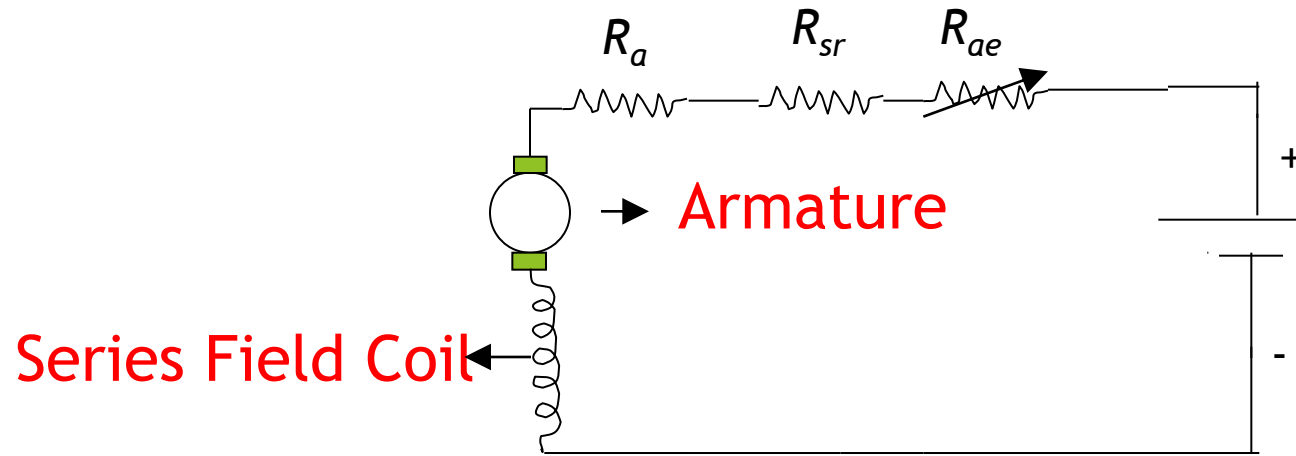- i) Determine V_t if the motor has to operate at 1200 rpm under no-load.
- ii) Determine Φ (flux/pole) if the motor has to operate at 2400 rpm under no-load; given that $K = 400/\pi$.
- iii) Determine the rated flux per pole of the machine.


Solution on Greenboard

Series Excited DC Motor Torque-Speed Characteristics




$$\omega_m = \frac{V_t}{\sqrt{K_{sr} T}} - \frac{R_a + R_{sr} + R_{ae}}{K_{sr}}$$

Losses in dc machines

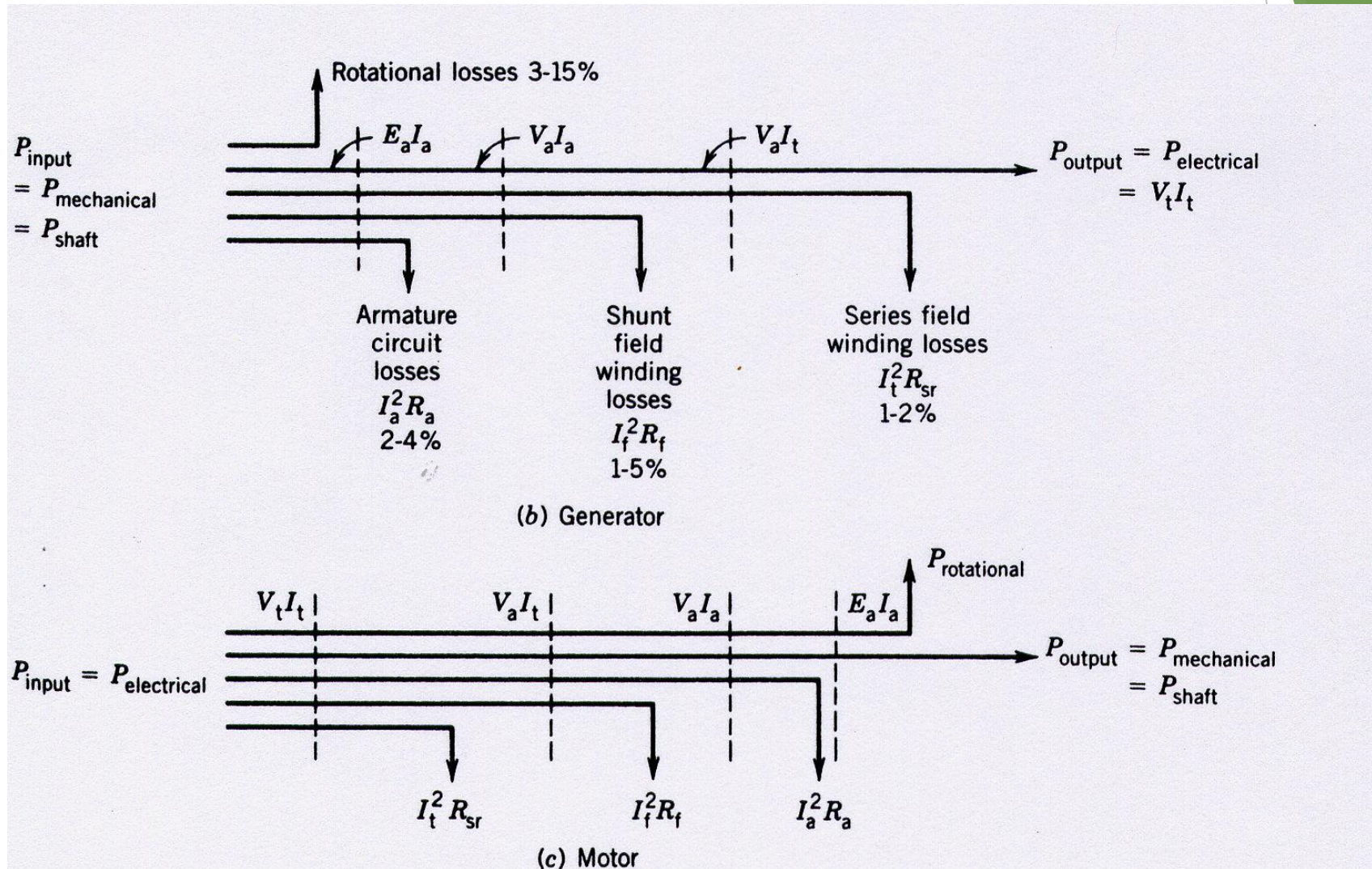

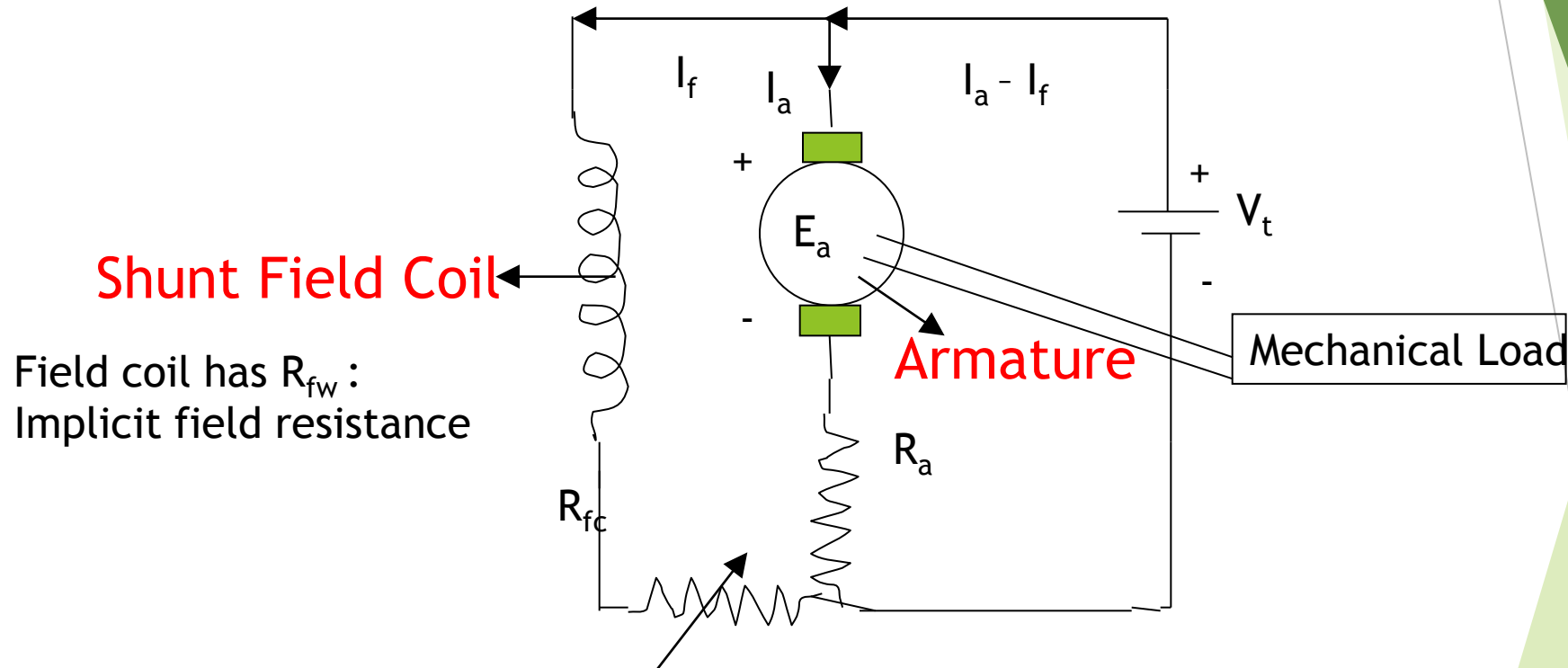Losses in dc machines-shunt motor example



Field equation: $V_t = R_f I_f$

$R_f = R_{fw} + R_{fc}$

Armature equation: $V_t = E_a + I_a R_a$

$E_a = K_a \Phi \omega_m$