

Active Power: (P)

- ▶ Alternative words used for Real Power (Actual Power, True Power, Watt–full Power, Useful Power, Real Power, and Active Power)
- ▶ In a DC Circuit, power supply to the DC load is simply the product of Voltage across the load and Current flowing through it i.e., $P = V I$. because in DC Circuits, there is no concept of phase angle between current and voltage. In other words, there is no Power factor in DC Circuits.
- ▶ But the situation is Sinusoidal or AC Circuits is more complex because of phase difference between Current and Voltage. Therefore average value of power (Real Power) is $P = VI \cos\theta$ is in fact supplied to the load.
- ▶ In AC circuits, When circuit is pure resistive, then the same formula used for power as used in DC as $P = V I$.

Real Power formulas:

- ▶ $P = V I$ (In DC circuits)
- ▶ $P = VI \cos\theta$ (in Single phase AC Circuits)
- ▶ $P = \sqrt{3} V_L I_L \cos\theta$ or (in Three Phase AC Circuits)
- ▶ $P = 3 V_{Ph} I_{Ph} \cos\theta$
- ▶ $P = \sqrt{(S^2 - Q^2)}$ or
- ▶ $P = \sqrt{(VA^2 - VAR^2)}$ or
- ▶ Real or True power = $\sqrt{(\text{Apparent Power}^2 - \text{Reactive Power}^2)}$ or
- ▶ kW = $\sqrt{(kVA^2 - kVAR^2)}$

Reactive Power: (Q)

- ▶ Also known as (Use-less Power, Watt less Power)
- ▶ The powers that continuously bounce back and forth between source and load is known as reactive Power (Q)
- ▶ Power merely absorbed and returned in load due to its reactive properties is referred to as reactive power
- ▶ The unit of Active or Real power is Watt where $1W = 1V \times 1A$.
- ▶ Reactive power represent that the energy is first stored and then released in the form of magnetic field or electrostatic field in case of inductor and capacitor respectively.
- ▶ Reactive power is given by $Q = V I \sin\theta$ which can be positive (+ve) for inductive, negative (-Ve) for capacitive load.
- ▶ The unit of reactive power is Volt-Ampere reactive. I.e. VAR where $1 \text{ VAR} = 1V \times 1A$.
- ▶ In more simple words, in Inductor or Capacitor, how much magnetic or electric field made by $1A \times 1V$ is called the unit of reactive power.

Reactive power formulas:

- ▶ $Q = V I \sin\theta$
- ▶ Reactive Power = $\sqrt{(\text{Apparent Power}^2 - \text{True power}^2)}$

$$\text{VAR} = \sqrt{(\text{VA}^2 - \text{P}^2)}$$

$$\text{kVAR} = \sqrt{(\text{kVA}^2 - \text{kW}^2)}$$

Apparent Power: (S)

- ▶ The combination of reactive power and true power is called apparent power
- ▶ The product of voltage and current if and only if the phase angle differences between current and voltage are ignored.
- ▶ Total power in an AC circuit, both dissipated and absorbed/returned is referred to as apparent power
- ▶ In an AC circuit, the product of the r.m.s voltage and the r.m.s current is called apparent power.
- ▶ **Apparent power formulas:**
- ▶ $S = V I$
- ▶ $\text{Apparent Power} = \sqrt{(\text{True power}^2 + \text{Reactive Power}^2)}$

Power Triangle

