

Basic Electric Circuits

Concept of linearity and linear network

Basic Electric Circuits

Linearity and Superposition: Linearity.

Basically, a mathematical equation is said to be linear if the following properties hold.

- homogeneity
- additivity

What does this mean? We first look at the property of homogeneity.

Basic Electric Circuits

Linearity : Homogeneity.

Homogeneity requires that if the input (excitation) of a system (equation) is multiplied by a constant, then the output should be obtained by multiplying by the same constant to obtain the correct solution.

Sometimes equations that we think are linear, turn out not to be linear because they fail the homogeneity property. We next consider such an example.

Basic Electric Circuits

Linearity : Homogeneity (scaling).

Illustration: Does homogeneity hold for the following equation?

Given,

$$y = 4x$$

If $x = 1$, $y = 4$. If we double x to $x = 2$ and substitute this value into Eq 9.1 we get $y = 8$.

Now for homogeneity to hold, scaling should hold for y . that is, y has a value of 4 when $x = 1$. If we increase x by a factor of 2 when we should be able to multiply y by the same factor and get the same answer and when we substitute into the right side of the equation for $x = 2$.

Basic Electric Circuits

Linearity : Homogeneity (scaling).

Illustration: Does homogeneity hold for the following equation?

Given,

$$y = 4x + 2$$

If $x = 1$, then $y = 6$. If we double x to $x=2$, then $y = 10$.



Now, since we doubled x we should be able to double the value that y had when $x = 1$ and get $y = 10$. In this case we get $y = (2)(6) = 12$, which obviously is not 10, so homogeneity does not hold.

We conclude that Eq 9.2 is not a linear equation. In some ways that goes against the grain of what we have been taught about linear equations.

Basic Electric Circuits

Linearity : Homogeneity (scaling).

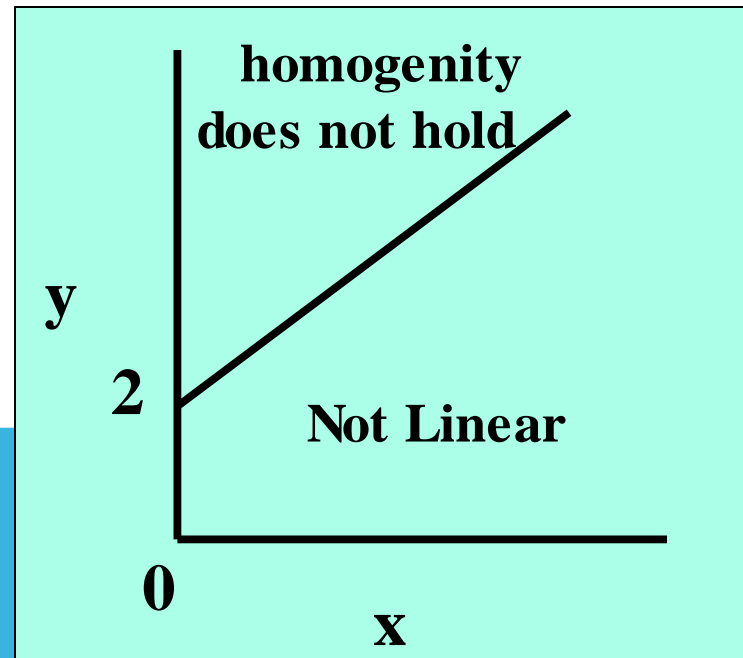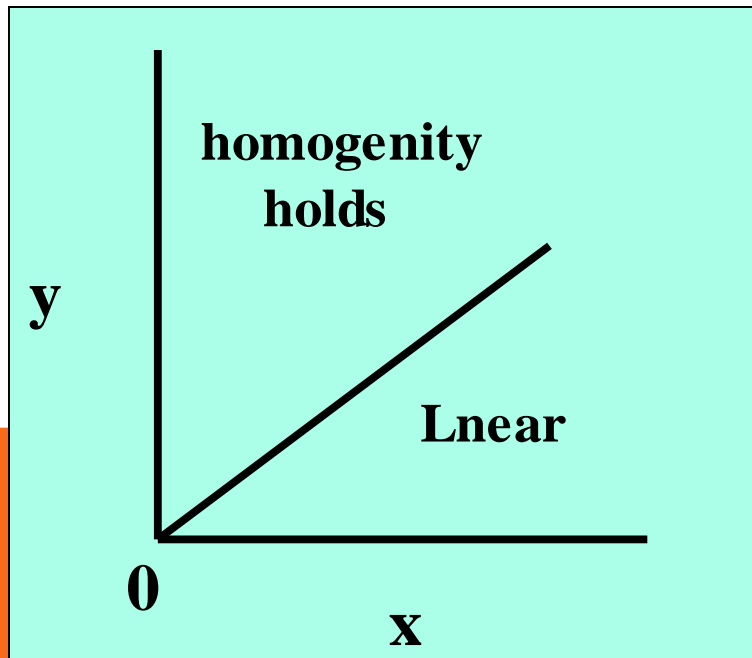Many of us were brought-up to think that if plotting an equation yields a straight line, then the equation is linear. From the following illustrations we have;



Basic Electric Circuits

Linearity : Additivity Property.

The additivity property is equivalent to the statement that the response of a system to a sum of inputs is the same as the responses of the system when each input is applied separately and the individual responses summed (added together).

This can be explained by considering the following illustrations.

Basic Electric Circuits

Linearity : Additivity Property.

Illustration: Given, $y = 4x$.

Let $x = x_1$, then $y_1 = 4x_1$

Let $x = x_2$, then $y_2 = 4x_2$

Then $y = y_1 + y_2 = 4x_1 + 4x_2$

Also, we note,

$$y = f(x_1 + x_2) = 4(x_1 + x_2) = 4x_1 + 4x_2$$

Since Equations (9.3) and (9.4) are identical,
the additivity property holds.

Basic Electric Circuits

Linearity : Additivity Property.

Illustration: Given, $y = 4x + 2$.

Let $x = x_1$, then $y_1 = 4x_1 + 2$

Let $x = x_2$, then $y_2 = 4x_2 + 2$

Then $y = y_1 + y_2 = 4x_1 + 2 + 4x_2 + 2 = 4(x_1 + x_2) + 4$

Also, we note,

$$y = f(x_1 + x_2) = 4(x_1 + x_2) + 2$$


Since Equations (9.5) and (9.6) are not identical,
the additivity property does not hold.

Basic Electric Circuits

Linearity Given the circuit shown

in Figure Use the concept of linearity

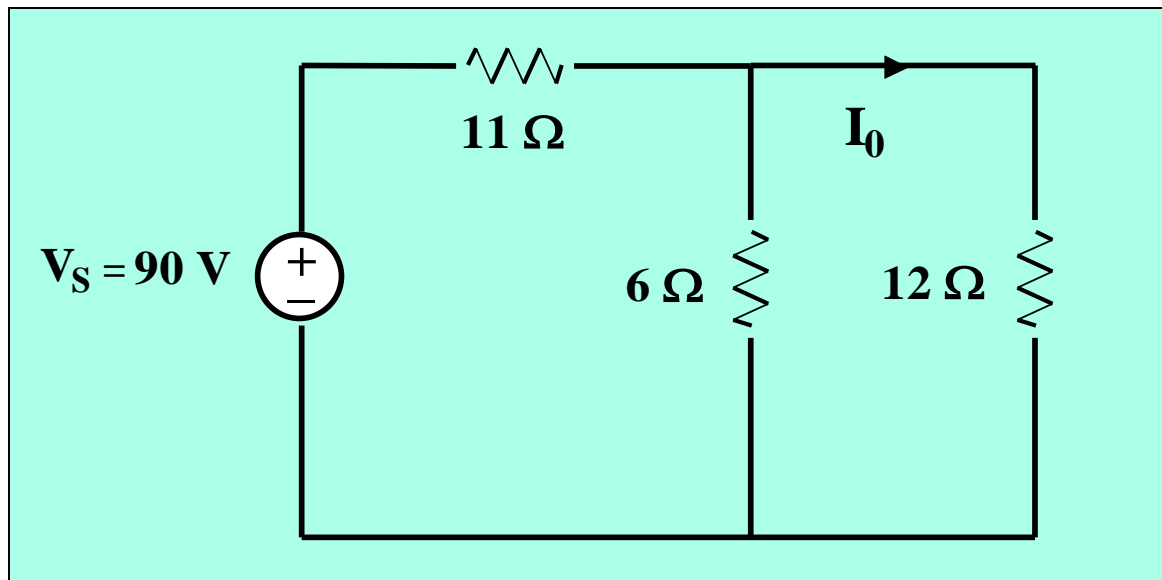(homogeneity or scaling) to find the current I_0 .




Circuit for Example

Assume $I_0 = 1$ A. Work back to find that this gives $V_S = 45$ V. But since $V_S = 90$ V this means the true $I_0 = 2$ A.

Basic Electric Circuits

Linearity : In the circuit shown

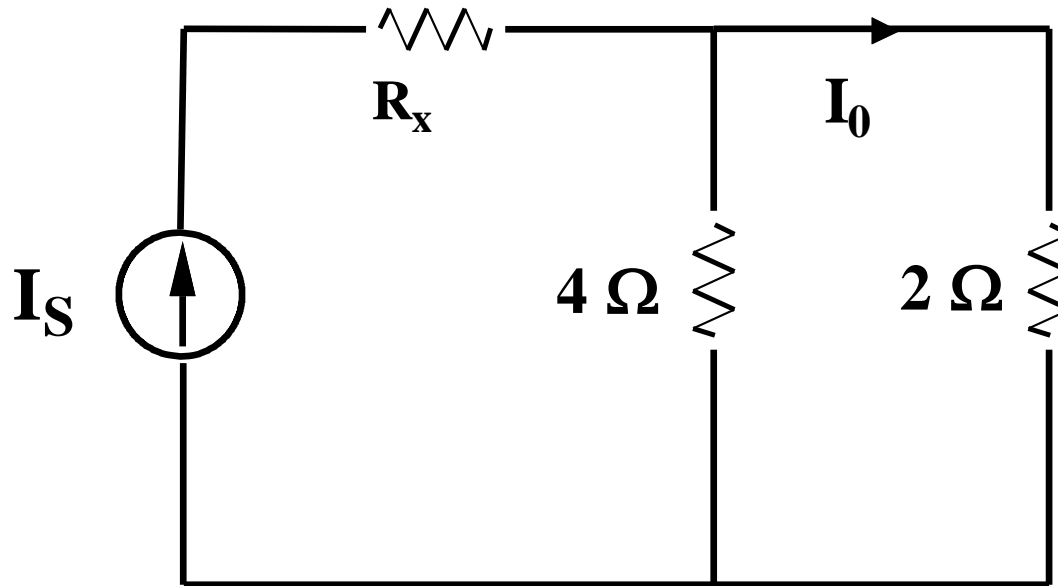below it is known that $I_0 = 4 \text{ A}$ when $I_S = 6 \text{ A}$. Find I_0 when $I_S = 18 \text{ A}$.



Since $I_{S \text{ NEW}} = 3 \times I_{S \text{ OLD}}$ we conclude $I_{0 \text{ NEW}} = 3 \times I_{0 \text{ OLD}}$.
Thus, $I_{0 \text{ NEW}} = 3 \times 4 = 12 \text{ A}$.

Basic Electric Circuits

Linearity : Question.

For Example, one might ask, “how do we know the circuit is linear?” That is a good question. To answer, we assume a circuit of the same form and determine if we get a linear equation between the output current and the input current. What must be shown for the circuit below?

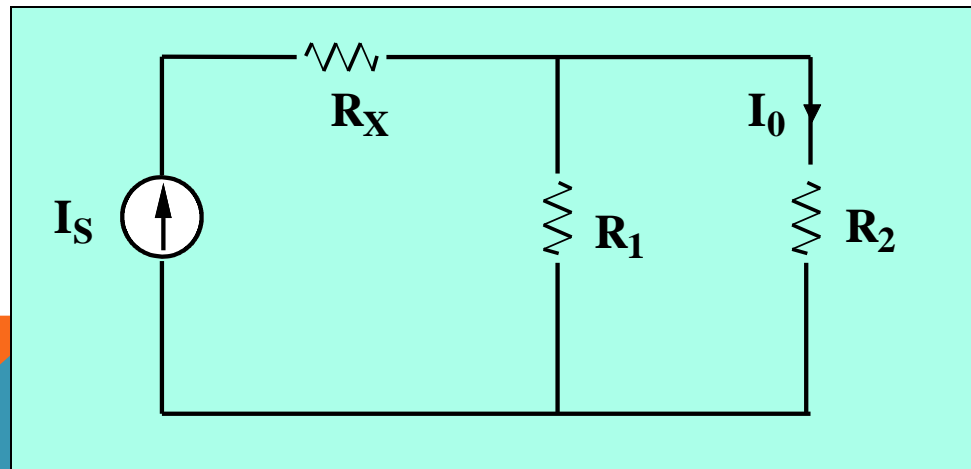


Figure 9.3: Circuit for investigating linearity.

Basic Electric Circuits

Linearity : Question, continued.

We use the current splitting rule (current division) to write the following equation.

$$I_0 = \frac{(I_s)(R_1)}{(R_1 + R_2)} = (K)(I_s)$$

The equation is of the same form of $y = mx$, which we saw was linear. Therefore, if R_1 and R_2 are constants then the circuit is linear.

Unilateral circuits

In unilateral circuits, the property of circuit changes with the change of direction of supply voltage or current. In other words, unilateral circuit allows the current to flow only in one direction. Diode rectifier is the best example of unilateral circuit because it does not perform the rectification in both direction of supply.

Bi-lateral circuits

In bilateral circuits, the property of circuit does not change with the change of direction of supply voltage or current. In other words, bilateral circuit allows the current to flow in both directions. Transmission line is the best example of bilateral circuit because, if you give supply from any direction, the circuit properties remain constant