


Generation of three-phase voltages and currents

Each of three-phase generators can be connected to one of three identical loads.

This way the system would consist of three single-phase circuits differing in phase angle by 120° .


The current flowing to each load can be found as

$$I = \frac{V}{Z}$$

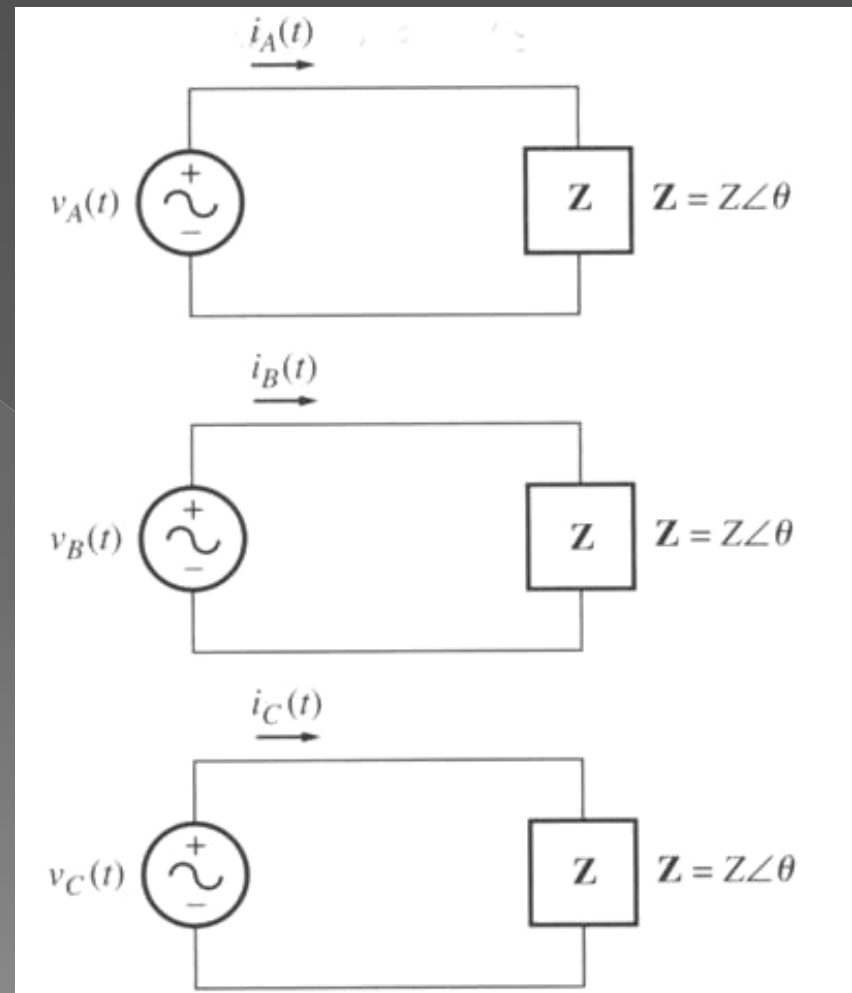

Generation of three-phase voltages and currents

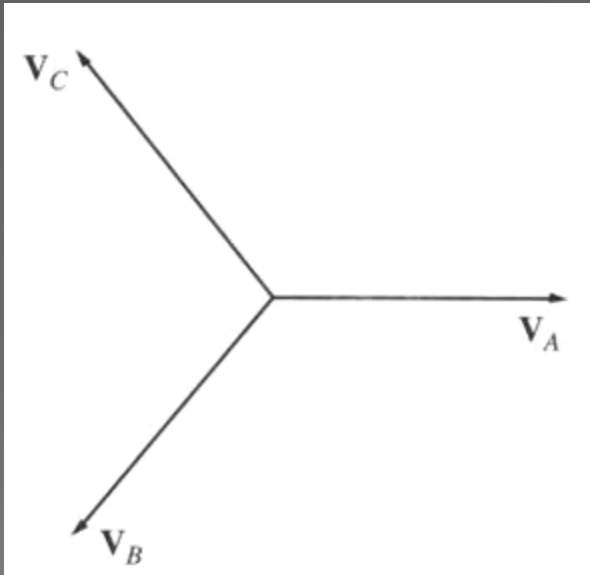Therefore, the currents flowing in each phase are



$$I_A = \frac{V \angle 0^\circ}{Z \angle \theta} = I \angle -\theta$$

$$I_B = \frac{V \angle -120^\circ}{Z \angle \theta} = I \angle -120 - \theta$$

$$I_C = \frac{V \angle -240^\circ}{Z \angle \theta} = I \angle -240 - \theta$$

Generation of three-phase voltages and currents

The current flowing through a neutral can be found as

$$\begin{aligned} I_N &= I_A + I_B + I_C = I\angle -\theta + I\angle -\theta - 120^\circ + I\angle -\theta - 240^\circ \\ &= I \cos(-\theta) + jI \sin(-\theta) + I \cos(-\theta - 120^\circ) + jI \sin(-\theta - 120^\circ) + I \cos(-\theta - 240^\circ) + jI \sin(-\theta - 240^\circ) \\ &= I \left[\cos(-\theta) + \cos(-\theta - 120^\circ) + \cos(-\theta - 240^\circ) \right] + jI \left[\sin(-\theta) + \sin(-\theta - 120^\circ) + \sin(-\theta - 240^\circ) \right] \\ &= I \left[\cos(-\theta) + \cos(-\theta) \cos(120^\circ) + \sin(-\theta) \sin(120^\circ) + \cos(-\theta) \cos(240^\circ) + \sin(-\theta) \sin(240^\circ) \right] \\ &\quad + jI \left[\sin(-\theta) + \sin(-\theta) \cos(120^\circ) - \cos(-\theta) \sin(120^\circ) + \sin(-\theta) \cos(240^\circ) - \cos(-\theta) \sin(240^\circ) \right] \end{aligned}$$

Which is:

$$\begin{aligned} I_N &= I \left[\cos(-\theta) - \frac{1}{2} \cos(-\theta) + \frac{\sqrt{3}}{2} \sin(-\theta) - \frac{1}{2} \cos(-\theta) - \frac{\sqrt{3}}{2} \sin(-\theta) \right] \\ &\quad + jI \left[\sin(-\theta) - \frac{1}{2} \sin(-\theta) + \frac{\sqrt{3}}{2} \cos(-\theta) - \frac{1}{2} \sin(-\theta) - \frac{\sqrt{3}}{2} \cos(-\theta) \right] \\ &= 0 \end{aligned}$$


Generation of three-phase voltages and currents

As long as the three loads are equal, the return current in the neutral is zero!

Such three-phase power systems (equal magnitude, phase differences of 120° , identical loads) are called balanced.


In a balanced system, the neutral is unnecessary!

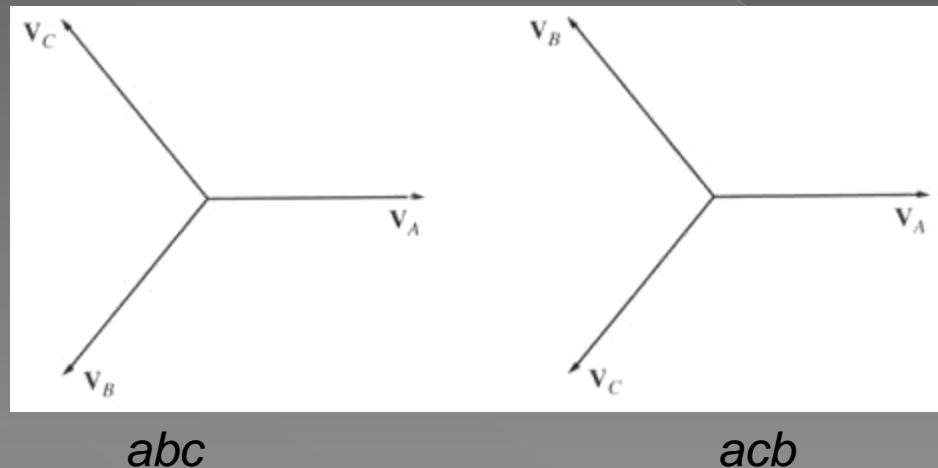Phase Sequence is the order in which the voltages in the individual phases peak.



Voltages and currents

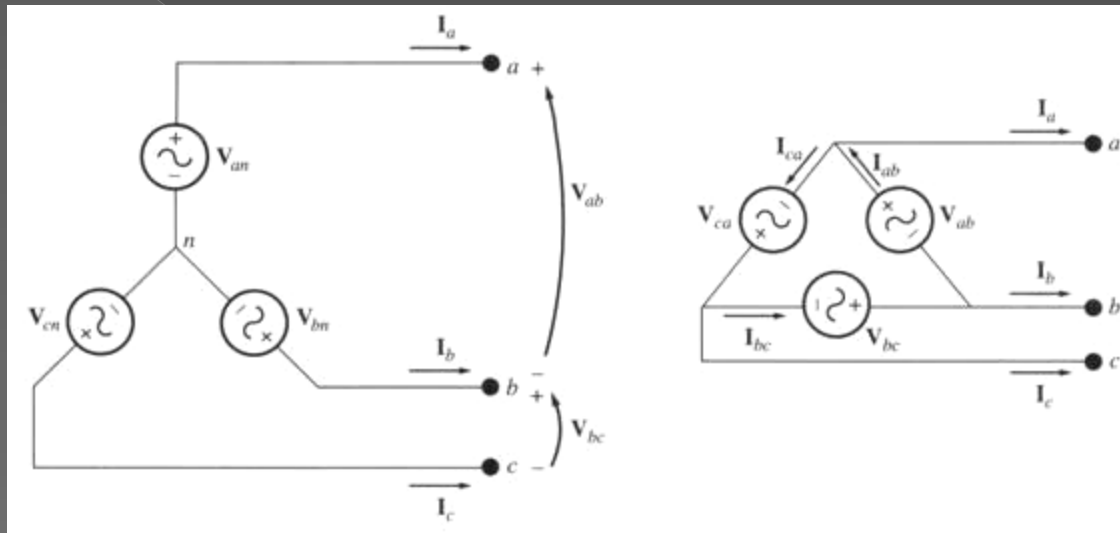There are two types of connections in three-phase circuits: Y and Δ .



Each generator and each load can be either Y - or Δ -connected. Any number of Y - and Δ -connected elements may be mixed in a power system.


Phase quantities - voltages and currents in a given phase.

Line quantities – voltages between the lines and currents in the lines connected to the generators.

Voltages and currents

Y-connection

Assuming
a resistive
load...

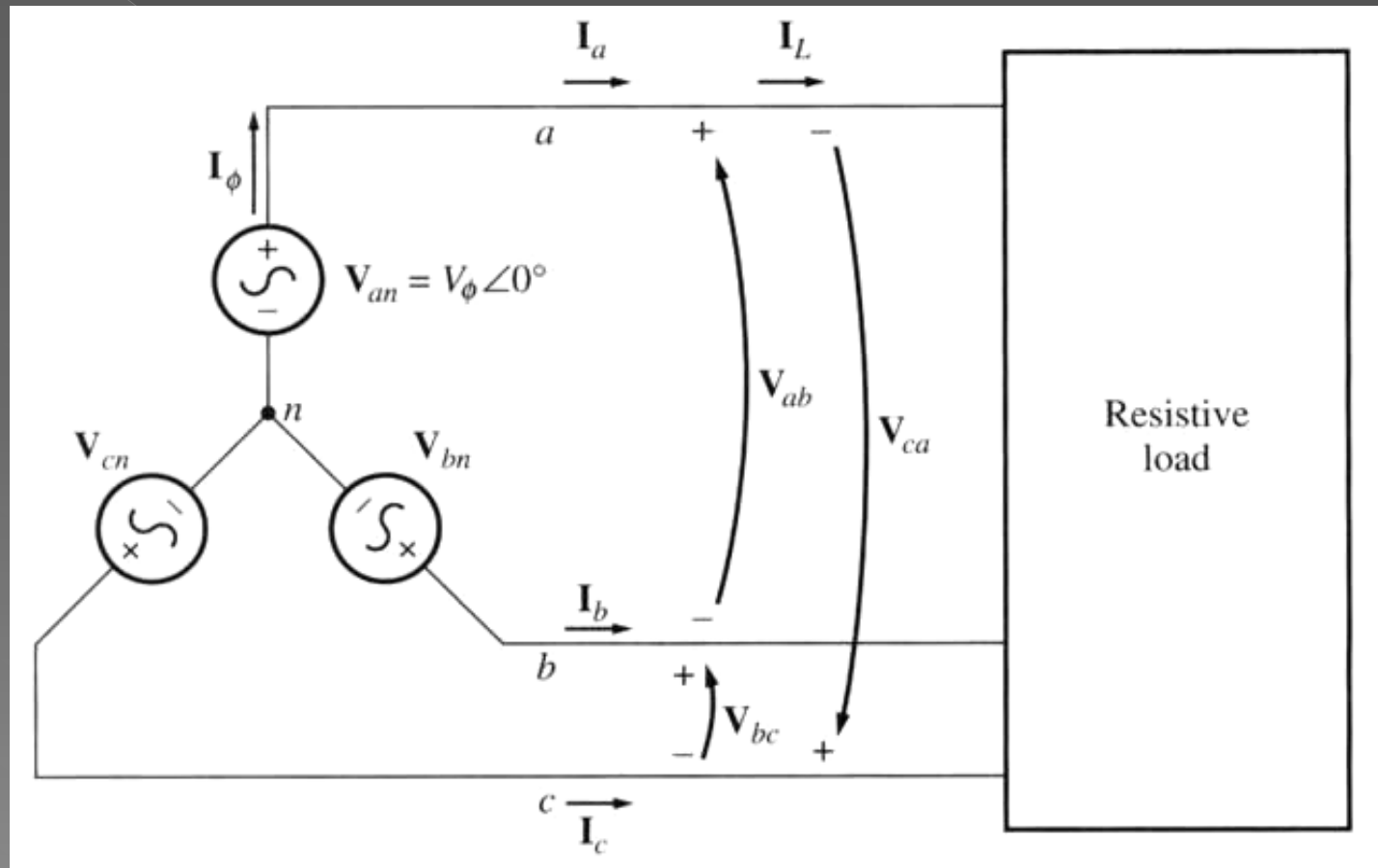

Voltages and currents

Y-connection (cont)

$$V_{an} = V_{\phi} \angle 0^{\circ}$$

$$V_{bn} = V_{\phi} \angle -120^{\circ}$$

$$V_{cn} = V_{\phi} \angle -240^{\circ}$$

Since we assume a resistive load:

$$I_a = I_{\phi} \angle 0^{\circ}$$

$$I_b = I_{\phi} \angle -120^{\circ}$$

$$I_c = I_{\phi} \angle -240^{\circ}$$

Voltages and currents

Y-connection (cont. 2)

The current in any line is the same as the current in the corresponding phase.

$$I_L = I_\phi$$

Voltages are:

$$\begin{aligned} V_{ab} &= V_a - V_b = V_\phi \angle 0^\circ - V_\phi \angle -120^\circ = V_\phi - \left(-\frac{1}{2}V_\phi - j\frac{\sqrt{3}}{2}V_\phi \right) = \frac{3}{2}V_\phi + j\frac{\sqrt{3}}{2}V_\phi \\ &= \sqrt{3}V_\phi \left(\frac{\sqrt{3}}{2} + j\frac{1}{2} \right) = \sqrt{3}V_\phi \angle 30^\circ \end{aligned}$$

Voltages and currents


Y-connection (cont. 3)

Magnitudes of the line-to-line voltages and the line-to-neutral voltages are related as:

$$V_{LL} = \sqrt{3}V_{\phi}$$

In addition, the line voltages are shifted by 30° with respect to the phase voltages.

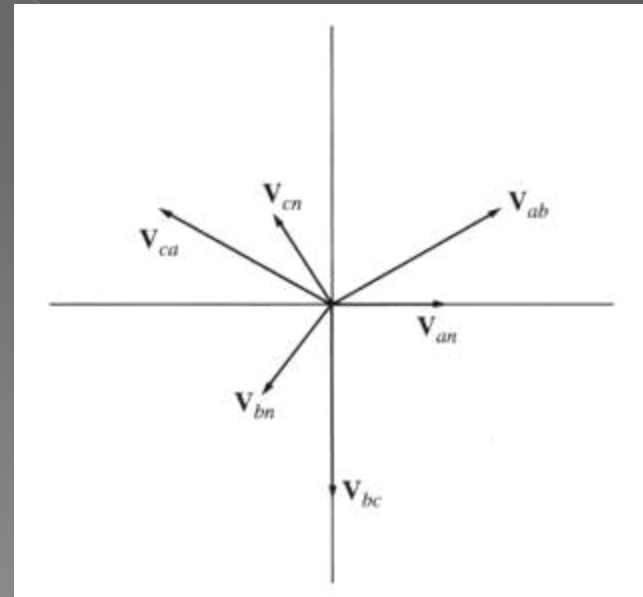
In a connection with *abc* sequence, the voltage of a line **leads** the phase voltage.



Voltages and currents

Δ -connection

assuming a
resistive load:

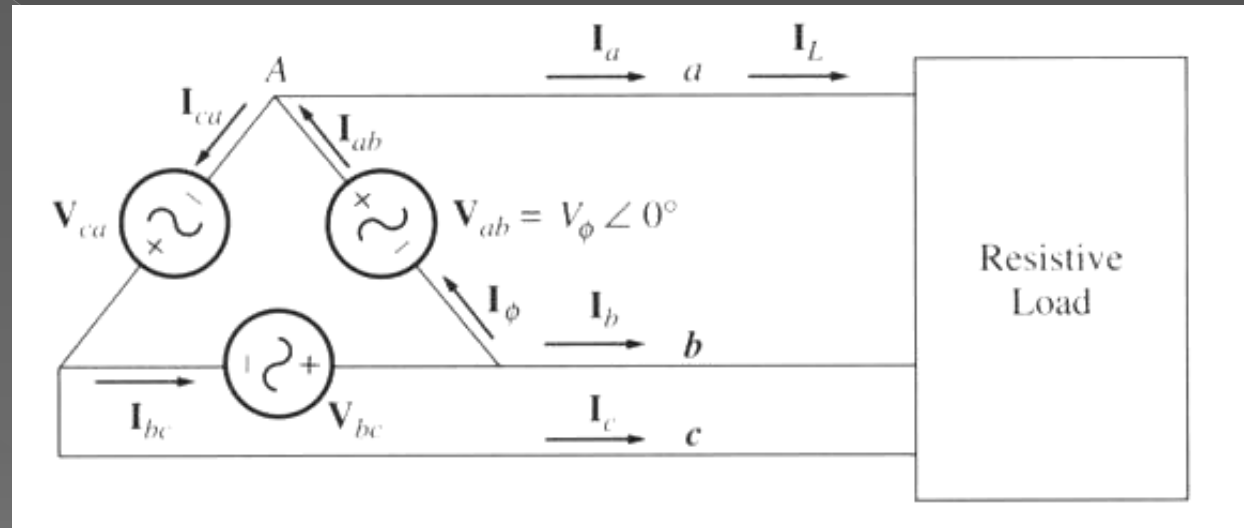

$$V_{ab} = V_\phi \angle 0^\circ$$

$$V_{bc} = V_\phi \angle -120^\circ$$

$$V_{ca} = V_\phi \angle -240^\circ$$

(3.14.1)

$$I_{ab} = I_\phi \angle 0^\circ$$

$$I_{bc} = I_\phi \angle -120^\circ$$

$$I_{ca} = I_\phi \angle -240^\circ$$

Voltages and currents

Δ -connection (cont.)

$$V_{LL} = V_{\phi}$$

The currents are:


$$\begin{aligned} I_a &= I_{ab} - I_{ca} = I_{\phi} \angle 0^{\circ} - I_{\phi} \angle 240^{\circ} = I_{\phi} - \left(-\frac{1}{2} I_{\phi} + j \frac{\sqrt{3}}{2} I_{\phi} \right) \\ &= \frac{3}{2} I_{\phi} - j \frac{\sqrt{3}}{2} I_{\phi} = \sqrt{3} I_{\phi} \left(\frac{\sqrt{3}}{2} - j \frac{1}{2} \right) = \sqrt{3} I_{\phi} \angle -30^{\circ} \end{aligned}$$

The magnitudes:

$$I_L = \sqrt{3} I_{\phi}$$

Voltages and currents

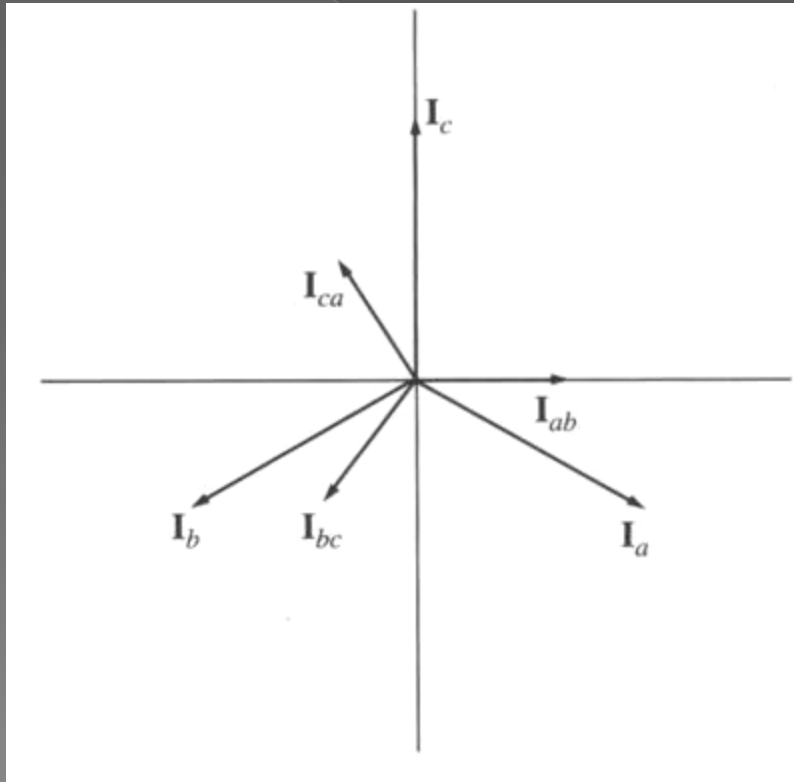For the connections with the *abc* phase sequences, the current of a line **lags** the corresponding phase current by 30° (see Figure below).



For the connections with the *acb* phase sequences, the line current **leads** the corresponding phase current by 30° .

Power relationships

For a balanced Y-connected load with the impedance $Z_\phi = Z\angle\theta^\circ$:

and voltages:

$$v_{an}(t) = \sqrt{2}V \sin \omega t$$

$$v_{bn}(t) = \sqrt{2}V \sin(\omega t - 120^\circ)$$


$$v_{cn}(t) = \sqrt{2}V \sin(\omega t - 240^\circ) \quad (3.17.1)$$

The currents can be found:

$$i_a(t) = \sqrt{2}I \sin(\omega t - \theta)$$

$$i_b(t) = \sqrt{2}I \sin(\omega t - 120^\circ - \theta)$$
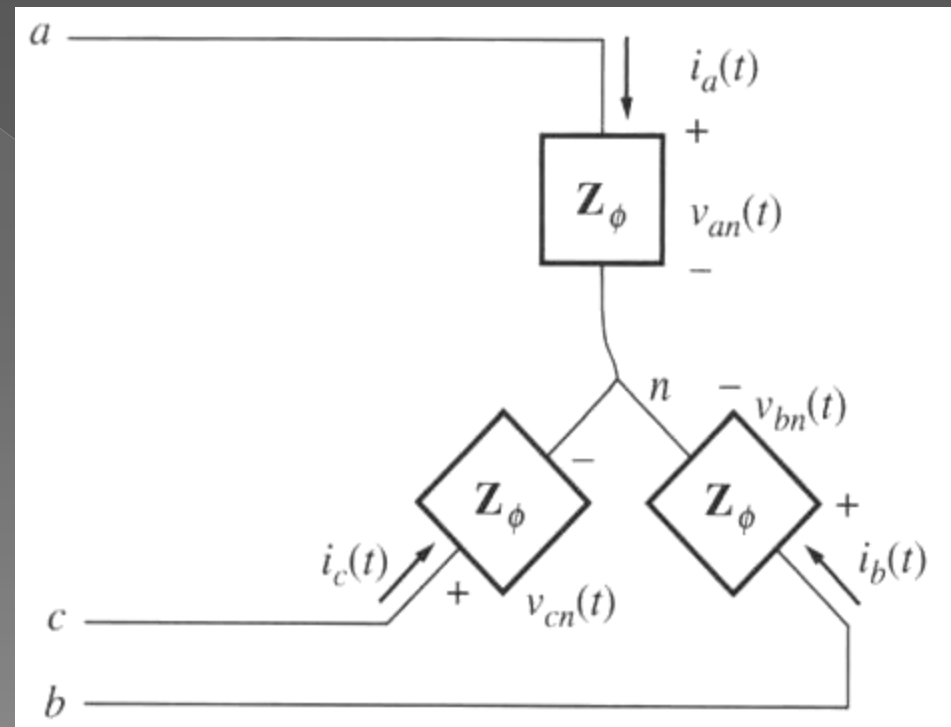
$$i_c(t) = \sqrt{2}I \sin(\omega t - 240^\circ - \theta) \quad (3.17.2)$$



Power relationships

The instantaneous power is:

$$p(t) = v(t)i(t)$$

Therefore, the instantaneous power supplied to each phase is:

$$p_a(t) = v_{an}(t)i_a(t) = 2VI \sin(\omega t) \sin(\omega t - \theta)$$

$$p_b(t) = v_{bn}(t)i_b(t) = 2VI \sin(\omega t - 120^\circ) \sin(\omega t - 120^\circ - \theta)$$

$$p_c(t) = v_{cn}(t)i_c(t) = 2VI \sin(\omega t - 240^\circ) \sin(\omega t - 240^\circ - \theta)$$

Since

$$\sin \alpha \sin \beta = \frac{1}{2} [\cos(\alpha - \beta) - \cos(\alpha + \beta)]$$

Power relationships

Therefore

$$p_a(t) = VI [\cos \theta - \cos(2\omega t - \theta)]$$

$$p_b(t) = VI [\cos \theta - \cos(2\omega t - 240^\circ - \theta)]$$

$$p_c(t) = VI [\cos \theta - \cos(2\omega t - 480^\circ - \theta)]$$

The total power on the load


$$p_{tot}(t) = p_a(t) + p_b(t) + p_c(t) = 3VI \cos \theta$$

The pulsing components cancel each other because of 120° phase shifts.

Power relationships

The instantaneous power in phases.

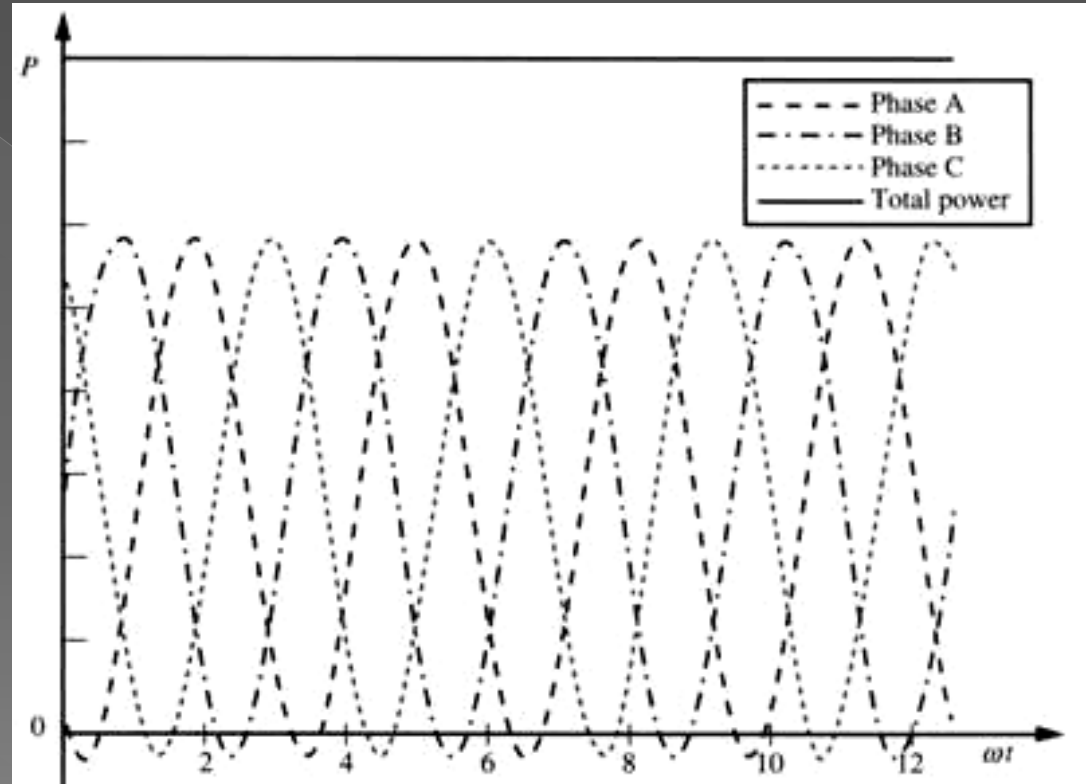The total power supplied to the load is constant.



Power relationships

Phase quantities in each phase of a Y- or Δ -connection.

Real

$$P = 3V_{\phi}I_{\phi} \cos \theta = 3I_{\phi}^2 Z \cos \theta$$

Reactive

$$Q = 3V_{\phi}I_{\phi} \sin \theta = 3I_{\phi}^2 Z \sin \theta$$

Apparent

$$S = 3V_{\phi}I_{\phi} = 3I_{\phi}^2 Z$$

Note: these equations are valid for balanced loads only.

Power relationships

Line quantities: Y-connection.

Power consumed by a load: $P = 3V_{\phi}I_{\phi} \cos \theta$

Since for this load $I_L = I_{\phi}$ and $V_{LL} = \sqrt{3}V_{\phi}$

Therefore: $P = 3 \frac{V_{LL}}{\sqrt{3}} I_L \cos \theta$

Finally: $P = \sqrt{3}V_{LL}I_L \cos \theta$

Note: these equations are valid for balanced loads only.

Power relationships

Line quantities: Δ -connection.

Power consumed by a load: $P = 3V_{\phi}I_{\phi} \cos \theta$

Since for this load $I_L = \sqrt{3}I_{\phi}$ and $V_{LL} = V_{\phi}$

Therefore: $P = 3 \frac{I_L}{\sqrt{3}} V_{LL} \cos \theta$

Finally: $P = \sqrt{3}V_{LL}I_L \cos \theta$

Same as for a Y-connected load!

Note: these equations were derived for a balanced load.

Power relationships

Line quantities: Y- and Δ -connection.

Reactive power

$$Q = \sqrt{3}V_{LL}I_L \sin \theta$$

Apparent power

$$S = \sqrt{3}V_{LL}I_L$$

Note: θ is the angle between the phase voltage and the phase current – the impedance angle.