

Multiplier and Shunt

Any voltmeter will be designed so that when a known magnitude of voltage appears across it, this voltage produces a full-scale deflection (FSD) of the pointer. Any ammeter will be designed so that when a known magnitude of current passes through it, this current produces a full-scale deflection (FSD) of the pointer.

Multiplier and Shunt

In order to extend the upper limit of either of these instruments, a resistor is connected in series with the voltmeter or a resistor in parallel the ammeter. In the case of a voltmeter, the resistor is known as a **multiplier**; in the case of an ammeter, it is known as a **shunt**.

For Shunt:

$$I R_{shunt} = R_m \text{ FSD}$$

whence:

$$R_{shunt} = I R_m \text{ FSD}$$

For Multiplier:

$$\text{FSD} (R_{mult} + R_m) = V$$

and so:

$$R_{mult} = (V \text{ FSD}) - R_m$$

Where:

FSD = Meter Full Scale Deflection

I = Current Range

V = Voltage Range

R_{shunt} = Shunt Resistance

R_{mult} = Multiplier Resistance

R_m = Meter Resistance