
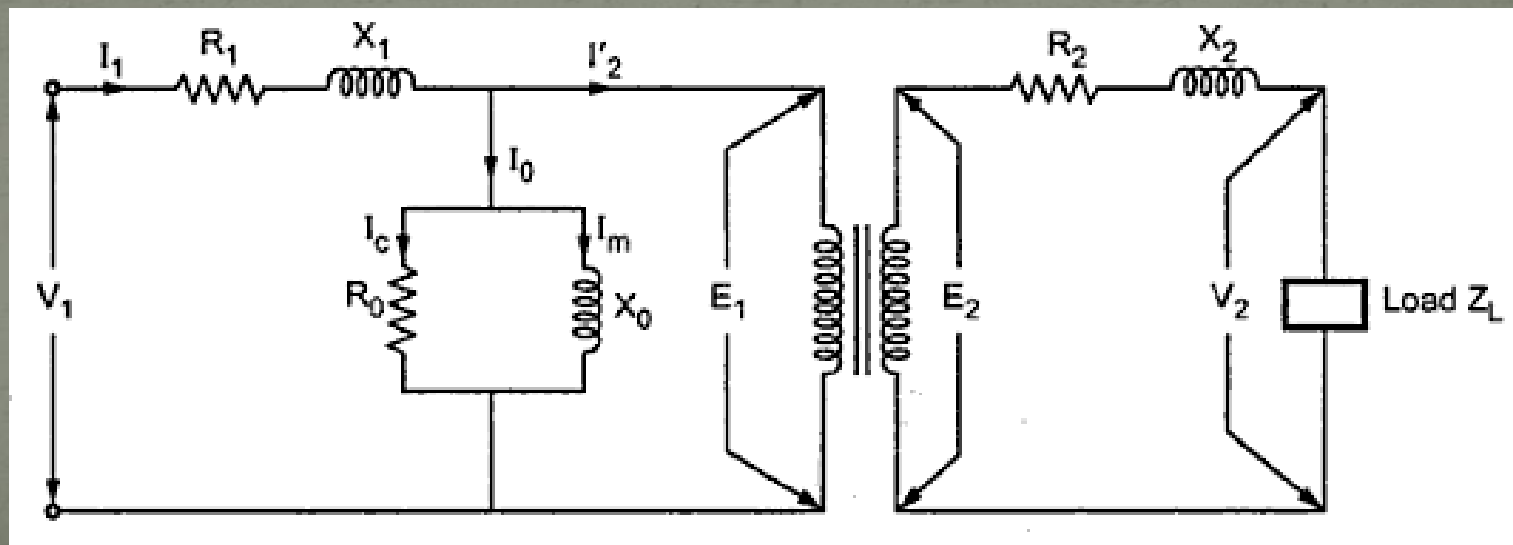


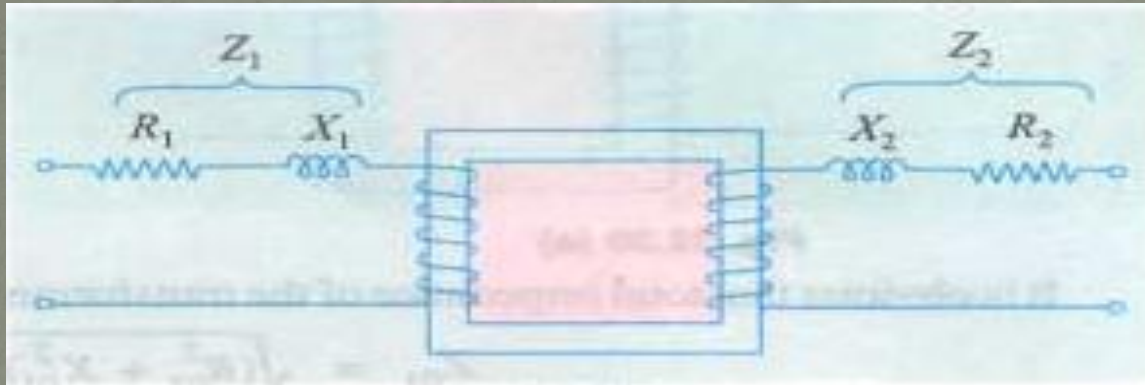Equivalent circuit parameters referred to primary and secondary sides respectively



Contd.,

- The effect of circuit parameters shouldn't be changed while transferring the parameters from one side to another side
- It can be proved that a resistance of R_2 in sec. is equivalent to R_2/k^2 will be denoted as R_2' (ie. Equivalent sec. resistance w.r.t primary) which would have caused the same loss as R_2 in secondary,

$$\begin{aligned} I_1^2 R_2' &= I_2^2 R_2 \\ R_2' &= \left(\frac{I_2}{I_1} \right)^2 R_2 \\ &= \frac{R_2}{k^2} \end{aligned}$$

Transferring secondary parameters to primary side


$$R'_2 = \frac{R_2}{K^2}, \quad X'_2 = \frac{X_2}{K^2}, \quad Z'_2 = \frac{Z_2}{K^2}$$

While

$$E'_2 = \frac{E_2}{K}, \quad I'_2 = KI_2$$

where

$$K = \frac{N_2}{N_1}$$

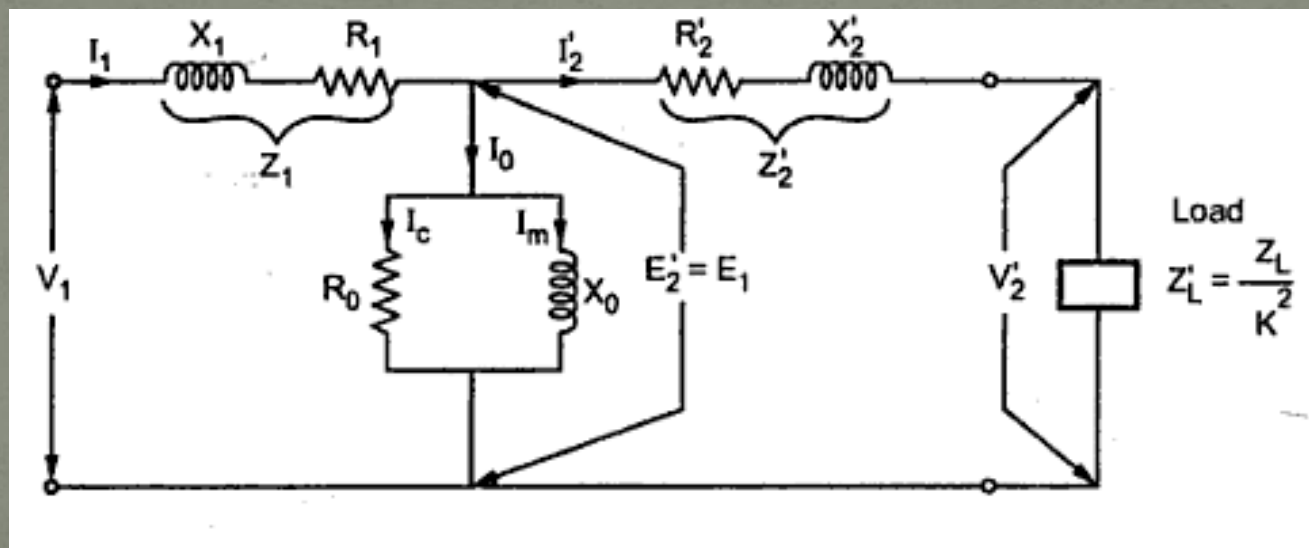

Exact equivalent circuit referred to primary


Equivalent circuit referred to secondary side

- Transferring primary side parameters to secondary side



$$R'_1 = K^2 R_1, \quad X'_1 = K^2 X_1, \quad Z'_1 = K^2 Z_1$$

$$E'_1 = K E_1, \quad I'_1 = \frac{I_1}{K}, \quad I'_0 = \frac{I_0}{K}$$

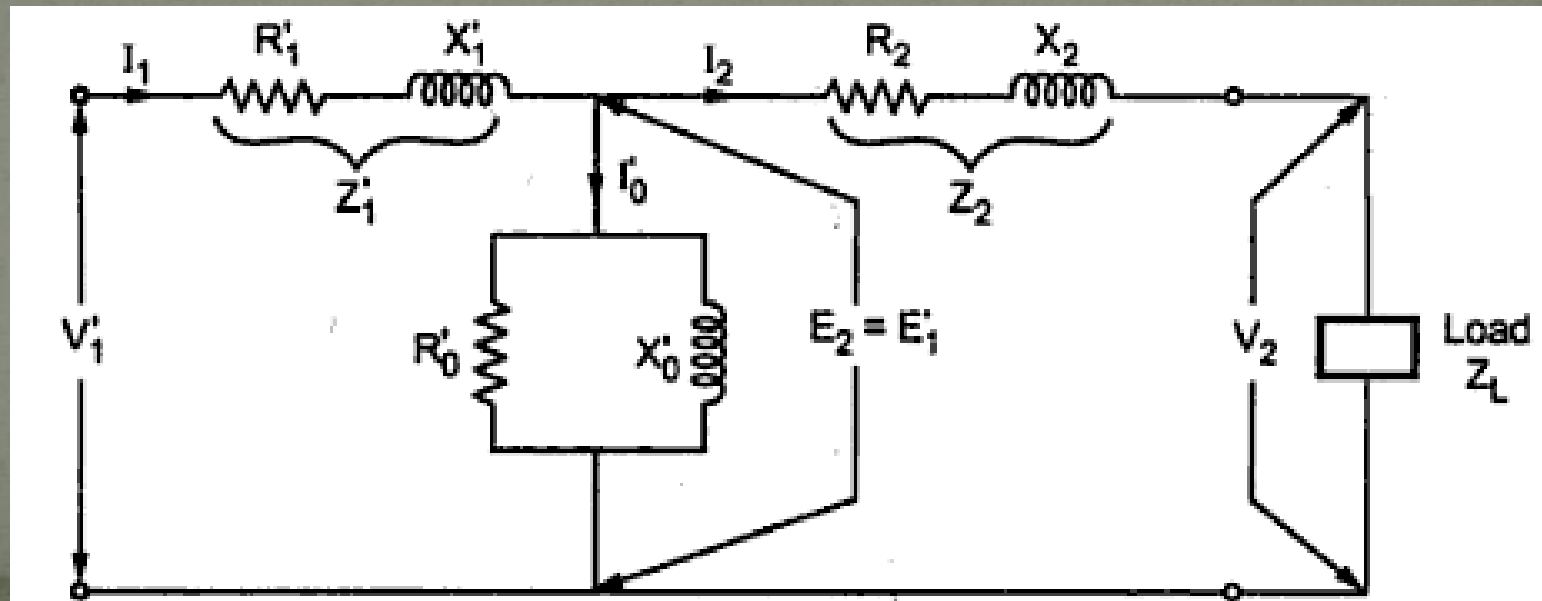Similarly exciting circuit parameters are also transferred to secondary as R'_0 and X'_0



equivalent circuit w.r.t primary

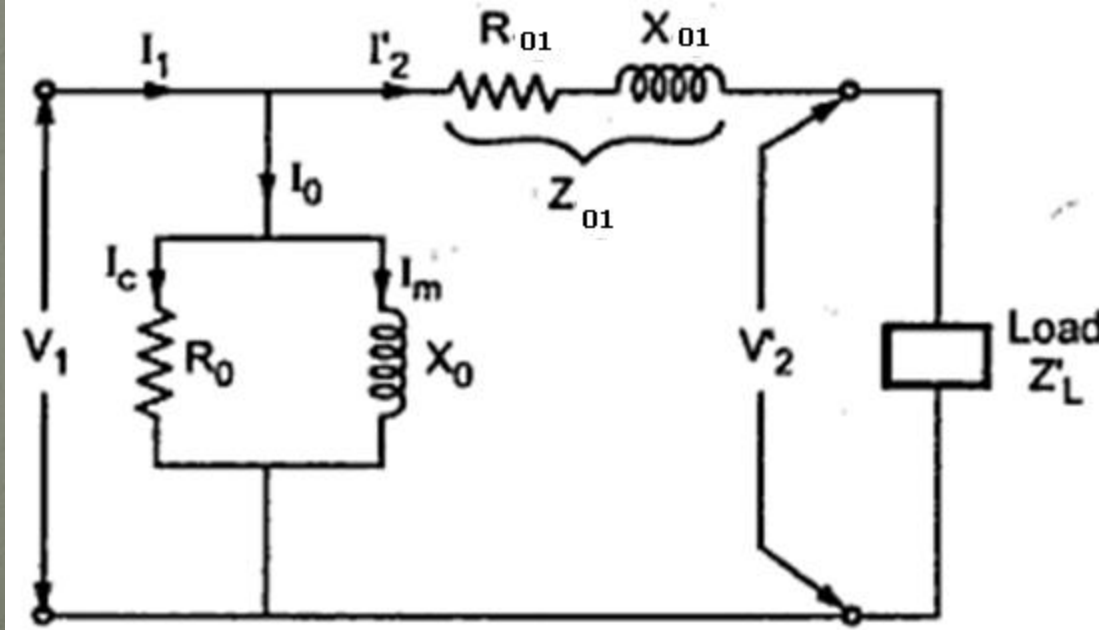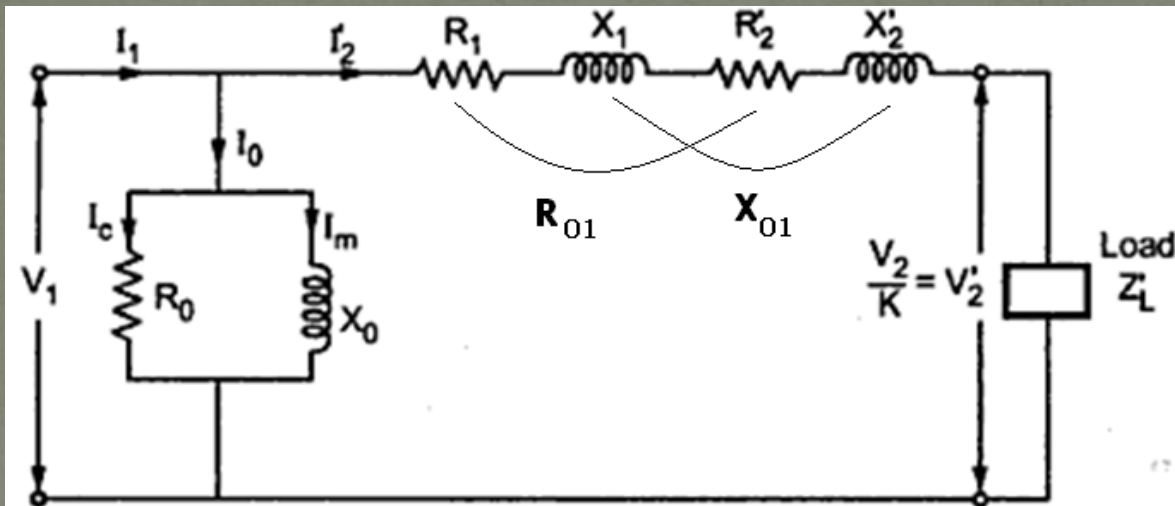

where

$$R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2}$$

$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2}$$

$$Z_{01} = R_{01} + j X_{01}$$

Approximate equivalent circuit

- Since the no-load current is 1% of the full load current, the no-load circuit can be neglected

