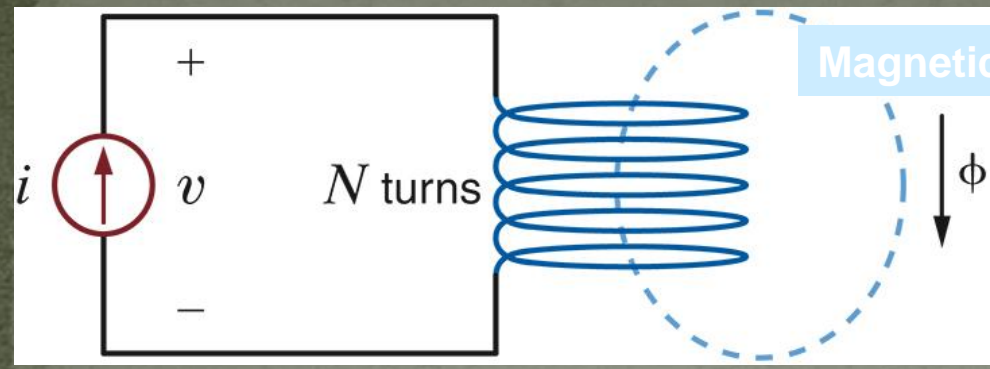


Mutual coupling with dot convention,

BASIC CONCEPTS – A REVIEW



Magnetic field

$$\lambda = N\phi$$


Total magnetic flux linked by N-turn coil

$$\lambda = Li$$

Ampere's Law (linear model)

$$v = \frac{d\lambda}{dt}$$

Faraday's Induction Law

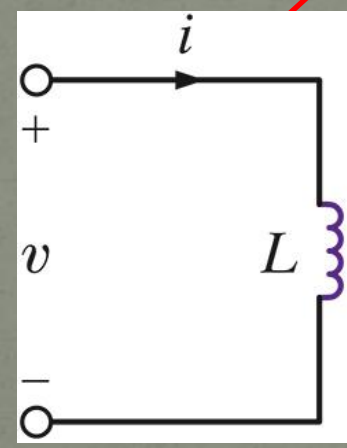

$$v = L \frac{di}{dt}$$


Assumes constant L and linear models!

Ideal Inductor



MUTUAL INDUCTANCE

Overview of Induction Laws

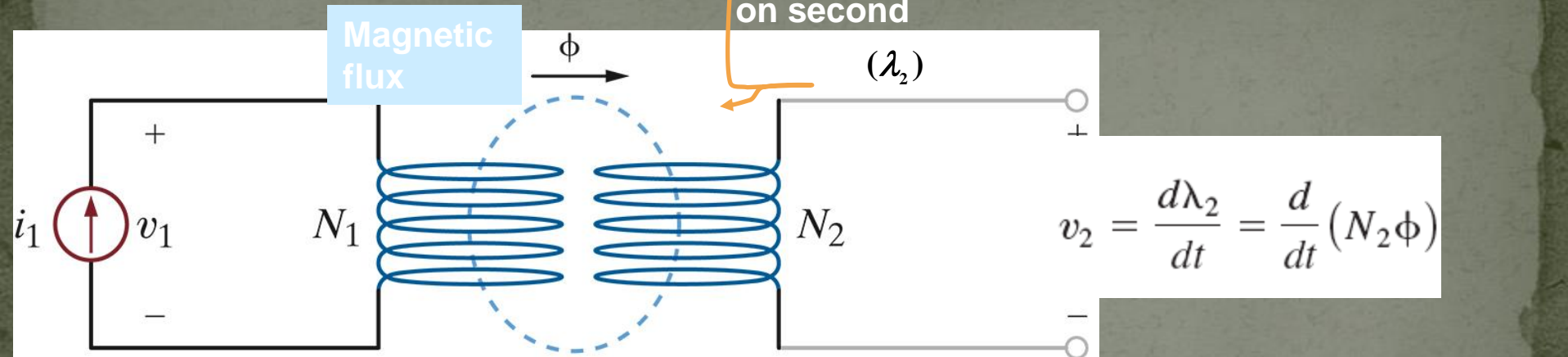

Total flux linkage

$$\lambda = N\phi \text{ (webers)}$$

If linkage is created by a current flowing through the coils...

$$\lambda = \mathbf{L}i \quad \text{(Ampere's Law)}$$

$$= \frac{d}{dt} \left(N_2 \left(\frac{L_1}{N_1} i_1 \right) \right) = \frac{N_2}{N_1} L_1 \frac{di_1}{dt} = L_{21} \frac{di_1}{dt}$$

The voltage created at the terminals of the components is

$$v = \mathbf{L} \frac{di}{dt} \quad \text{(Faraday's Induction Law)}$$


One has the effect of mutual inductance

Basic Electrical Engineering (BEE-101)



TWO-COIL SYSTEM

(both currents contribute to flux)

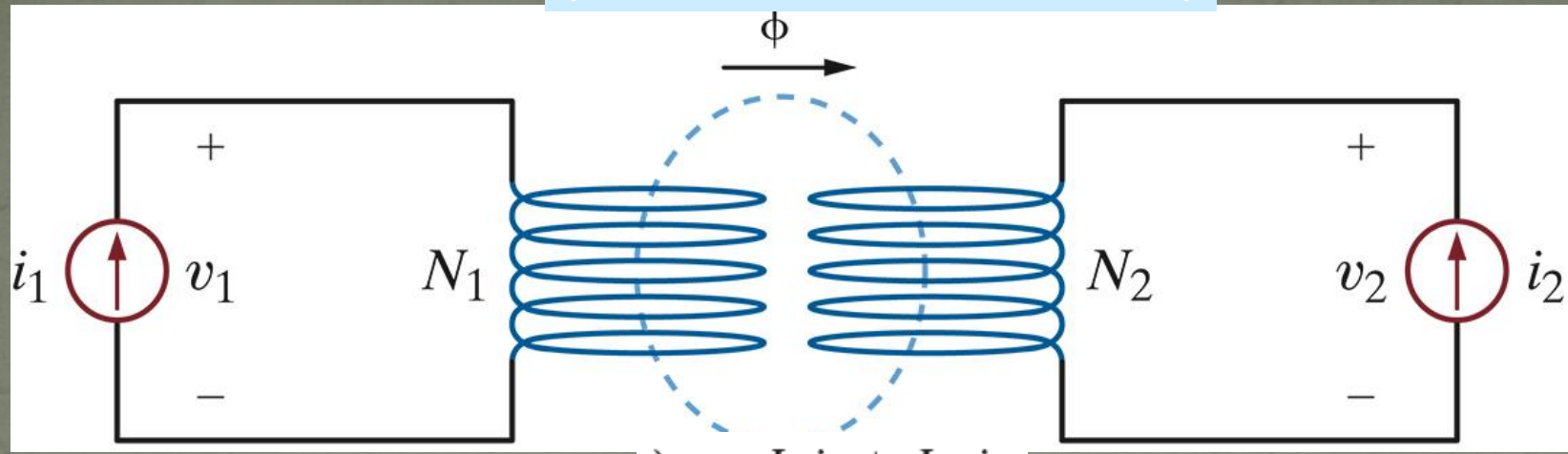

$$\lambda_1 = L_1 i_1 + L_{12} i_2$$
$$\lambda_2 = L_{21} i_1 + L_2 i_2$$

$$v_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} + L_{12} \frac{di_2}{dt}$$


$$v_2 = \frac{d\lambda_2}{dt} = L_{21} \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

Self-induced

Mutual-induced

$$L_{12} = L_{21} = M$$

Linear model simplifying notation

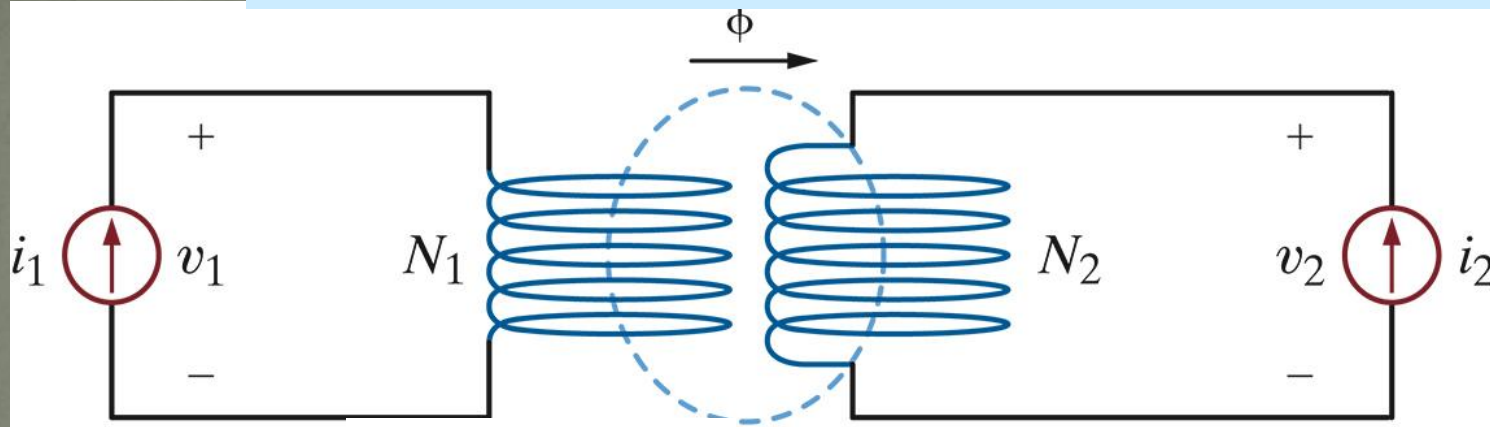


$$\lambda_1 = L_1 i_1 - M i_2$$


$$\lambda_2 = -M i_1 + L_2 i_2$$

$$v_1 = \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$


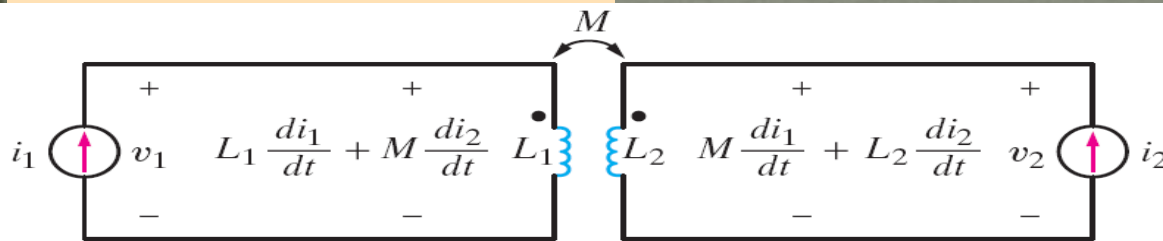
$$v_2 = \frac{d\lambda_2}{dt} = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



(a)

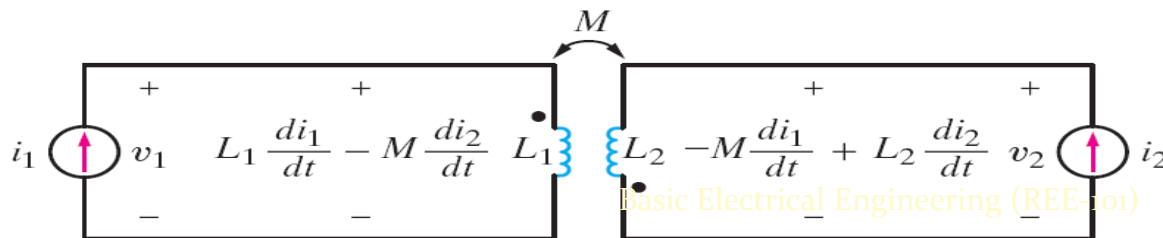


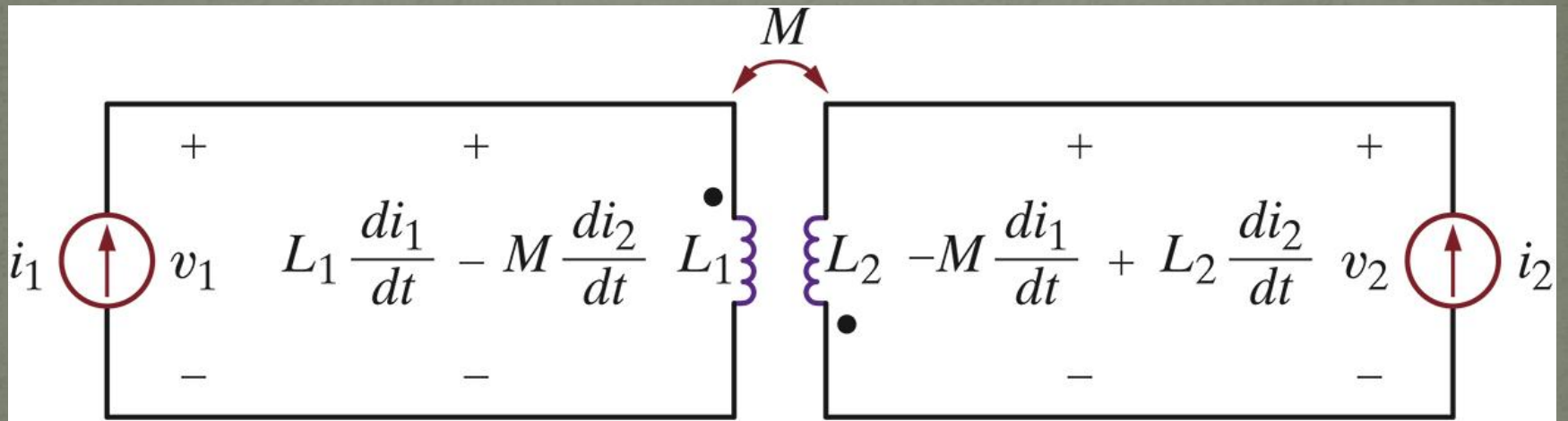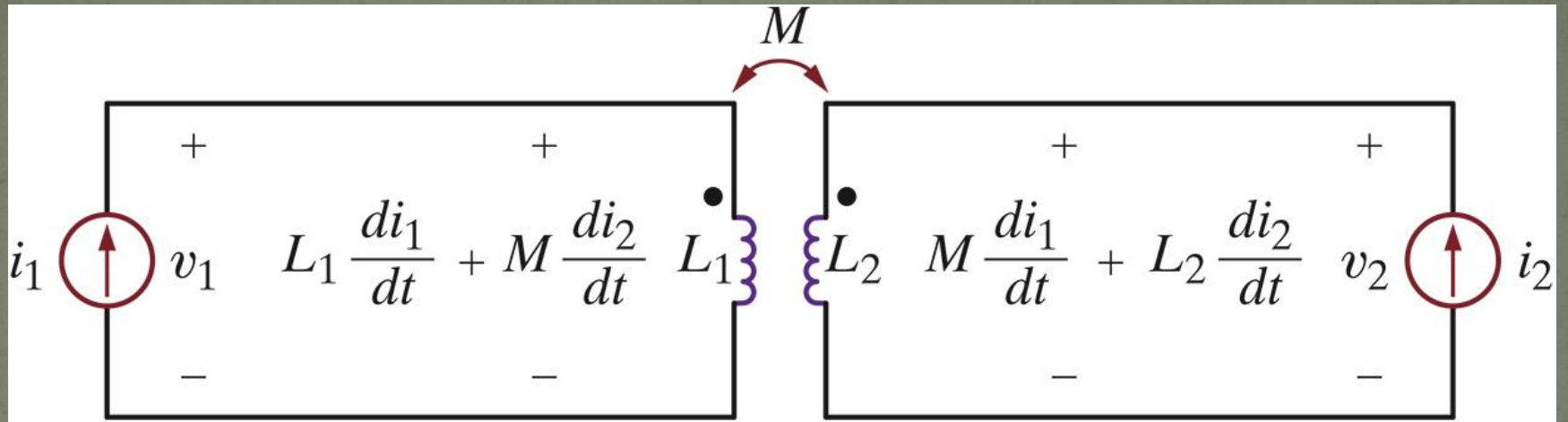Dots mark reference polarity for voltages induced by each flux



THE DOT CONVENTION REVIEW

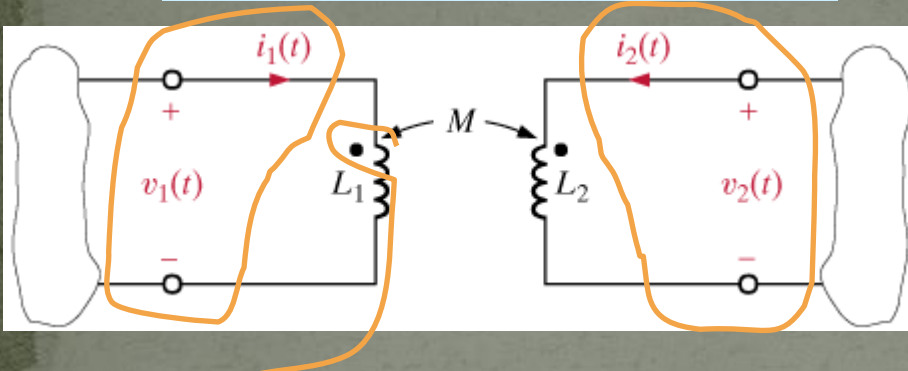Currents and voltages follow passive sign convention




Flux 2 induced voltage has + at dot

$$v_1(t) = L_1 \frac{di_1}{dt}(t) + M \frac{di_2}{dt}(t)$$

$$v_2(t) = M \frac{di_1}{dt}(t) + L_2 \frac{di_2}{dt}(t)$$

For other cases change polarities or current directions to convert to this basic case

LEARNING EXAMPLE

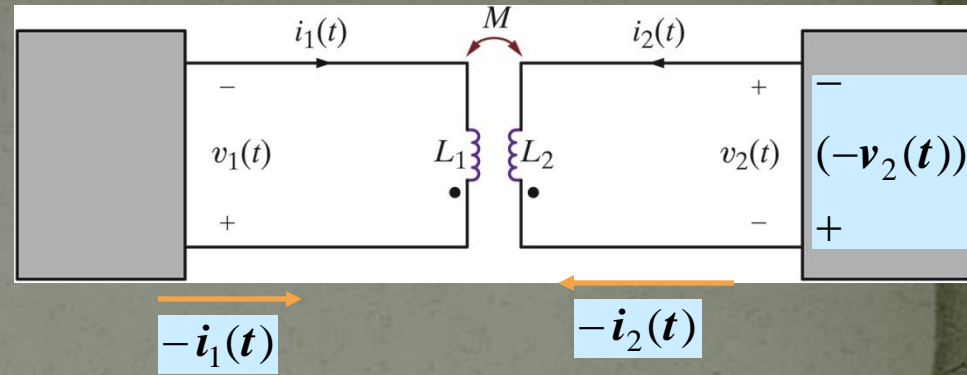

$$v_1(t) = L_1 \left(-\frac{di_1}{dt} \right) + M \left(-\frac{di_2}{dt} \right)$$


$$-v_2(t) = M \left(-\frac{di_1}{dt} \right) + L_2 \left(-\frac{di_2}{dt} \right)$$

$$v_1 = -L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$


$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

LEARNING EXAMPLE

Write mesh equations for the circuit using the assigned mesh currents.

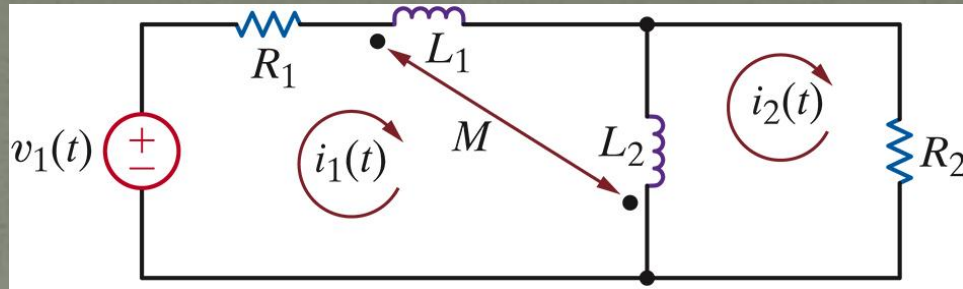


Mesh 1

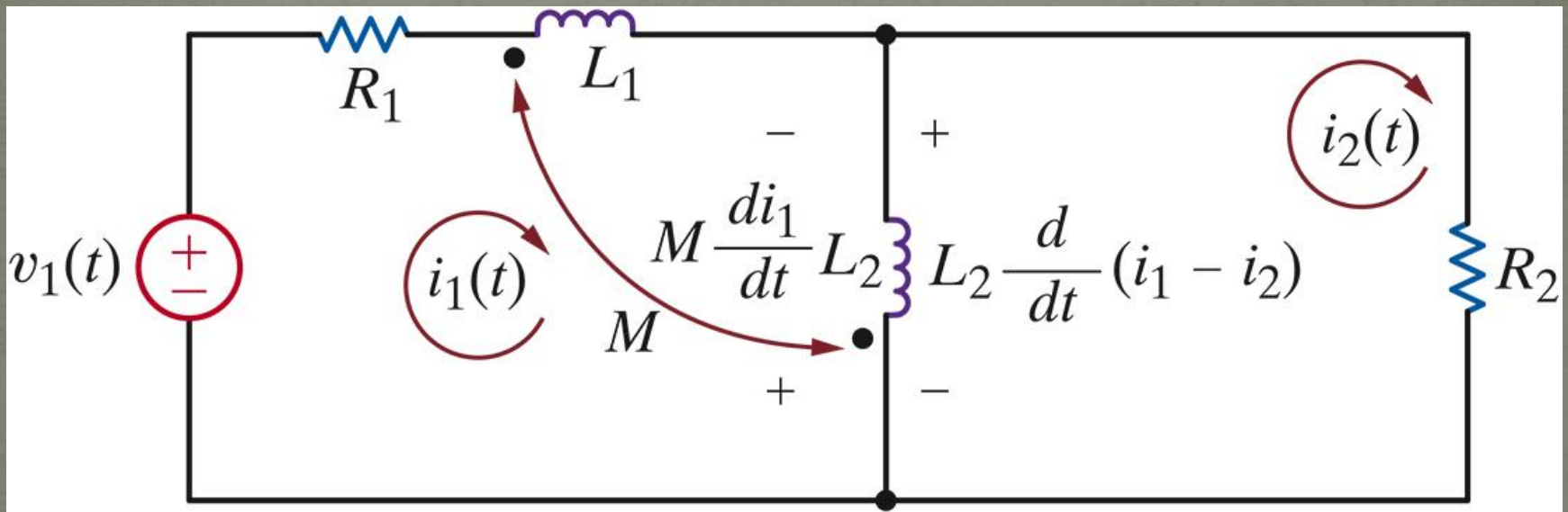


$$v_1(t) = R_1 i_1(t) + L_1 \frac{di_1}{dt} + M \frac{d}{dt} (i_2 - i_1) + L_2 \frac{d}{dt} (i_1 - i_2) - M \frac{di_1}{dt}$$

LEARNING EXAMPLE - CONTINUED

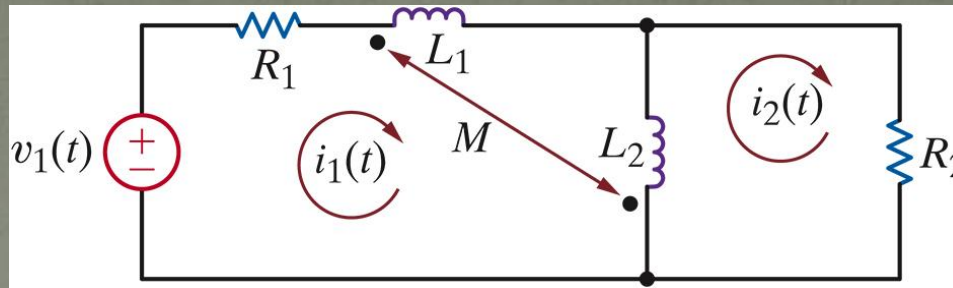

Mesh 2

Voltage Terms

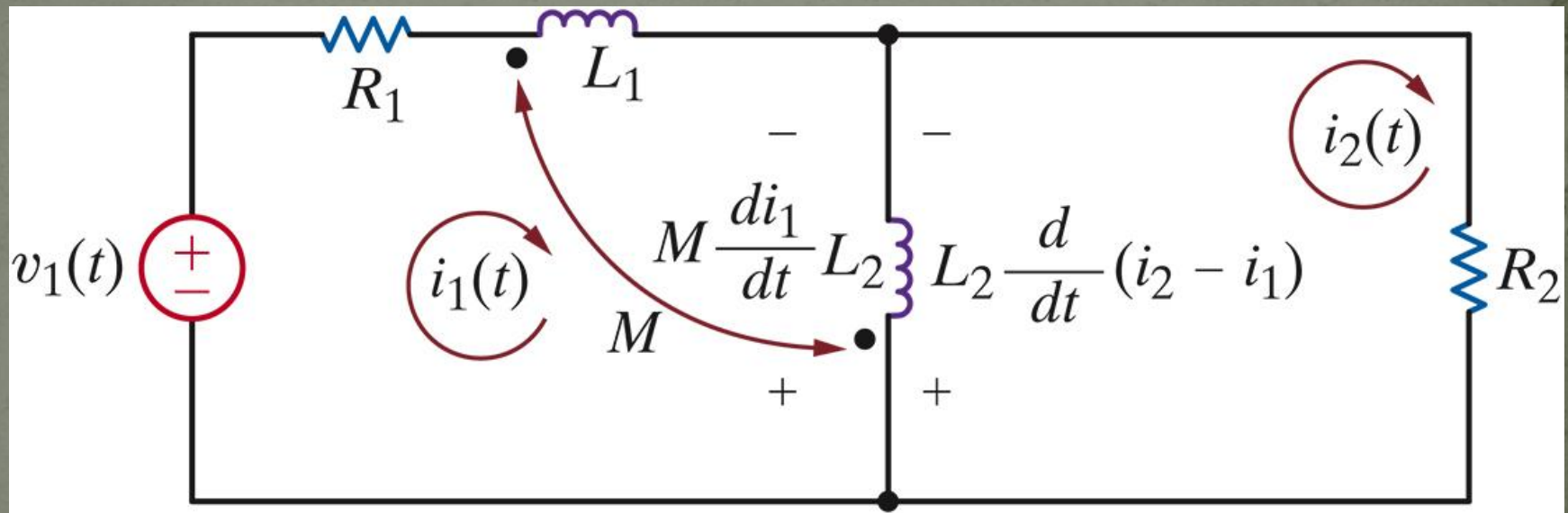

$$R_2 i_2(t) + L_2 \frac{d}{dt} (i_2 - i_1) + M \frac{di_1}{dt} = 0$$