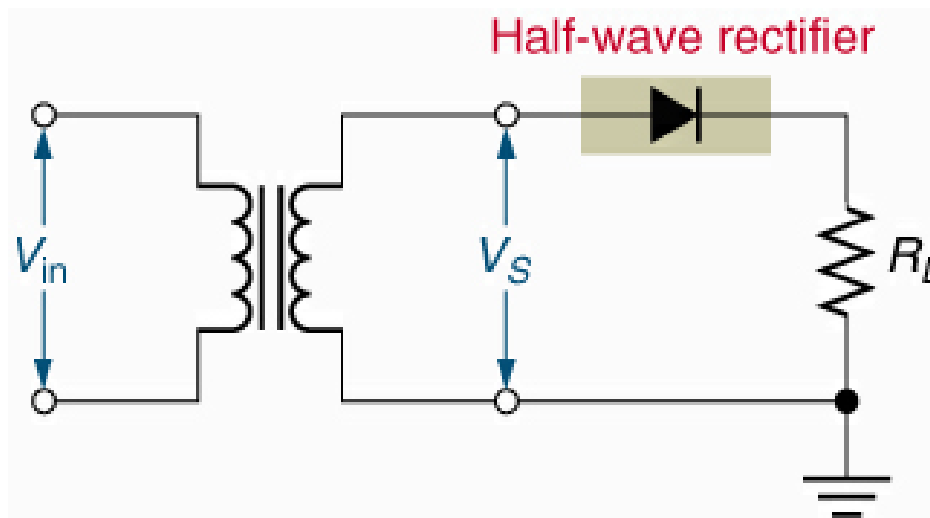





Half-wave Rectifiers

- Half-wave rectifier – A diode placed in series between a transformer (or ac line input) and its load.



Positive Half-wave Rectifiers

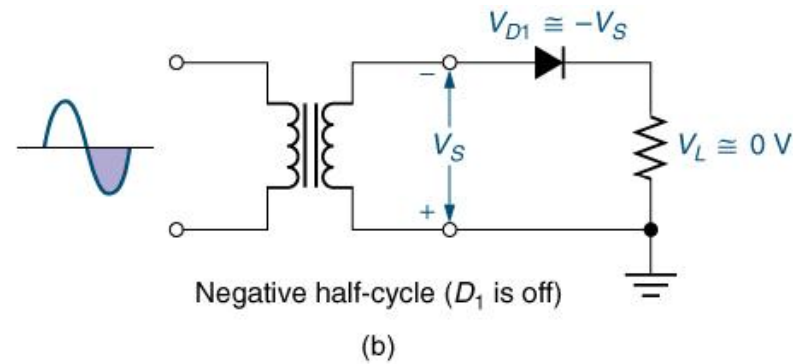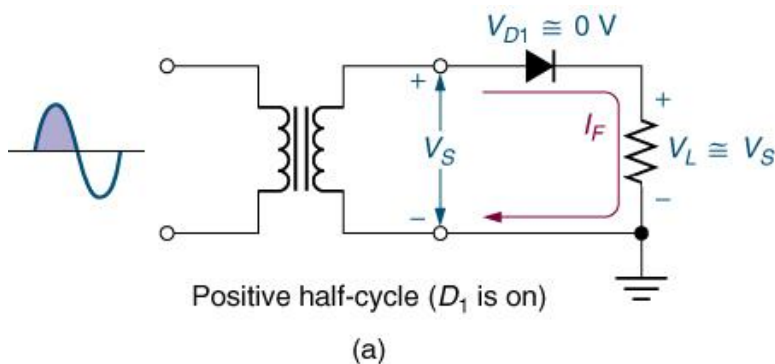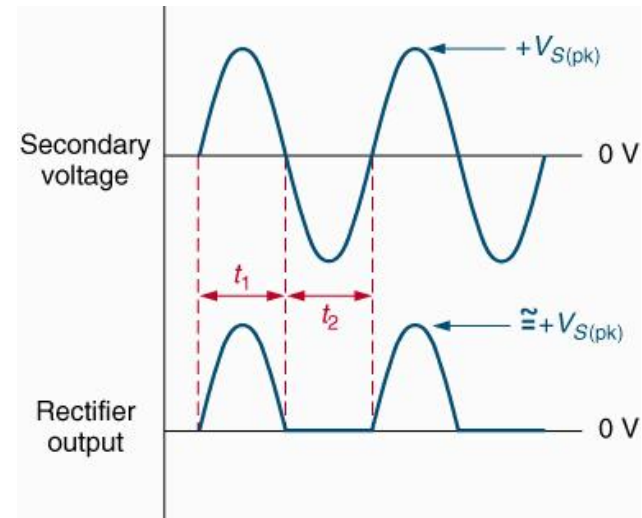This circuit converts an ac input to a series of positive pulses.



Average Load Voltage and Current

- Average voltage (V_{ave}) – The dc equivalent of a voltage waveform.
- Average current (I_{ave}) – The dc equivalent of a current waveform.



For the output from a *half-wave* rectifier:

$$V_{ave} = \frac{V_{pk}}{\pi}$$


$$I_{ave} = \frac{I_{pk}}{\pi}$$

Negative Half-wave Rectifiers

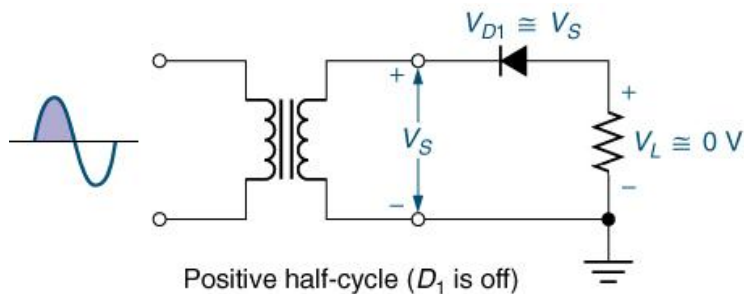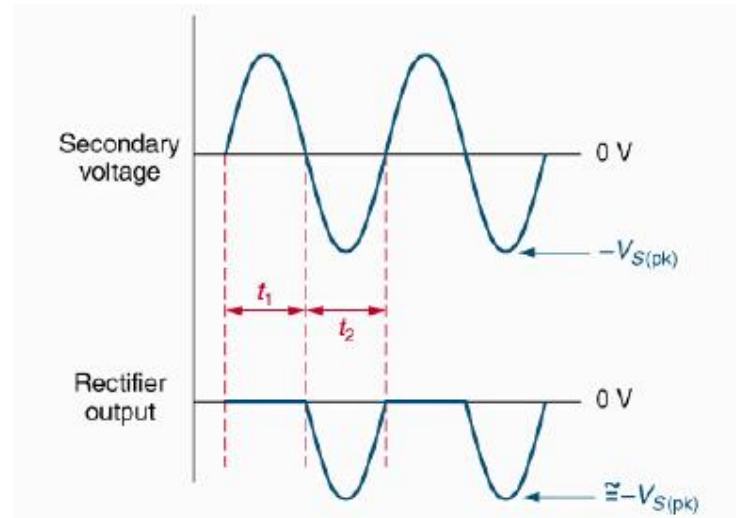This circuit converts an ac input to a series of negative pulses.



(a)

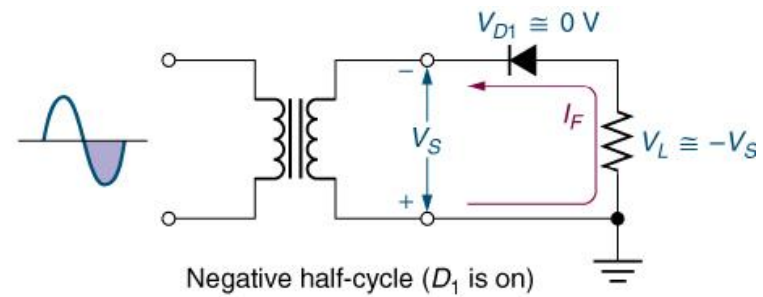

(b)

Peak Inverse Voltage (PIV)

Peak inverse voltage (PIV) – The maximum diode reverse bias produced by a given circuit.

For the diode in a half-wave rectifier:

$$\text{PIV} = V_{S(\text{pk})}$$

