
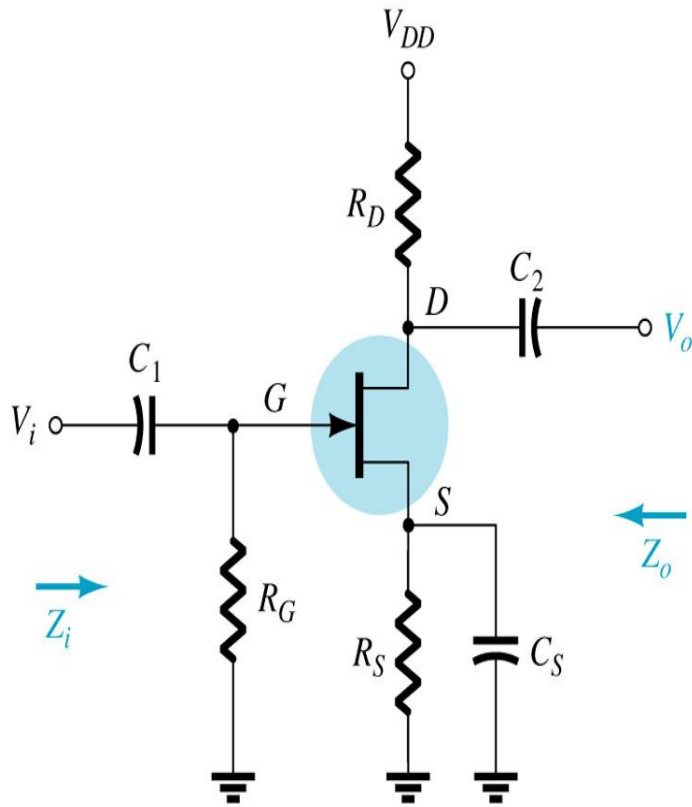


**Figure** Common-source amplifier.

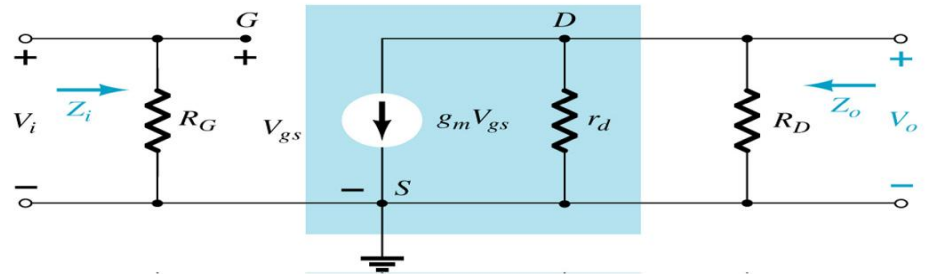


For drawing an ac equivalent circuit of Amp.


- Assume all Capacitors  $C_1$ ,  $C_2$ ,  $C_S$  as short circuit elements for ac signal
- Short circuit the d c supply
- Replace the FET by its small signal model




# Analysis of CS Amplifier

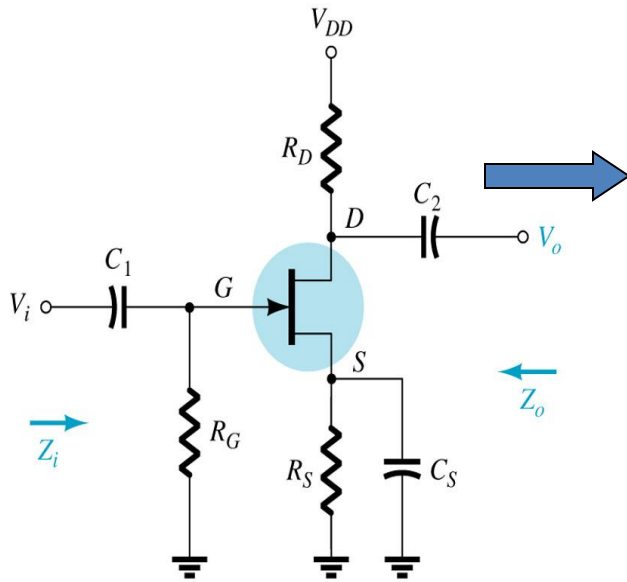

A C Equivalent Circuit

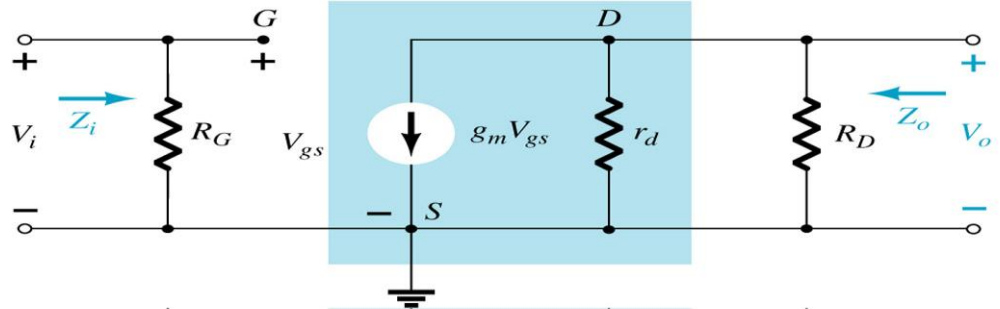

Simplified A C Equivalent Circuit

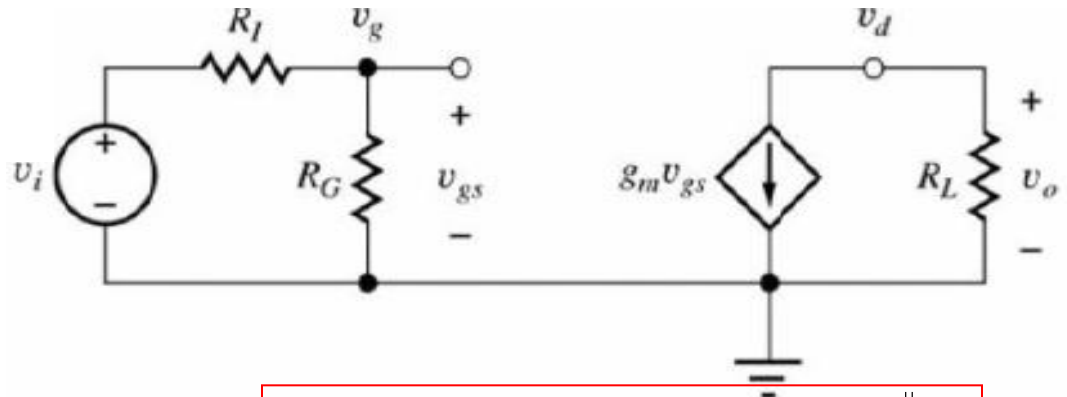

Voltage gain,  $A_v = \frac{v_o}{v_{gs}}$



$$\therefore v_o = i_o R_L = -g_m v_{gs} R_L$$

$$\therefore A_v = \frac{v_o}{v_{gs}} = -g_m R_L, R_L = R_D \parallel r_d$$

Input imp.,  $Z_{in} = R_G = R_1 \parallel R_2$

Out put imp.,  $Z_o = r_d \parallel R_D = \frac{r_d R_D}{r_d + R_D}$
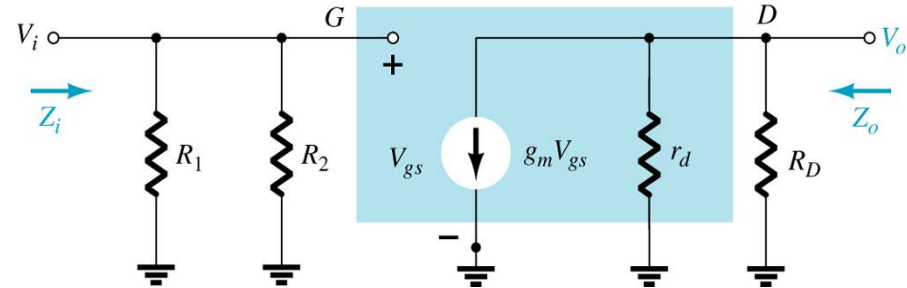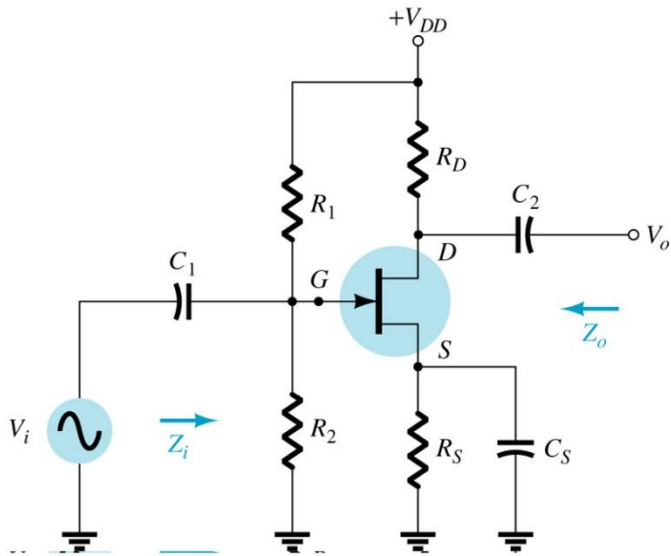
# Analysis of CS Amplifier with Potential Divider Bias



This is a CS amplifier configuration therefore the input is on the gate and the output is on the drain.

$$A_v = -g_m(r_d \parallel R_D)$$

$$A_v \cong -g_m R_D, \quad \because r_d \geq 10 R_D$$

$$Z_i = R_1 \parallel R_2$$

$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \quad / \quad r_d \geq 10 R_D$$