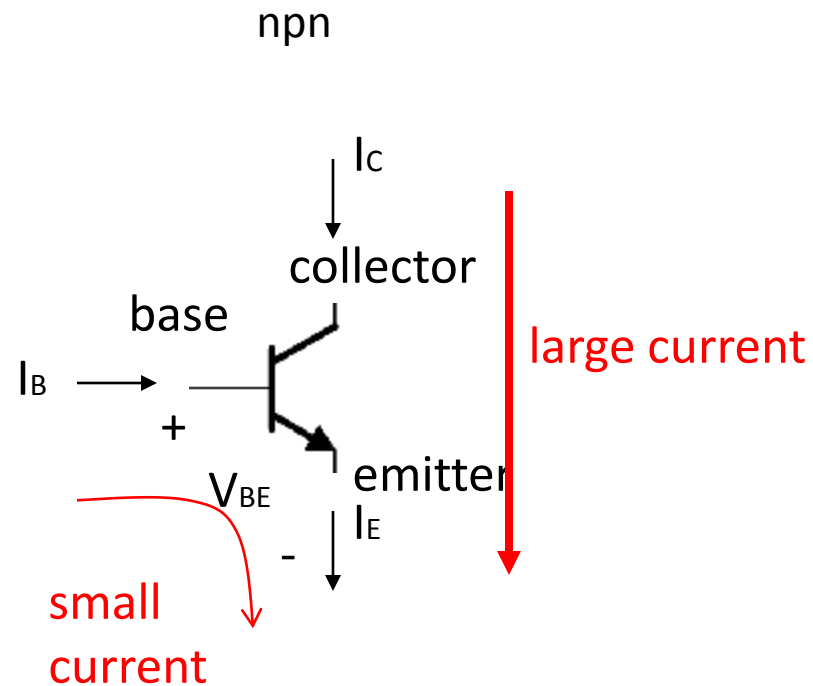


Summary of DC problem

- Bias transistors so that they operate in the linear region B-E junction forward biased, C-E junction reversed biased
- Use $V_{BE} = 0.7$ (npn), $I_C \approx I_E$, $I_C = \beta I_B$
- Represent base portion of circuit by the Thevenin circuit
- Write B-E, and C-E voltage loops.
- For analysis, solve for I_C , and V_{CE} .
- For design, solve for resistor values (I_C and V_{CE} specified).



Summary of npn transistor behavior



Transistor as an amplifier

- Transistor circuits are analyzed and designed in terms of DC and ac versions of the same circuit.
- An ac signal is usually superimposed on the DC circuit.
- The location of the operating point (values of I_C and V_{CE}) of the transistor affects the ac operation of the circuit.
- There are at least two ac parameters determined from DC quantities.

Small-signal equivalent circuit models

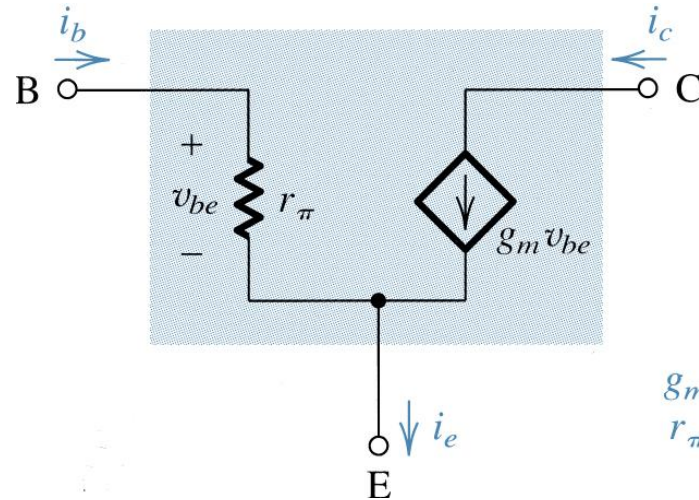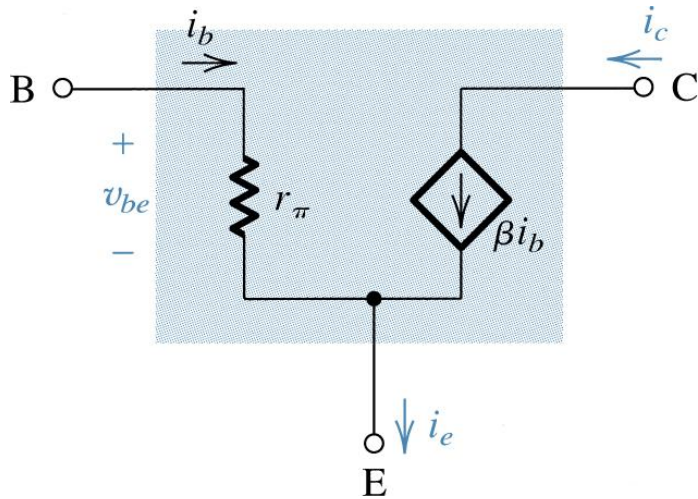

$$g_m = I_C / V_T$$
$$r_\pi = \beta / g_m$$

- ac model
- Hybrid- π model
- They are equivalent
- Works in linear region only

Steps to analyze a transistor circuit

- 1 DC problem
Set ac sources to zero, solve for DC quantities, I_C and V_{CE} .
- 2 Determine ac quantities from DC parameters
Find g_m , r_π , and r_e .
- 3 ac problem
Set DC sources to zero, replace transistor by hybrid- π model, find ac quantities, R_{in} , R_{out} , A_v , and A_i .