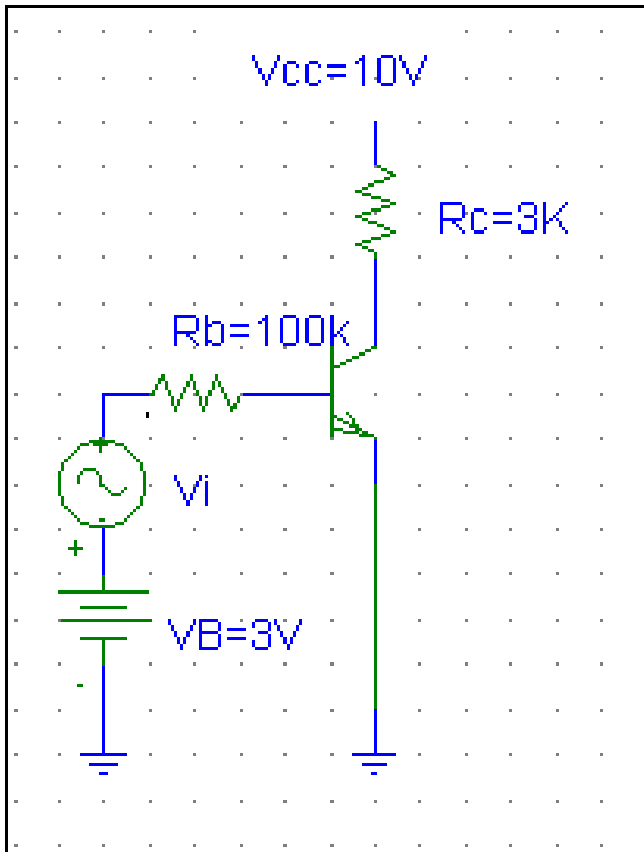


Example 1

Find v_{out}/v_{in} , ($\beta = 100$)



DC problem

Short v_i , determine I_C and V_{CE}

B-E voltage loop

$$3 = I_B R_B + V_{BE}$$

$$I_B = (3 - .7)/R_B = 0.023mA$$

C-E voltage loop


$$V_{CE} = 10 - I_C R_C$$

$$V_{CE} = 10 - (2.3)(3)$$

$$V_{CE} = 3.1V$$

Q point: $V_{CE} = 3.1V$, $I_C = 2.3mA$

Example 2

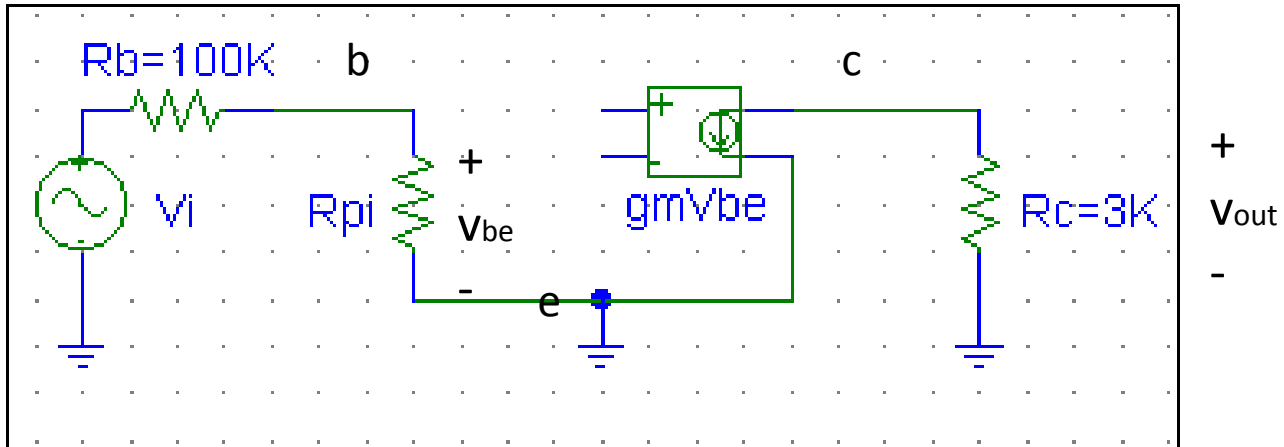

ac problem

Short DC sources, input and output circuits are separate, only coupled mathematically

$$g_m = I_c / V_T = 2.3\text{mA} / 25\text{mV} = 92\text{mA/V}$$

$$r_\pi = V_T / I_B = 25\text{mV} / .023\text{mA} = 1.1\text{K}$$

$$V_{be} = V_i [r_\pi / (100\text{K} + r_\pi)] = 0.011v_i$$

$$V_{out} = -g_m V_{be} R_c$$

$$V_{out} = -92 (0.011v_i) 3\text{K}$$

$$V_{out}/V_i = -3.04$$

Example 3

Find g_m , r_π , and r_o , given: $\beta = 100$, $V_A = 100V$, $I_C = 1 \text{ mA}$

$$g_m = I_C / V_T = 1 \text{ mA} / 25 \text{ mV} = 40 \text{ mA/V}$$

$$r_\pi = V_T / I_B = 25 \text{ mV} / .01 \text{ mA} = 2.5 \text{ K}$$

$r_o =$ output resistance of transistor

$r_o =$ 1/slope of transistor output characteristics

$$r_o = |V_A| / I_C = 100 \text{ K}$$

Summary of transistor analysis

- Transistor circuits are analyzed and designed in terms of DC and ac versions of the same circuit.
- An ac signal is usually superimposed on the DC circuit.
- The location of the operating point (values of I_C and V_{CE}) of the transistor affects the ac operation of the circuit.
- There are at least two ac parameters determined from DC quantities.